



Bashundhara
Exercise Book
Write Your Future

Sadman Sec: A
Electrical Circuits
UTU 011221572

Mid(DC Circuit) ~~Answers~~

* Basic Elements

* Law of Ohm / Kirchhoff's law

* Node : Analysis

* Mesh : Analysis



or ~~for~~ ~~in~~ ~~out~~ Capacitor

~~from~~ inductor

~~to~~ diode

charge :-

Electron : -1.6×10^{-19} C

Proton : $+1.6 \times 10^{-19}$ C

Neutron : 0 C

P.T.

Quantification

6M
Date _____

Conversion

(k) kilo $\times 10^3$

(m) milli $\times 10^{-3}$

(M) mega $\times 10^6$

(μ) micro $\times 10^{-6}$

(G) Giga $\times 10^9$

(n) nano $\times 10^{-9}$

(T) Tera $\times 10^{12}$

(p) pico $\times 10^{-12}$

short \rightarrow

\rightarrow short $\times 10^3$ = nanometer

\rightarrow short $\times 10^{-6}$ = micrometer

P.T.

\rightarrow short $\times 10^{-9}$ = nanometer

Q

* (t) $\int_0^t \{ u_A + b_L t + b_R t \} dt$
 given $\left\{ \begin{array}{l} u_A > 0 \\ u_A + b_L t + b_R t > 1 \end{array} \right.$
 \rightarrow all forms not fit;

A. $\left(\frac{1}{2} \cos t + 3t \right) \cos t + 2 \leq (t) \leq \dots$

$$u_A = \int_0^t \{ \dots \} dt$$

$$(t) = \left(u_A + \int_0^t \{ \dots \} dt \right) \cos t + \int_0^t \{ u_A + b_L t + b_R t \} dt$$

$$= \left[u_A \right]_0^t + \left[\frac{u_A}{2} t^2 \right]_0^t + \left[\frac{b_L}{2} t^2 \right]_0^t + \left[\frac{b_R}{3} t^3 \right]_0^t$$

P.T.

* find the charge $q(t)$ flowing through a device if the current is :-

$$(i) i(t) = 20 \cos(10t + \frac{\pi}{6}) \text{ mA}$$

$$q(0) = 2 \text{ nC}$$

$$\begin{aligned} q &= \int i dt \\ &= \int 20 \cos(20t + \frac{\pi}{6}) dt \\ &= \frac{20}{10} \sin(20t + \frac{\pi}{6}) + C \end{aligned}$$

$$I = 20 \sin(10t + \pi/6)$$

$$\int I = \int 20 \cos(10t + \pi/6) dt$$

$$= 20 \sin(10t + \pi/6) + C$$

$$2 \sin(10t + \pi/6) + C = q(t)$$

$$q(0) = 2$$

$$2 = 2 \cdot \sin(10 \cdot 0 + \pi/6) + C$$

$$2 = 2 \cdot \sin 0 + C$$

$$2 = 2 \cdot \frac{1}{2} + C$$

$$2 = 1 + C$$

$$q(t) = 2 \sin(10t + \pi/6) + 1$$

~~q(0) = 2~~

~~Practice~~
30.1.23

Circuit

* current, $i = \frac{dv}{dt}$

* charge, $Q = \int_{t_0}^t i dt$

Example : 1-2

$$v = 5 + \sin 4\pi t$$

$$i = \frac{dv}{dt} \rightarrow \frac{d}{dt} (5 + \sin 4\pi t)$$

$$= 5t \cos 4\pi t \cdot 4\pi + \sin 4\pi t \cdot 5$$

$$\Rightarrow 20\pi t \cos 4\pi t + 5 \sin 4\pi t$$

$$t = 0.5 \text{ s}$$

$$\therefore i = 10\pi \cos 2\pi + 5 \sin 2\pi$$

$$\Rightarrow 10\pi + 0$$

$$\Rightarrow 31.4159 \text{ mA}$$

~~Irreducible~~

~~Ex 7~~

$$v = 10 - 10e^{-2t} \quad \text{of } t = 1 \text{ sec}$$

$$i = \frac{dv}{dt} \quad \text{by}$$

$$= \frac{d}{dt} (10 - 10e^{-2t})$$

$$= -10e^{-2t} (-2) \quad \text{fb}$$

$$= 20e^{-(2t-1)} \quad \text{+}$$

$$= 20e^{-2(2)}$$

$$= 2 \cdot \left(\frac{70}{7} \text{ mA} \right)$$

$$\left(\frac{70}{7} - 1 \right) - \left(\frac{70}{7} - 2 \right) \quad \text{A}$$

P.T.O.

79

~~Ex: 22~~

~~1. 22~~

$$d = 2s \text{ to } 2s$$

$$j = (3t^{\sim} - t)$$

$$\Theta = \int_{+0}^{+1} j dt = \frac{v_0 b}{b + v_0 t} = j$$

$$= \left\{ \begin{array}{l} (3t^{\sim} - t) \\ (3t^{\sim} - t) \end{array} \right\}_{-2}^2$$

$$= \left[\frac{3t^3}{3} - \frac{t^2}{2} \right]_{-1}^2$$

$$= \left(2^3 - \frac{2^2}{2} \right) - \left(1 - \frac{1}{2} \right)$$

$$= 5 \cdot 5$$

Ans

P.T.O

~~Practice: 2.3~~

$$\lambda = \begin{cases} 4A_m & (8 + t) \leq 1 \\ 4 + A_m & t > 1 \end{cases}$$

$t = 0$ s to 2 s

$$Q = \int \lambda dt = \int_0^2 (8 + t) dt =$$

$$= \int_0^2 (8 + t) dt = \left[8t + \frac{t^2}{2} \right]_0^2 = 8 \cdot 2 + \frac{2^2}{2} = 18$$

$$= 8 \cdot 2 + \frac{4 + 3}{2} = 18$$

$$= (8 \cdot 2) + \frac{7}{2} = 18.5$$

$$= 18.5$$

$$= 18.5$$

$$= 18.5$$

Page 24 Exercises

~~1.2~~

~~Exercises~~

(a) $v(t) = (3t + 8) \text{ mACP}$

$$i = \frac{dv}{dt}$$

$$= \frac{d}{dt} (3t + 8)$$

$$= 3 \text{ mA}$$

(b) $v(t) = (8t^2 - 4t - 2) \text{ C}$

$$i = 16t - 4 \text{ A}$$

(c) $v(t) = (3e^{-t} - 5e^{-2t}) \text{ V}$

$$i = (-5e^{-2t}) - 2 + (0 - 1)$$

$$= 10e^{-2t} \text{ A}$$

P.T.O.

$$(d) v(t) = 10 \sin 120\pi t \text{ pC}$$

$$i = (10 \cos 120\pi t + 120\pi)$$

$$= 1200\pi \cos 120\pi t \text{ pA}$$

$$(e) v(t) = 20 e^{-4t} \cos 50t \text{ uC}$$

$$i = 20 e^{-4t} (-\sin 50t \cdot 50) + 20 \cos 50t (-80 e^{-4t})$$

$$A \sim (j + j_s) = (j) i \text{ uA}$$

$$= 20 \cos 50t (-80 e^{-4t}) + 20 \cos 50t (-80 e^{-4t})$$

$$\underline{\text{P.T.O}} + \underline{j_e} + \underline{j_s}$$

$$0 = j + j_e + j_s$$

$$0 = j - e$$

~~1-3~~ $\int q \text{ f} \rightarrow \text{ osz wiz } \Omega t = (t) \rho^{\circ}$ (6)

(a) $i(t) = 3A$ $i(0) = 2i$

$$Q = \int i dt \quad t=0$$
$$= 3t + C$$

$\int u \text{ f} \rightarrow \text{ osz } \Omega t = (t) \rho^{\circ}$ (3)

$$3t + C = 2 \quad \text{f} \rightarrow \text{ osz } \Omega t = i$$

(b) $i(t) = (2t + 5) \text{ m A}$

$$Q = \int i dt$$
$$\Rightarrow t^2 + 5t + C$$

$$t^2 + 5t + C = 0$$

$$\Rightarrow C = 0$$

$$(4) i(t) = 20 \cos(10t + \frac{\pi}{6}) \text{ mA}$$

~~for~~ $I = \text{forw} - \text{opp}$

$$a(\omega) = 2 \mu C$$

$$Q = \int 20 \cos(10t + \frac{\pi}{6}) dt$$

$$= 20 \left\{ -\sin(10t + \frac{\pi}{6}) \right\}$$

$$+ \frac{20}{10} \left[-\frac{\sin(10t + \frac{\pi}{6})}{10} \right] + C$$

$$I = \frac{-20 \left\{ -\sin(\frac{\pi}{6}) \right\}}{10} + C = 2$$

$$\Rightarrow 10 \left\{ -\sin(\frac{\pi}{6}) \right\} + C = 2$$

$$C = 2 - 10 \left\{ -\sin(\frac{\pi}{6}) \right\}$$

$$= 7$$

$$+ b \left\{ \text{opp} \right\} \frac{10}{10} = 7$$

~~0.79~~

$$I = \cos 40t \cdot \frac{e^{-30t}}{-30} - \int \left[-\sin 40t \cdot \frac{e^{-30t}}{-30} + \right.$$

$$\left. - \frac{\cos 40t \cdot e^{-30t}}{30} - \int \left[-40 \sin 40t \cdot \frac{e^{-30t}}{-30} \right] dt \right]$$

$$I = \cancel{\int 10e^{-30t} - \sin 40t dt}$$

$$= \sin 40t \cdot \cancel{\int 10e^{-30t} dt}$$

$$I = - \int \left[\frac{d}{dt} (\sin 40t) \cdot \int 10e^{-30t} dt \right] dt$$

$$= \sin 40t \cdot \frac{10e^{-30t}}{-30} - \int 40 \cos 40t \cdot \frac{10e^{-30t}}{-30} dt$$

$$= - \frac{1}{30} \sin 40t \cdot 10e^{-30t} + \frac{40}{30} \int \cos 40t \cdot 10e^{-30t} dt$$

$$= P + \frac{40}{30} \left[\cos 40t \int 10e^{-30t} dt - \int \left[\frac{d}{dt} \cos 40t \cdot \int 10e^{-30t} dt \right] dt \right]$$

$$= P + \frac{40}{30} \left[\cos 40t \cdot \frac{10}{-30} e^{-30t} + \int 40 \sin 40t \cdot \frac{10}{-30} e^{-30t} dt \right]$$

$$= P + \frac{40}{30} \left[-\frac{1}{3} \cos 40t \cdot e^{-30t} - \frac{40}{30} \int \sin 40t \cdot e^{-30t} dt \right] \quad I$$

$$I = P + \frac{4}{3} \left[-\frac{1}{3} \cos 40t \cdot e^{-30t} - \frac{4}{3} I \right]$$

$$I = P - \frac{4}{9} \cos 40t e^{-30t} - \frac{16}{9} I$$

$$I + \frac{16}{9} I = P - \frac{4}{9} \cos 40t e^{-30t}$$

$$\frac{25}{9} I = P - \frac{4}{9} \cos 40t e^{-30t}$$

$$\therefore I = \frac{9}{25} P \left(x \right)$$

Circuit

$$C.W \\ 21.21$$

Voltage

$$V = \frac{E}{q}$$

$$F.A.OJ V = 20 J/C$$

$$\frac{dq}{dt} \rightarrow \frac{dw}{dt} \text{ with } \frac{dw}{dt}$$

Electrical Power & Energy

$$P = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt}$$

$$W = \int_{q_0}^{q_f} P dt = \int_{q_0}^{q_f} vi dt$$

* Cell/Battery: $\xrightarrow{\text{I}} + | - \xleftarrow{\text{I}}$ $P = + vi$

* Resistance: $\xrightarrow{\text{I}} + | - \xrightarrow{\text{I}}$ $P = + vi$

(N)

$$i = 5 \cos 60\pi t \text{ A}$$

$$\int 5 \cos 60\pi t$$

$$= \frac{5 \sin 60\pi t}{60\pi}$$

$$V = 10 + 5 \left\{ \begin{array}{l} 5 \\ \frac{5 \sin 60\pi t}{60\pi} \end{array} \right\}_0^5$$

$$= 10 + 5 \left[\frac{5 \sin 60\pi t}{60\pi} \right]_0^5$$

$$= 10 + 5 \times \frac{5 \sin (300 \times 180)}{60\pi}$$

$$= 10 - \cancel{5} V$$

$$P = V I = 10 \times 5 \{ \cos 60\pi \times (5 \times 10^{-3}) \}$$

$$= 10 \times \{ 5 \times \cos (0.3\pi) \}$$

$$= 10 \times 2.938$$

$$= 29.38 \text{ A}$$

~~2.23~~

$$(a) i = \frac{dv}{dt}$$

$$= \frac{d}{dt} (5 \sin 4\pi t)$$

~~$$= 5 \cos 4\pi t$$~~

$$= 5 \sin 4\pi t - 4\pi b$$

$$= (20\pi \sin 4\pi t) \frac{b}{4\pi}$$

$$+ 12 \left\{ 20\pi \sin 4\pi (0.3) \right\} \times 10^{-3}$$

$$= \left\{ 20\pi \times (-0.588) \right\} \times 10^{-3}$$

$$\{ (0.0 \times 10^3) \times 3600 \} 45 \times 10^{-3}$$

$$V = -2.427$$

~~$$i_s = 0.01 \text{ A} = 100 \text{ mA}$$~~

(b)

$$E = \int_{0}^{0.6} 20\pi \sin 4\pi t \cdot \frac{3 \cos 4\pi t}{4\pi} dt$$
$$= \left(-\frac{1}{4\pi} \sin 8\pi t \right) \Big|_0^{0.6}$$

~~2.23~~

(c)

$$P = V i$$

$$= V \cdot \frac{d\varphi}{dt} \text{ far side } z$$

$$= V \cdot \frac{d}{dt} (5 \sin 4\pi t)$$

$$= 3 \cos 4\pi t \cdot 20\pi \cos 4\pi t$$

$$= 60\pi \cos^2 4\pi t$$

$$= 60\pi \cos^2 \left(180 \times (4 \times 0.3) \right)$$

$$= 60\pi \times 0.65$$

$$\Rightarrow 122.52 \text{ mW}$$

$$\Rightarrow 122.52$$

$$(b) 0.6$$

$$E = \int_0^{0.6} 60\pi \cos^2 4\pi t \, dt$$

$$= 60\pi \int_0^{0.6} \frac{1}{2} + 2\cos^2 4\pi t \, dt$$

$$= 60\pi \times \frac{1}{2} \int_0^{0.6} 2\cos^2 4\pi t \, dt$$

$$= 30\pi \int_0^{0.6} (1 + \cos 8\pi t) \, dt$$

$$= 30\pi \left[t + \frac{\sin 8\pi t}{8\pi} \right]_0^{0.6}$$

$$= 30\pi \left[0.6 + \frac{\sin (180 \times (8 \times 0.6))}{8\pi} \right]$$

$$= 30\pi \times 0.623$$


$$= 58.726 \text{ mJ} \quad \underline{\underline{}}$$

Circuit

~~1.16~~
~~4.2.23~~

~~1.16~~
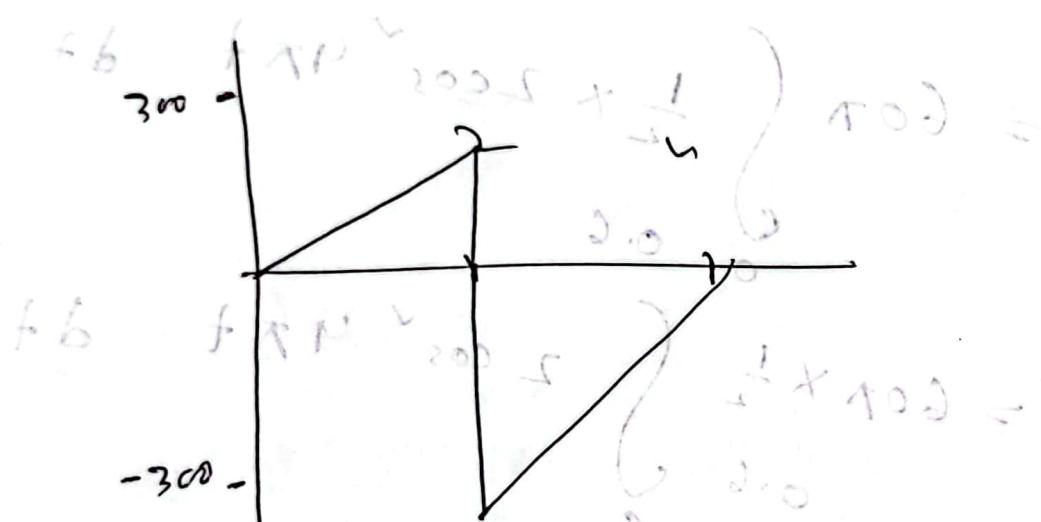
$$V = V_i + \text{I} E_{\text{loss}} = \int_{t_0}^t p \cdot d t = I$$




$$600 = f \Delta t \left(200 + \frac{1}{2} \right) 100 =$$

$$600 = f \Delta t \left(200 + \frac{1}{2} \right) 100 =$$

$$\frac{600}{f \Delta t} = 200 + \frac{1}{2}$$

Independent Power Sources :-

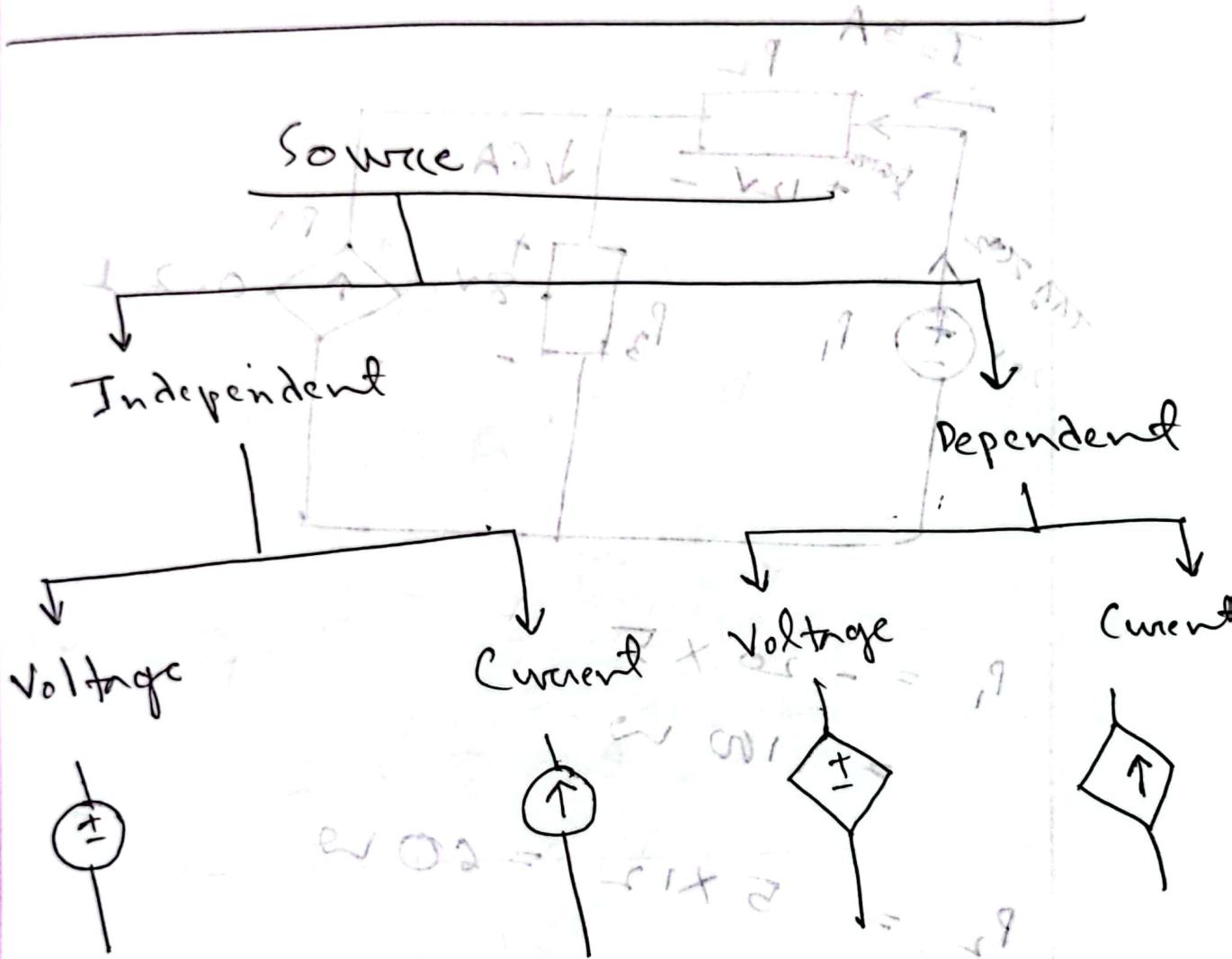


Ct : Next week

Chapter - 2

$$0.578 = 3N \quad \text{P.T.O}$$

$$1001 = 9$$

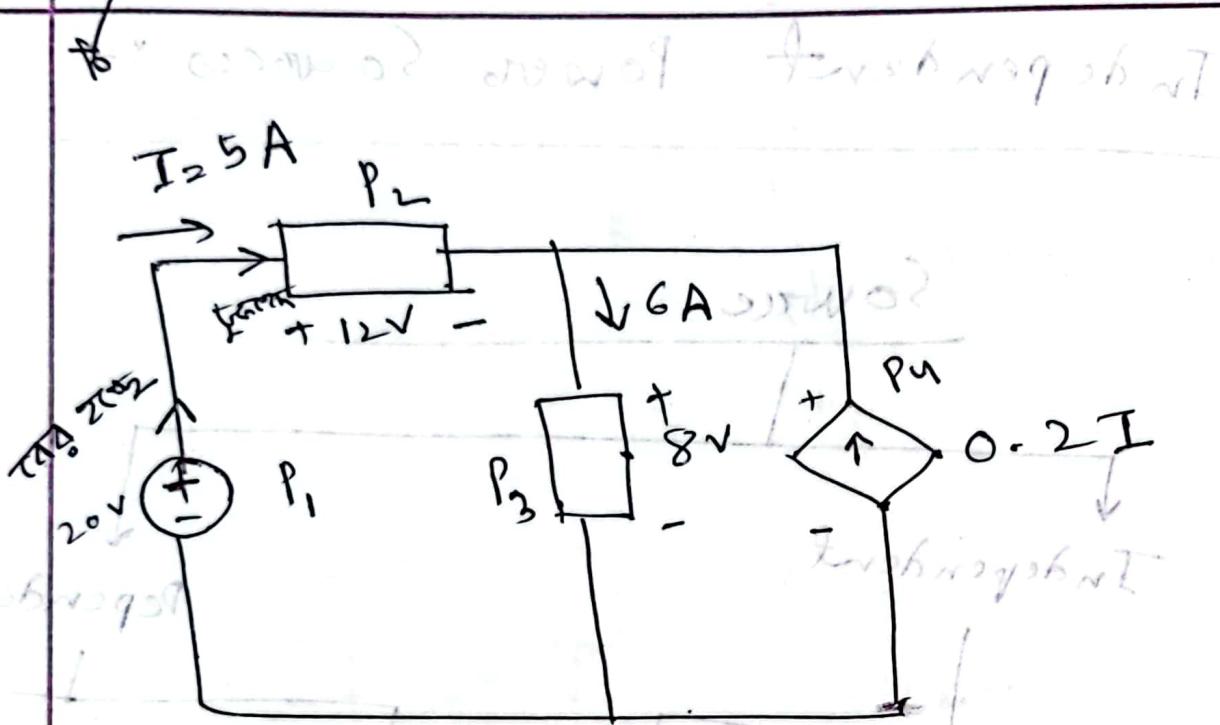

$$P_1 = -20 \times 5 \text{ (arrow)} \\ 100 \text{ W}$$

$$P_2 = 5 \times 12 = 60 \text{ W}$$

$$P_3 = 6 \times 8 = 48 \text{ W}$$

$$P_4 = 1 \times 8 = -8 \text{ W}$$

$$\sum P = -100 + 60 + 48 - 8 = 0$$

1-18

1

$$P_1 = -300 \text{ } \cancel{\text{psi}} \text{ } \rightarrow -19$$

$$P_2 = 100 \text{ } \textcircled{A} \text{ } \textcircled{v}$$

$$P_3 = 280 \text{ at } 20^\circ\text{C}$$

$$P_4 = -32 \quad \text{W} \quad 2.2 + 2.9$$

$$P_5 = -48 \frac{w}{\omega} \text{ N/m}^2$$

$$\sum p \rightarrow 0 \approx 2 - \alpha^k g + q$$

$$81 = \frac{2n}{n} + 9$$

P.T.O.

~~1.20~~

~~1.81-1~~

$$P_1 = -280 \text{ W}$$

$$P_2 = +72 \text{ W}$$

$$P_3 = 3V_0 \text{ W}$$

$$P_4 = +56 \text{ W}$$

$$P_5 = +28 \text{ W}$$

$$P_6 = -30 \text{ W}$$

$$\sum P = 3V_0 - 54 = 0$$

$$\Rightarrow V_0 = \frac{54}{3} = 18$$

A

P.T.

Chaptw-2

Basic Law

- * Ohm's Law
- * Kirchhoff Law
- * Nodal Analysis
- * Mesh Analysis

Conductor: $T \uparrow$, $R \uparrow$

Semiconductor: $T \uparrow$, $R \downarrow$

$$R = \rho \frac{l}{A} = \text{Resistivity}$$

Ohm's law

$$V = iR$$

$$\underline{i_{T=0}}$$

C.V
7.2.23

Ec

Series :- Same current

Parallel :- Same Terminal voltage

and
Same Voltage

Kirchhoff's Current Law -

Incoming current = outgoing current


$$\sum I = 0 \quad (\text{Node})$$

$$KVL : \quad (\text{Voltage drop})$$

Voltage produced = voltage consumed

$$\sum V = 0 \quad (\text{Loop})$$


P.T.O.

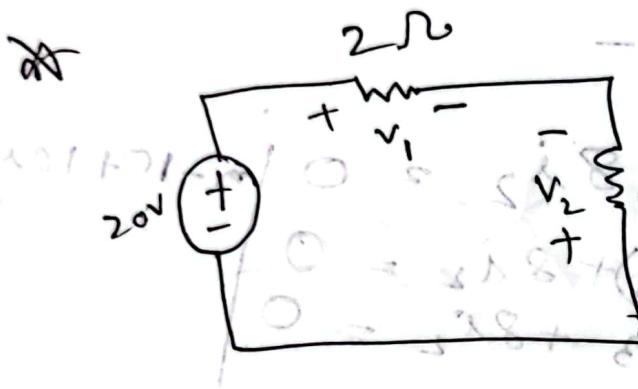

- ① Assign current in all the branches with the directions. $i_1 = \text{IP} = -\alpha$

② Name all the necessary nodes.

③ Assign voltage polarity.

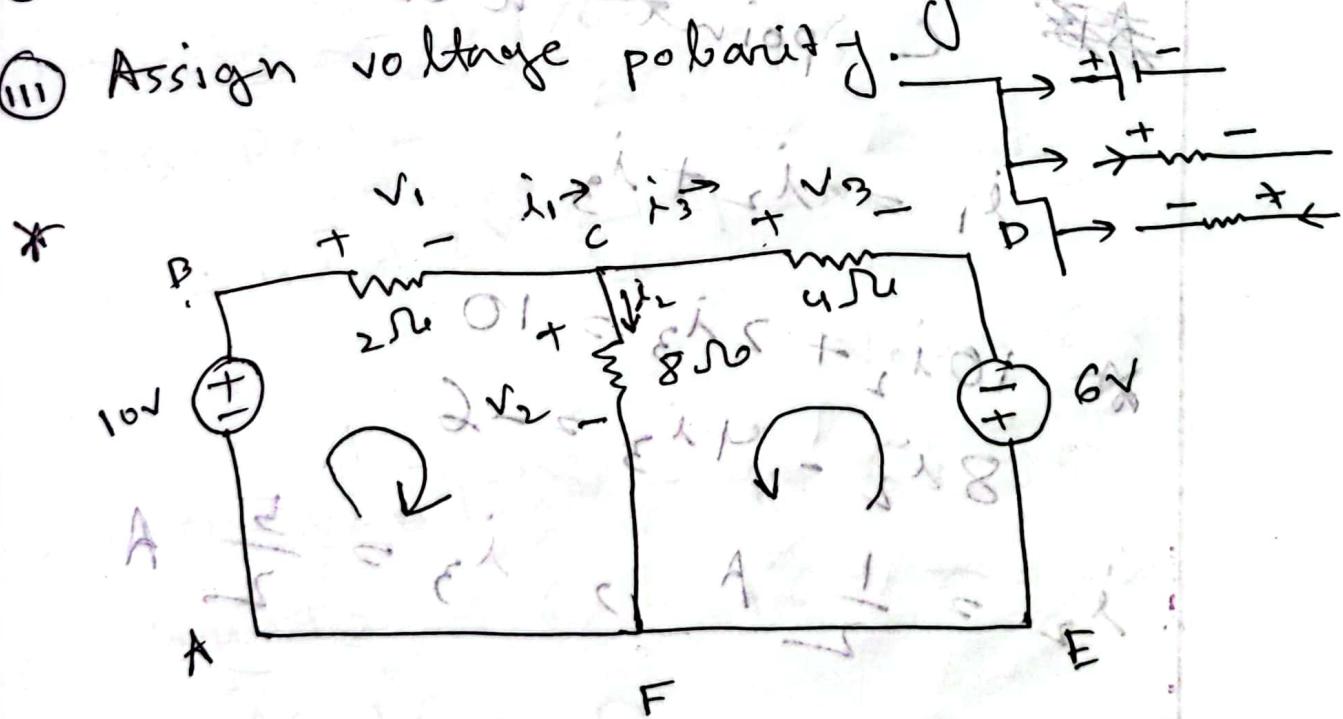

④ Apply KVL in Loop ~~in~~ ⁱⁿ ~~out~~ ^{out} direction.

$$V_{01} = V_D + 1.5 = 1V$$

$$V_P = 3.8 = 5V$$

Loop ABCFA :-

$$-10 + 2i_1 + 8i_2 = 0 \quad \text{--- (1)}$$

$$-10 + 2(i_2 + i_3) + 8i_2 = 0 \quad \text{--- (2)}$$

$$\Rightarrow -10 + 2i_2 + 2i_3 + 8i_2 = 0 \quad \text{--- (3)}$$

F E D C F

$$6 - 4i_3 + 8i_2 = 0 \quad \text{--- (4)}$$

~~C point~~ at C --- N.H. (ii)

~~6 points~~ question required (iii)

$$i_1 = i_2 + i_3$$

$$10i_2 + 2i_3 - 10 = 0 \quad \text{--- (5)}$$


$$8i_2 - 4i_3 = 6 \quad \text{--- (6)}$$

$$i_2 = \frac{1}{2} A, \quad i_3 = \frac{5}{2} A$$

$$i_{1A} = 3 A \quad \text{and} \quad i_{3A} = 5 A \quad \text{--- (7)}$$

$$\therefore V_1 = 2i_1 = 6V, \quad V_3 = 4i_3 = 10V$$

$$V_2 = 8i_2 = 4V$$

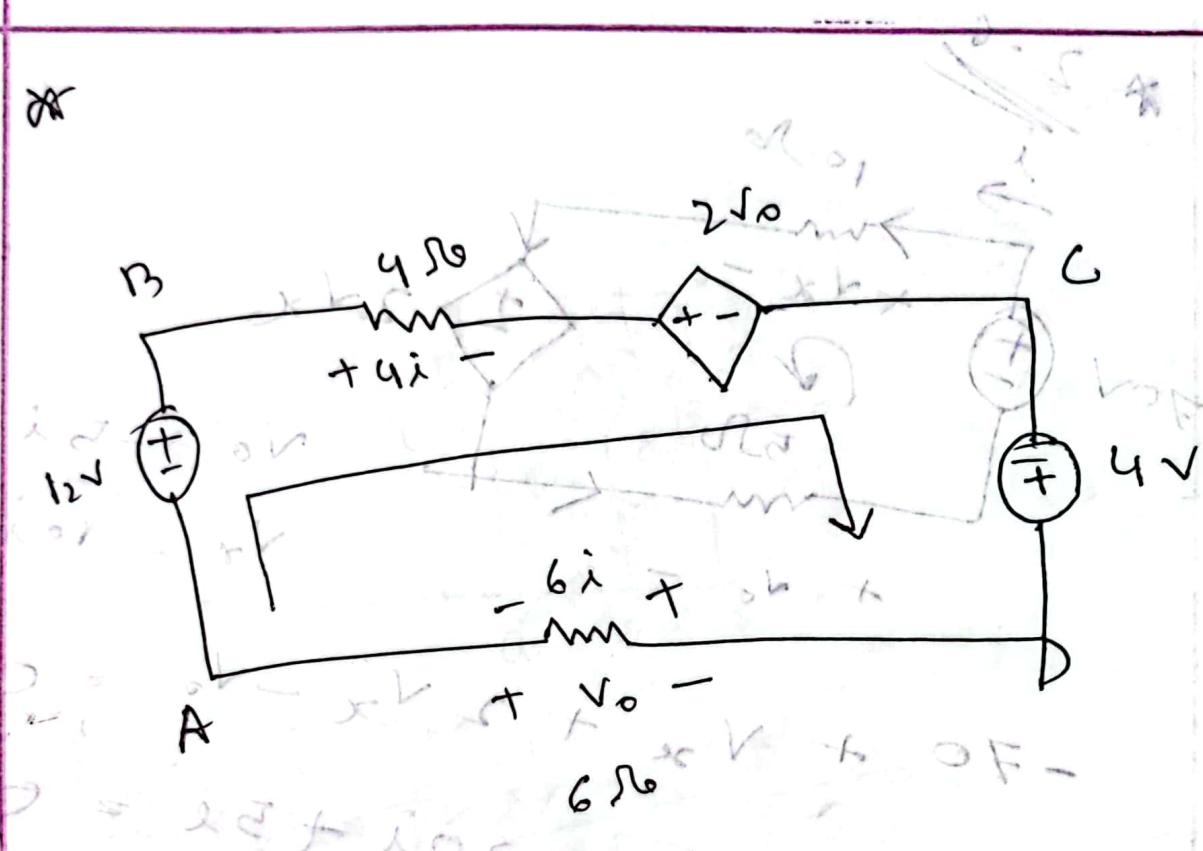

ABCD A°:-

$$-12 + ui + 2v_0 - 4 - v_0 = 0$$

$$-12 + ui + 2v_0 - 4 + 6i = 0$$


$$v_0 = -6i$$

$$\cancel{-12} + ui \cancel{+ 12} - 4 + 6i = 0$$

$$ui - 12i + 6i - 4 = 0$$

$$-2i - 4 = 0$$

$$i = -2A$$

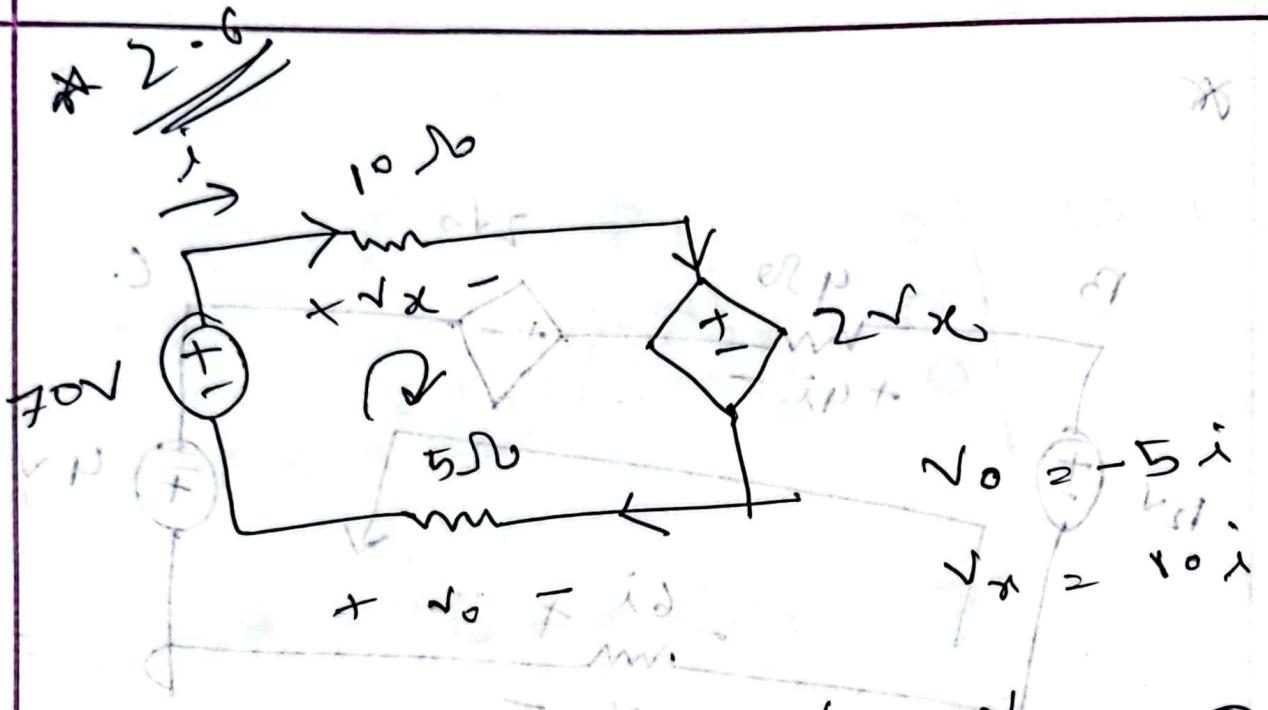

$$-70 + \sqrt{x} i_1 + 2\sqrt{x} i_2 - \sqrt{0} = 0$$

$$\Rightarrow -70 + 10i_1 + 20i_2 + 5i_2 = 0$$


$$\Rightarrow 35i_2 = +70$$

$$\Rightarrow i_2 = 2$$

$$V_o = -10\sqrt{x} = -20V$$

$$17^\circ$$

~~2.7~~

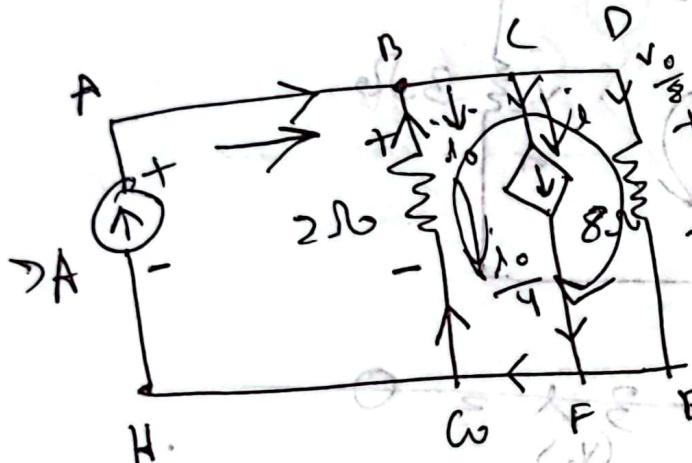

$$V_0 = 8i$$

$$i = \frac{V_0}{8}$$

~~VCL~~: $i_s = V$

$$9 = i_0 + \frac{i_0}{4} + \frac{V_0}{8}$$

~~KVL~~: $i_0 + \frac{i_0}{4} + \frac{2i_0}{8} = 9$

$$6i_0 = 9$$

~~B D E C B~~

~~P~~

~~$V = 6i_0 = 36$~~

$$\cancel{\frac{V_0}{8}} - 2i_0 = 0 \Rightarrow i_0 = 6 \text{ A}$$


$$\Rightarrow V_0 = 2i_0$$

$$\Rightarrow i_0 + \frac{i_0}{4} + \frac{2i_0}{8} = 9$$

$$= r_2 V$$

$$\Rightarrow i_0 + \frac{i_0}{4} + \frac{i_0}{2} = 9$$

Ex: 2.5

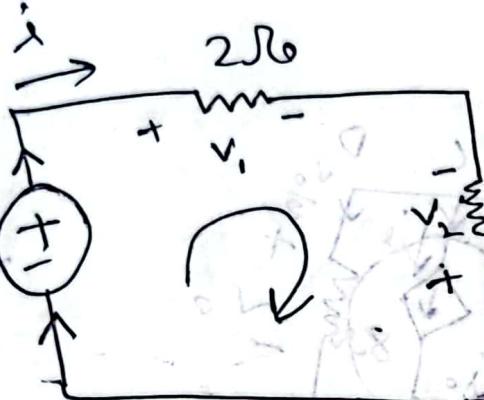

KVL

$$-20 + 2i - 3i = 0$$

~~$$\Rightarrow -i = 20$$~~

~~$$\Rightarrow i = -20$$~~

~~$$V_2 = -40$$~~

~~$$V_2 = 60$$~~

$$V_1 = 2i$$

~~$$V_2 = i - 3i$$~~

$$-20 + V_1 - V_2 = 0$$


$$\Rightarrow -20 + 2i + 3i = 0$$

~~$$5i = 20$$~~

$$\Rightarrow i = 4$$

$$V_1 = 8V$$

$$V_2 = -12V$$

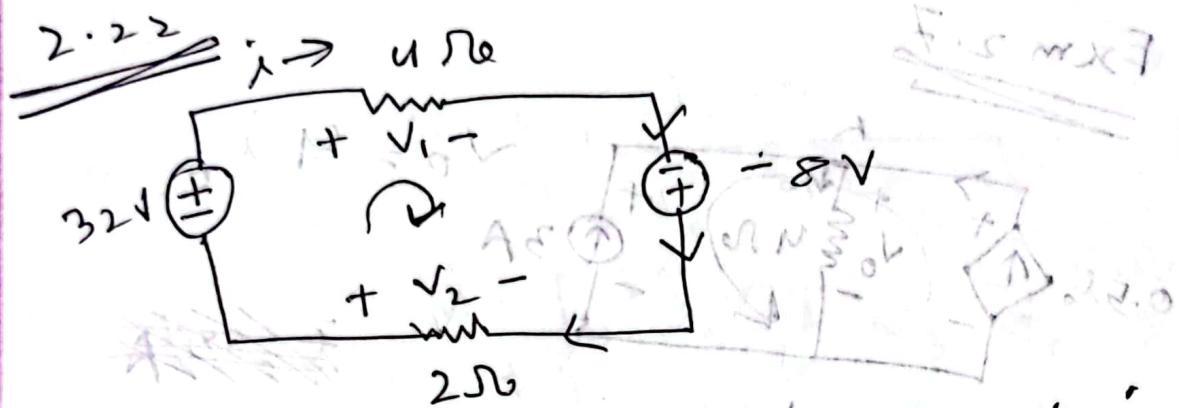

$$-32 + V_1 + 8 - V_2 = 0$$

$$\Rightarrow -32 + 4i + 8 + 2i = 0$$


$$\Rightarrow 6i - 24 = 0$$

$$\Rightarrow i = 4$$

$$V_1 = 16V$$

$$V_2 = -8V$$

Exm 2.7

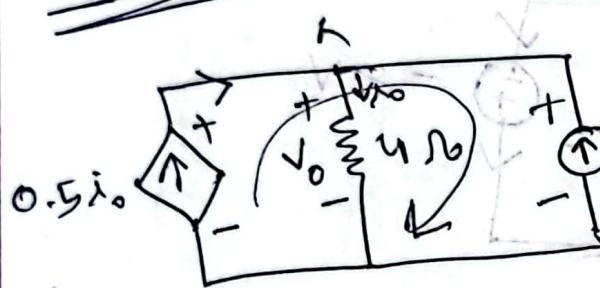

$$-0.5i_0 + 3 = 0$$

$$\Rightarrow i_0 = 6$$

$$V_0 = 24V$$


$$P = 1$$

$$V_{21} = 12V$$

P.T.O

$$V_{82} = 12V$$

~~Exm~~ 2.8

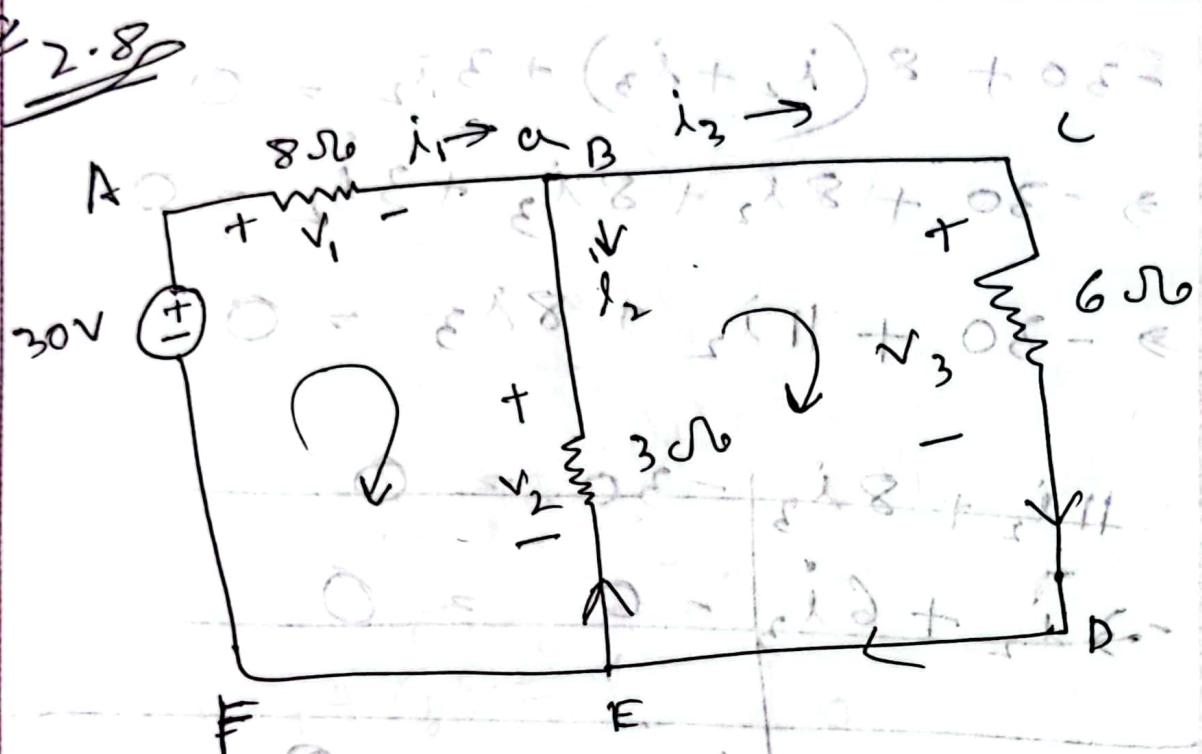

ABEF A Loop

$$-30 + V_1 + V_2 = 0$$

$$V_1 = 8i_1$$

$$V_2 = 3i_2$$

$$\Rightarrow -30 + 8i_1 + 3i_2 = 0$$

B C D E B Loop

$$6i_3 - 3i_2 = 0$$

A E in a point

KCL,

$$i_1 = i_2 + i_3$$

PT.

$$V_3 = \epsilon$$

$$-30 + 8(i_2 + i_3) + 3i_2 = 0$$

$$\Rightarrow -30 + 8i_2 + 8i_3 + 3i_2 = 0$$

$$\Rightarrow -30 + 11i_2 + 8i_3 = 0$$

$$\cancel{11i_2 + 8i_3} \mid -30 = 0$$

$$\cancel{-3i_2 + 6i_3} \mid -0 = 0$$

$$\cancel{8i_2 + 14i_3} \mid 30 = 0$$

BY ELIMINATION

$$11i_2 + 8i_3 = 30$$

$$-3i_2 + 6i_3 = 0$$

$$i_2 = 2A \quad i_3 = 3A$$

$$i_1 = 3A$$

$$i_1 = 24V$$

$$i_2 = 6V$$

$$i_3 = 6V$$

1.15

(e) $v = \int i dt$

$$v = \left[6e^{-2t} \right]_0^{\infty}$$

$$\rightarrow 2 \cdot 945e^{-\infty} \cdot mF$$

(d) $v = 10 \frac{d}{dt} 6e^{-2t}$

$$= 10 \cdot 6e^{-2t} \cdot -2$$

$$= -120 e^{-2t}$$

$$P = \sqrt{i} = 6e^{-2t} \cdot -120 e^{-2t}$$

$$= -720 e^{-4t}$$

A

(c)

$$E = \int p dt$$

$$\Rightarrow \int -720 e^{-4t} dt$$
$$\Rightarrow -720 \cdot \frac{e^{-4t}}{-4}$$

$$\Rightarrow -180 \cdot e^{-4t}$$

$$fs = 300 \cdot \frac{6}{fb} \cdot 01 = 60$$

$$fs = 300 \cdot 01$$

$$fs = 300 \cdot 1$$

$$fs = 300 \cdot 1 - fs = 300 - 60 = 240$$

$$fP = 300 \cdot 1 = 300$$

Ans

~~11.2 23~~

~~C.T - 1~~

Feb - 18


Lecture - 2, 2
Chapter 2 Part - 1

~~2.22~~

$$V_o = i \cdot 10T$$

~~10Ω + 10Ω + 10Ω~~

~~10Ω + 10Ω + 10Ω~~

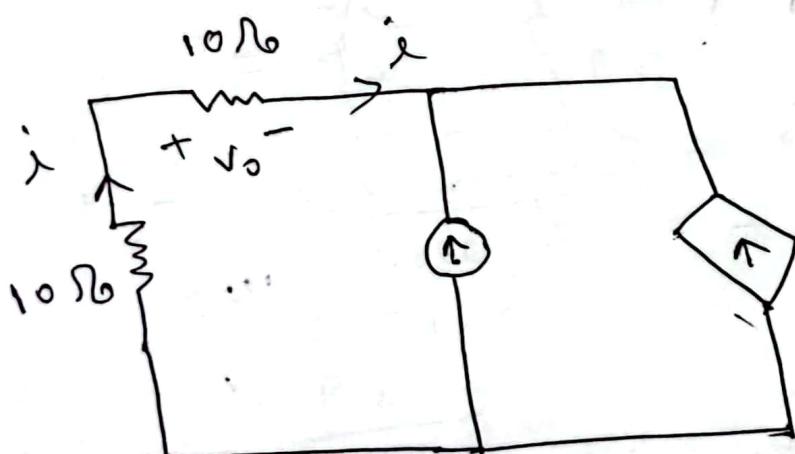

$$25 = 2V_o + \cancel{10i}$$

$$i_1 = \frac{V_o}{10}$$

$$V_o = 10i$$

$$\therefore i = \frac{V_o}{10}$$

$$25 + 2V_o + i = 0$$

$$\Rightarrow 25 + 2V_o + \frac{V_o}{10} = 0$$

$$\Rightarrow V_o = -11.90 \text{ V}$$

~~2-23~~

B

~~1-7-0~~

81 - dist


$$i_1 + i_2 = 2 \rightarrow i_1 \text{ (outward)}$$

$$0 = I_2 + 3 + 7 \rightarrow I_2 = -10$$

$$I_2 = -10$$

$$7 + I_4 = I_3$$

$$2 = I_4 + 4$$

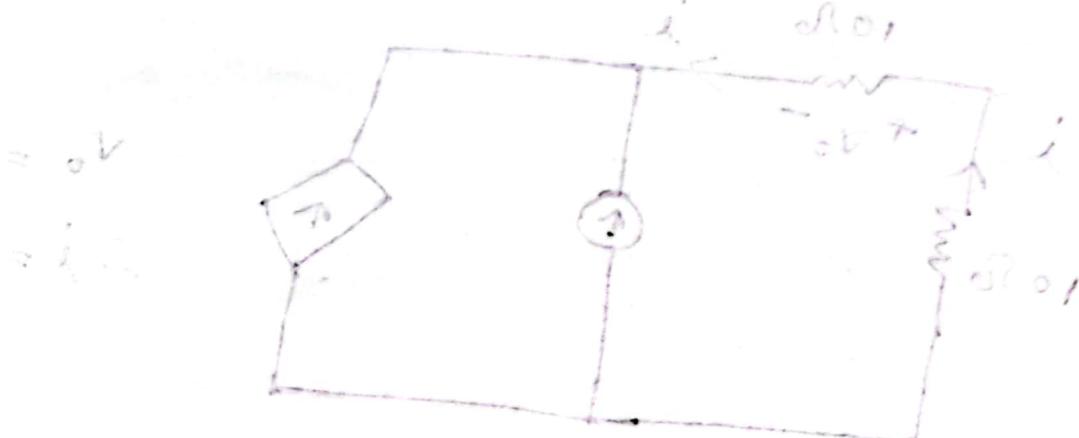

$$0 = i_1 + i_2 + i_3$$

$$0 = \frac{v}{3} + 2v + 2v \rightarrow v = 0$$


$$V_{D.C} = 3 \times 0 = 0$$

$$* \frac{V_1}{V_2} = \frac{IR_1}{IR_2} = \frac{R_1}{R_2}$$

$$* V_1 = \frac{R_1}{R_1 + R_2} V$$

$$* V_2 = \frac{R_2}{R_1 + R_2} V$$

for Parallel:

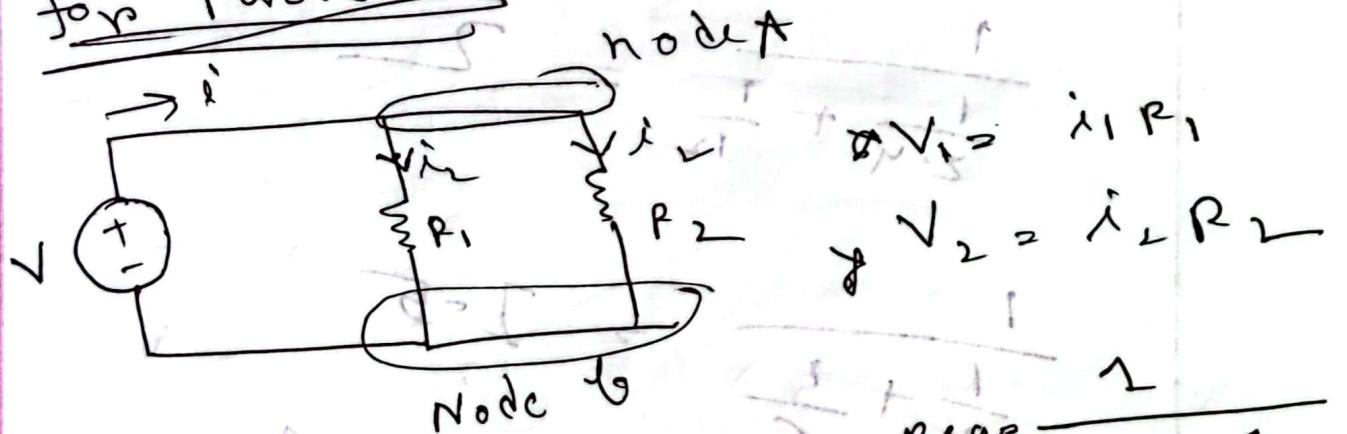

$$* \frac{i_1}{i_L} = \frac{R_2}{R_1}$$

$V = V$
(Voltage Same)

~~2-70~~

~~2-9~~

~~4-15-23~~

656

$$\frac{1}{\frac{1}{6} + \frac{1}{n}}$$

$$\frac{1}{\frac{1}{6} + 2 - 4}$$

$$\frac{1}{\frac{1}{2-4} + \frac{1}{12}} = \frac{1}{2}$$

Follows 9 out of 10




$$\frac{1}{\frac{1}{12} + \frac{1}{6}} = 1-5$$

Follows 9 out of 10

$$\cancel{2-8-7-5} = 0.$$

$$0. \frac{5}{9} = 0.5555555555555555$$

(last pattern)

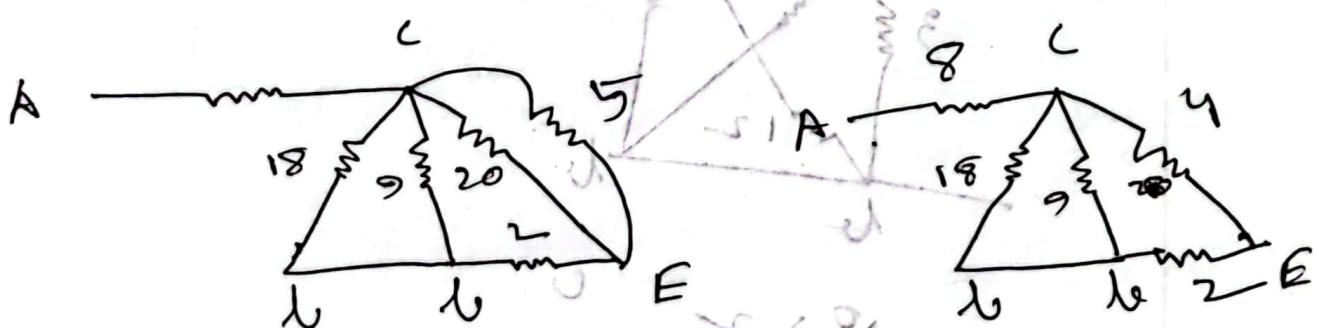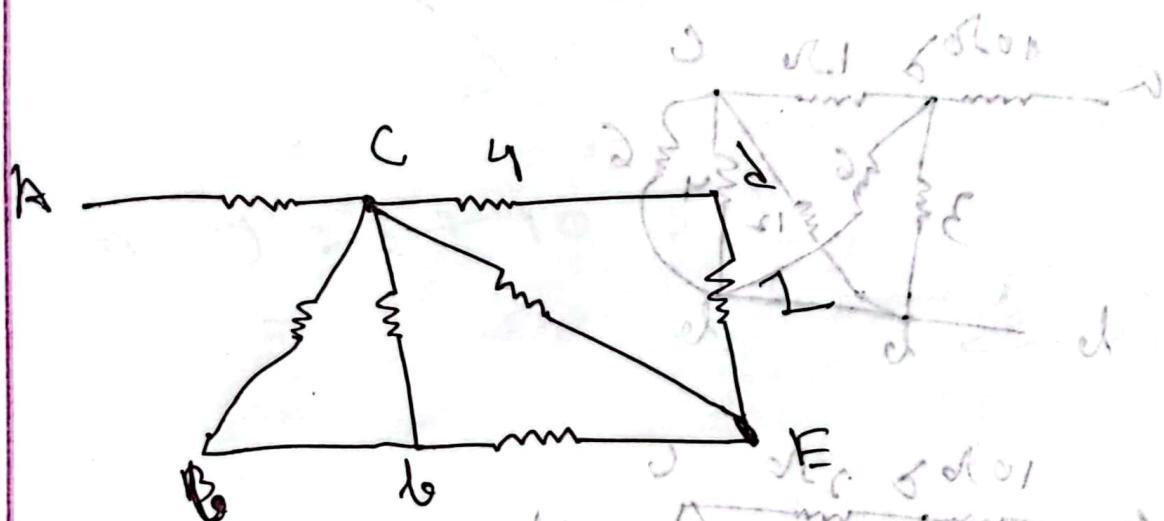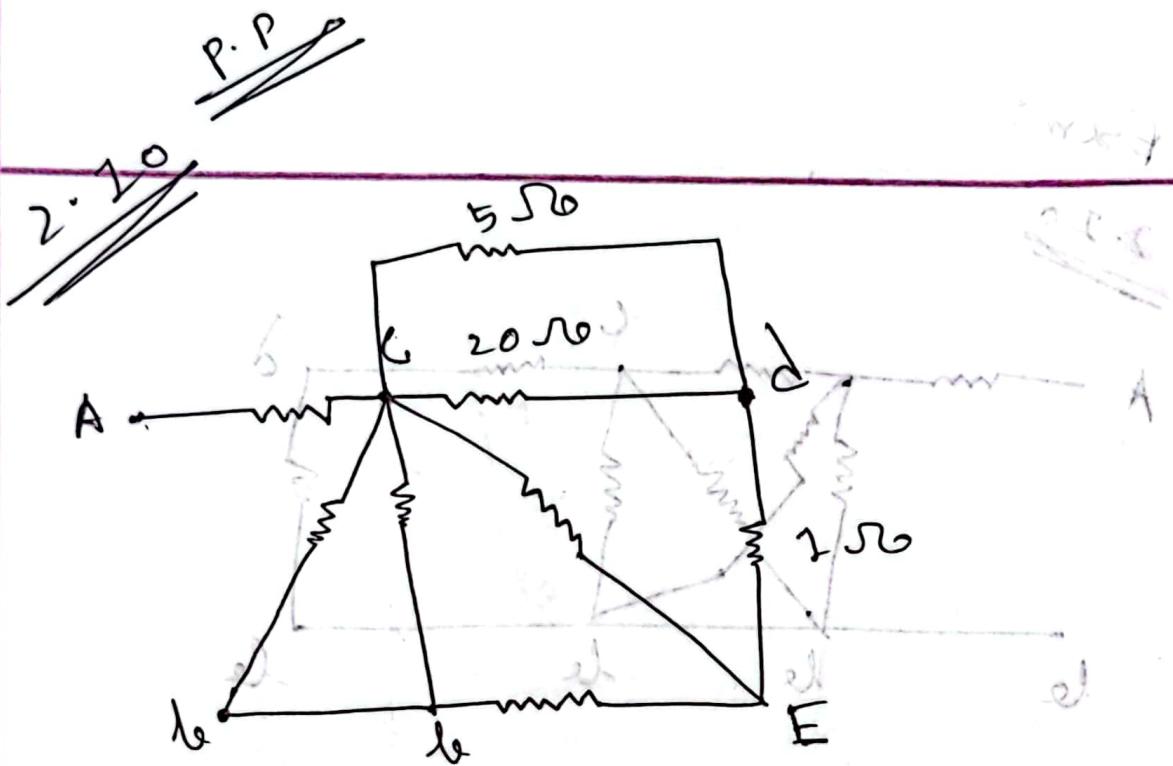

$$\begin{aligned}
 & 10.67 \\
 & \approx 11 \\
 & \frac{1}{\frac{1}{8} + \frac{1}{n}} = 2.67 \\
 & \underline{\text{P.T.}}
 \end{aligned}$$

Exm:

2.10

A

C

D

A

b

b

b

b

b

a

10Ω

15Ω

c

b

b

15Ω

A

a

10Ω

2Ω

c

2.4

b

b

c

A

a

10

2Ω

2Ω

c

2


b

b



c

fd. Jy


11.5

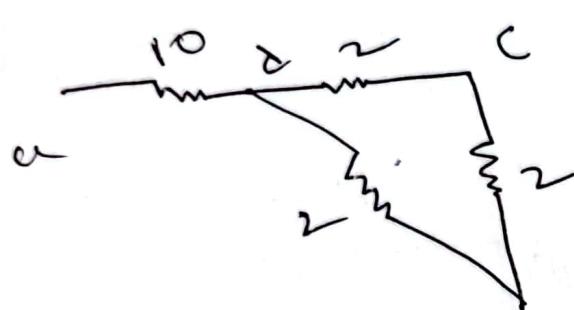
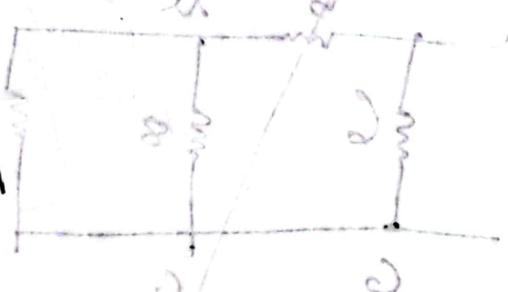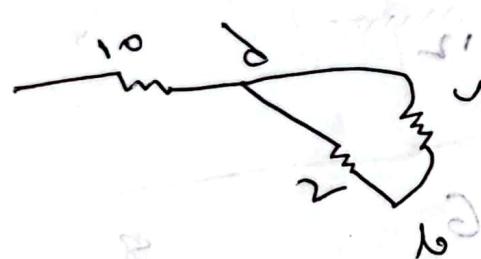
$$\frac{1}{R_{eq}} = \frac{1}{10} + \frac{1}{2} \Rightarrow R_{eq} = 2.33 \Omega$$




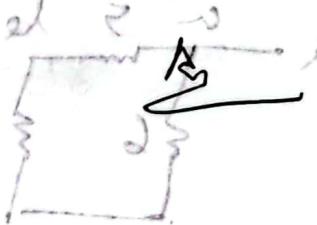
$$\Rightarrow 2.33 + 10 \Rightarrow 11.33 \Omega$$



~~6V
13.2 2.2~~

Ec


~~2.0 12~~

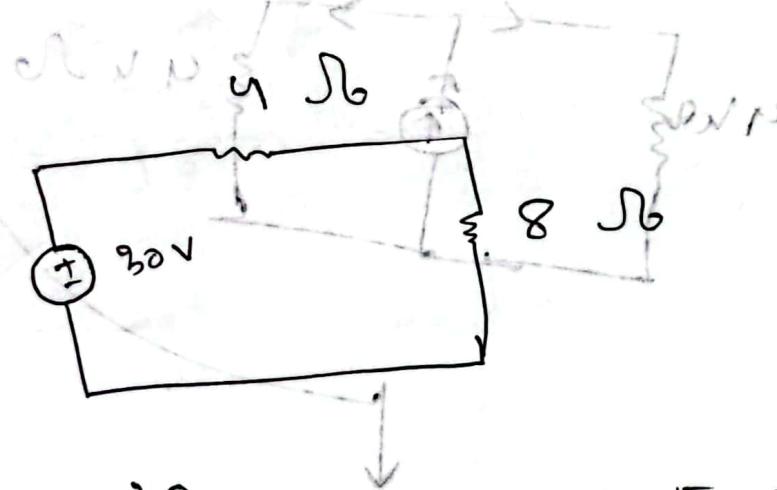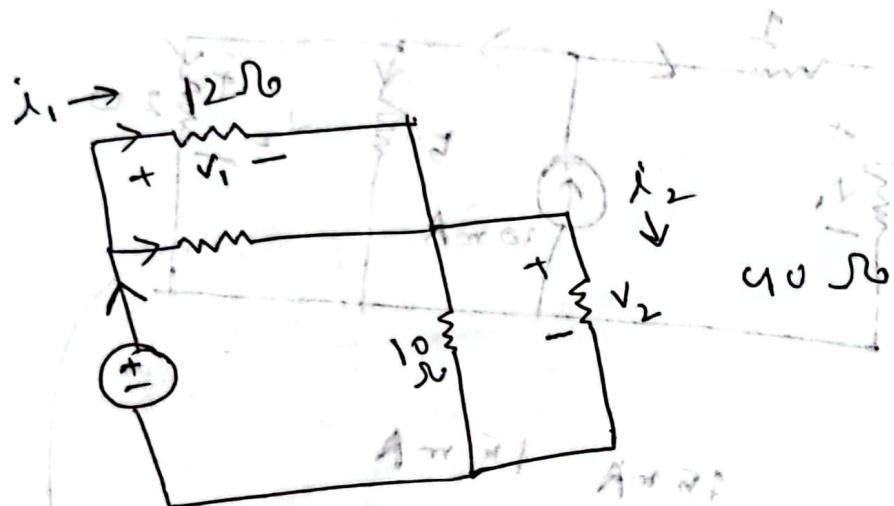

$$I = \frac{30}{4+8} = 2.5 \text{ A}$$

$$\lambda_1 = \frac{1}{2+1} \times 2.5 = 0.833$$
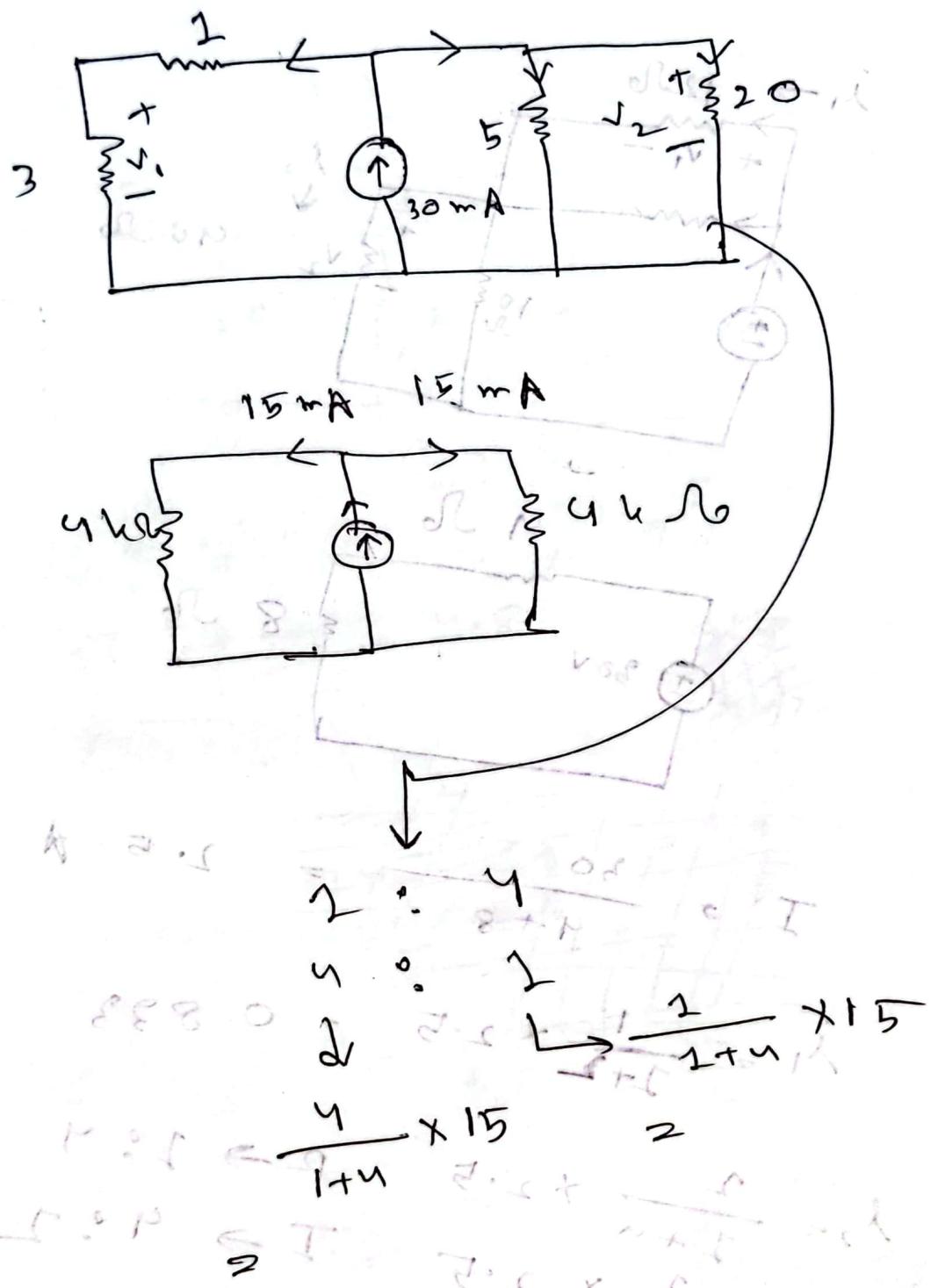
$$\begin{aligned}\lambda_2 &= \frac{2}{2+4} + 2.5 \rightarrow 1.0 \\ &= \frac{2}{5} \times 2.5 \quad I \rightarrow 4 : 2 \\ &= 2\end{aligned}$$



$$V_1 = 3 \times 15$$

$$= 45 \text{ V}$$

20.00 A.C. coil

$$V_2 = 3 \times 20$$

$$60 \text{ V}$$

$$P = (300 \times 60) \text{ W}$$

$$= 1800 \text{ W}$$

20.00 A.C. coil

$$200 \text{ V}$$

$$+2.0$$

$$52.0 \text{ V}$$

$$H = 120$$

$$\cancel{P.T.O}$$



$$F.S. + P$$

A 20.00 A.C. coil
A 100.0 A.C. coil


$$R \rightarrow 2^{\circ} 2$$

$$T \rightarrow 2^{\circ} 1$$



~~2.31~~

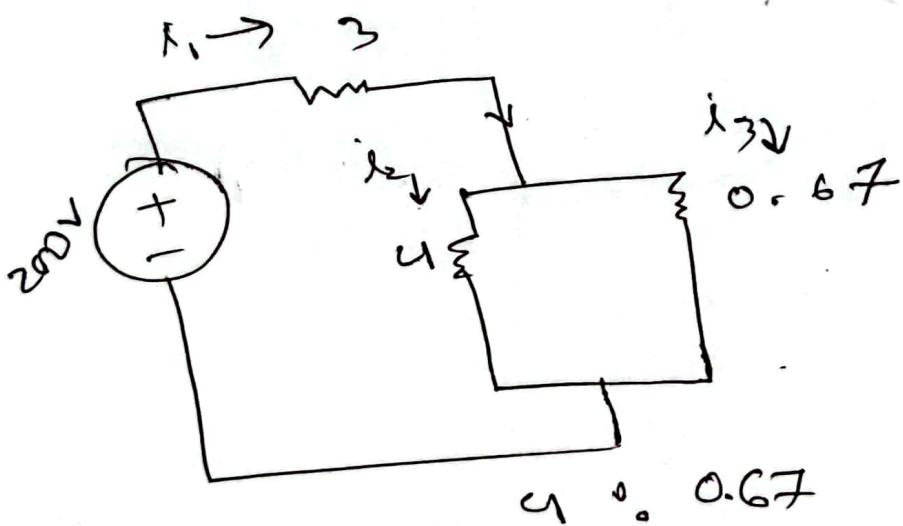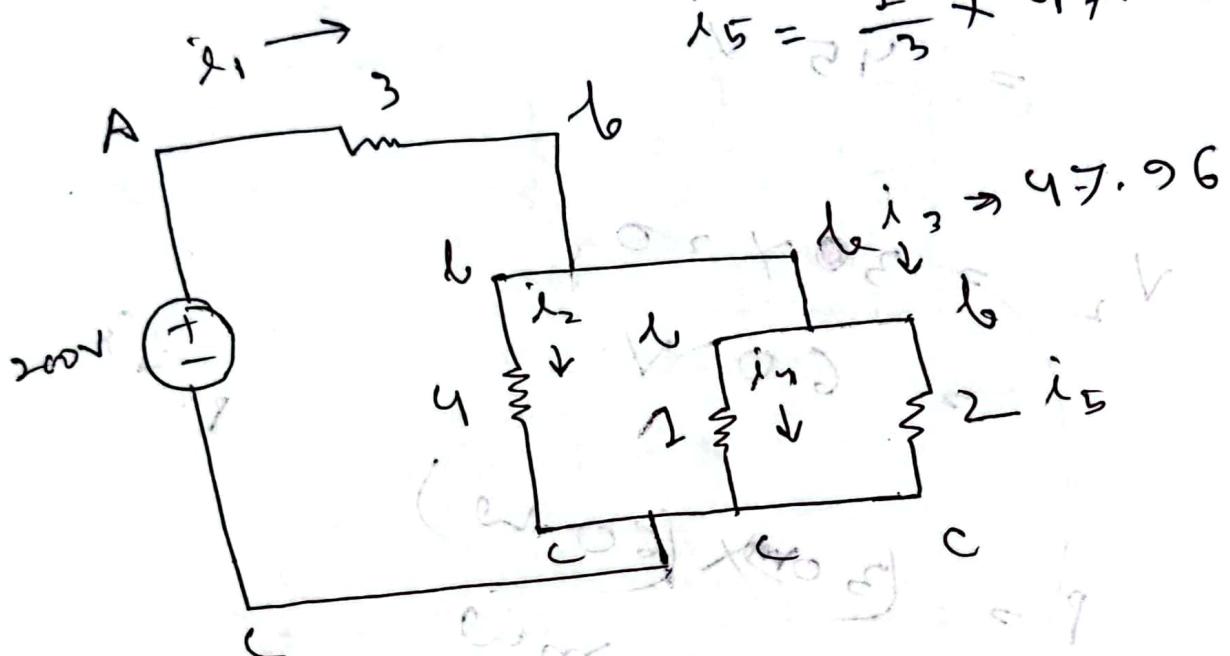

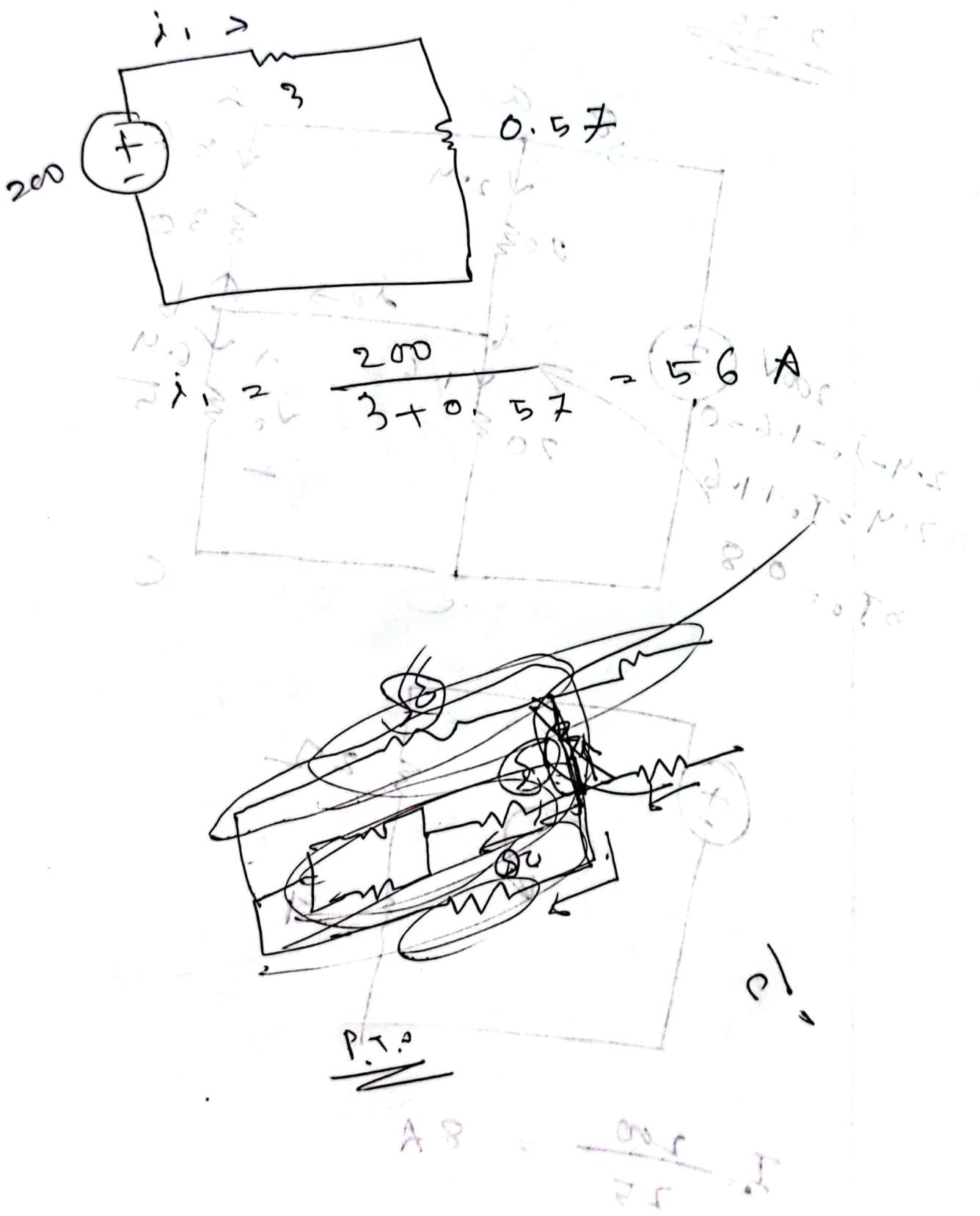
$$i_2 = \frac{0.67}{4 + 0.67} \times 56 = \frac{9}{4.67} \times 56 = 47.96 \text{ A}$$



~~2.35~~

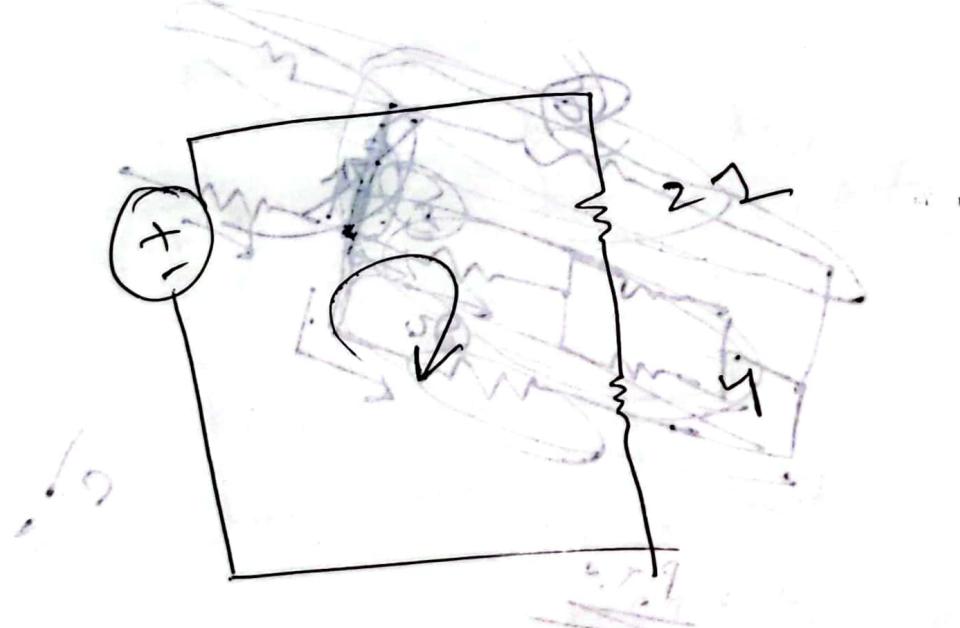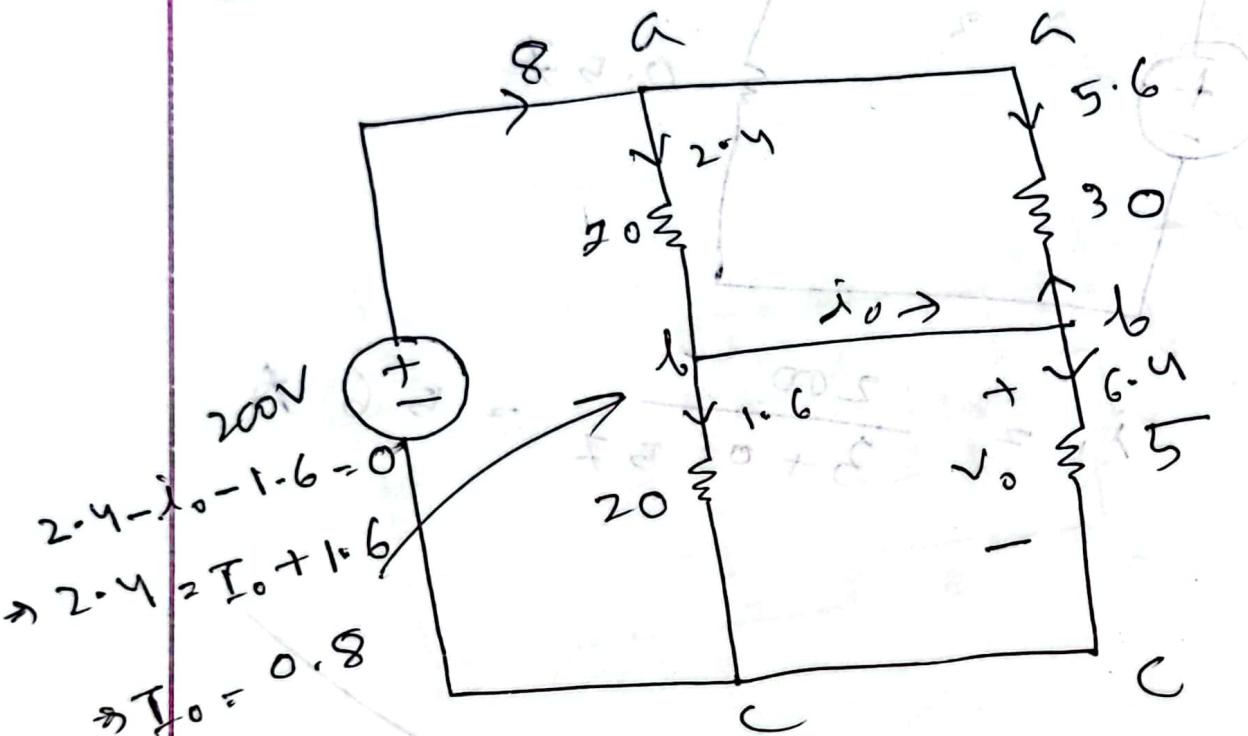


$$I_0 = \frac{200}{25} = 8A$$

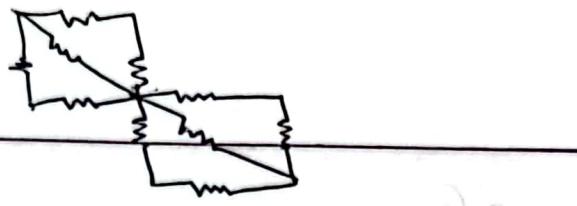

70 30

7 0 3

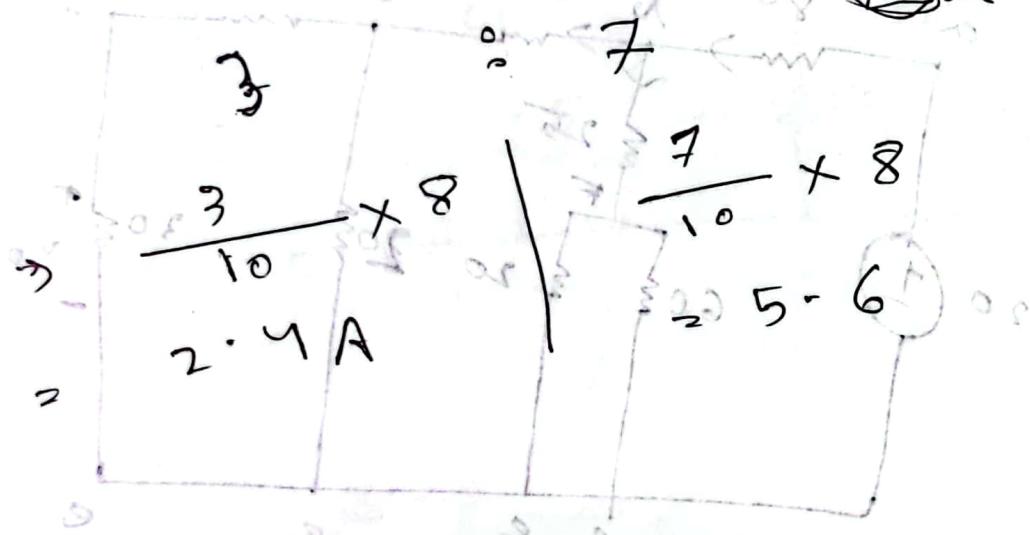


R → 20 : 5
 4 : 2

A - 5.0 = $\frac{0.5}{10}$ 4 $\times \frac{4}{5} = 1$

$\Rightarrow \frac{1}{5} \times 8$ $\frac{4}{5} \times 8$
= 1.6 = 6.4

~~2.36~~

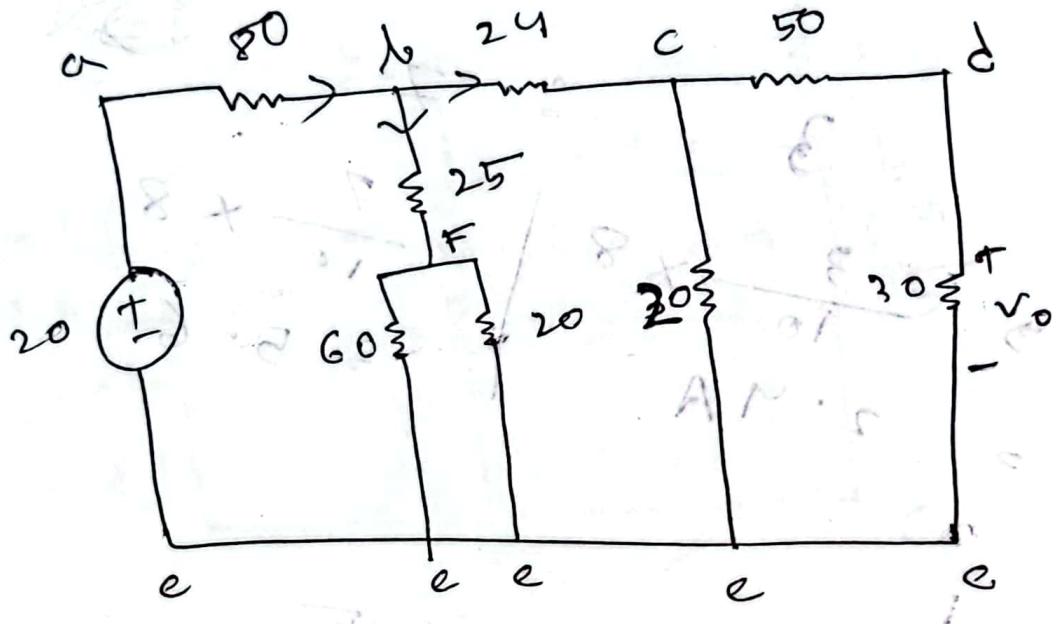

$$R = 100 \Omega$$

$$I = \frac{V}{R} = \frac{20}{100} = 0.2 \text{ A}$$



$$8 \times \frac{1}{2} = 4$$



$$8 \times \frac{1}{2} = 4$$

~~600~~
14.2.23


EC

*

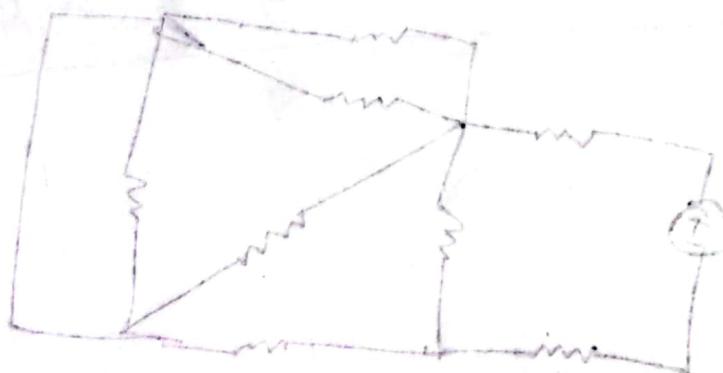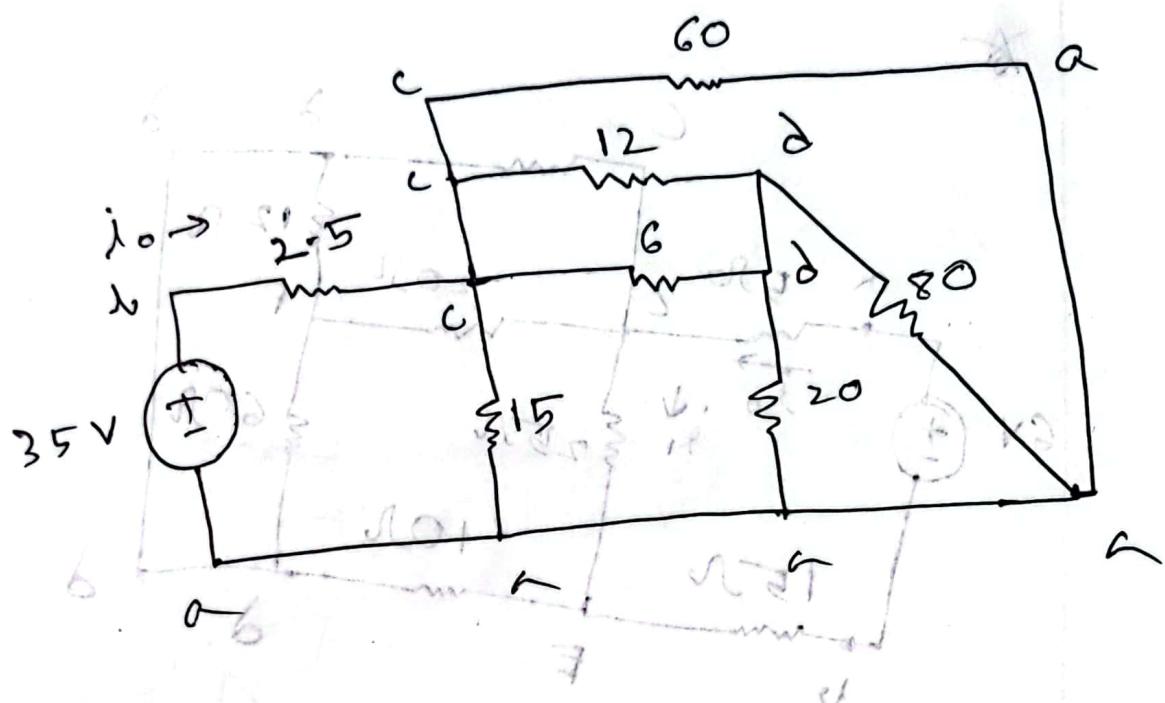

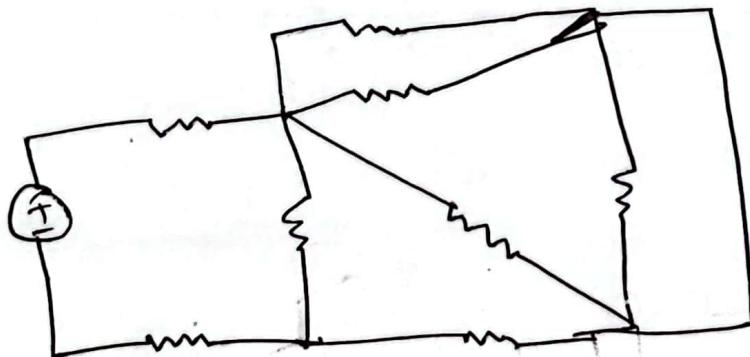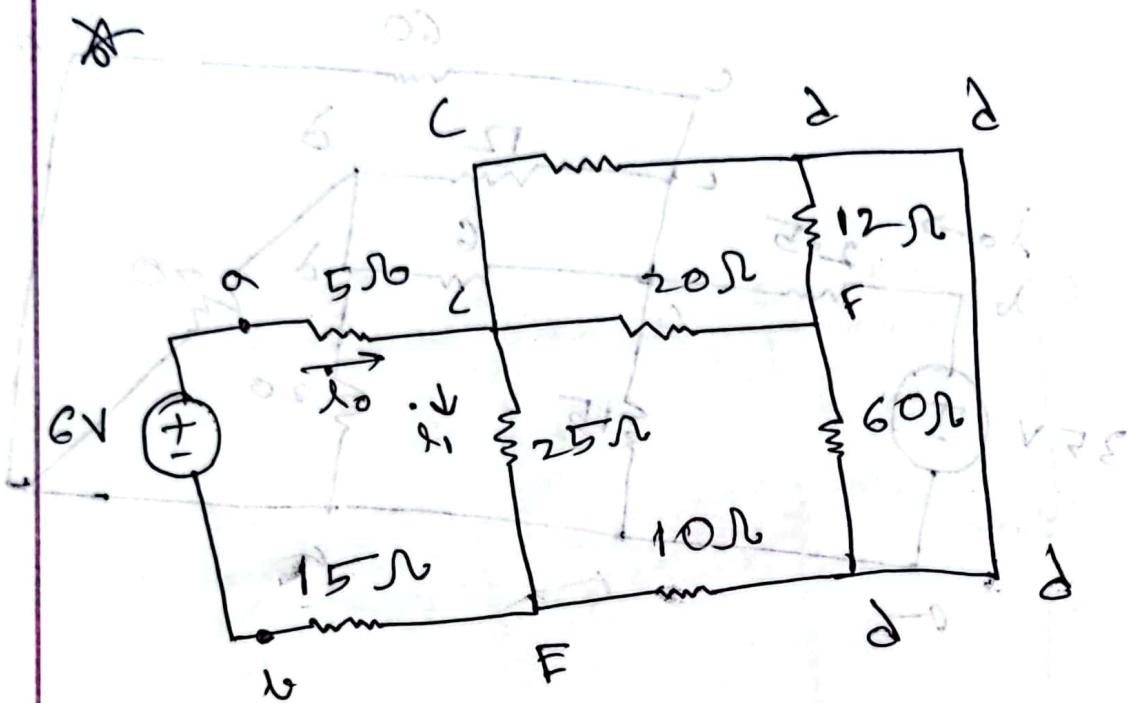

* Formulae

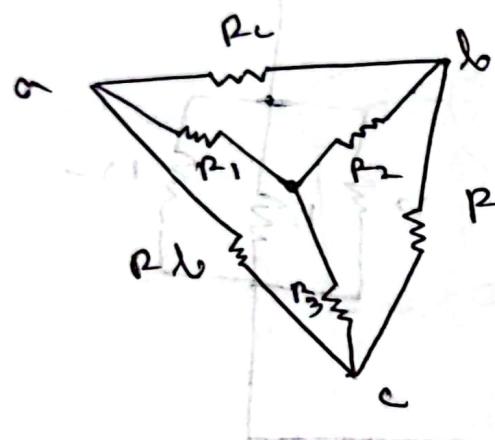

$\Delta \rightarrow J$

$$R_1 = \frac{R_L R_C}{R_L + R_C + R_C}$$

$$J \rightarrow \Delta : R_A = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$\sigma = 1 + e^{-\frac{\phi}{k}}$$


$$\sigma = 1 + \phi - \sqrt{k}$$

$$\phi = S = \sqrt{k}$$

$$\sigma = 1 + \phi + \ln S$$

$$\sigma = S - \ln \phi$$

$$\phi = S - \ln \sigma$$

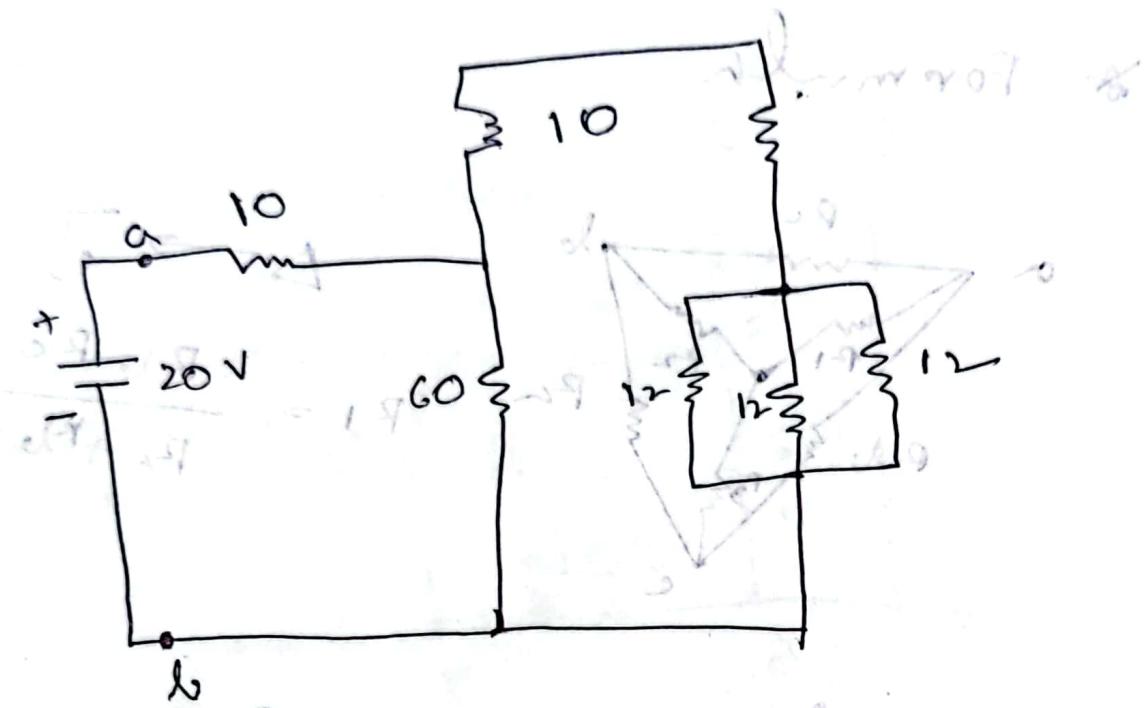

~~$$2 \cdot 17 = 34$$~~

$$V_3 = -10 \text{ V}$$

b

$$V_2 + V_3 + 12 = 0$$

$$\Rightarrow V_2 - 10 + 12 = 0$$

$$\Rightarrow V_2 = -2$$

$$-24 + V_1 - V_2 = 0$$

$$\Rightarrow V_1 - 22 = 0$$

$$\Rightarrow V_1 = 22$$

2.18

$$-30 + 3i - 10 + 5i + 8 = 0$$

$$\Rightarrow -40 + 8i + 8 = 0$$

$$\Rightarrow -32 + 8i = 0$$

$$\Rightarrow \cancel{0} i = 32$$

$$-V_{ab} + 20 + 8 = 0$$

$$V_{ab} = 28 \text{ V}$$

A

$$= 20$$

$$-20 = 8 + i\omega + dv$$

$$0 = 8 + i\omega - dv$$

$$P_2 \propto V_i$$

~~1~~

~~2~~

$$6 - 3 - 2 - I_o = 0$$

$$\Rightarrow 2 = I_o$$

$$\Rightarrow I_o = 2$$

$$5 \times 2 = 10V = V$$

$$V_o = 20V$$

$$-7 + V_p + 10 = 0$$

$$\Rightarrow V_p = -3$$

A

$$+1+0 \quad 1+0 \xrightarrow{1} \cancel{0+1=0}$$

2
1



$$\frac{(-1)^n + 1}{2}$$

$$-v_0 + 5 - 10 \rightarrow$$

$$\rightarrow -v_0 - 5 \rightarrow 0$$

$$\rightarrow v_0 = -5$$

~~$$-7 + v_p - 5 \rightarrow 0$$~~

$$\rightarrow v_p = 12$$

$$q_r = \int idt \quad \text{or} \quad q_r = \frac{1}{P} \int_{0}^{T} i dt$$

$$\frac{dV}{dt} = \frac{dV}{P} \cdot \frac{P}{dt} = \frac{dV}{P} \cdot \frac{P}{T} = \frac{dV}{T}$$


$$Q_r = \int V dt \quad \text{or} \quad Q_r = \frac{1}{P} \int_{0}^{T} V dt$$

6W

Basics of Circuit Analysis

EC

Node Analysis

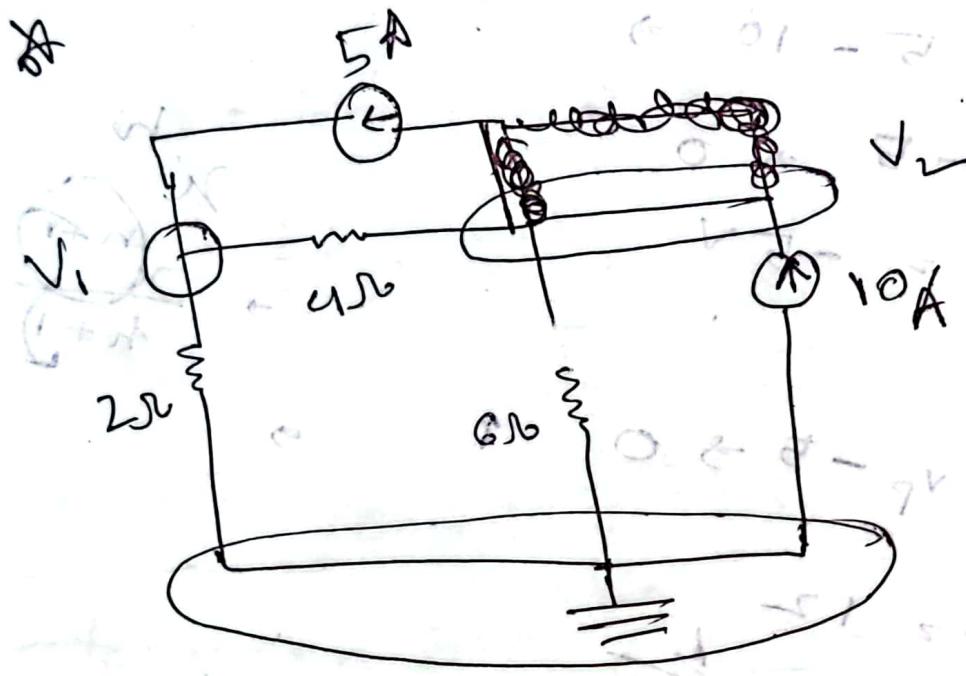


$$\frac{V_1 - 0}{2} + \frac{V_1 - V_2}{4} = 5 \quad \cancel{\text{At } V_2 = 0}$$

$$5 + \frac{V_2 - 0}{6} = 10 + \frac{V_1 - V_2}{4}$$

$$\Rightarrow -3V_1 + 5V_2 = 60$$
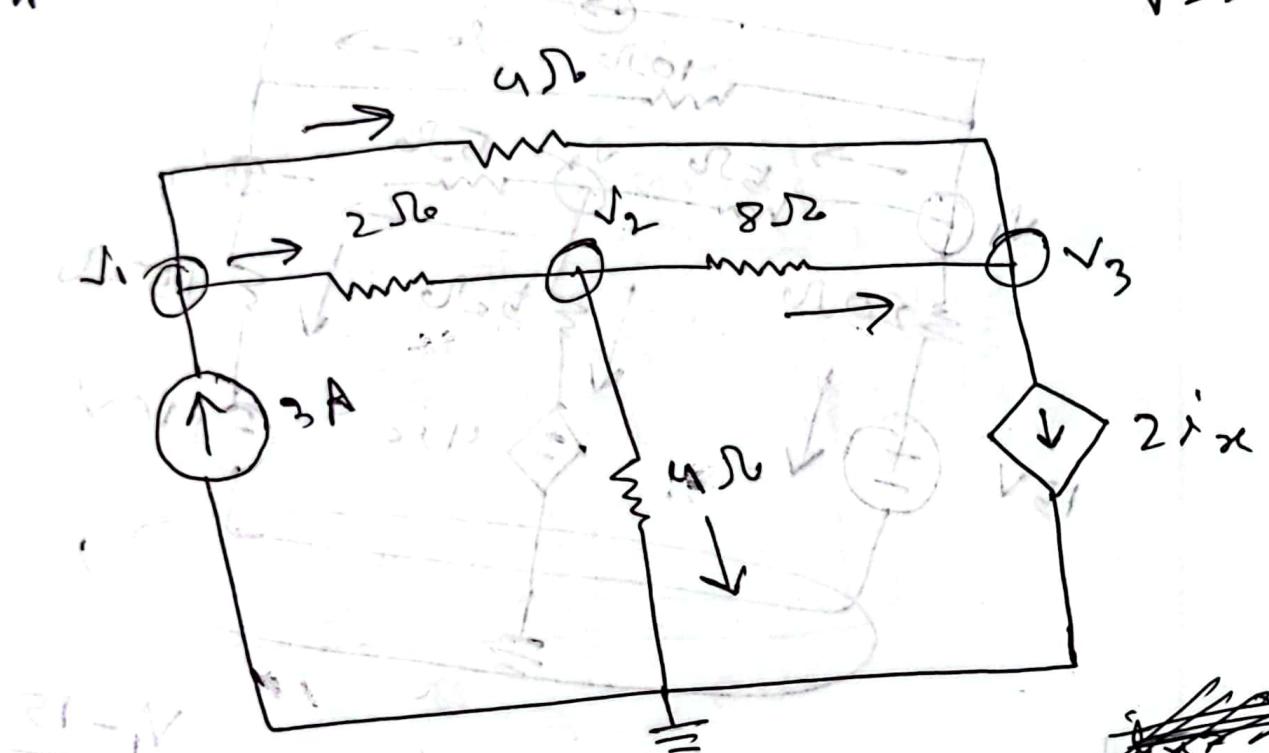
$$i_x = \frac{v_1 - v_2}{2} \quad V_2 = IR$$



~~$$V_1$$~~

$$3 = \frac{v_1 - v_3}{4} + \frac{v_1 - v_2}{2}$$


~~$$V_2 = ?$$~~

$$\frac{v_1 - v_2}{2} = \frac{v_1 - 0}{4} + \frac{v_2 - v_3}{8}$$

~~$$V_3:$$~~

$$\frac{v_2 - v_3}{8} + \frac{v_1 - v_3}{4} = 2i_x$$

$$j_0 = \frac{v_1 - v_3}{10}$$

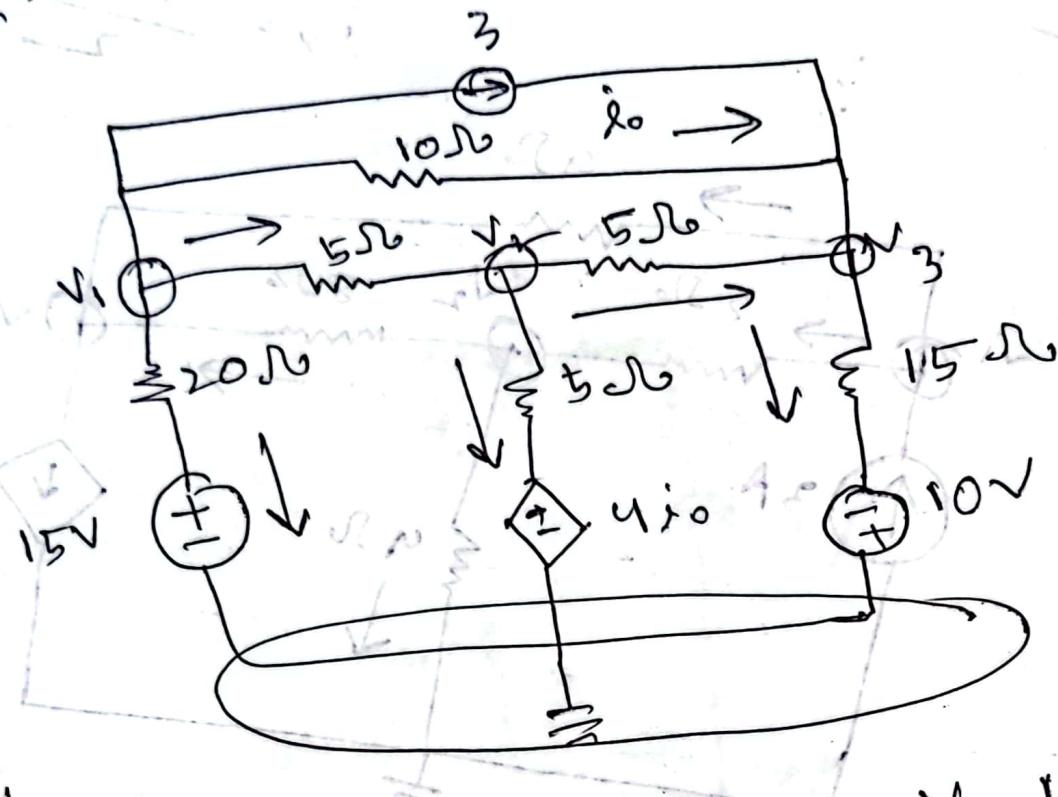


$$3 + \frac{v_1 - v_3}{10} + \frac{v_1 - v_2}{5} + \frac{v_1 - 15}{20} = 0$$

~~$$\frac{v_1 - v_2}{5} + \frac{v_2 - 4j10}{5} + \frac{v_2 - v_3}{5}$$~~

~~$$3 + \frac{v_1 - v_3}{10} + \frac{v_2 - v_3}{5} = \frac{v_3 - (-10)}{15}$$~~

$$6\omega \\ 25 \cdot 2 \cdot 2^2$$

$$\frac{5L}{R} \frac{D^2}{R}$$

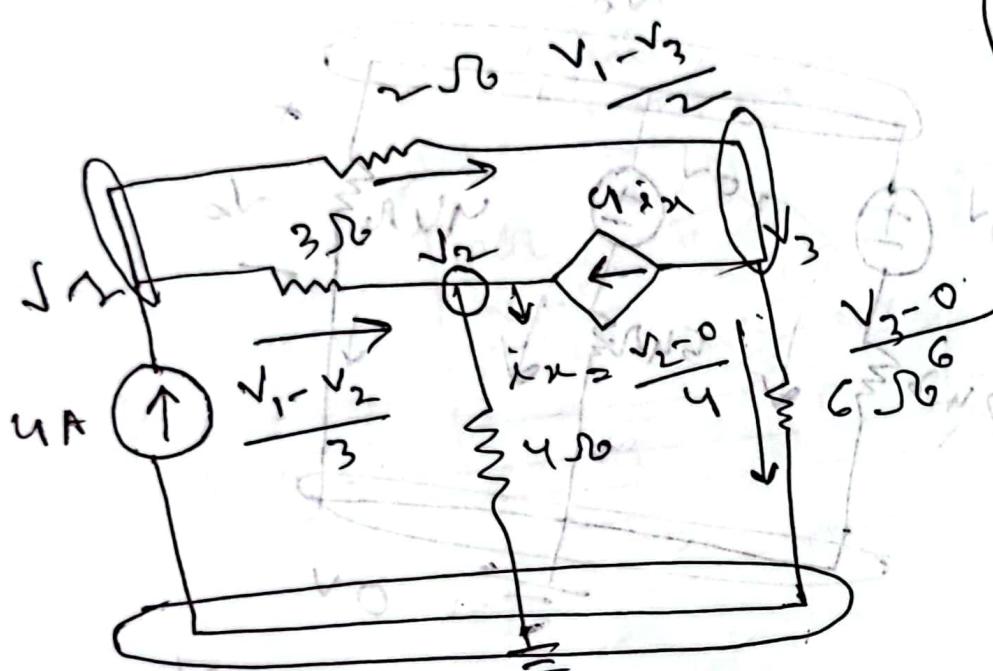

$$V = \frac{V_1 - V_2}{3} + \frac{V_1 - V_3}{2}$$

$$\cancel{V_2 = 0}$$


$$i_x = \frac{V_2}{4}$$

$$\frac{V_1 - V_3}{3} + 4i_x = \frac{V_2}{4}$$

$$\cancel{V_3 = 0}$$

$$\frac{V_1 - V_3}{2} = 4i_x + \frac{V_3}{6}$$


~~3.5~~

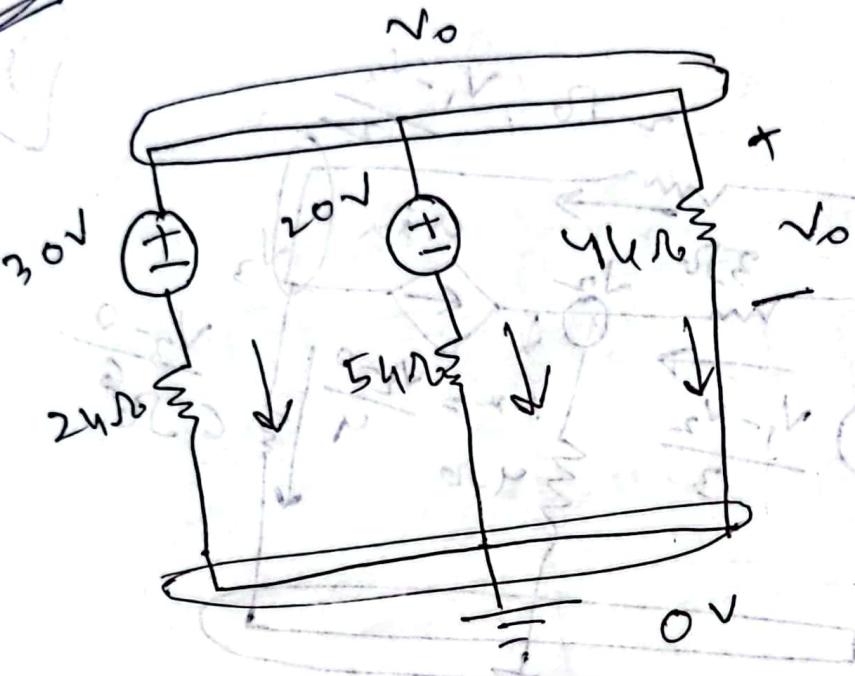

$$\frac{V_o - 30}{2k\Omega} + \frac{V_o - 20}{5k\Omega} + \frac{V_o}{4k\Omega} = 0$$


$$\frac{V_o}{2k\Omega} = \sin \theta + \frac{V_o - 20}{5k\Omega}$$
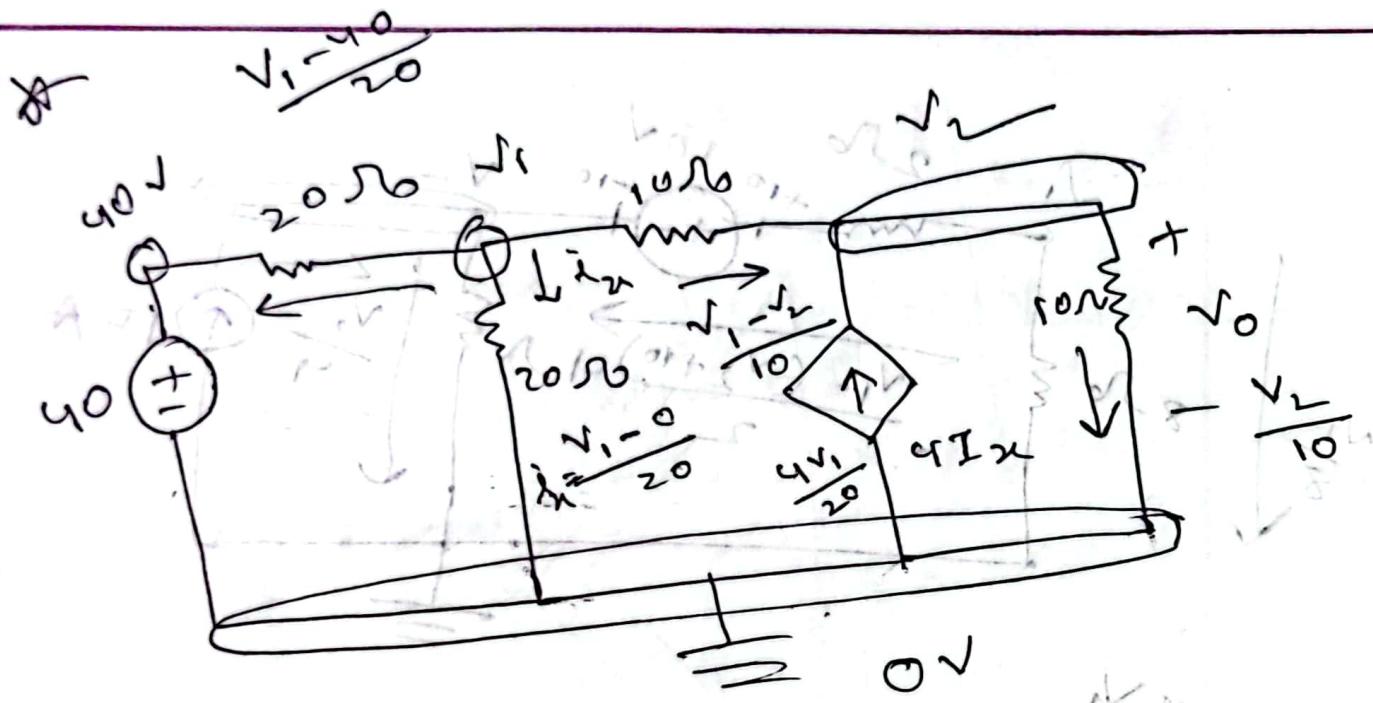
$$\frac{V_o}{2k\Omega} = \sin \theta + \frac{V_o - 20}{5k\Omega}$$



$$\frac{V}{P} = \sqrt{f} \cdot \sqrt{0.1 - \frac{V_r}{V}} \cdot \sqrt{qIX}$$


PT.0

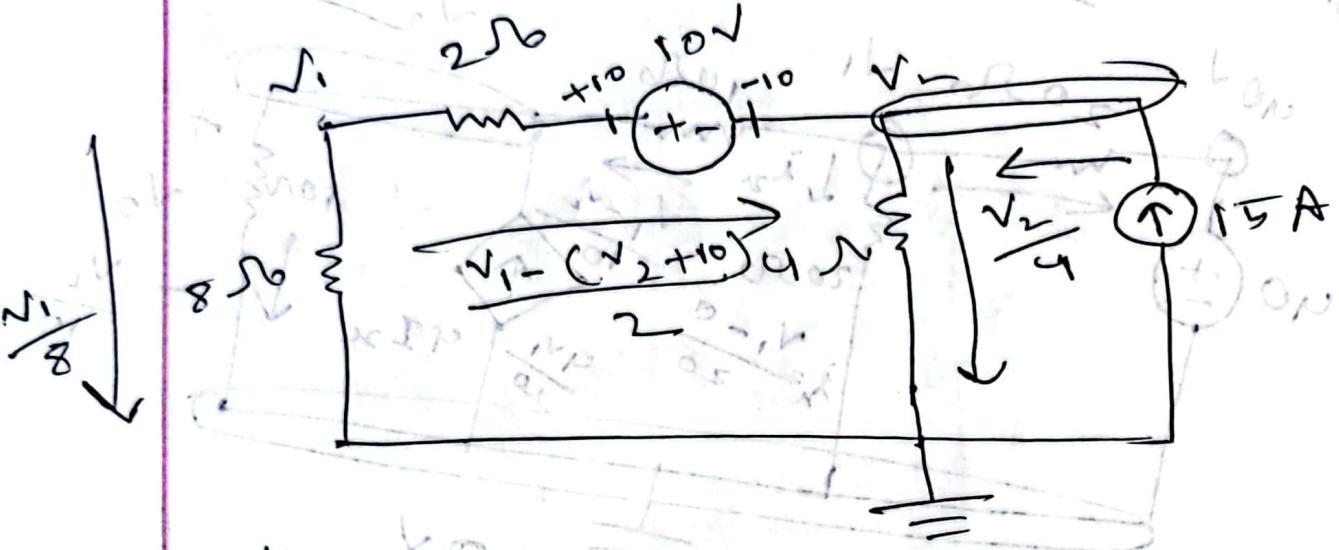

$$\frac{V_1}{8} + \frac{V_1 - V_2 - 10}{2} = 0$$

$$\frac{V_1 - V_2 - 10}{2} + 15 = \frac{V_L}{2}$$

P.T.O

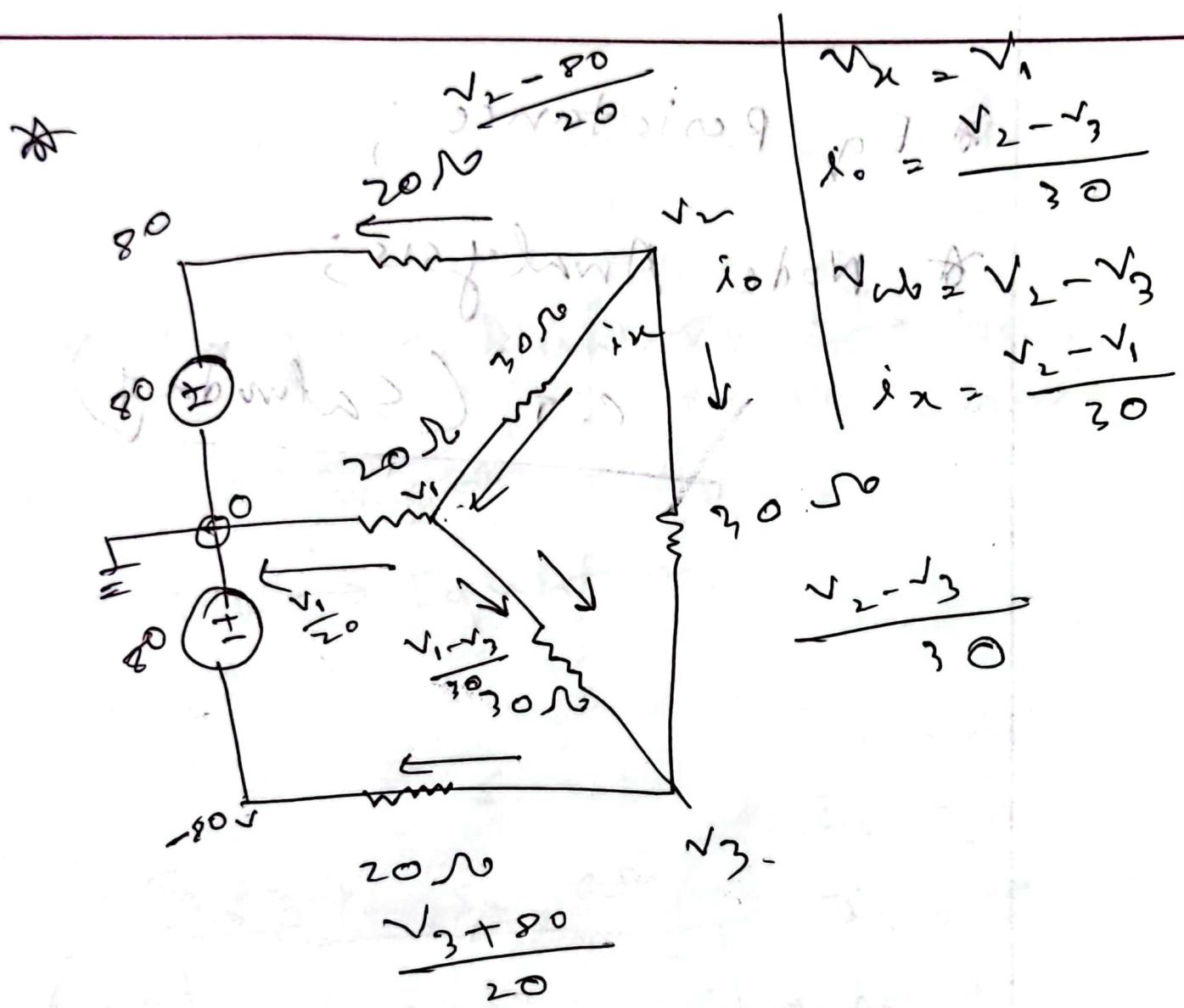

$$\textcircled{1} \quad \frac{V_1}{20} + \frac{V_1 - V_3}{30} = \frac{V_2 - V_1}{30}$$

$$\textcircled{11} \quad \frac{V_2 - 80}{20} + \frac{V_2 - V_1}{30} + \frac{V_2 - V_3}{30} = 0$$

$$\textcircled{111} \quad \frac{V_1 - V_3}{30} + \frac{V_2 - V_3}{30} = \frac{\sqrt{3} + 80}{20}$$

$$6V$$

$$2A$$

$$2 \cdot 2^2$$

Ec

Node Analysis \rightarrow Node \rightarrow KCL \rightarrow Node Voltage


Mesh Analysis \rightarrow Mesh \rightarrow KVL \rightarrow Mesh Current

- Mesh Current
- KVL \rightarrow Equation
- Solve

$$I_1 = i_1$$


$$I_2 = i_2$$

$$I_3 = i_1 - i_2$$

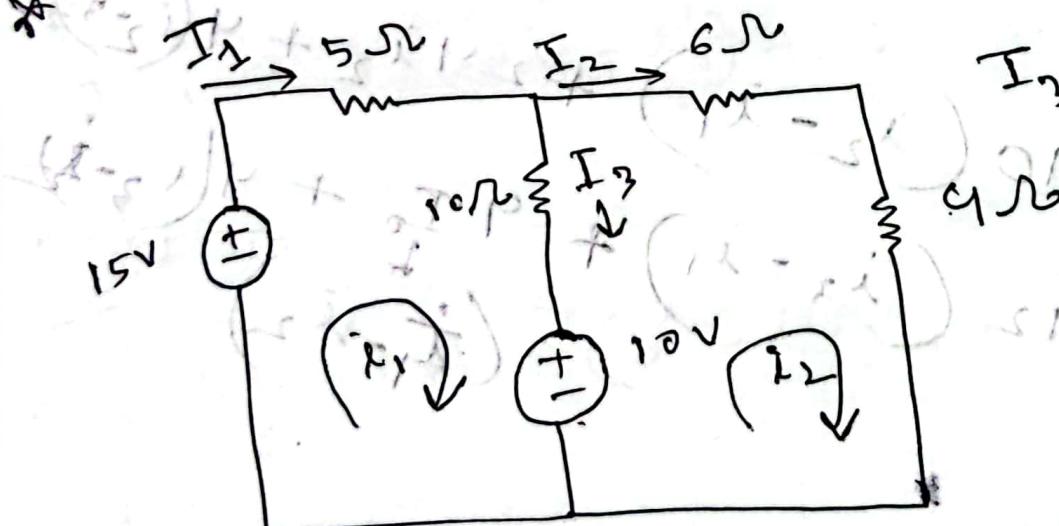

$$\text{Mesh 1: } -15 + 5i_1 + 10(i_1 - i_2) + 10 = 0$$
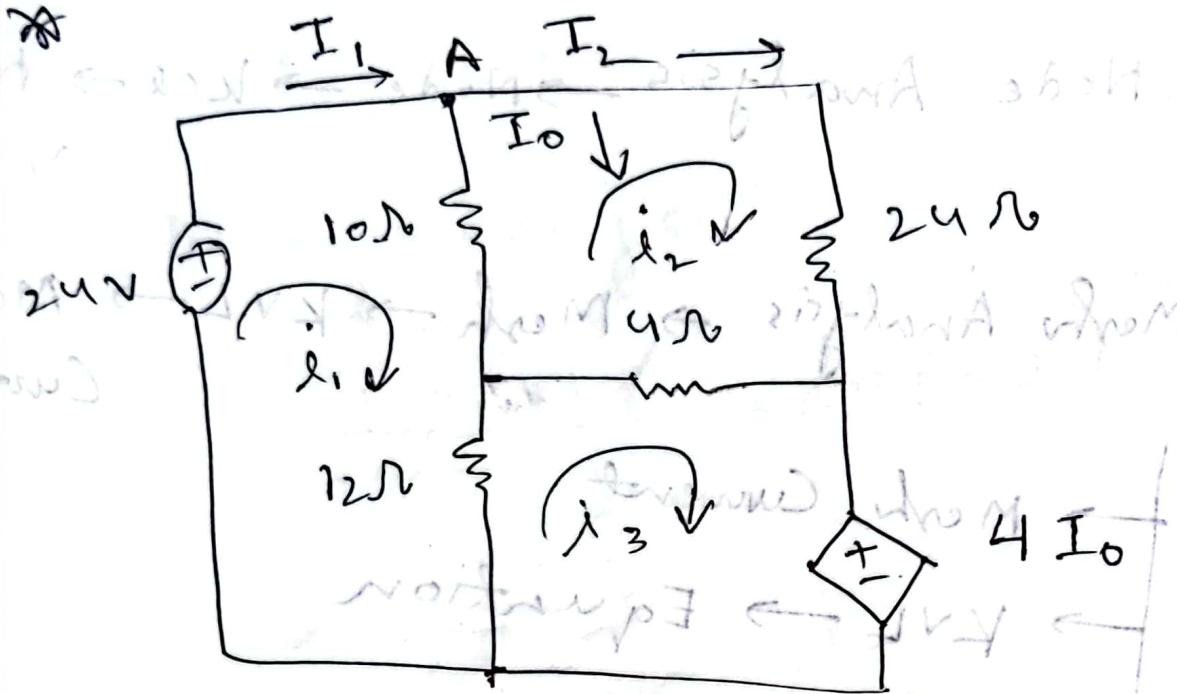
$$\text{Mesh 2: } -10 + 10(i_2 - i_1) + 6i_2 + 4i_2 = 0$$



~~for i₁~~

$$-24 + 10(i_1 - i_2) + 12(i_1 - i_3) = 0$$


~~$$10(i_2 - i_1) + 24i_2 + 4(i_2 - i_3) = 0$$~~

~~$$10(i_2 - i_1) + 9i_0 + 4(i_3 - i_2) = 0$$~~

~~$$12(i_3 - i_1) + (i_1 - i_2) = 0$$~~

~~so $i_1 = i_0$ or $i_1 = 0$ & $i_2 = i_3$~~

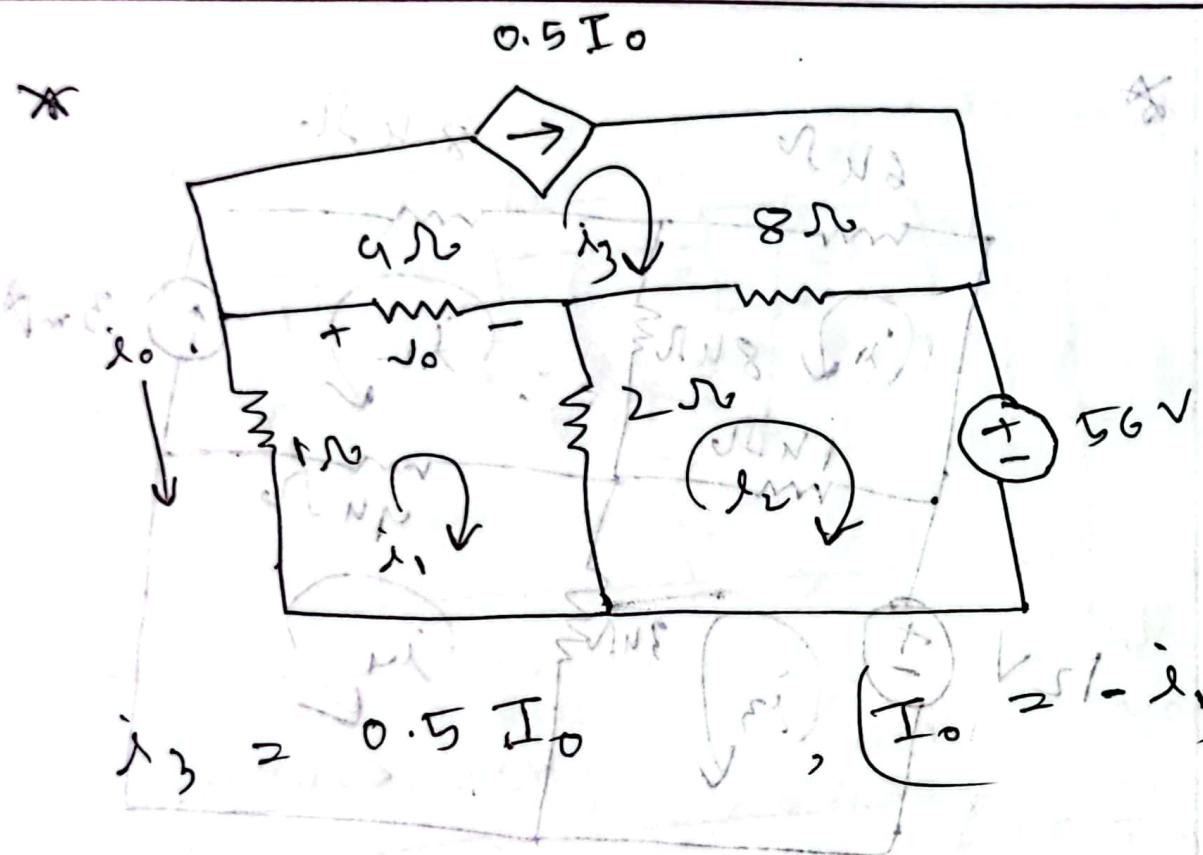~~$i_1 = 0$ & $i_2 + i_3 = 0$ or $i_2 = -i_3$~~



~~Mesh 1:~~

$$2i_1 + 4(i_1 - i_3) + 2(i_1 - i_2) = 0$$


~~Mesh 2:~~

$$2(i_2 - i_1) + 8(i_2 - i_3) + 56 = 0$$

~~Mesh 3:~~

$$i_3 = -0.5 i_1$$

$$(i_1 - i_2) \text{ up} + (i_2 - i_3) \text{ up}$$

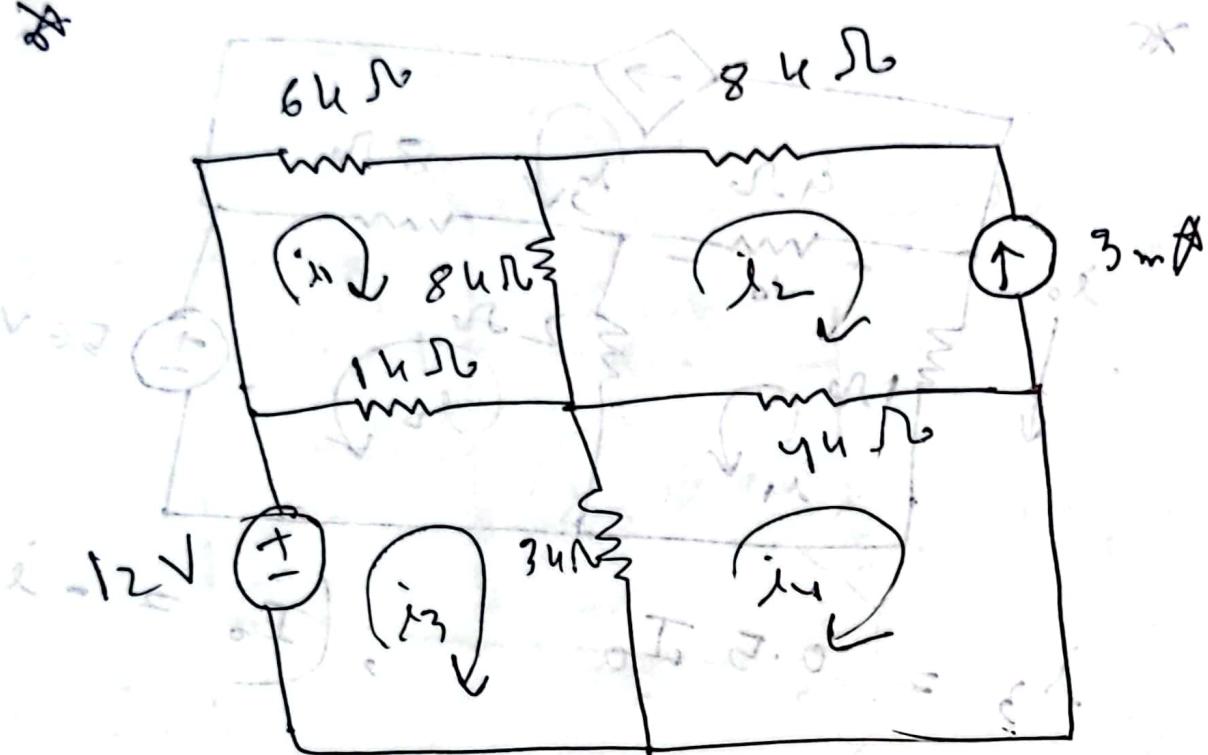

Mesh 1:

$$6k(i_1) + 8k(i_1 - i_2) + 1k(i_1 - i_3) = 0$$

Mesh 2:


$$-12 + 1k(i_3 - i_1) + 3k(i_3 - i_4) = 0$$

Mesh 3:

$$3k(i_4 - i_3) + 4k(i_4 - i_2) = 0$$

$$I_1 = -$$

$$I_2 = -$$

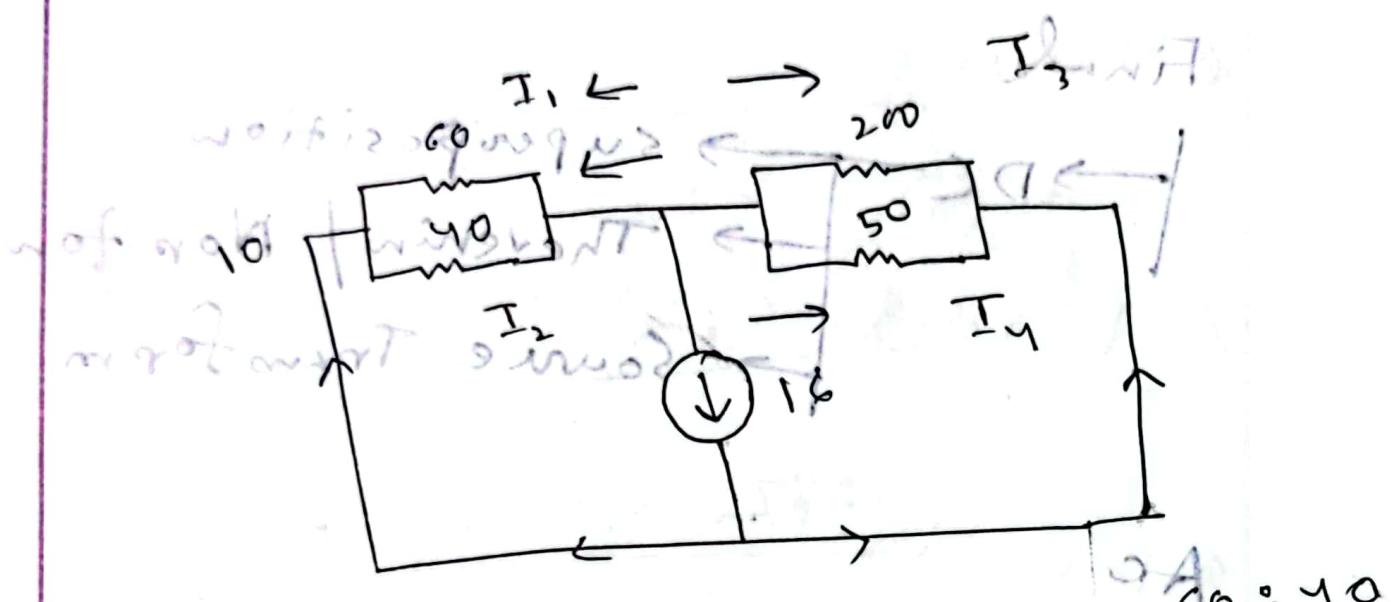


$$60 : 40$$

$$40 : 60$$

$$\frac{40}{100} \times 10$$

$$\frac{60}{100} \times 10$$

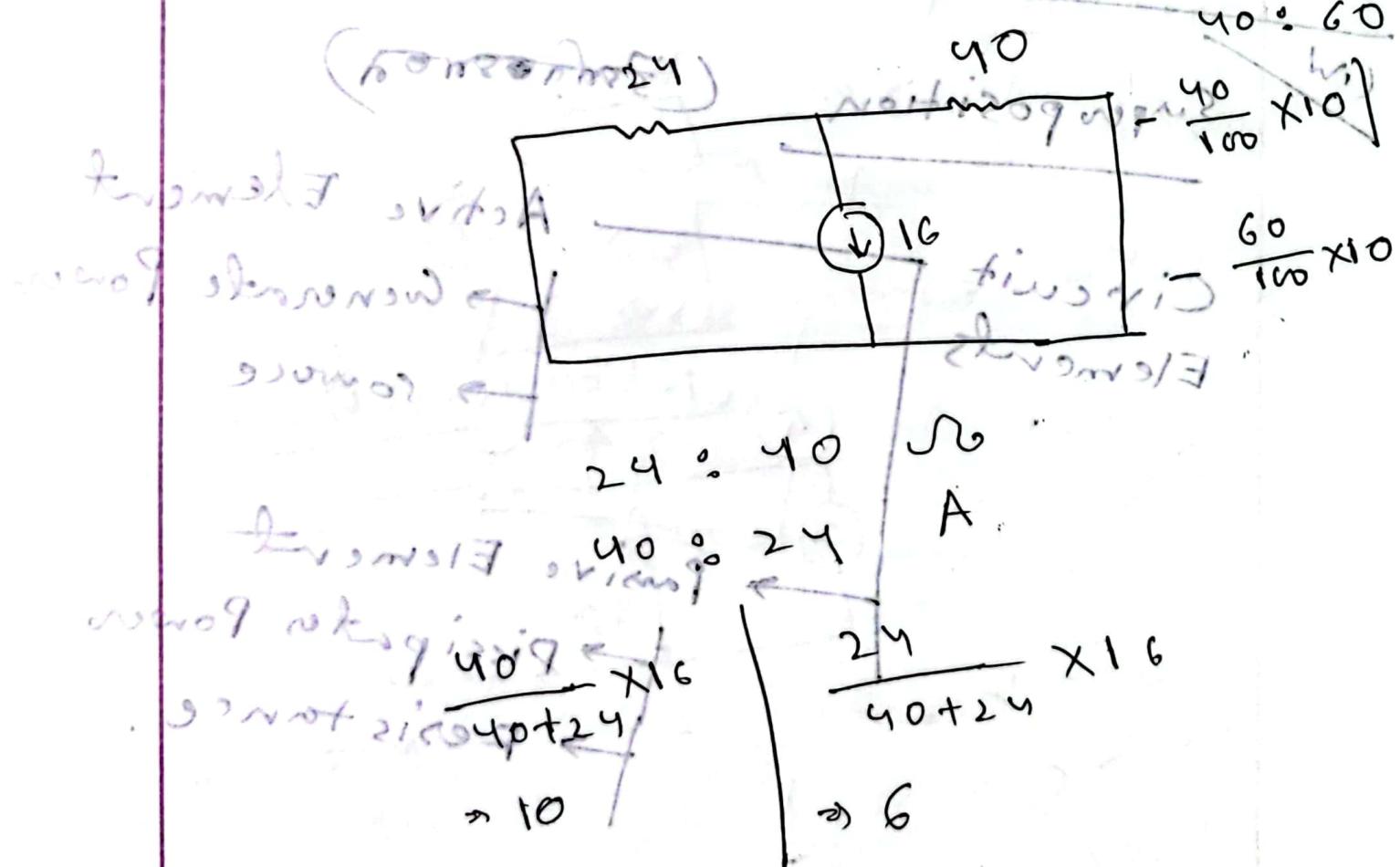

$$24 : 40$$

$$40 : 24$$

A.

$$\frac{24}{40+24} \times 16$$

$\Rightarrow 6$

Final

→ DC → superposition
AC → Thevenin / Norton
→ Source Transform

AC

(in)

Superposition

(Transformation)

Circuit
Elements

Active Element


→ Generate Power

→ source



Passive Element

→ Dissipates Power

→ resistance.

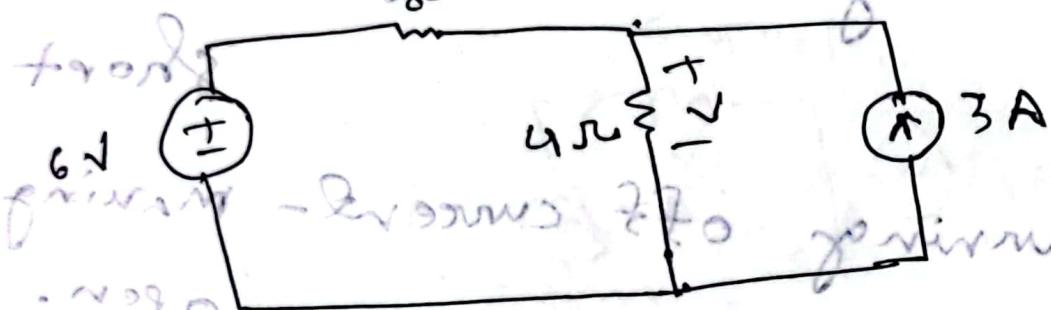

~~6V on, 3A off:~~

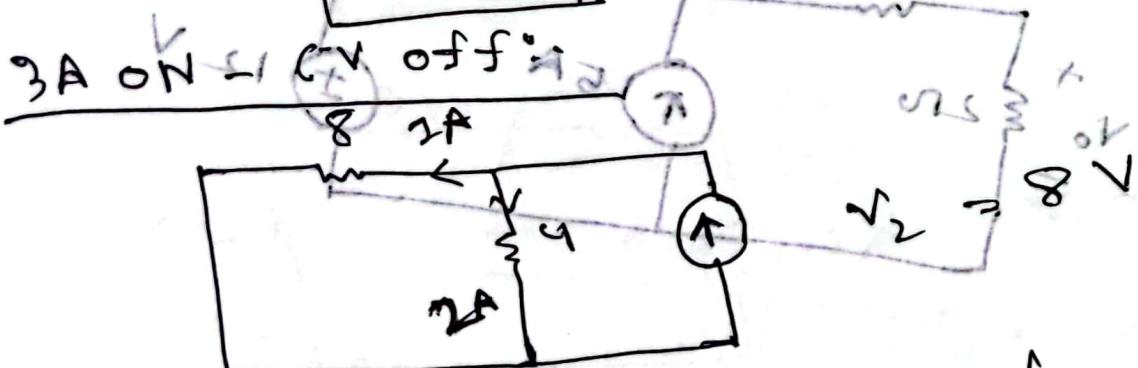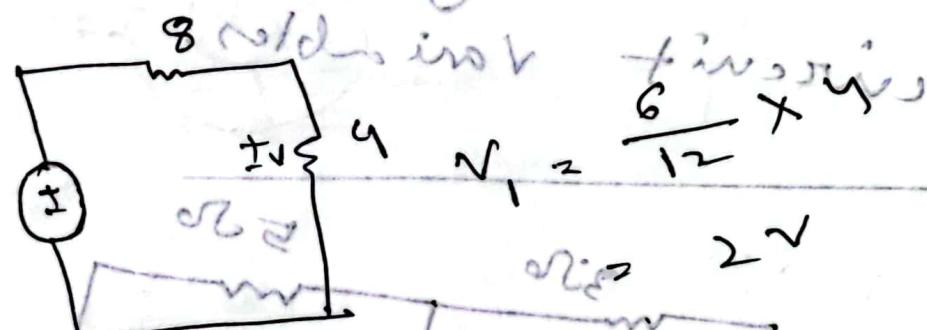

$$8:4$$

$$2:1$$

$$1:2$$


$$\frac{1}{3} \times 3 = 1A$$

$$\frac{2}{3} \times 3 = 2A$$

$$\begin{aligned} V &= V_1 + V_2 \\ &= (2 + 8) \\ &= 12V \end{aligned}$$


- * Turning off voltage - Making it short
- * Turning off current - making it open.

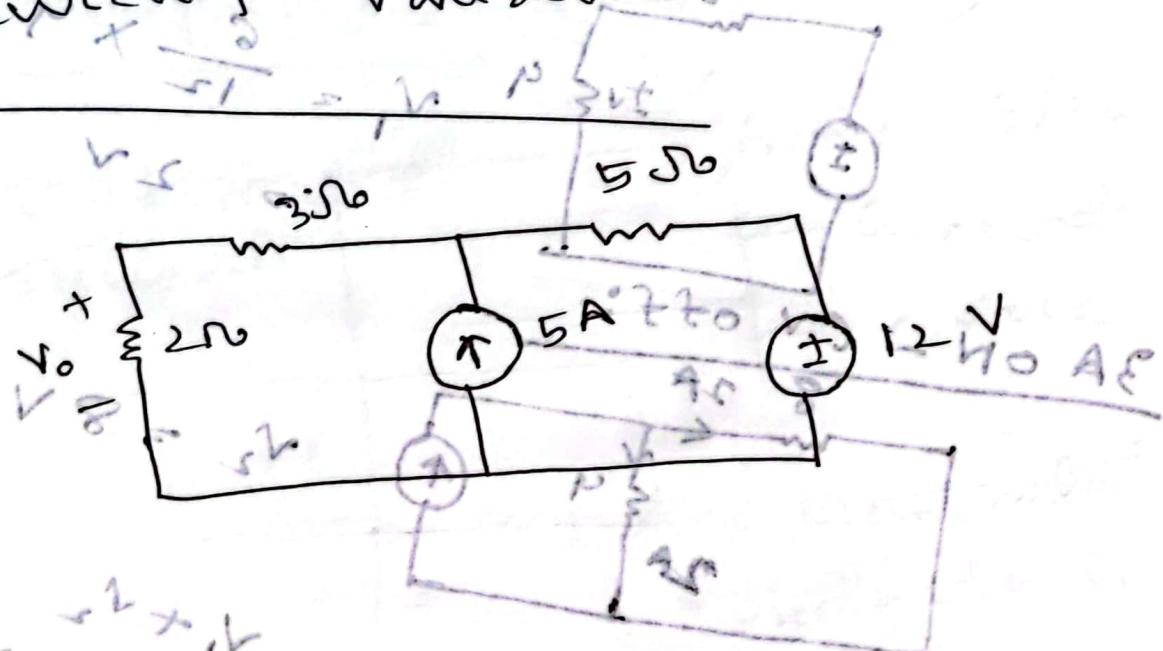* Dependent sources are left intact because they are controlled by circuit variables.




$$\begin{aligned}
 & (8 + 5) = \underline{\underline{P_{T1}}} \\
 & V_{S1} = \frac{1}{2} \\
 & I_1 = 5 + 1 \\
 & 45 = 8 + \frac{1}{2} / \frac{1}{2} \\
 & 45 = 8 + \frac{1}{4} / \frac{1}{4}
 \end{aligned}$$

~~5A ON~~

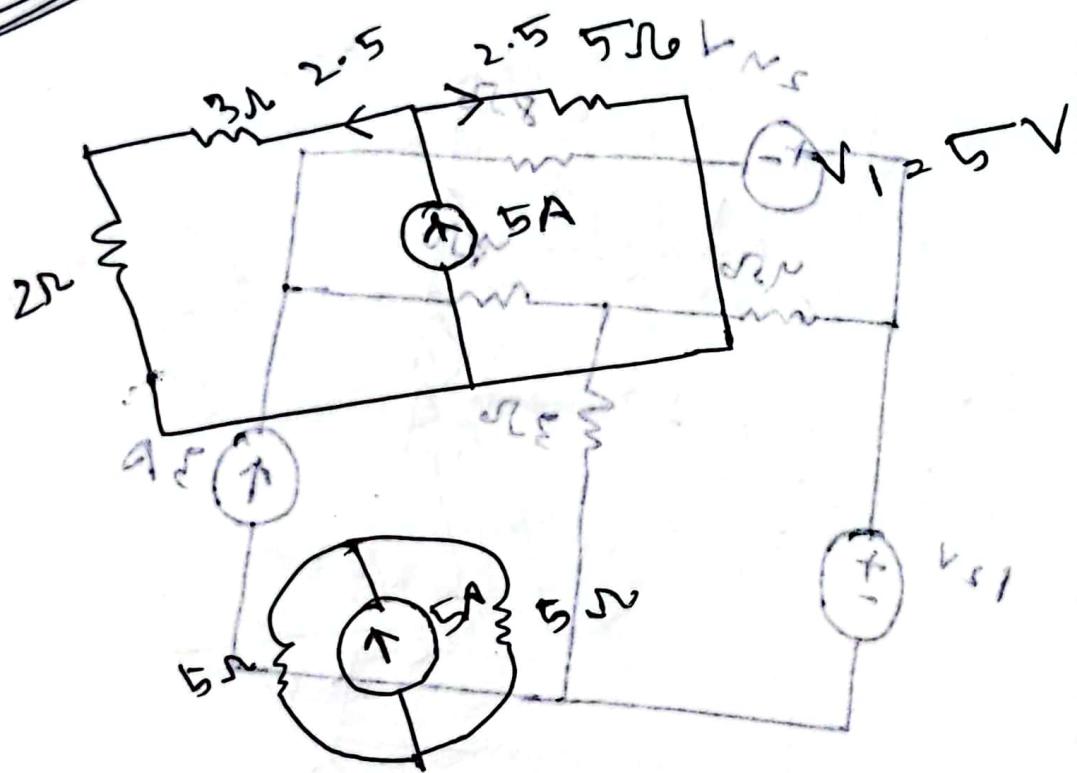



~~12V ON~~

~~work 51~~

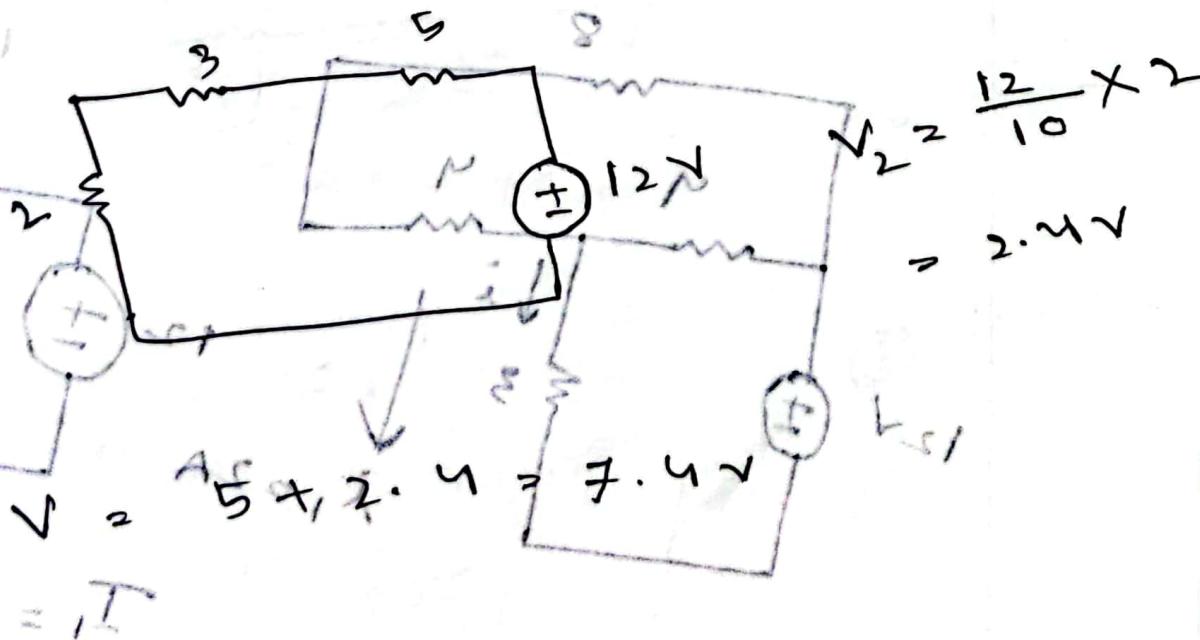


Ans
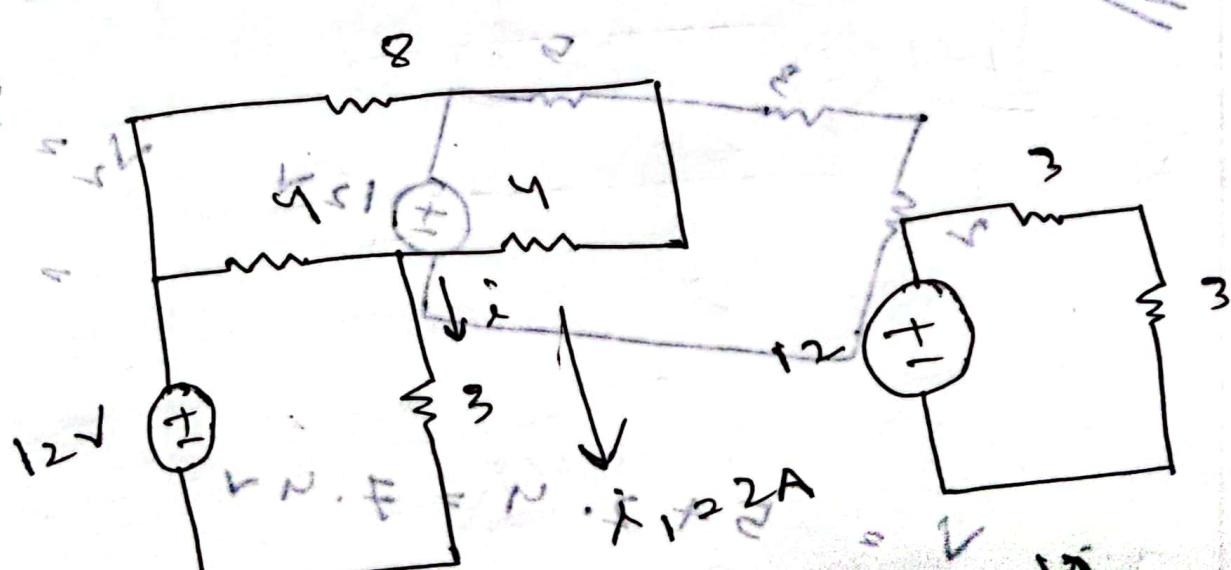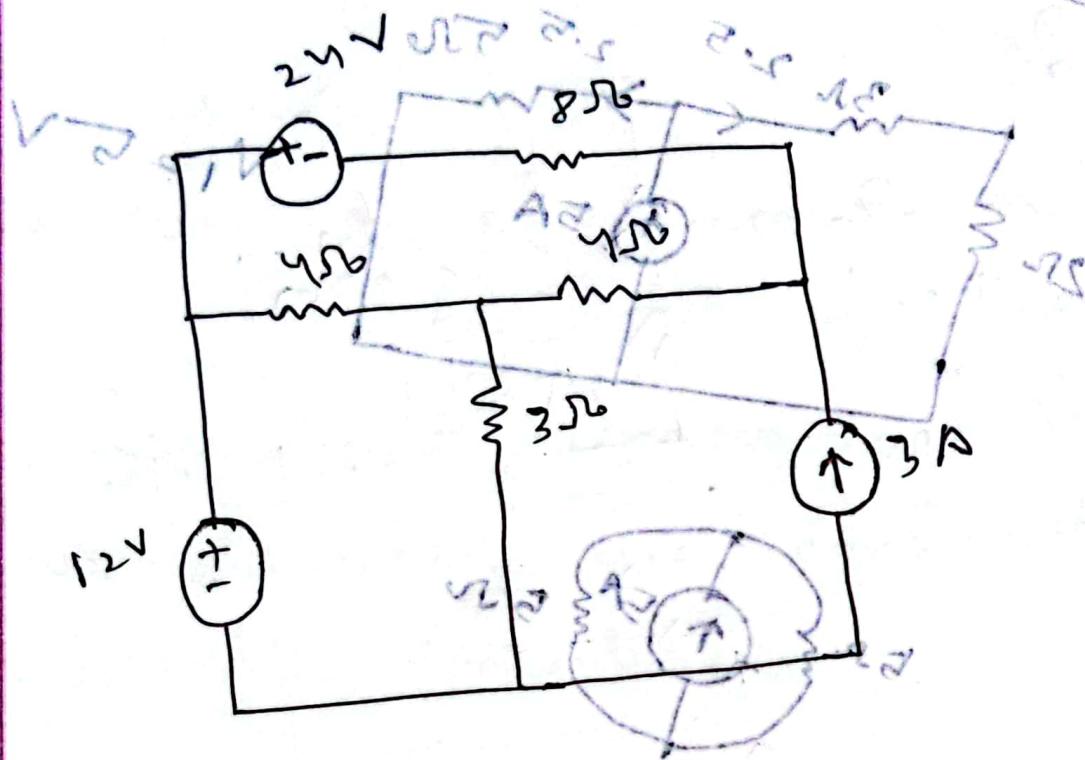
$$I = \frac{V_1}{R_{\text{parallel}}} = \frac{12}{5 + 2.4} = 1.7$$



$$I_1 = \frac{12}{6} = 2 \text{ A}$$

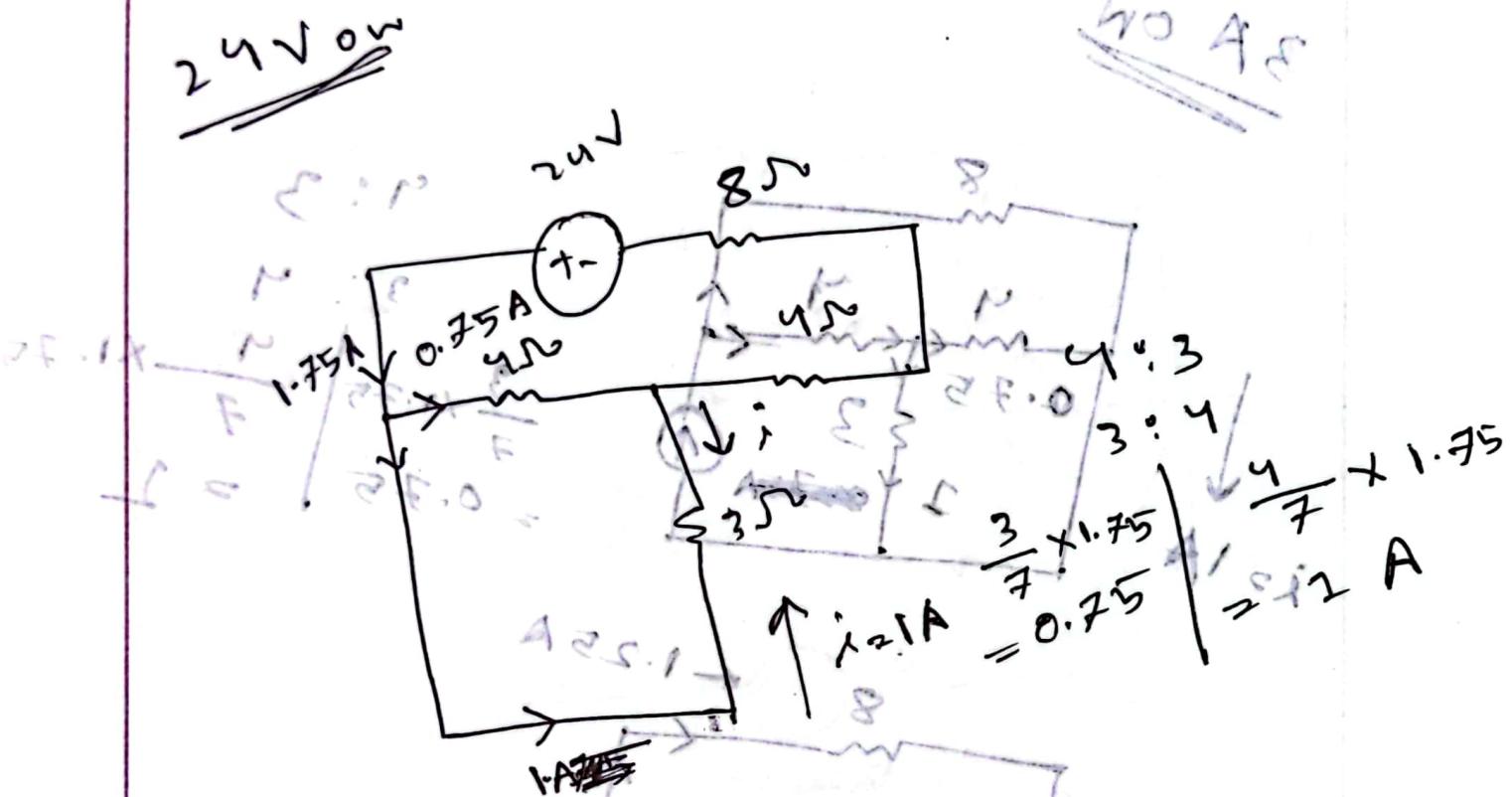


$$i_1 = \frac{V}{R}$$


$$= \frac{24}{\frac{12}{7} + 1.2}$$

$$= 1.75 A$$

$$\frac{12}{7} + 1.2$$

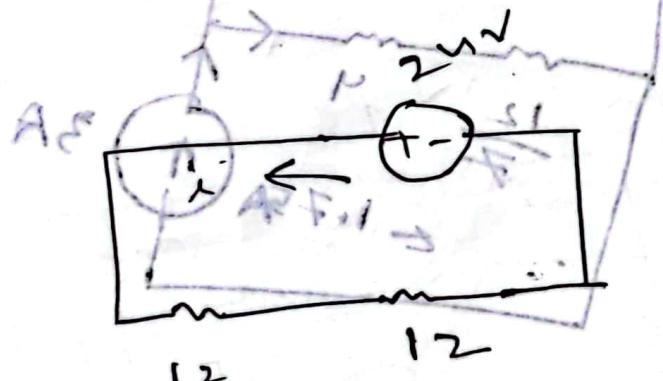

$$\frac{12}{7}$$

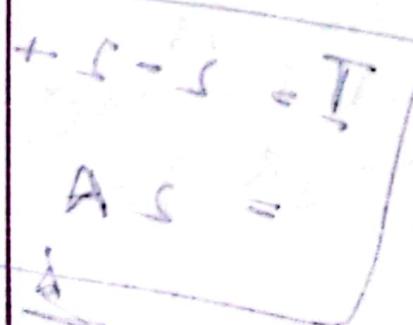

$$20V : 1.2 \Omega$$


$$= 17.5 A$$

~~3A ON~~

~~no VNs~~



$$\frac{9}{7} \times 1.75 = 1.25$$

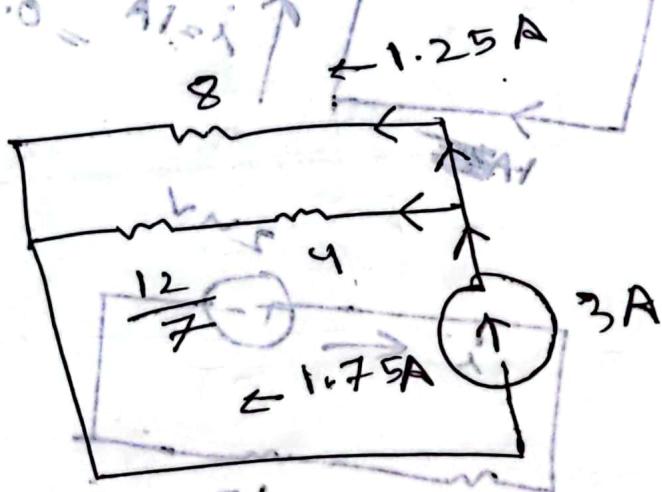


$$\frac{12}{7} + \frac{4}{7} = \frac{90}{7}$$

$$8 : \frac{40}{7}$$

$$= \frac{40}{7} \times 3 \\ = \frac{90}{7} \\ = 1.25$$

$$\frac{8}{\frac{90}{7}} \times 3 \\ = 1.75$$

$$I = 2 - 2 + 2 \\ = 2 A$$

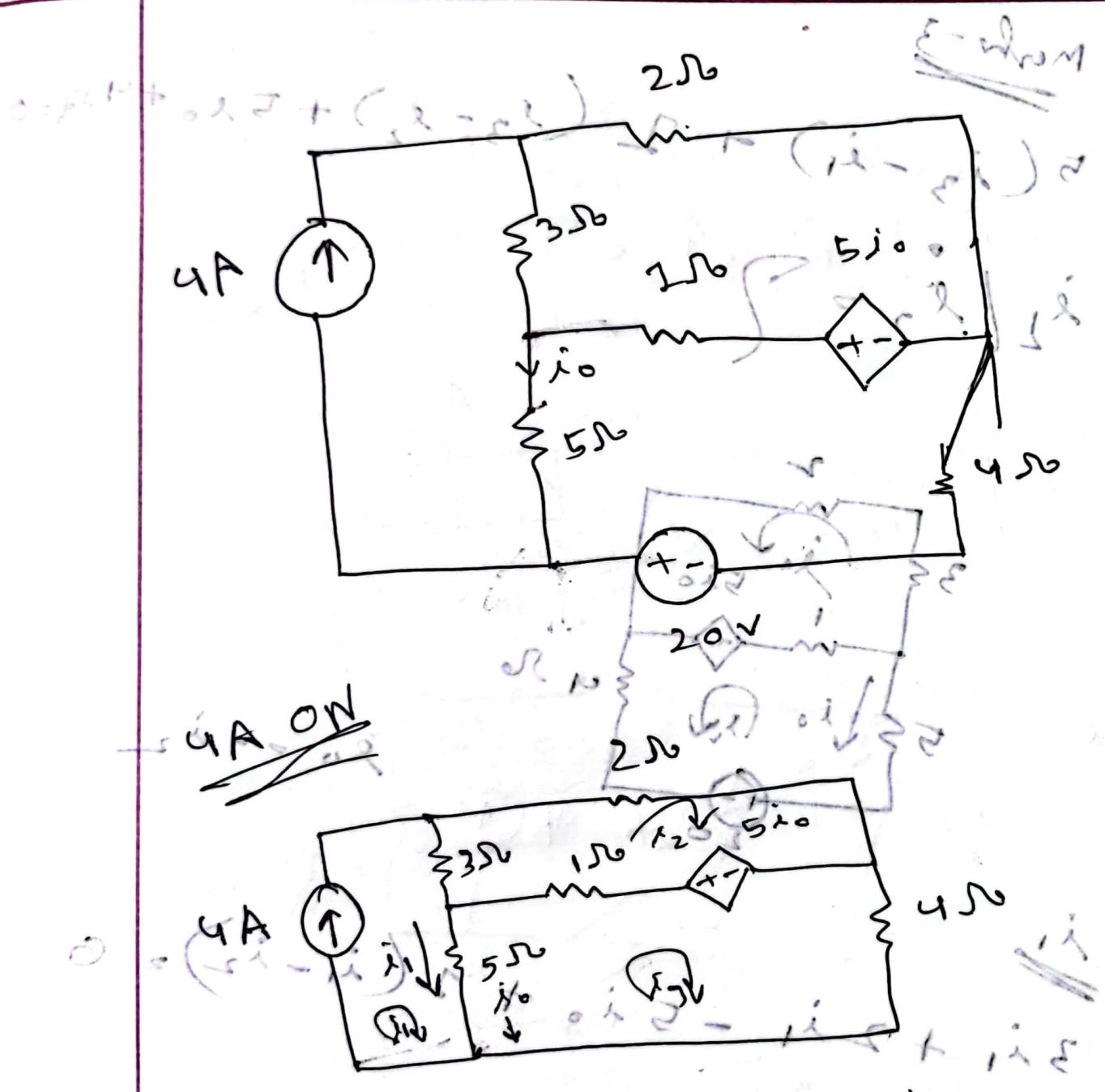

b7

Maths - 3



~~Mern~~
 $\sqrt{3} (i_3 - i_1) + \sqrt{3} (i_3 - i_2) + 5i_0 + 4i_{32}$
 $i_2 / \frac{R_{32}}{2}$
 $i_1 / \frac{R_{21}}{2}$
 $i_3 / \frac{R_{13}}{2}$
 $i_0 / \frac{R_{12}}{2}$
 $i_{32} / \frac{R_{32}}{2}$
 V_m
 A_N
 i_1
 i_2
 i_3
 i_0
 i_{32}
 $V_m - A_N - i_1 = 0$
 $3i_1 + 2i_1 - 5i_0 + \sqrt{3}i_{32} = 0$


$$\cancel{5i_2 + 1(i_2 - i_1)} + 5i_0 + 4(i_2) = 20 \quad | \quad \text{Eq. 2}$$

Q12


Superposition


EC

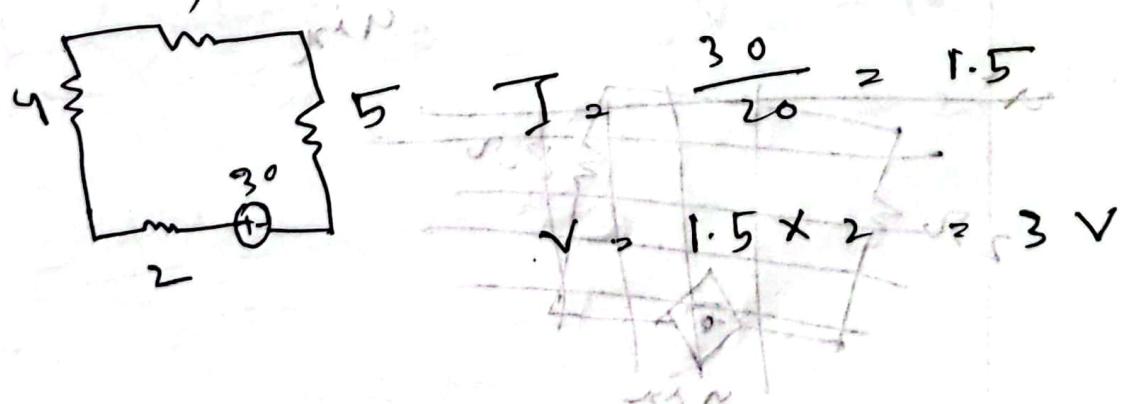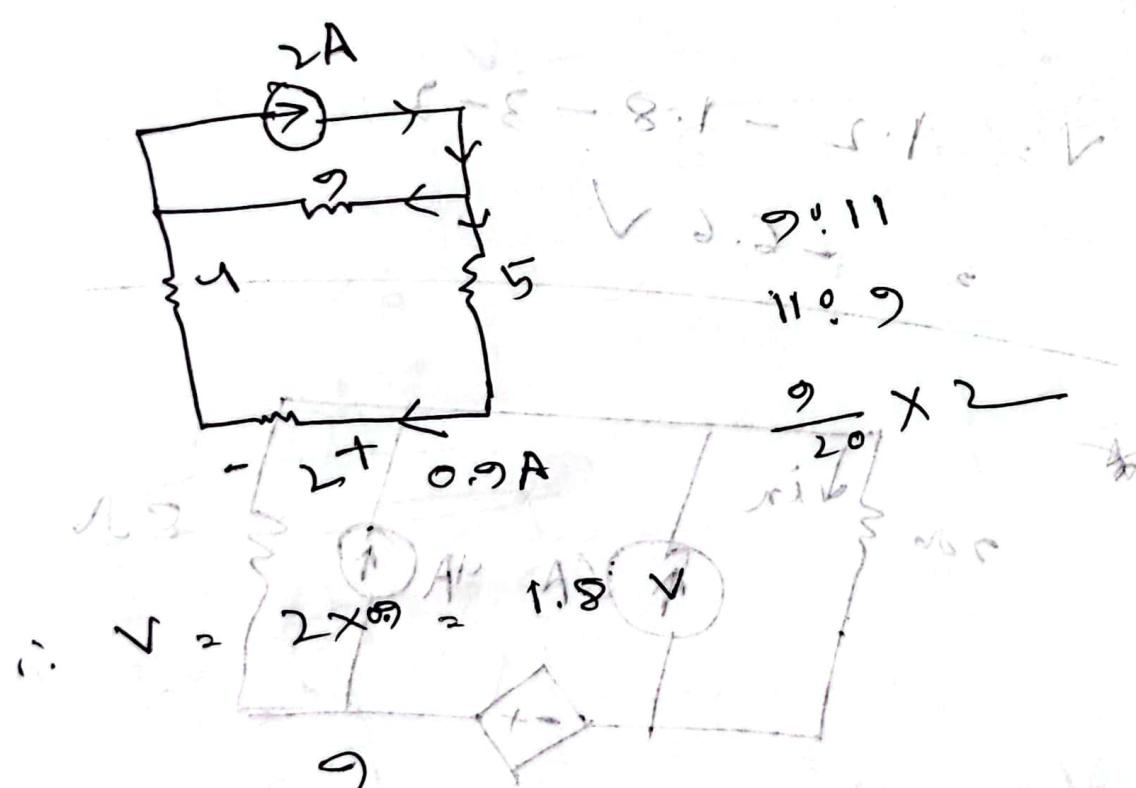

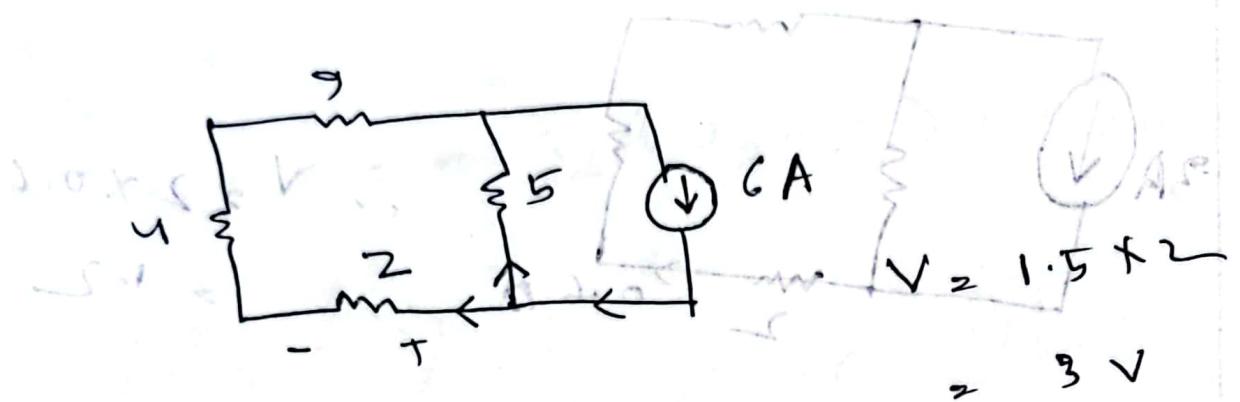
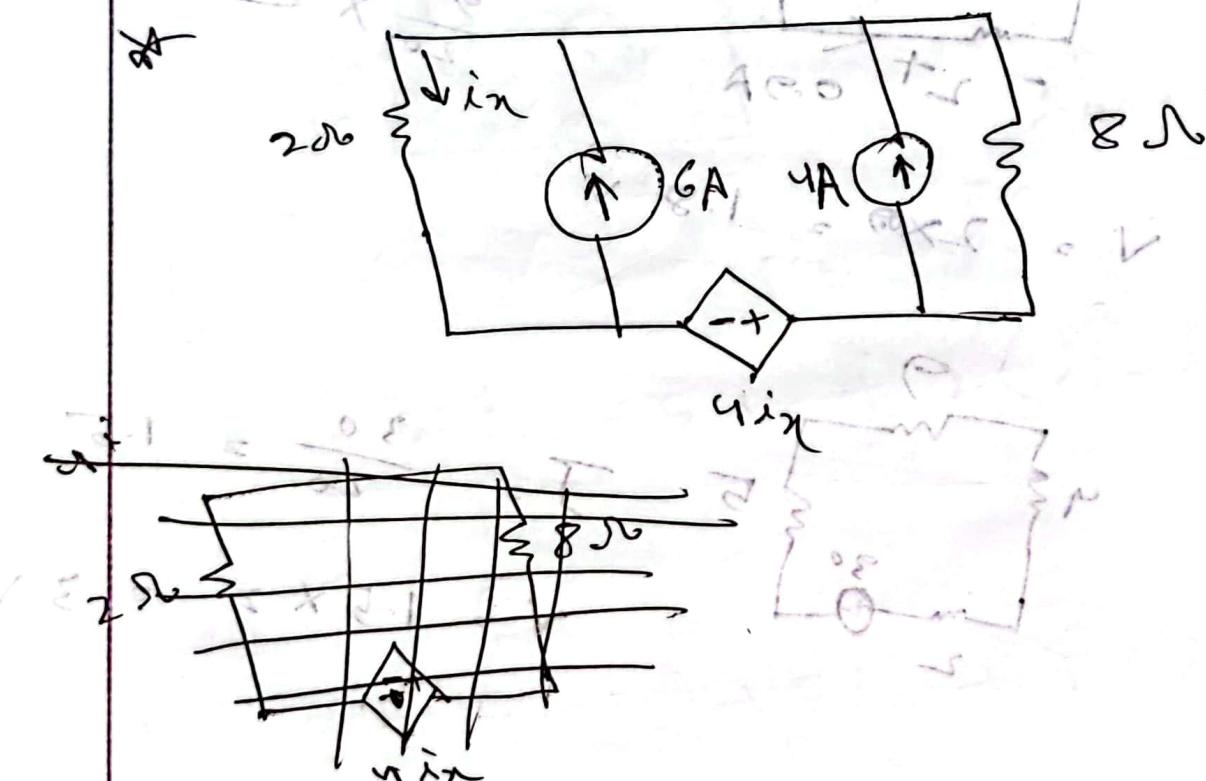
$$\begin{aligned}
 V_2 &= 1.2 - 1.8 - 3 = -6.6 \text{ V} \\
 &\quad \text{with } A_{\text{in}} = 3
 \end{aligned}$$



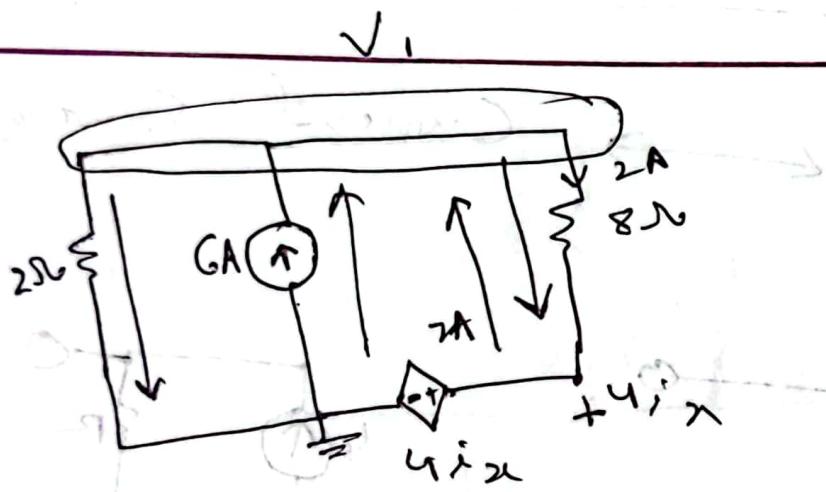


$$I_2 = \frac{V_1}{2}$$

$$6 = \frac{V_1}{2} + \frac{V_1 - 4\text{V}}{8}$$

$$\Rightarrow V_1 = 16\text{V}$$

~~$$= \frac{V_1 - 32}{8}$$~~

$$\Rightarrow -2A$$

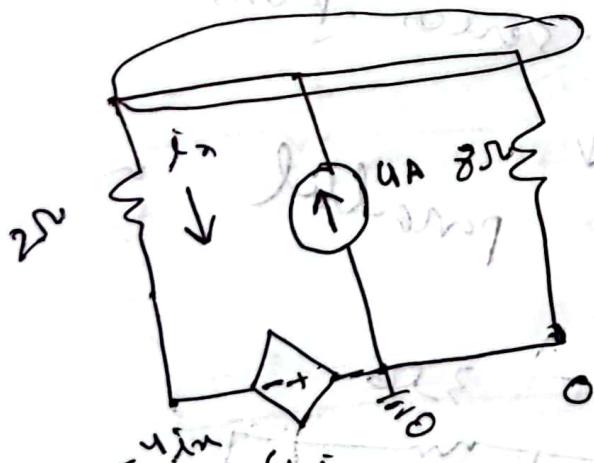

$$V_2 = 16 - 10.67$$

$$= 26.67$$


$$U_{\text{op}} = \frac{V_1 + 4\text{V}}{2} + \frac{V_1}{8}$$

$$\Rightarrow V_1 = -10.67$$


CW
2.3.2.8

Source Transformation

Voltage
Source

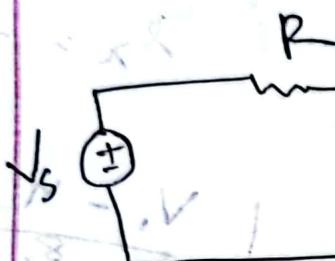

Current Source


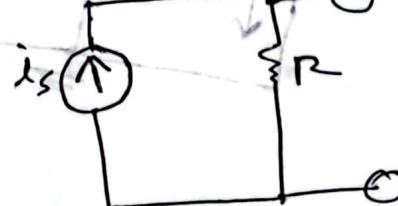





$$i_{sc} = \frac{V_s}{R}$$

$$V_s = i_s R$$

voltage source series resistance

current

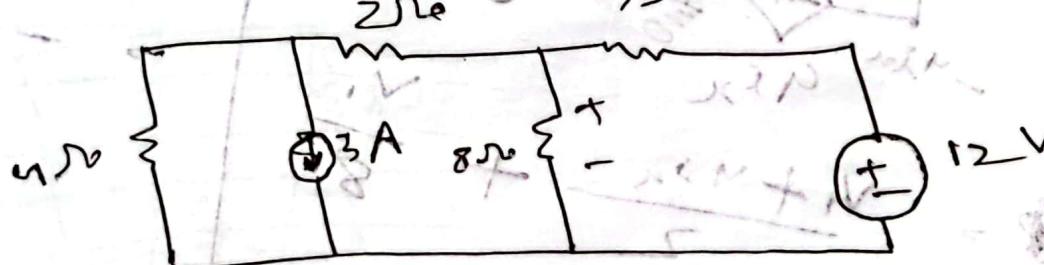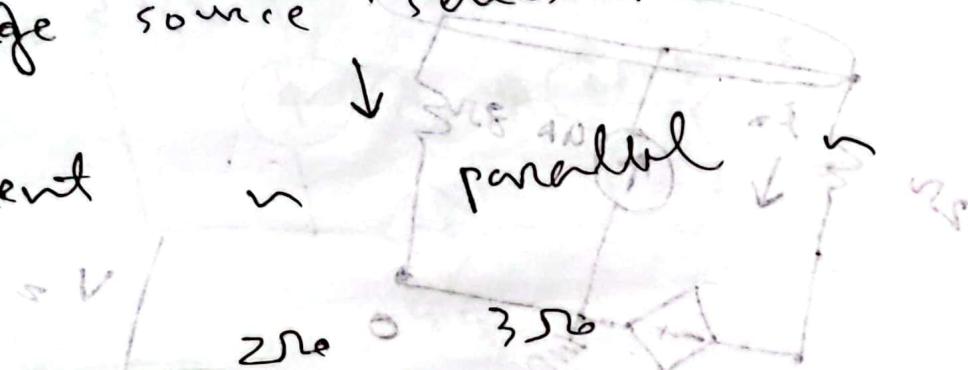


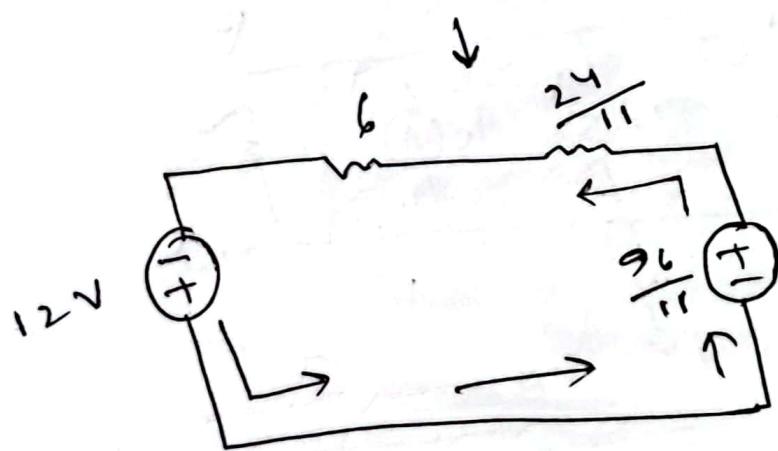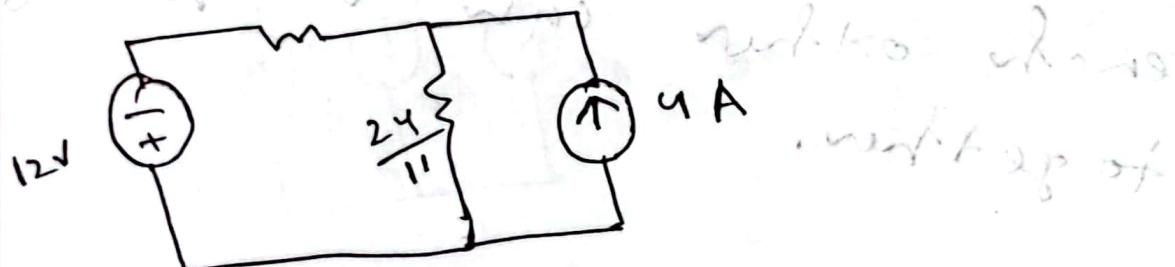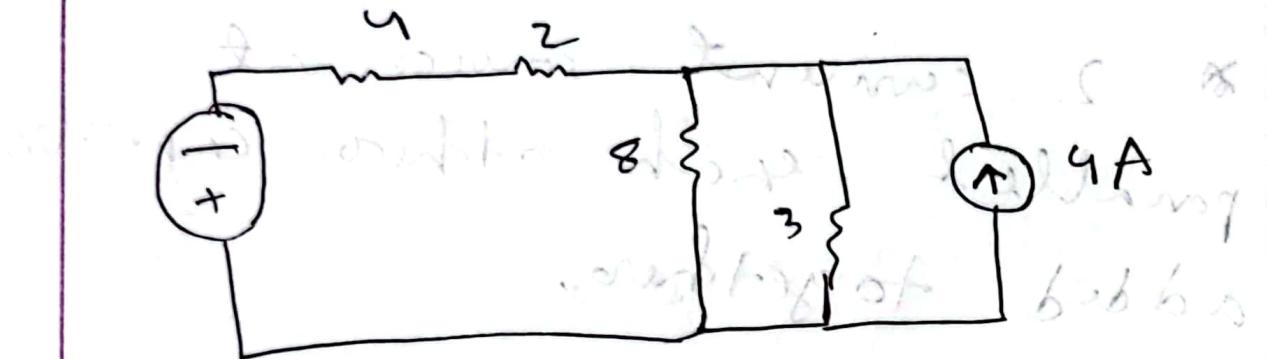

$$I = \frac{12 + \frac{20}{11}}{6 + \frac{24}{11}}$$





* 2 current sources at parallel each other can be added together.

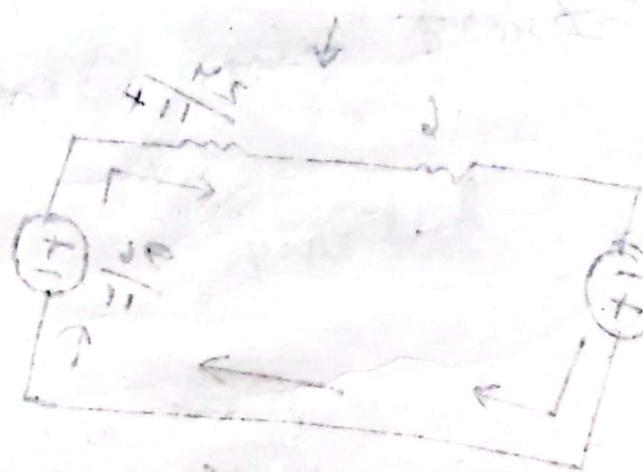* 2 voltage source at series to each other can be added together.




$$\frac{V_A + V_C}{V_{AB}} = \frac{V_A}{V_{AB}}$$


~~EC~~

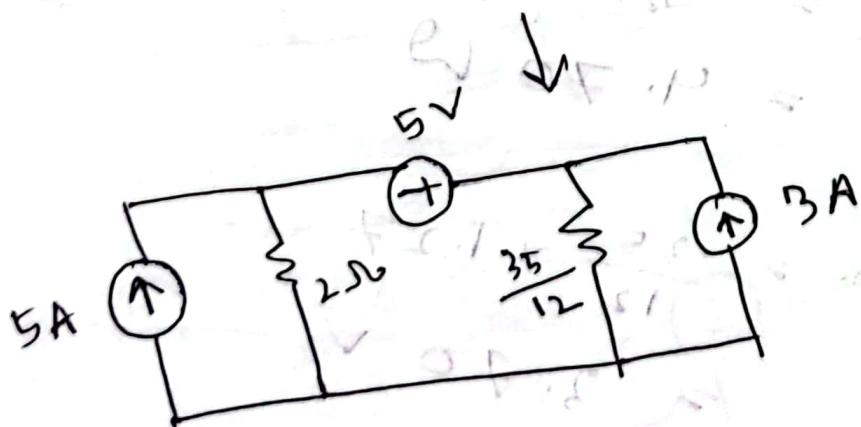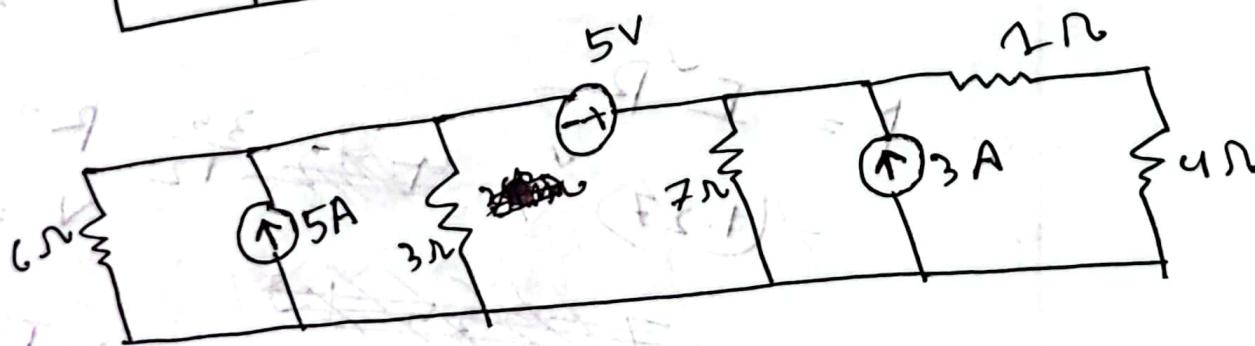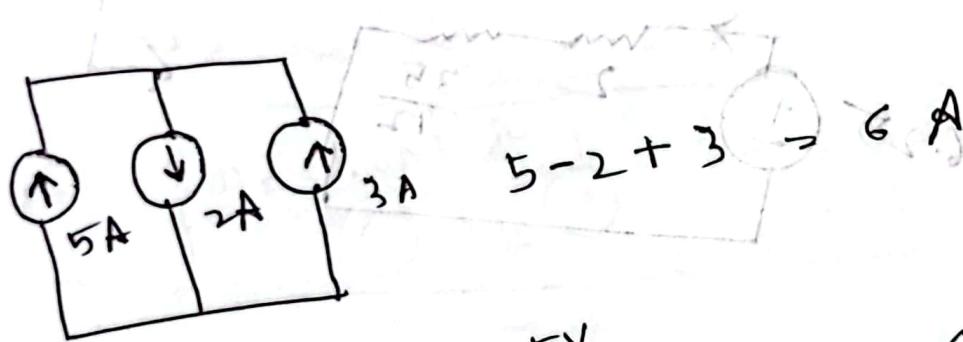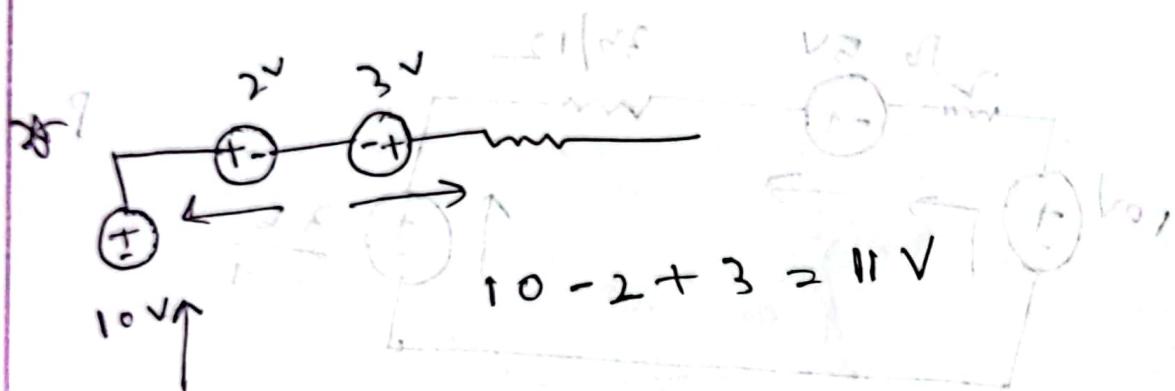

P.T.O.
~~1/2~~

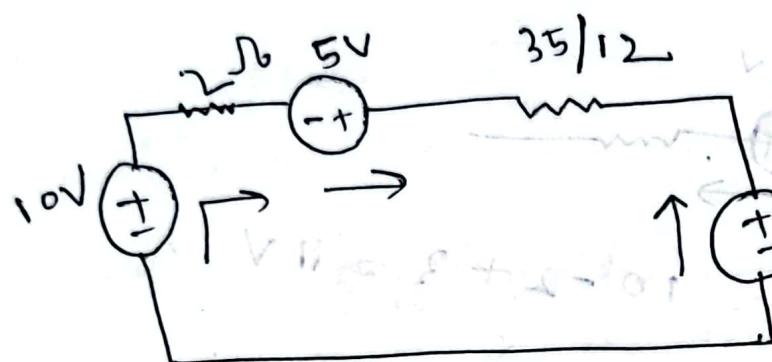

$$P_2 = \frac{V^2}{R}$$

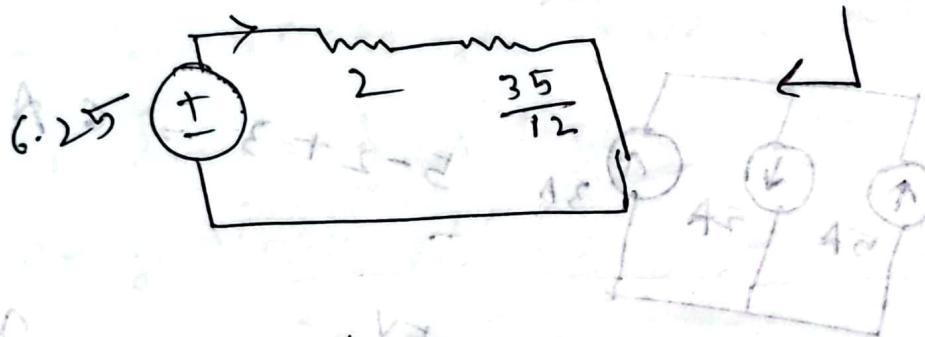

$$10 + 5 - \frac{35}{4} = 6.25 V$$

$$2 + \frac{35}{12}$$

$$\therefore P = I^2 R$$

$$\rightarrow (1.27)^2 \times \cancel{\frac{35}{12}}$$

$$R = 4.92 \Omega$$

$$V = 6.25 V$$





$$= \cancel{7.935} \quad \cancel{A}$$

$$\therefore I = \frac{6.25}{4.92}$$


$$\rightarrow 1.27 A$$


$$\begin{aligned} \therefore \frac{35}{12} \Omega &= \frac{35}{12} \times 1.27 \\ &= 3.70 V \end{aligned}$$

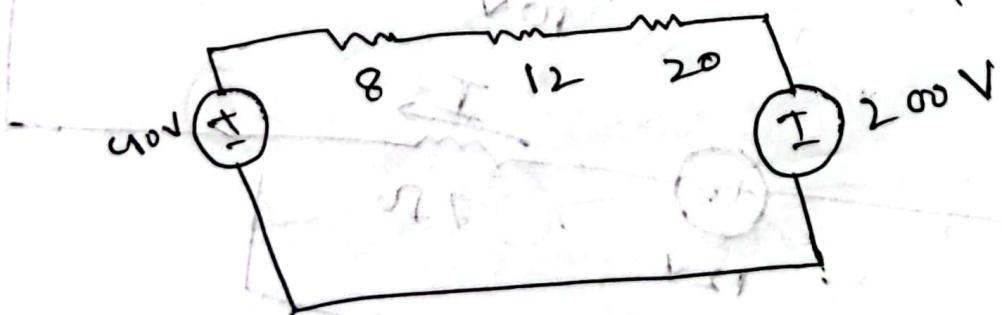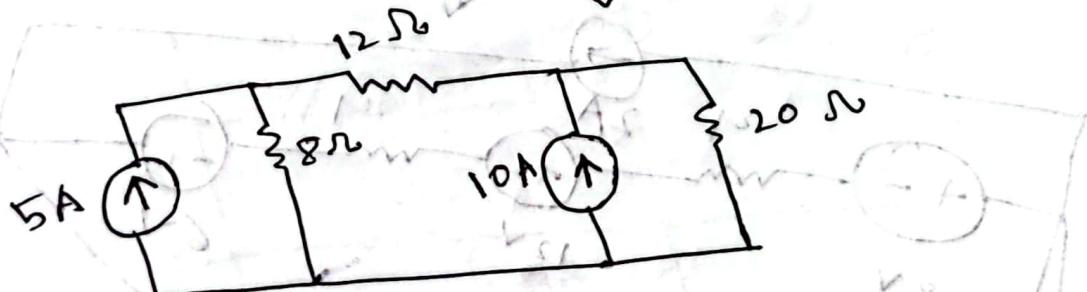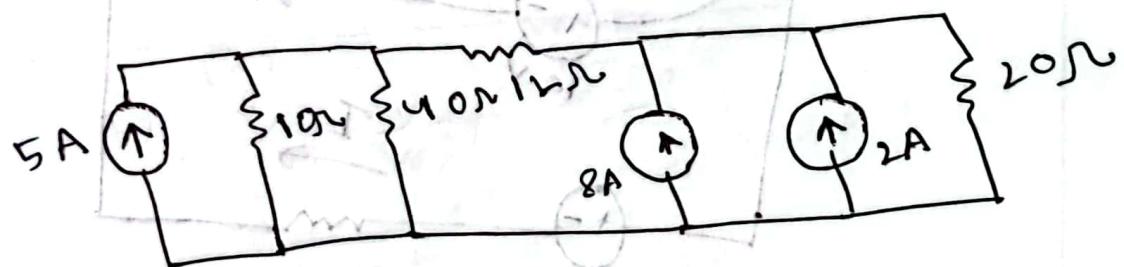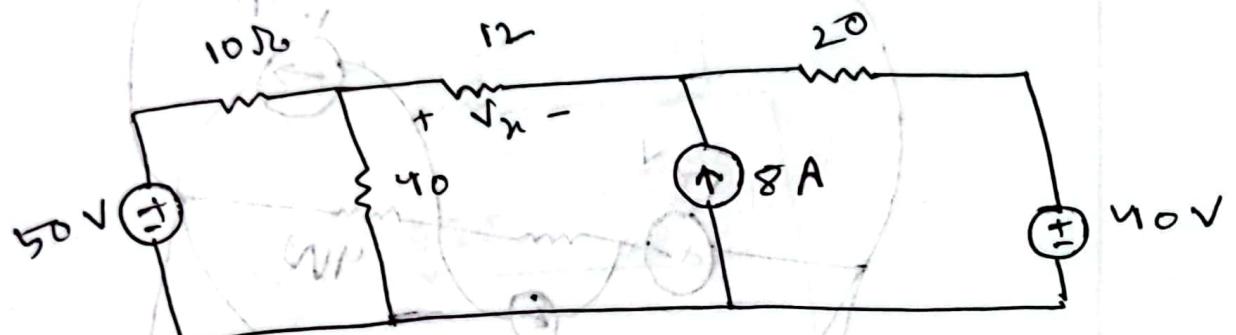
$$\therefore P = \frac{(3.70)^2}{35/12} = 4.69 W$$



P.T.O.

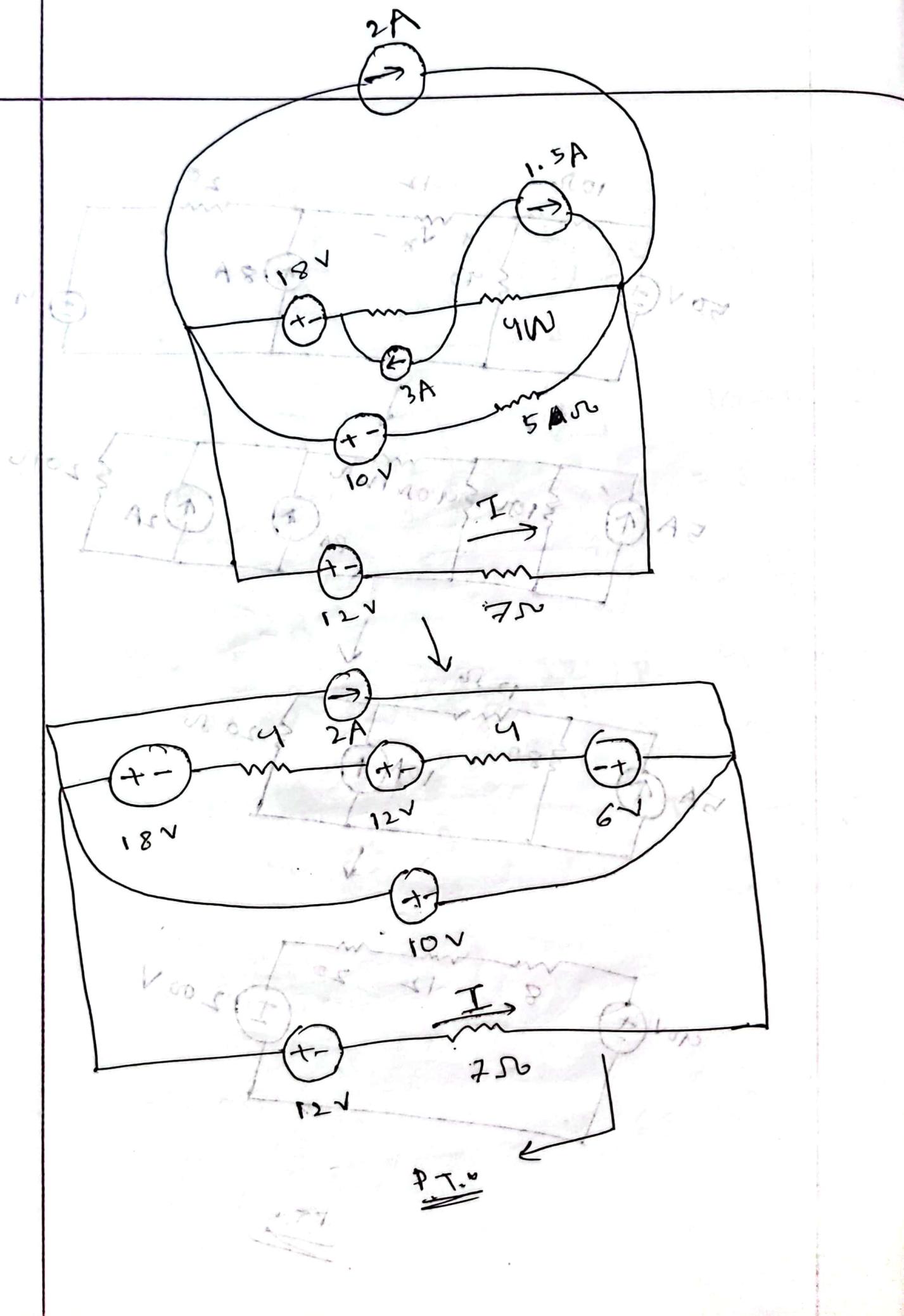

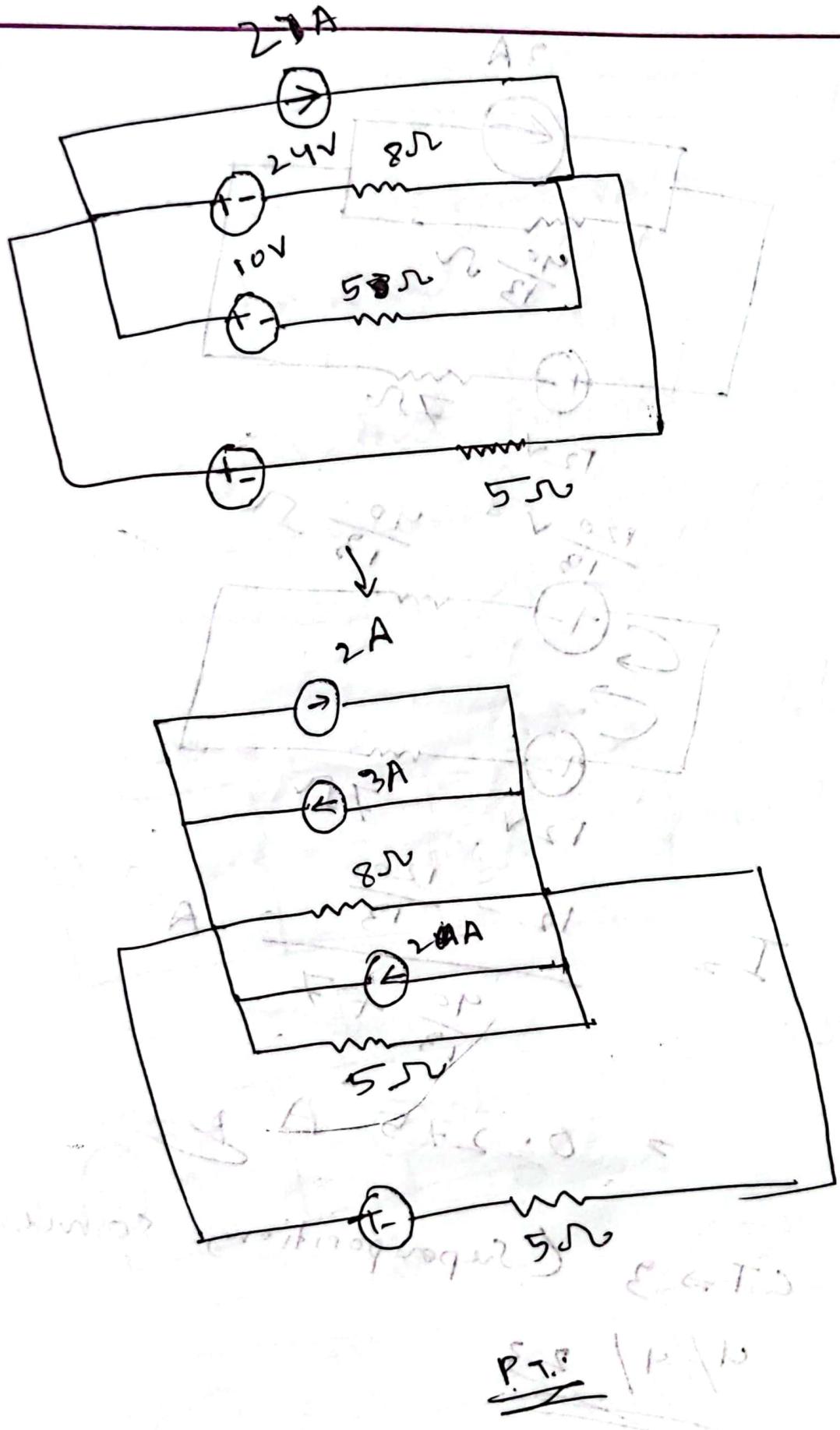

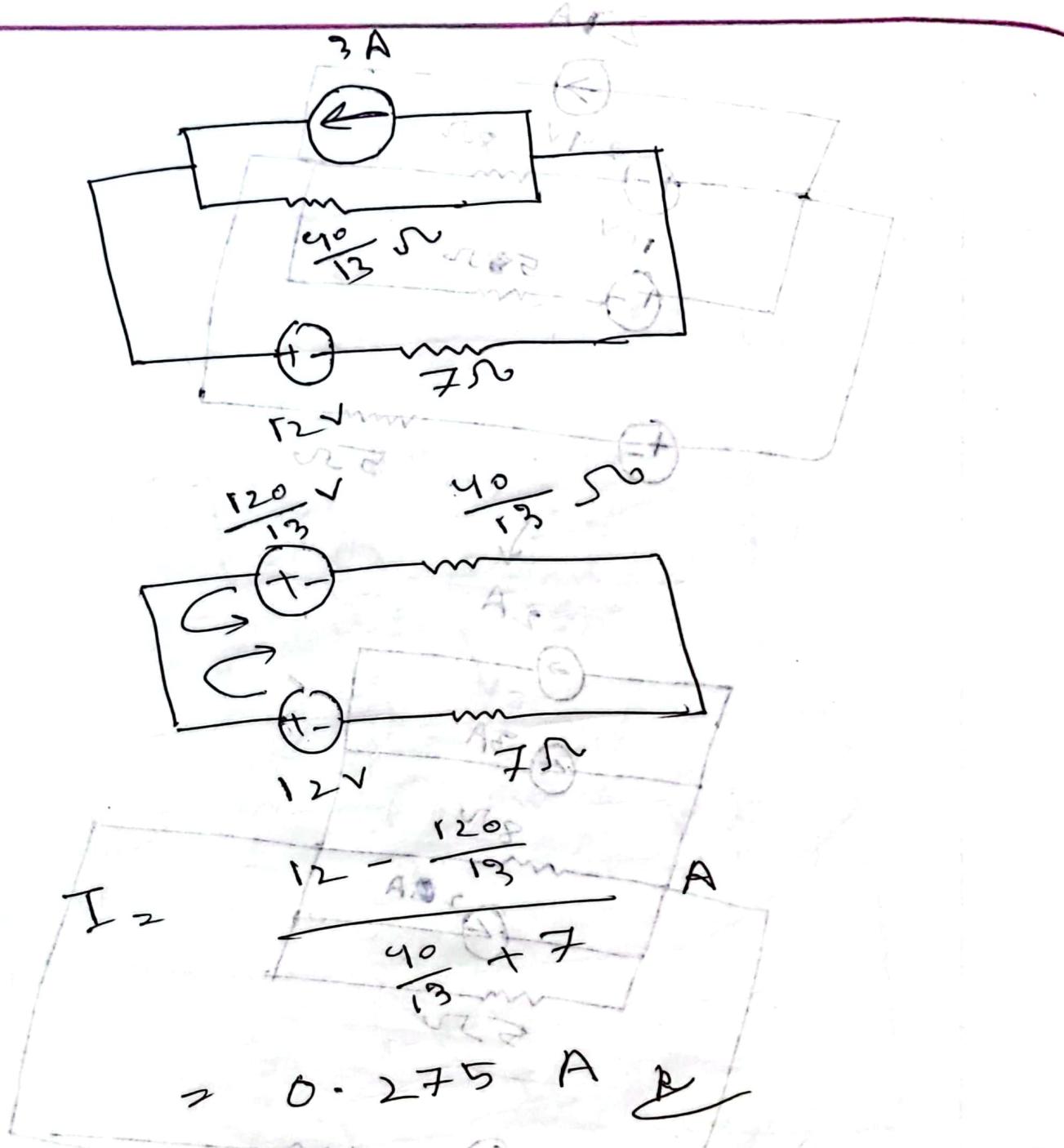





$\text{CT} \Rightarrow 3$ (superposition, source transform)

~~4/4/23~~

Thevenin & Norton Circuit


V_{th} : - \rightarrow open circuit voltage at the terminal P.

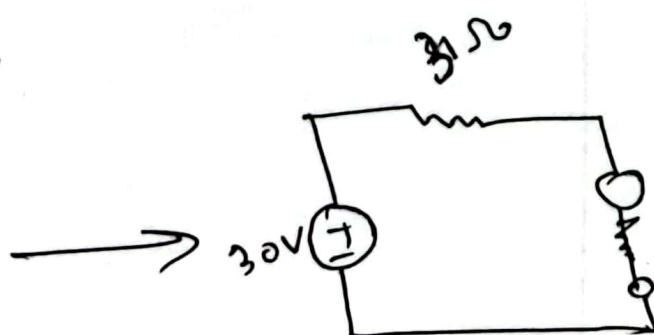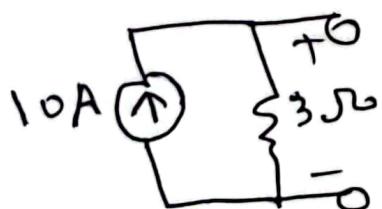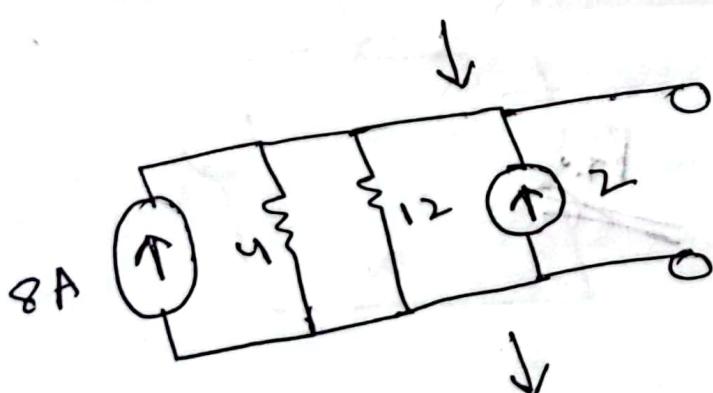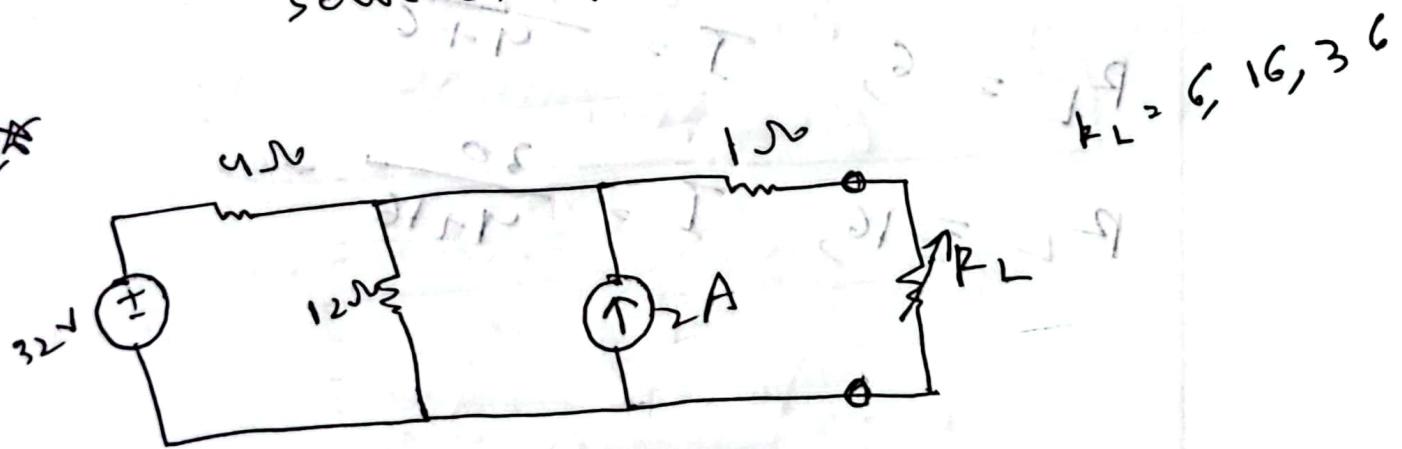R_{th} : - Equivalent resistance seen from the terminal with all the sources turned off.



~~P_{th}~~

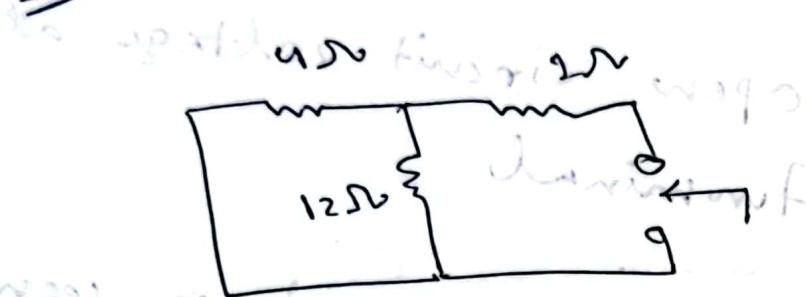Find equivalent resistance by shorting source




$$R_{eq} = \frac{4 \times 12}{4 + 12} \Rightarrow 3 \Omega$$



$$R_S = 3 + 1 \Rightarrow 4 \Omega$$

$$\rightarrow R_{eq} = 4 \Omega$$


$$R_L = 6, I = \frac{30}{4+6} A$$

$$R_L = 16, I = \frac{30}{4+16} A$$

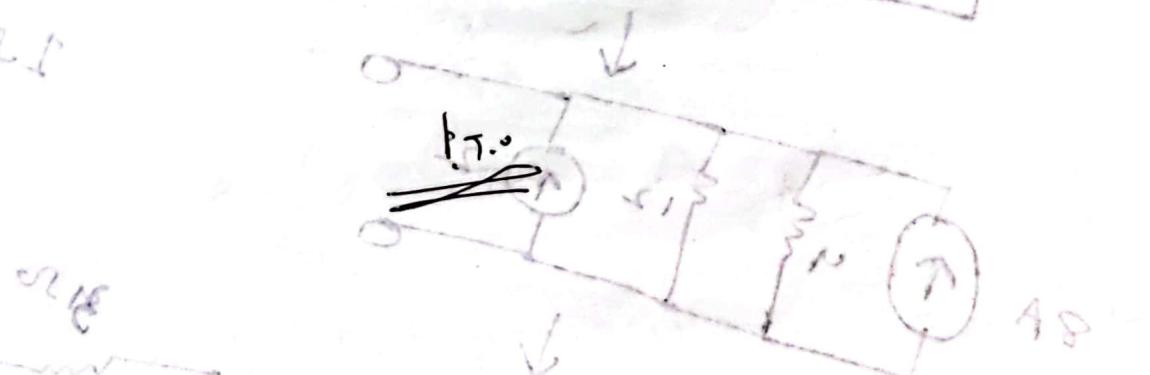

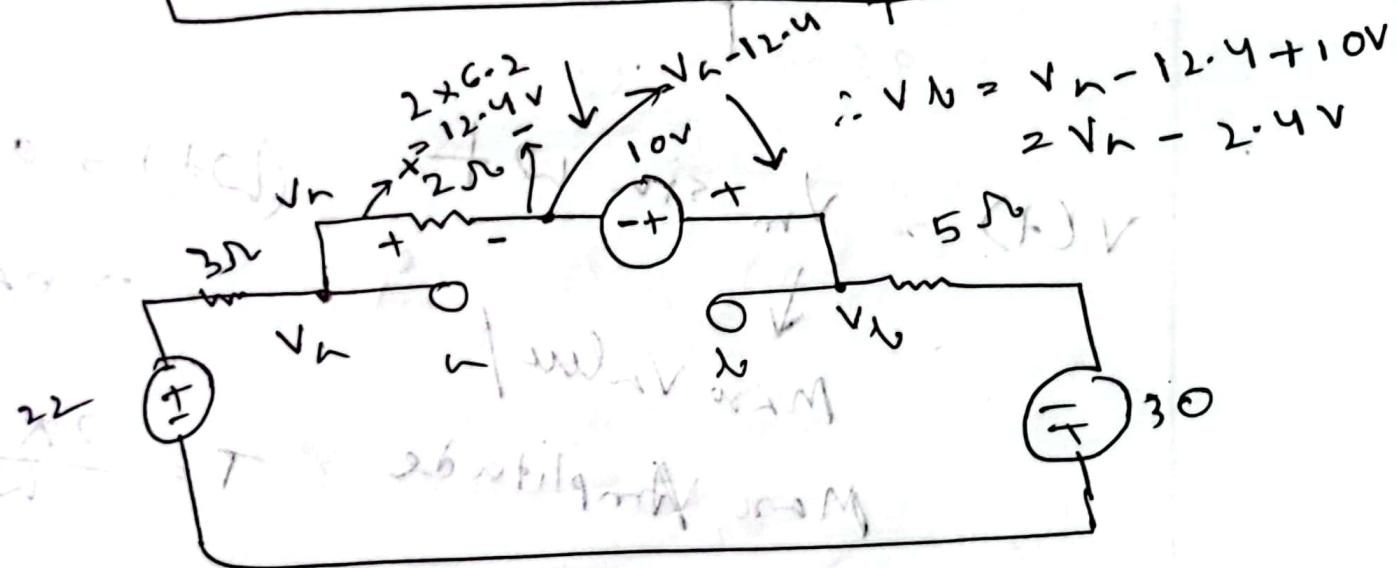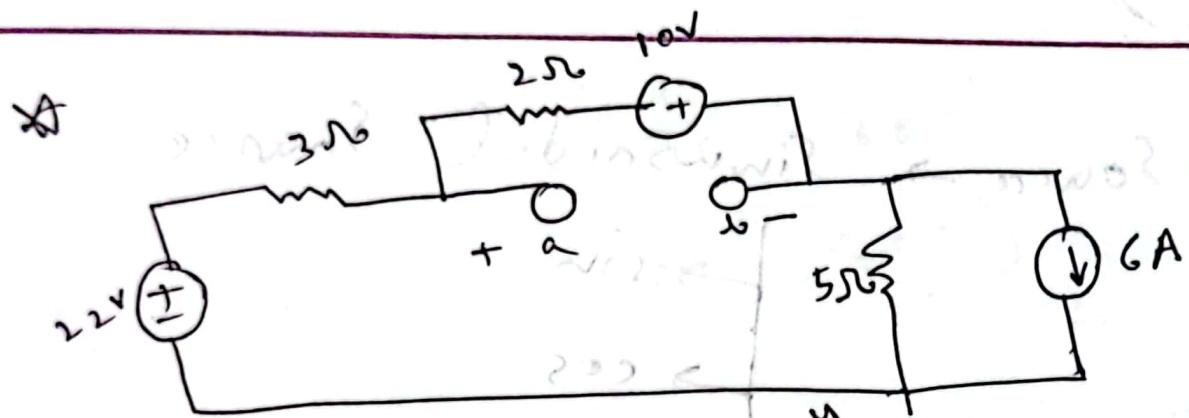

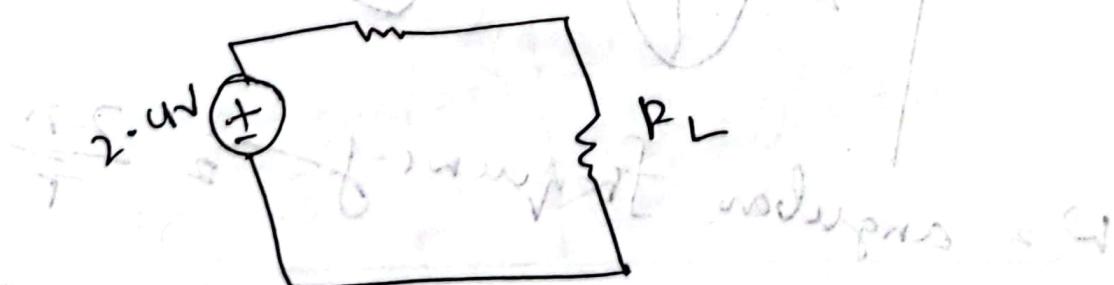
$$I = \frac{22 + 10 + 30}{3 + 2 + 5} = 6.2 \text{ A}$$



6.1
8.7 4.23

Chapter -


AC Circuit

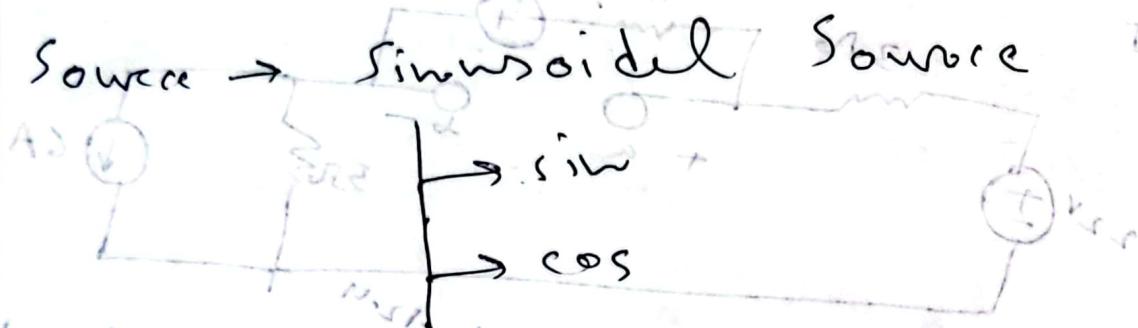

$$v(t) = V_m \sin(\omega t + \phi) \rightarrow \text{angle}$$

Max Value / Max Amplitude
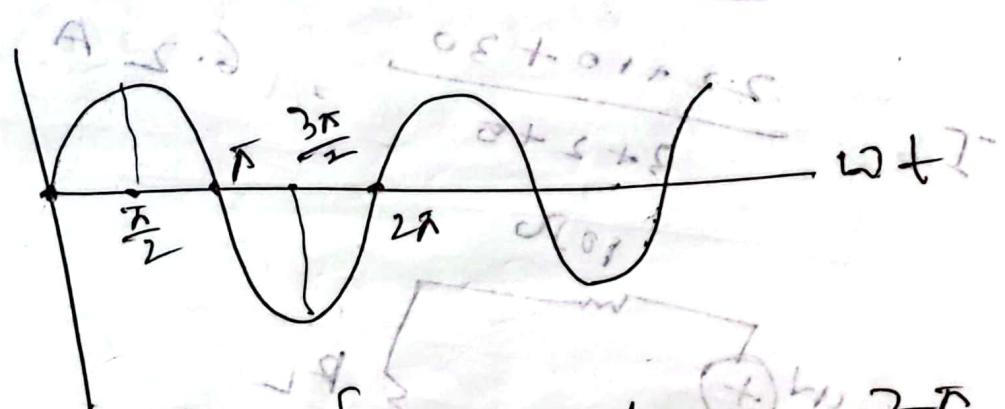
$$T = \frac{2\pi}{\omega} \rightarrow \text{radian}$$



$$\begin{aligned}\omega &= \text{angular frequency} \\ &= 2 \cdot \frac{2\pi}{T} \\ &= 2\pi f\end{aligned}$$

$$V_1 = V_m \sin(\omega t + 30^\circ)$$


$$V_2 = V_m \sin(\omega t - 30^\circ)$$

$$\phi_1 = 30^\circ \quad \phi_2 = -30^\circ$$

$$V_1 \text{ leads } V_2 \text{ by } 60^\circ$$

$$V_2 \text{ lags } V_1 \text{ by } 60^\circ$$
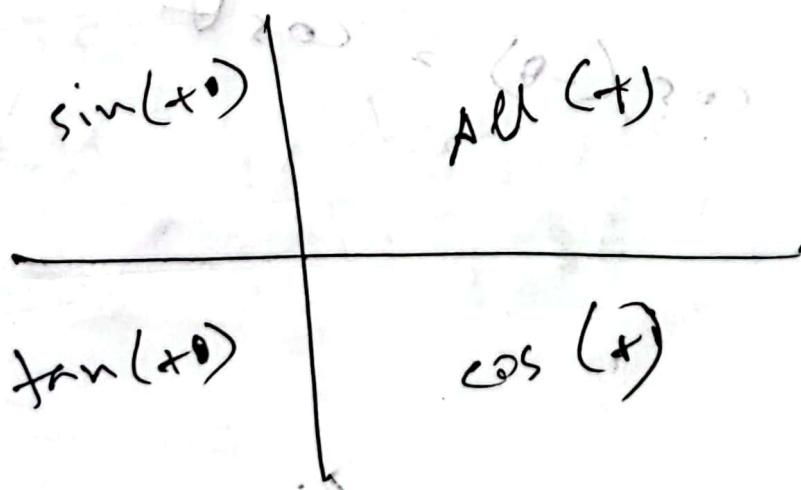
$$\Delta\phi = \phi_1 - \phi_2 = 30 - (-30) = 60^\circ$$



$\sin \rightarrow 90^\circ$ in front of axis $\rightarrow \cos$

$\sin \rightarrow 90^\circ$ in front of axis $\rightarrow \sin$

$$\sin(\omega t \pm 90^\circ) = \pm \cos \omega t$$

$$\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$$

$$\sin(\omega t \pm 180^\circ) = -\sin \omega t$$

$$\cos(\omega t \pm 180^\circ) = -\cos \omega t$$

$$\star \sin(-\theta) = -\sin \theta$$

$$\star \cos(-\theta) = \cos \theta$$

(2) \sin

(3) \cos

$$V_1 = -10 \cos(\omega t + 50^\circ)$$

$$V_2 = 12 \sin(\omega t - 10^\circ)$$

$$\rightarrow V_1 = 20 \sin(\omega t + 50 - 90^\circ)$$

$$(20 \sin(-40^\circ) + 10 \sin)(\omega t - 40^\circ)$$

$$\phi_1 = -40^\circ, \quad \phi_2 = -10^\circ$$

$$\Delta \phi = \phi_2 - \phi_1$$

$$= (-10) - (-40^\circ)$$

$$= 30^\circ$$

N_2 leads V_1 by 30°

V_1 lags V_2 by 30°

$$i_1 = -4 \sin(377t + 55^\circ)$$


$$i_1 \rightarrow 4 \cos(377t + 55^\circ + 90^\circ)$$
$$= 4 \cos(377t + 145^\circ)$$

$$i_2 = 5 \cos(377t - 65^\circ)$$

$$\therefore \phi_1 = 145^\circ, \quad \phi_2 = -65^\circ$$

$$\Delta \phi = 145 + 65 - 180^\circ = 20^\circ$$
$$\Delta \phi > \phi_2$$

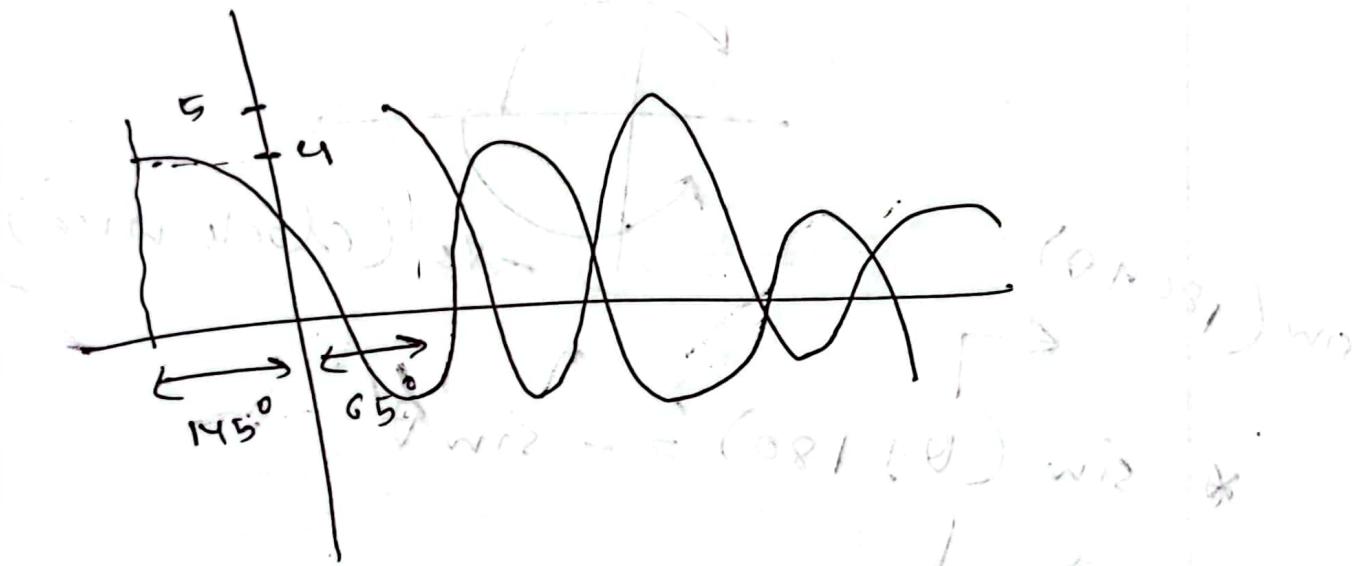$\therefore i_1$ leads i_2 with 210°
lagged by 60°



~~9.6~~


$$V_1 = 4 \cos(377t + 10^\circ)$$

$$V_2 = -20 \cos(377t + 180^\circ)$$

$$\phi_1 = 10^\circ, \quad \phi_2 = 180^\circ \quad \phi_2 > \phi_1$$

$$V_2 \text{ lags } V_1 \text{ with } 180 - 10^\circ = 170^\circ$$


→ 20 A $\angle -170^\circ$

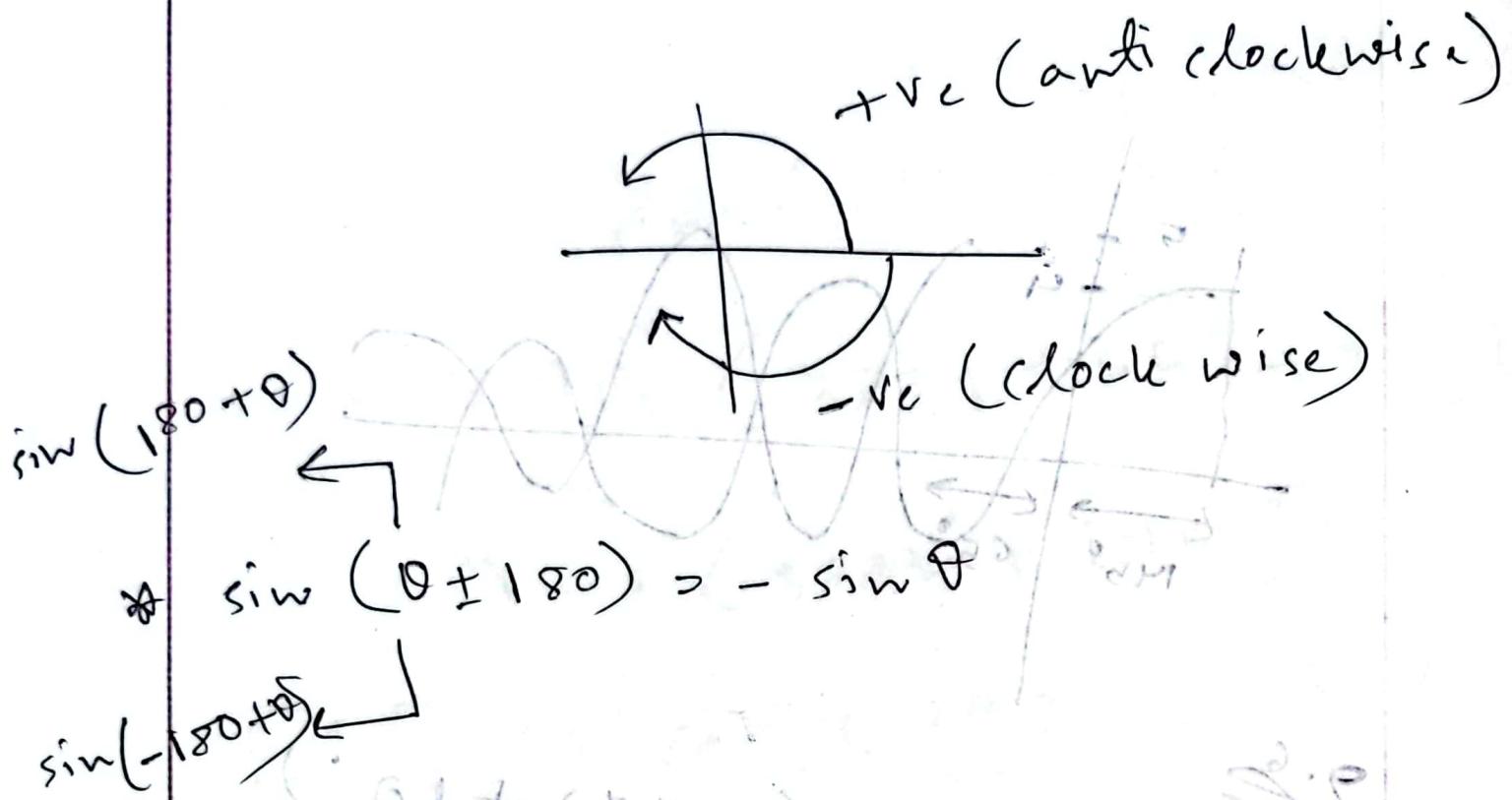

$$\cos(\theta \pm 180^\circ) = -\cos \theta$$

$$\sin(\theta \pm 90^\circ) = \pm \cos \theta$$
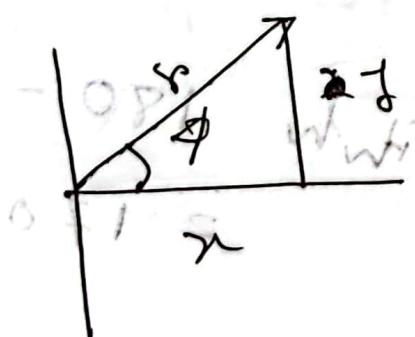
$$\cos(\theta \pm 90^\circ) = \mp \sin \theta$$



$$r = \sqrt{x^2 + j^2}$$

$$\tan \phi = \frac{j}{x}$$

$$\phi = \tan^{-1} \frac{j}{x}$$

$$x = r \cos \theta$$

$$j = r \sin \theta$$

$$V_{12} = 10 \cos \theta$$


$$\Rightarrow \text{int } 10 \sin (\theta - 90^\circ)$$

$$\Rightarrow 10 \sin (\omega t + 50^\circ - 90^\circ)$$

* Phasor

$$3+6j$$

$$r \angle \phi$$

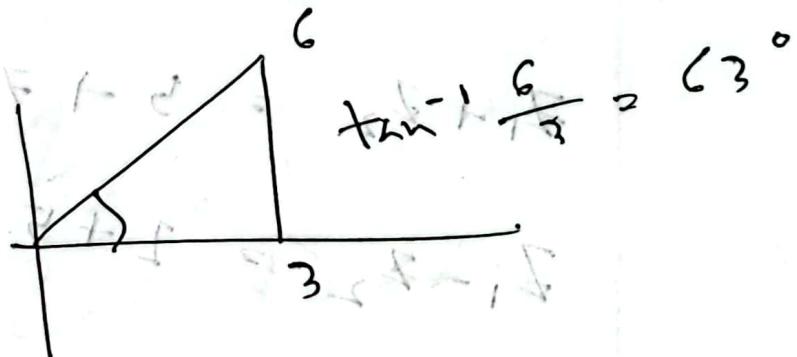

$$\sqrt{45} \angle 63^\circ$$

$$\sqrt{45} e^{j63^\circ}$$

$$e^{j\theta} = \cos \theta + j \sin \theta \rightarrow \text{Euler formula}$$

$$e^{j\pi} = \cos \pi + j \sin \pi = -1$$

$$e^{j\pi} = -1, \quad e^{j\pi} + 1 = 0$$

$\text{Re} \rightarrow \text{Real}$
 $\text{Im} = \text{Imaginary}$

$$z_1 = 3 + 6i$$

$$= \sqrt{45} \angle 63^\circ$$

$$\cos \theta = \text{Re}(e^{j\theta})$$
$$\sin \theta = \text{Im}(e^{j\theta})$$

$$z_2 = 2 + i$$

$$= \sqrt{5} \angle 26^\circ$$

$$z_1 + z_2 = 5 + 7i$$

$$z_1 - z_2 = 1 + 5i$$

$$|z_1 z_2| = \sqrt{45} \cdot \sqrt{5} \angle 63^\circ + 27^\circ$$

$$\frac{z_1}{z_2} = \frac{\sqrt{45}}{\sqrt{5}} \angle 63^\circ - 27^\circ$$

$$\frac{1}{z_1} = \frac{1}{\sqrt{45}} \angle -63^\circ$$

$$\sqrt{z_1} = \sqrt{(\sqrt{45})} \angle \frac{63^\circ}{2}$$

$$v(t) = V_m \cos(\omega t + \phi)$$



$$\rightarrow v(t) = V_m \operatorname{Re} \left(e^{j(\omega t + \phi)} \right)$$

$$\rightarrow v(t) = V_m \operatorname{Re} \left[e^{j\omega t} \cdot e^{j\phi} \right]$$

$$\rightarrow v(t) = V \operatorname{Re} \left[e^{j\phi} \right] \quad [V = V_m \operatorname{Re} \left[e^{j\omega t} \right]]$$

$$\rightarrow v(t) = V \angle \phi$$


$$v(t) = V_m \cos(\omega t + \phi) \leftrightarrow V, V_m \angle \phi$$

$$v_1(t) = 10 \cos(5t + 30^\circ)$$

$$\rightarrow 10 \angle 30^\circ$$

$$v_2(t) = 12 \cos(6t - 90^\circ)$$

$$\rightarrow 12 \angle -90^\circ$$

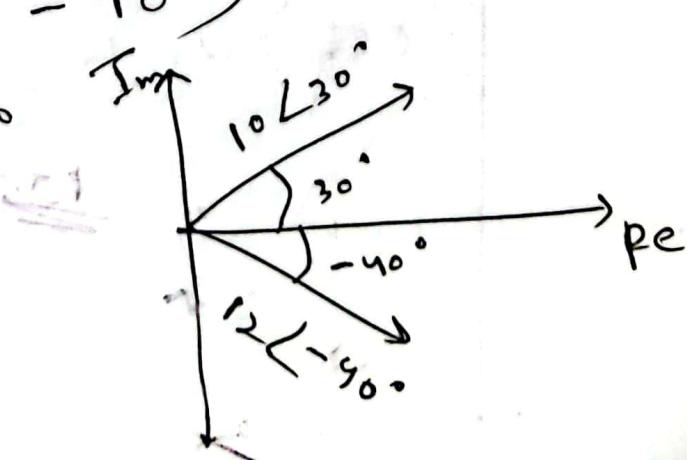

6W
11. 1. 23

Time Domain
Representation

AC

Phasor Domain
Representation

$$V_m \cos(\omega t + \phi) \xrightarrow{Z \rightarrow \infty} V_m \angle \phi$$

$$V_m \sin(\omega t + \phi) \xrightarrow{Z \rightarrow \infty} V_m \angle \phi - 90^\circ$$

$$\begin{aligned} & \text{DC bias} \\ & V_0 \xrightarrow{\text{DC bias}} V_0 \\ & \frac{dV}{dt} \xrightarrow{\text{DC bias}} j\omega V \end{aligned}$$

$$S \sqrt{2} \xrightarrow{\text{DC bias}} \frac{j\omega}{j\omega} V$$

$$4 \angle 30^\circ + 5 \angle 90^\circ$$

$$= 8 \angle 35^\circ \quad [\text{from calculator}]$$

$$\text{OP} = 8 \angle 35^\circ$$

$$\text{PT} = 8 \angle 35^\circ$$

$$\text{OP} = 8 \angle 35^\circ$$

$$\text{PT} = 8 \angle 35^\circ$$

$$\text{OP} = 8 \angle 35^\circ$$

$$\text{PT} = 8 \angle 35^\circ$$

$$\text{OP} = 8 \angle 35^\circ$$

$$* 4i + 8 \left(j\omega I - 3 \frac{dI}{dt} \right) = 50 \cos(2t + 75^\circ)$$

$$\Rightarrow 4I + 8 \frac{(I)}{j\omega} - 3 \cdot j\omega I = 50 \angle 75^\circ$$

$$I = \frac{50 \angle 75^\circ}{4 + \frac{8}{j\omega} - 3j\omega}$$

$$50 \angle 75^\circ$$

$$4 + 8(-j) \cdot \frac{1}{2} - 3j(2)$$

$$50 \angle 75^\circ$$

$$4 - 4j - 6j$$

$$4.64 \angle 143.199^\circ$$

$$= 4.64 \cos(2t + 143.199^\circ)$$

$$i = \sqrt{-1}$$


$$j^2 = -1$$

$$j = \frac{-1}{i}$$

$$-i = \frac{1}{i}$$

$$\text{Impedance} = \frac{V}{I}$$

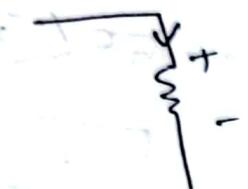Resistor (R) $R = 7\Omega, i(t) = 5 \cos(\omega t + 20^\circ)$




$$V = IR \Rightarrow V(t) = 35 \cos(\omega t + 20^\circ)$$

$$i = 5 \angle 20^\circ$$

$$V = 35 \angle 20^\circ$$

$$R = \frac{V}{I}$$

Capacitor (C) $V(t) = \frac{Q}{C} + P$

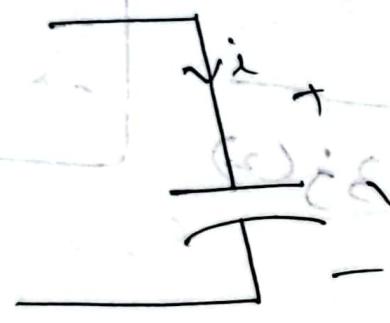

$$i(t) = \left(\frac{dV(t)}{dt} \right)$$

$$I = C j \omega V$$

$$\frac{V}{I} = \frac{1}{C j \omega}$$



Inductor (L) $V(t) = L - P$



$$V(t) = L \frac{di(t)}{dt}$$


$$V = L j \omega I$$

$$\frac{V}{I} = L j \omega$$

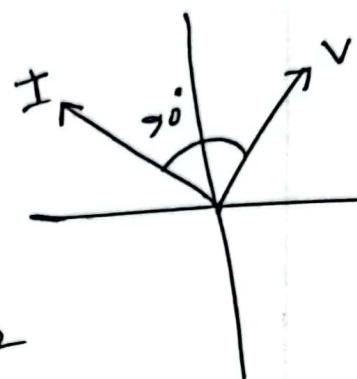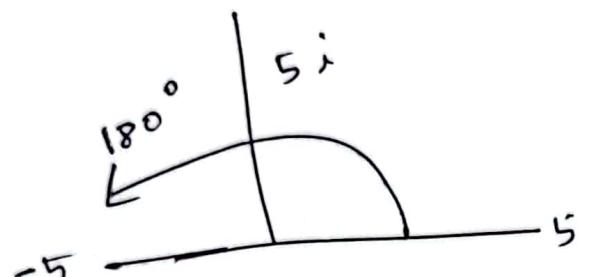

$$i = \sqrt{-1} = (-1)^{\frac{1}{2}}$$

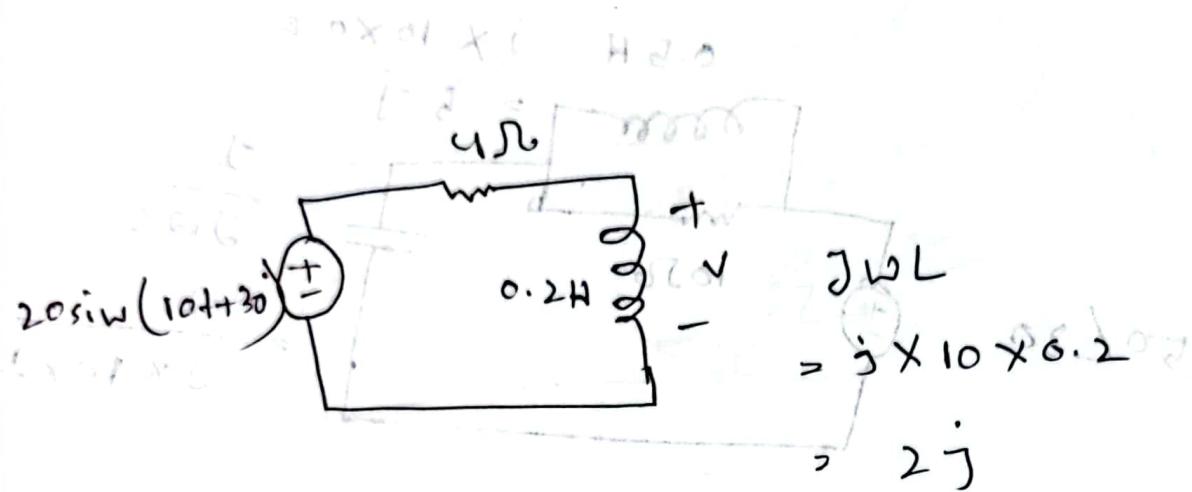$i \rightarrow 90^\circ \rightarrow$ Anti clockwise



$$i(t) = \frac{20e^{-60^\circ}}{9 + 2j}$$


$$= 4.47 e^{-86.5^\circ}$$

$$i(t) = 4.47 \cos(10t - 86.5^\circ)$$

$$V = 4.47 e^{-86.5^\circ} \times 2j$$

$$= 8.94 e^{(3.5^\circ)} \times \frac{j}{4.47}$$

ωL

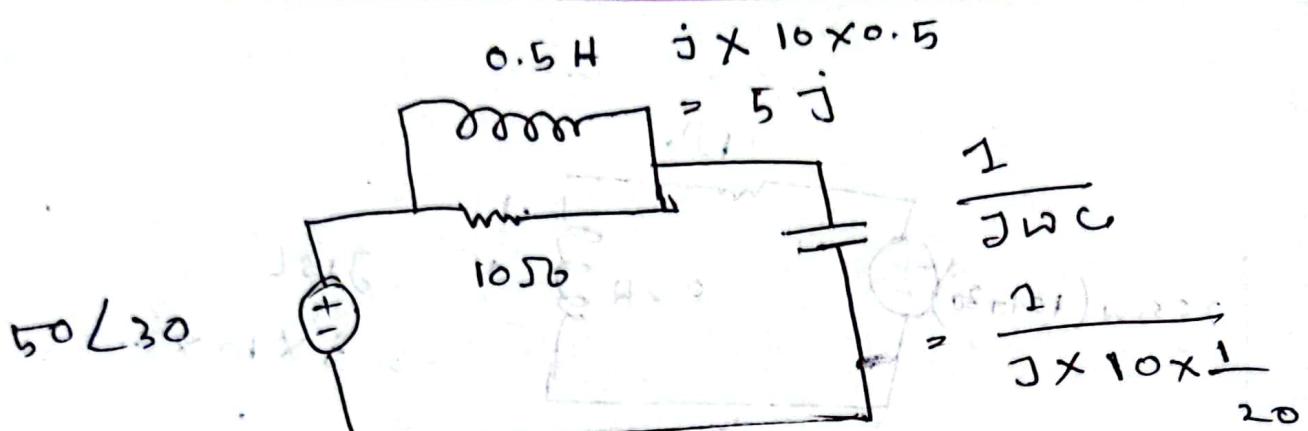



$$Z = \frac{5j \times 10}{10 + 5j} - 2j = -2j$$

$$\rightarrow 2.83 \angle 45^\circ$$

$$i = \frac{V}{Z} \rightarrow \frac{50 \angle 30^\circ}{2.83 \angle 45^\circ}$$

$$\rightarrow 17.67 \angle -15^\circ$$
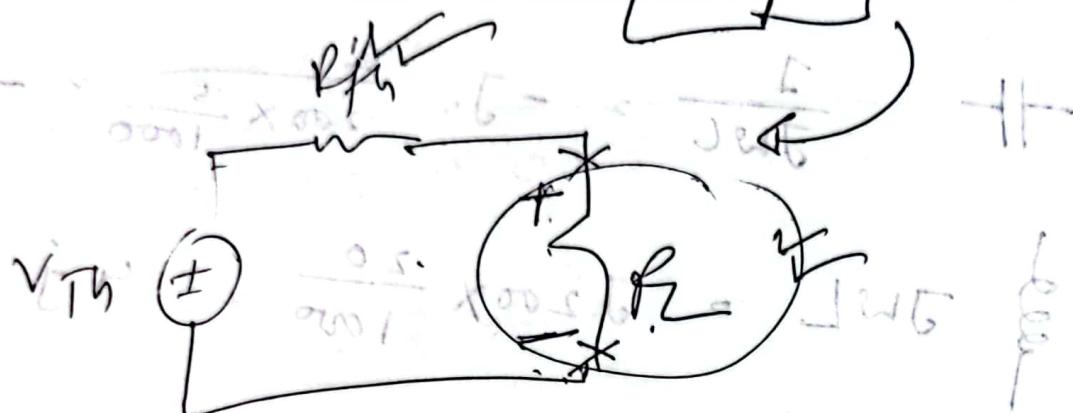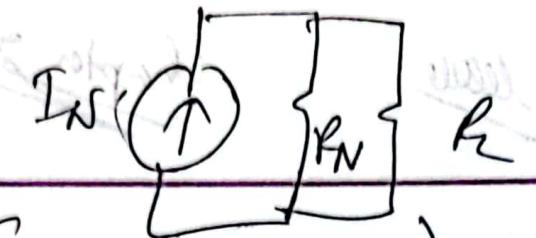
$$i = \frac{z_1}{z_1 + z_2} \times i(t)$$



$$\checkmark R_{Th} = R_L$$

$$I = \frac{V_{Th}}{R_{Th} + R_{Load}}$$

$$\frac{d(P_{RL})}{dR_L} > 0$$

$$P_{RL} = I^2 R_L$$

$$\left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 \times R_L$$

Hence

$$P_{RL} = \frac{V_{Th}^2}{R_{Th} + R_L + \frac{V_{Th}^2}{qR_L}}$$

(RTh = 12.5 + 0.1)

$$12.5 + 0.1 + 0.1 = 12.7$$

$$12.7 + 0.1 = 12.8$$

lecture

chapter-3

EC

$$+ \frac{1}{JWL} = -j \cdot \frac{1}{200 \times \frac{5}{1000}} = -j$$

$$\therefore JWL = J 200 \times \frac{20}{1000} = 4j$$

$$Z = 10 + 4j - j = 10 + 3j$$

$$\therefore I = \frac{50 \angle 0}{10 + 3j} =$$

$$= 4.789 \angle -16.699^\circ A$$

9.44

$$5mF = -j \frac{1}{200 \times \frac{5}{1000}} = -j$$

$$10mH = j 200 \times \frac{10}{1000} = 2j$$

$$\frac{(3-j) \times 2j}{3-j+2j} = \frac{(1.2 + 1.6j) \times 4}{1.2 + 1.6j + 4}$$

$$\Rightarrow 1.189 + 0.865j + 5 \\ \Rightarrow 6.189 + 0.865j$$

$$\therefore i = \frac{50 \angle 0^\circ}{6.189 + 0.85j}$$

(Ans)

$$i = 8 \cos(200t - 7.96^\circ) A$$

Q. 41

$$-I_H j \omega f = \frac{1}{j \omega C} = -j \quad I_H = j \omega L = j \quad V = 25 \angle 0^\circ$$



$$\frac{(1+j) \times (-j)}{2+j-j} \rightarrow \frac{j+1}{j+8+0j} = 2^{-j}$$

$$\therefore i = \frac{25 \angle 0^\circ}{2-j} = 10 + 5j$$

$$\therefore \frac{2+j}{2-j} = -j \rightarrow \frac{2+j}{2-j} \times (10+5j) = 5 + 15j$$

$$\therefore V = (5 + 15j) \times (-j) = 15 - 5j \\ = 15.81 \angle -18.43^\circ$$

4.23

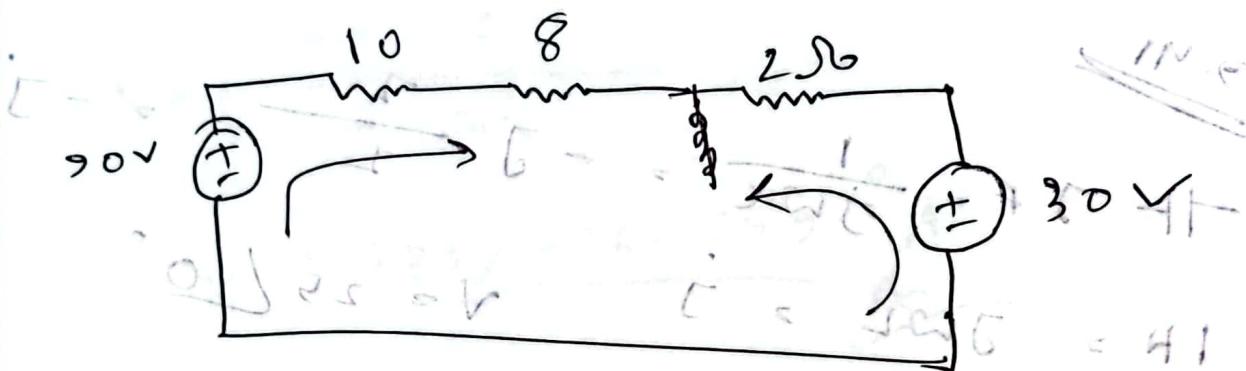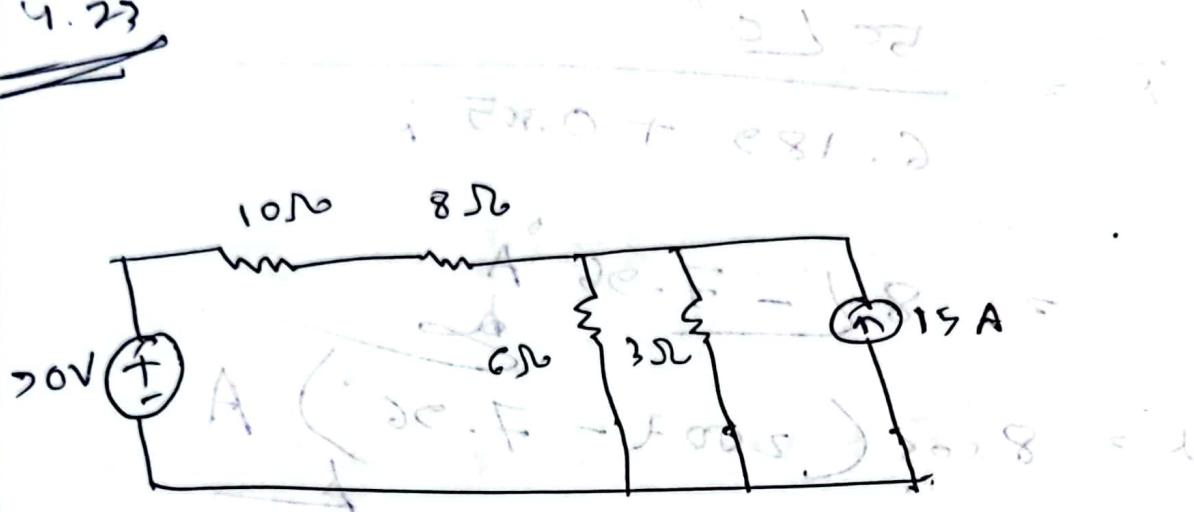


$$\therefore \text{I}_2 = \frac{90 - 30}{10 + 8 + 2} = \frac{(6)(4)}{18} = 4 \text{ A}$$

$$= 3 \text{ A}$$

$$\therefore P = I^2 R = 3^2 \times 8 = 72 \text{ W}$$

$$I_2 = 3 \text{ A} = (6) \times (4 + 3) / 18$$

$$P = 72 \text{ W}$$

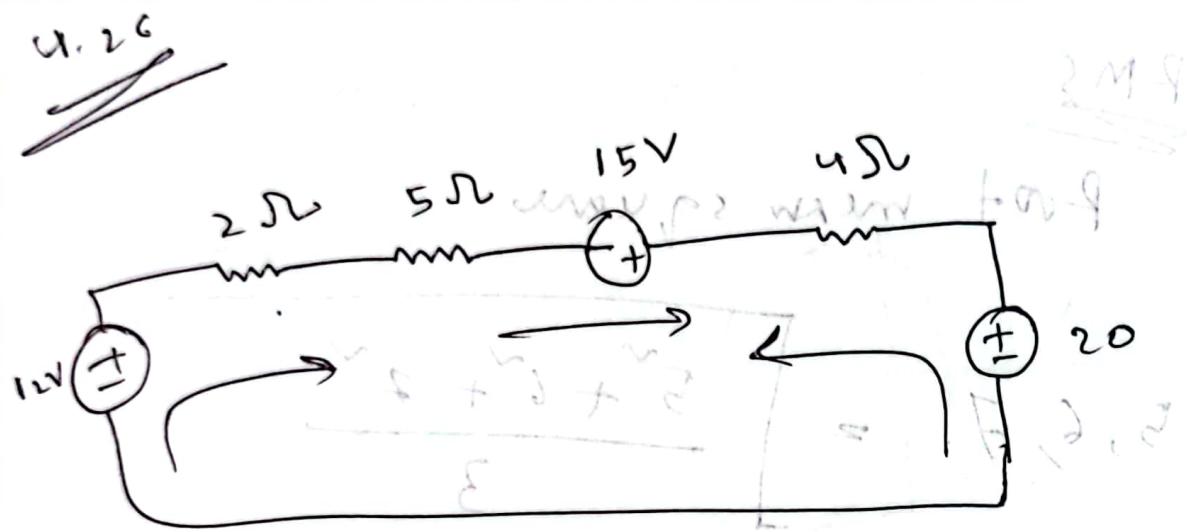

$$\therefore I_1 = \frac{12 + 15 - 20}{2 + 5 + 4} = 0.6363 \text{ A}$$

2M 8

U.W
29. 2.27

ES

RMS

Root mean square

$$\text{RMS} = \sqrt{\frac{5^2 + 6^2 + 7^2}{3}}$$

$x(t)$, Avg $\Rightarrow \frac{1}{T} \int_0^T x(t) dt$

RMS $\Rightarrow \sqrt{\frac{1}{T} \int_0^T x^2(t) dt}$


~~Ans - 3~~

$$i(t) \rightarrow 5 \cos 20\pi t$$

$$\omega = \frac{2\pi}{T}$$

$$\frac{2\pi}{T} = 20\pi$$

$$\therefore T = 0.1$$

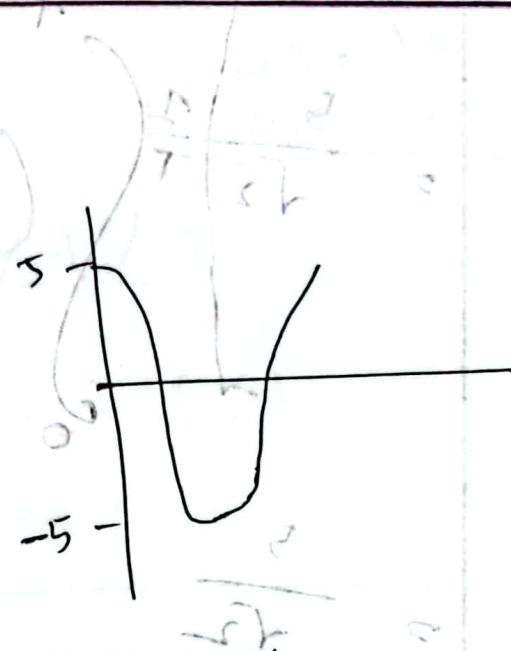

$$I_{rms} = \sqrt{\frac{2}{T} \int_0^T i^2(t) dt}$$

$$= \sqrt{\frac{2}{T} \int_0^T 25 \cos^2 20\pi t dt}$$

To write

$$\Rightarrow 5 \sqrt{\frac{2}{T} \int_0^T \cos^2 20\pi t dt}$$


using $\cos^2 \theta = \frac{1 + \cos 2\theta}{2}$

$$= 5 \sqrt{\frac{2}{2T} \int_0^T (1 + \cos 40\pi t) dt}$$

~~b.t:~~

$$2\cos^2 \theta = 1 + \cos 2\theta$$

$$2\sin^2 \theta = 1 - \cos 2\theta$$

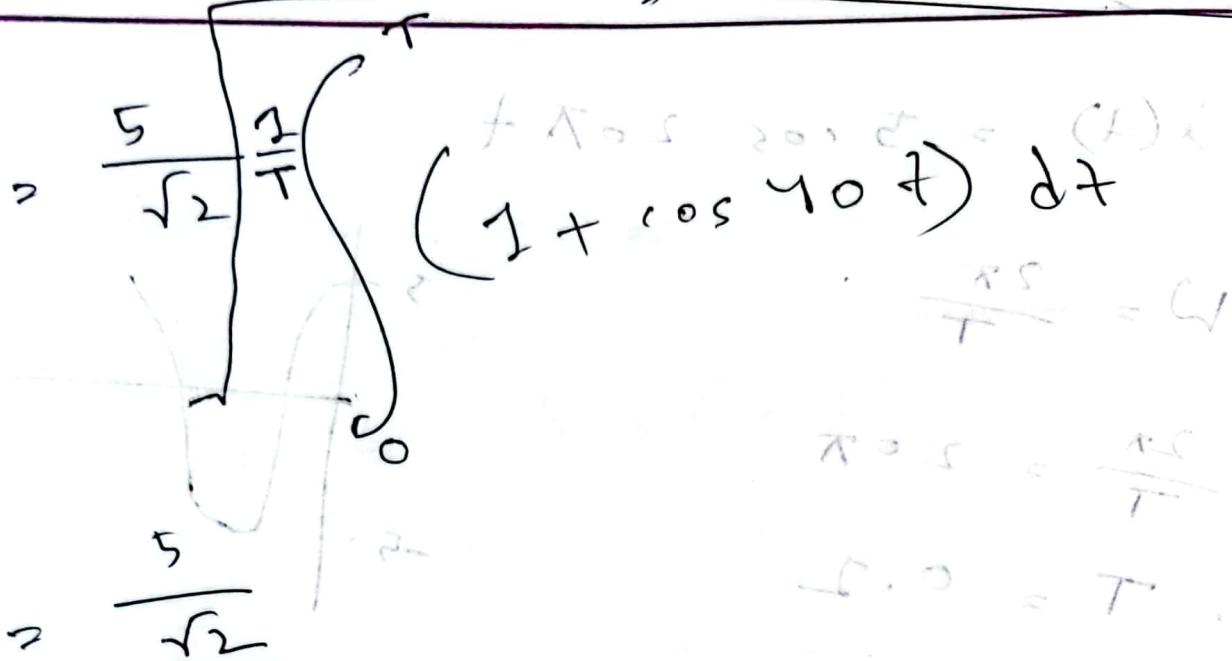

$$x(t) = A \cos \omega t + \frac{5}{\sqrt{2}}$$
$$x_{rms} = \frac{A}{\sqrt{2}}$$

* Full cycle integration of pure sin/cos wave is zero.

$$\int_0^T (A \cos \omega t + \frac{5}{\sqrt{2}})^2 dt$$

$$= \int_0^T A^2 \cos^2 \omega t + \frac{25}{2} dt$$

$$\begin{aligned} \delta &= mx \\ \Rightarrow i &= 5x \end{aligned}$$

$$\Delta S = 10 \quad \frac{10}{2} = 5$$

~~Exm. 11.7~~

$i(x) \rightarrow$ } $5x, 0 \leq x \leq 2$
 $-10, 2 \leq x \leq 4$

$$i(x) \quad \text{from } -5 \quad \text{to } 2$$


$$= \frac{1}{4} \left[\int_0^2 (5x)^2 dx + \int_2^4 (-10)^2 dx \right]$$

$$= \frac{1}{2} \left[25 \left[\frac{x^3}{3} \right]_0^2 + 100 [t]_2^4 \right]$$

~~PT:~~
~~for $x \in [-5, 4]$~~
 ~~$\int_{-5}^4 i(x) dx = \int_0^2 25x^2 dx + \int_2^4 100 dx$~~

$$j(x)$$

Follows

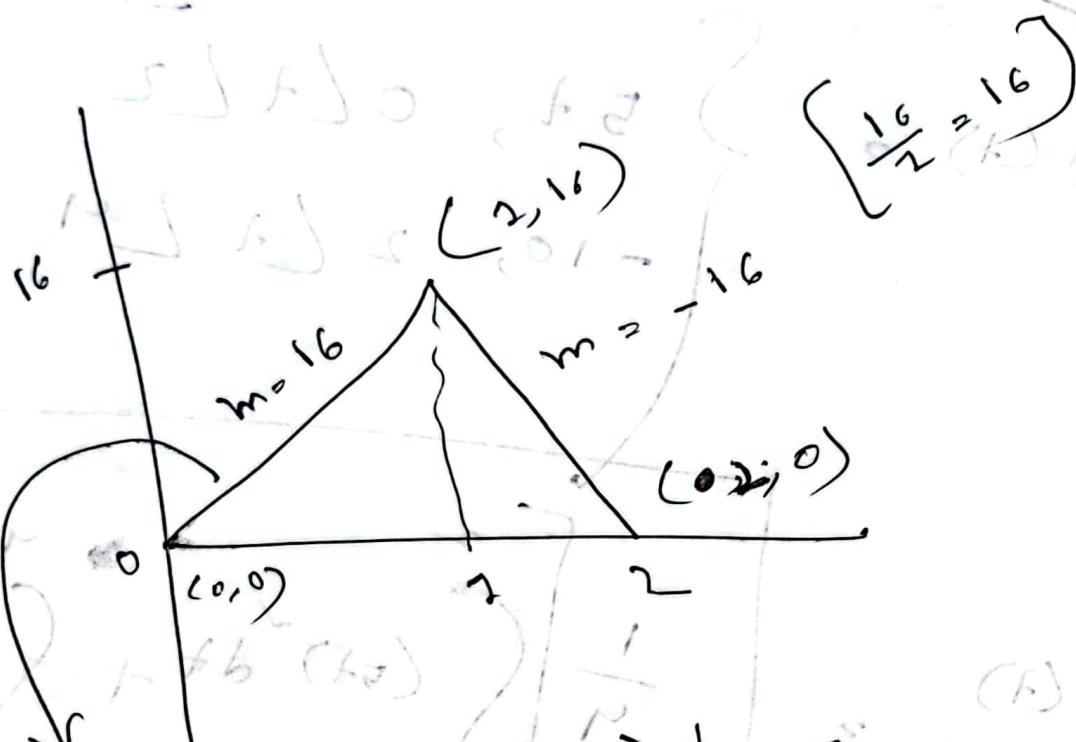

$$j = \begin{cases} 16x, & 0 \leq x \leq 2 \\ -8x + 32, & 2 < x \leq 4 \\ 0, & x < 0 \text{ or } x > 4 \end{cases}$$

$$j - 0 = 16(x - 0)$$

$$\Rightarrow j = 16x$$
$$\Rightarrow j = -8x + 32$$

$$\Rightarrow j = 16x$$

$$j(x) = \begin{cases} 16x, & 0 \leq x \leq 2 \\ -8x + 32, & 2 < x \leq 4 \\ 0, & x < 0 \text{ or } x > 4 \end{cases}$$

~~Ass-2~~

$i(t) = A \sin(\omega t)$

i_t

$\frac{\pi}{2}$

$\sin \cos$

$i_b = A \sin(\omega t + \frac{\pi}{2})$

~~next day~~

$\sin^2 \cos^2$



$i_b = A \sin(\omega t + \frac{\pi}{2})$

$T = 2\pi$

$T = 2\pi$

$$i(t) = A \sin \omega t$$

$$\left[\begin{array}{l} T = 2\pi \\ \omega = \frac{2\pi}{T} \end{array} \right]$$

$$\omega = 1$$

for representing $\sin \omega t$ we just

gives the value of

P.T.

A 585

T

$$= \frac{1}{\sqrt{\pi}}$$



$$\int_0^\pi (4 \sin^2 t)^2 dt$$

$$= \frac{1}{2\sqrt{\pi}}$$

T

$$\int_0^\pi (2 \cdot 2 \sin^2 t)^2 dt$$

$$= \frac{1}{2\sqrt{\pi}}$$

T

$$\int_0^\pi [2(1 - \cos 2t)]^2 dt$$

$$\Rightarrow \frac{2\pi}{2\sqrt{\pi}}$$

$$\int_0^\pi (2 - 2\cos 2t + \cos^2 2t) dt$$

$$\Rightarrow \frac{2}{2\sqrt{\pi}} \left[t \right]_0^\pi - \left[\frac{2 \sin 2t}{2} \right]_0^\pi$$

$$+ \int_0^\pi \frac{1}{2} \cdot 2 \cos^2 2t dt$$

$$= 1.382$$

A

~~complex power~~

$$v(t) = 60 \cos(\omega t - 10^\circ)$$

$$V_{\text{rms}} = \frac{60}{\sqrt{2}} \angle -50^\circ$$

$$I_{\text{rms}} = \frac{1.5}{\sqrt{2}} \angle -50^\circ$$

$$i(t) = -1.5 \angle 50^\circ$$

$$i_{\text{rms}} = \frac{1.5}{\sqrt{2}} \angle 50^\circ$$

$$(i_{\text{rms}})^* = \frac{1.5}{\sqrt{2}} \angle -50^\circ$$

$$P = V_{\text{rms}} \cdot (I_{\text{rms}})^*$$

$$= \left(\frac{60}{\sqrt{2}} \angle -10^\circ \right) \cdot \left(\frac{1.5}{\sqrt{2}} \angle -50^\circ \right)$$

Power in AC circuits

Complex power, $S = V_{rms} (I_{rms})^*$

$$(S = V_i - I_i) \Rightarrow S = P + jQ = (V_i)^2$$

$$\text{Apparent power } S = \sqrt{P^2 + Q^2}$$

$$\text{Real power, } P = \text{Re}(S) = S \cos(\phi_v - \phi_i)$$

$$\text{Reactive } Q = \text{Im}(S)$$

$$= S \sin(\phi_v - \phi_i)$$

$$P = V_i I_i \cos(\phi_v - \phi_i)$$

$$Q = V_i I_i \sin(\phi_v - \phi_i)$$

$$S = \sqrt{P^2 + Q^2}$$

~~EC Ass 2~~

~~8~~

~~Wave: 2~~

$$v(t) = \begin{cases} 10 \sin t, & 0 \leq t < \pi \\ 0, & \pi \leq t < 2\pi \end{cases}$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt} \text{, wave 2 A}$$

$$\Rightarrow \sqrt{\frac{1}{2\pi} \left[\int_0^\pi (10 \sin t)^2 dt + \int_\pi^{2\pi} 0^2 dt \right]}$$

$$\therefore P = \frac{V^2}{R} = \frac{25}{10} = 2.5 \text{ watt}$$

~~Wave: 2~~

~~Wave: 2~~ $v(t) = \text{wave 2 signal}$

$$v(t) = \begin{cases} 100 \sin t, & 0 \leq t < \pi \\ 0, & \pi \leq t < 2\pi \end{cases}$$

$$\therefore V_{rms} = \sqrt{\frac{1}{T} \int_0^T (100 \sin t)^2 dt} = 70.71 \text{ V}$$

$$\therefore P = \frac{V^2}{R} = \frac{(70.71)^2}{10} = 499.99 \text{ W}$$

~~real P, active P~~

$$P_{avg}, P = \overline{(I_{rms})^2} \times R$$

$$= \left(\frac{1.95}{\sqrt{2}} \right)^2 \times 8.19$$

$$\Rightarrow 15.57 \text{ watt}$$

App power, $S = \sqrt{I_{rms}^2 + V_{rms}^2}$

$$= \frac{16}{\sqrt{2}} \times \frac{1.95}{\sqrt{2}}$$

$$= 15.6 \text{ VA}$$

Reactive P, Q = $\sqrt{S^2 - P^2}$

$$= 0.964 \text{ VAR}$$

Complex Power = $(V_{rms}) \times (I_{rms}^*)$

$$= \left(\frac{16}{\sqrt{2}} \angle 45^\circ \right) \times \left(\frac{1.95}{\sqrt{2}} \angle -39.62^\circ \right)$$

$$\Rightarrow 15.53 + 1.465 i$$

$$\Rightarrow 15.6 \angle 5.39^\circ$$

~~ANS~~ 8

$$v(t) = \begin{cases} V_m \sin(\omega t + \phi) & t < 0 \\ 0, \text{ for } t \in [0, 2\pi/\omega] \end{cases}$$

$$\begin{aligned} V_{m\text{~avg}} &= \frac{1}{T} \int_0^T v(t) dt = \frac{1}{2\pi} \int_0^{2\pi} (V_m \sin t) dt \\ &= \frac{1}{2\pi} \left[\frac{V_m}{2} (1 - \cos 2t) \right]_0^{2\pi} \\ &= \frac{1}{2\pi} \cdot \frac{V_m}{2} \cdot [0] \\ &= \frac{V_m}{2\pi} \cdot 0 \end{aligned}$$

$$2.5 = \frac{\frac{V_m}{2\pi}}{10} \Rightarrow \frac{V_m}{2\pi} = 25 \Rightarrow V_m = 50\pi$$

$$V_m =$$

~~Formulas~~

$$\sin(wt \pm 180^\circ) = -\sin wt$$


$$\cos(wt \pm 180^\circ) = -\cos wt$$

$$\sin(wt \pm 90^\circ) = \pm \cos wt$$

$$\cos(wt \pm 90^\circ) = \mp \sin wt$$

* $\sin(-\theta) = -\sin \theta$

* $\cos(-\theta) = \cos \theta$

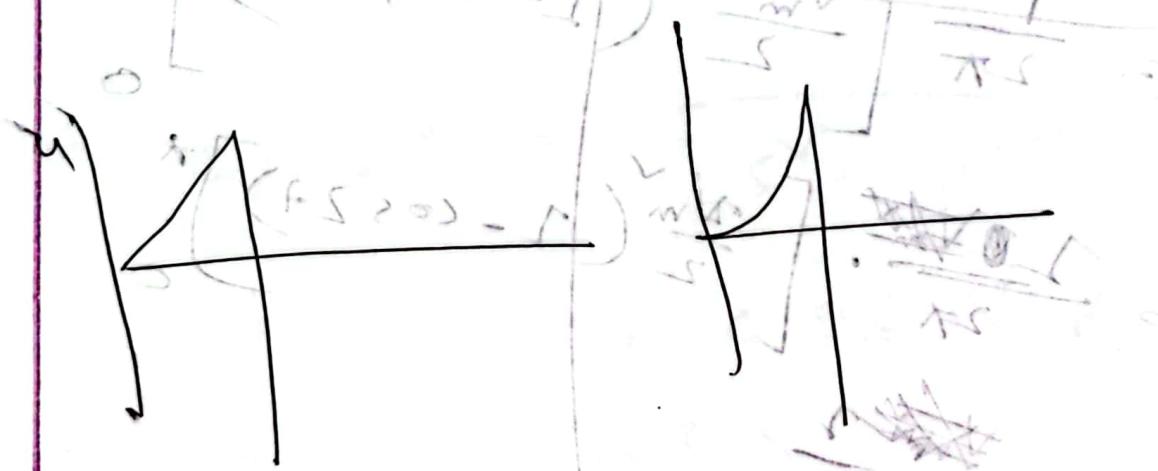


$$\omega S = \frac{wV}{\pi c}$$

$$\omega D = wV$$

$$= wV \alpha$$
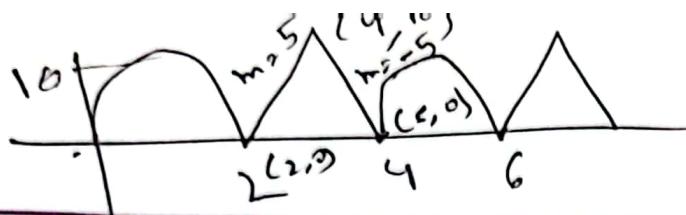
$$\frac{wV}{\pi c} \times 2 \cdot \alpha$$



$$v_m = \sqrt{\frac{1}{\pi}} \int_0^t (100 - \sin t)^2 dt$$

* $i(t) = \begin{cases} 10 \sin \frac{\pi t}{2} & 0 \leq t \leq 2 \\ 10t & 2 \leq t \leq 4 \\ -10t & 4 \leq t \leq 6 \end{cases}$

$$\Rightarrow \begin{cases} j - 0 = 5(x-2) \\ j = 5x - 10 \\ \Rightarrow 5t - 10 & 2 \leq t \leq 4 \end{cases} \quad \begin{aligned} j - 0 &= 5(x-0) \\ j &= 5x + 30 \\ -5t + 30 &\text{ (cancel)} \end{aligned}$$

$$i(t) = \frac{1}{6} \left[\int_0^t (10 \sin \frac{\pi t}{2})^2 dt + \int_2^t (5t - 10)^2 dt + \int_4^t (-5t + 30)^2 dt \right]$$