

# Bashudhara

Name : Sadman  
Institute : 011211592  
Subjects : Electronics  
Roll No : \_\_\_\_\_ Section : C

~~W  
28.5.23~~

## Electronics

# types of material based on conductivity → (conductors, insulators, semiconductors)

- (I) Conductors (metals) - e.g. Cu, Al, Ag, Fe, etc.
- (II) Insulators (Air, Glass, Wood, rubber, plastic)

- (III) Semiconductors

# Differences between electrical circuit & Electronic Circuit.

→ Electronic circuit has decision making capability.

Electrical circuit has no decision making capability.

## 1st chapter

Assignment - 2 (Submission next week sunday)

(Fall-22 - Spring 23)

\* basic facts to be quotes or print out  
\* mid. final exam (ii)  
(start writing)

# Characteristic of Semiconductors:

(i) Semiconductors can be elemental

or compound which consist of

(ii) Elemental semiconductors have

four valence electrons & they

form covalent bond.

(iii) Si & Ge etc are elemental

semiconductors.

(iv) Compound semiconductors are

like As, like P, like N etc.

and etc.

# Types of semiconductor :-

(i) Intrinsic (pure semiconductor)

(ii) Extrinsic (doped)

→ p-type  
→ n-type

$N \rightarrow I_P$   $I_D \rightarrow N$   
 $I_D \rightarrow P$

A, B, C, D, E, F, G, H, I, J, K, L, M, N, O, P, Q, R, S, T, U, V, W, X, Y, Z

1. Electrons  
2. Holes


1.2.3

C.V  
21.5.23

## Electronics
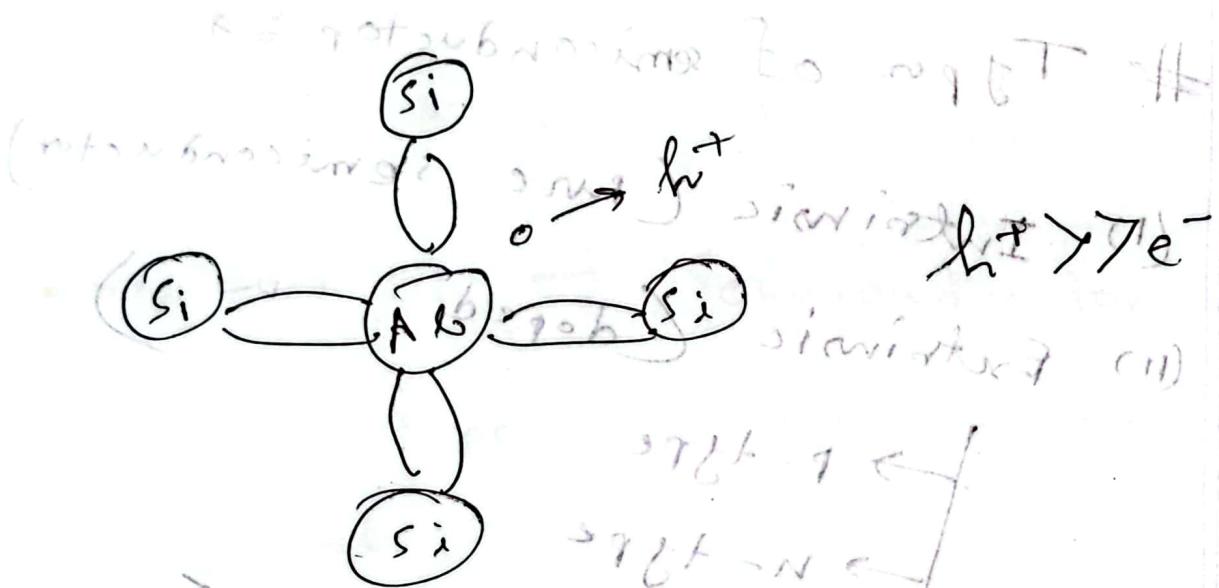
# P-type Semiconductor  $\rightarrow$  (foreign particle)

$$\text{O} = -1 \cdot 6 \times 10^{-19} (+1 \cdot 6 \times 10^{-19}) \text{ eV III} \rightarrow \text{B, Al, Ga}$$
$$= e^- + h^+$$
$$\text{IV} \rightarrow (\text{host})$$




majority carrier  $\rightarrow h^+$

minority carrier  $\rightarrow e^-$

# N-type :  $\rightarrow$

$$e^- \rightarrow h^+$$


group 5 :  $\rightarrow$  N, P, As

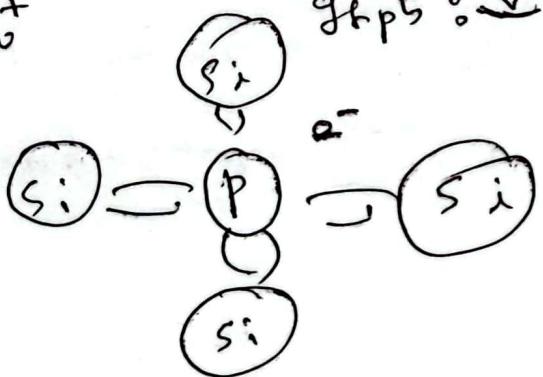

majority : e<sup>-</sup>

minority : h<sup>+</sup>
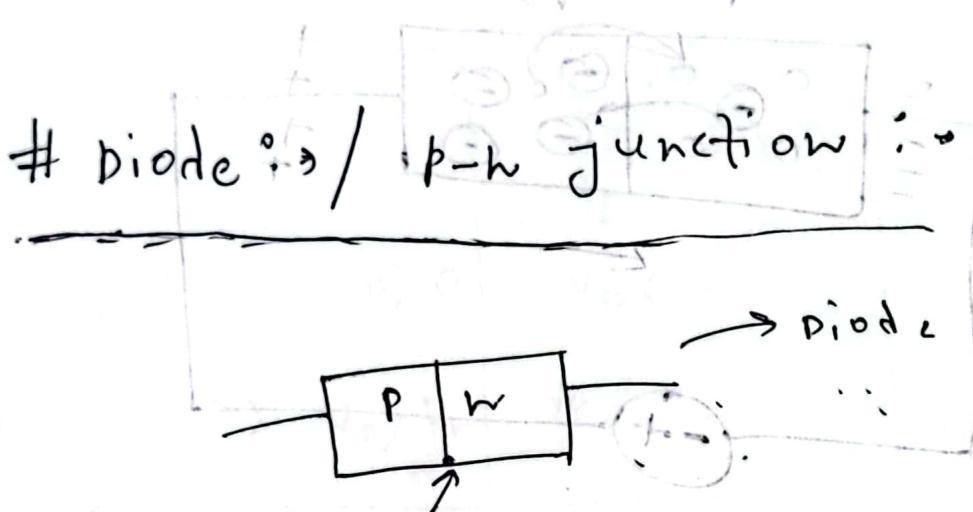
# Intrinsic semiconductor:  $e\tau = h^+$   
 So majority, minority carrier hot available.




# forward biasing:

$$(1) V_F (+) \sim P(P)$$

$$I_D \uparrow (P \rightarrow n)$$

(II) majority: ✓  
 (III) minority: X


(not moving)

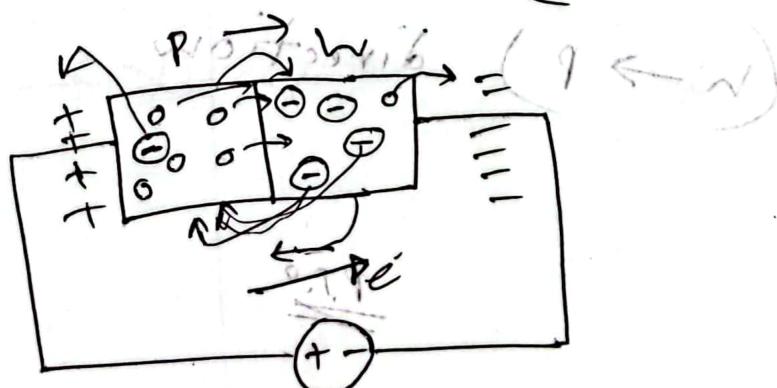

P.I.

# Reverse biasing  $\Rightarrow$  minority H

(I)  $V_S (+) \rightarrow P (-) (n)$

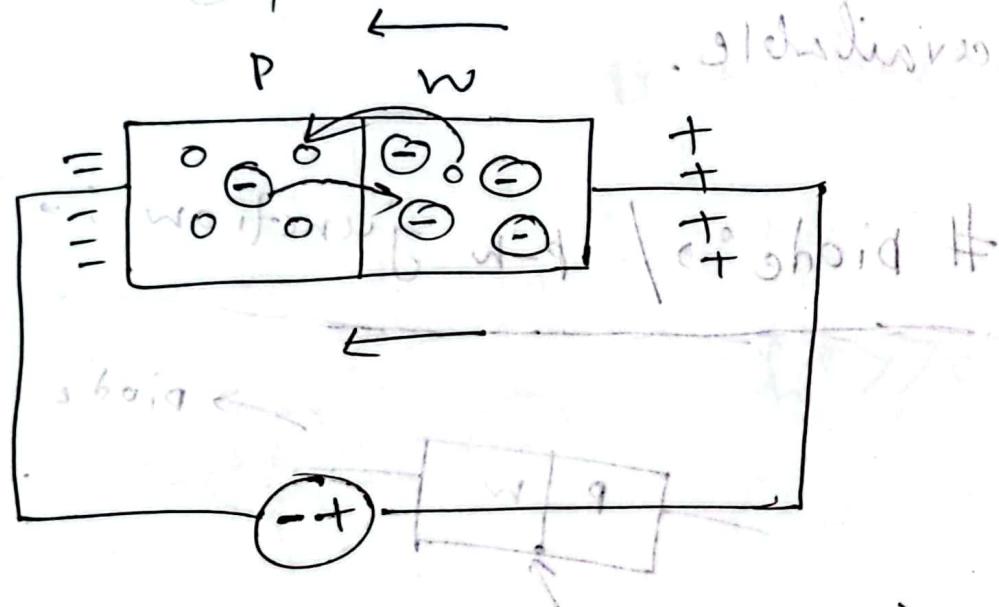


(II) majority: X (not moving)

(III) minority: ✓ (moving)

$I_b \approx 0$  but  $I_d \neq 0$

$(n \rightarrow p)$  direction

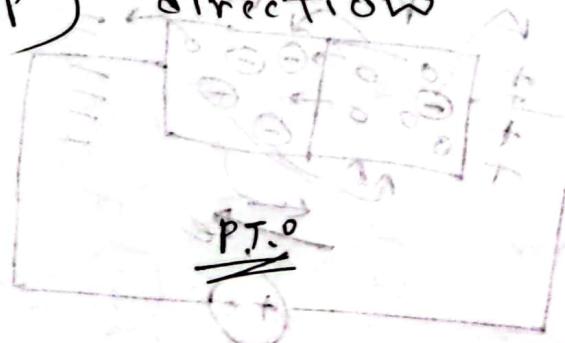


bias  $\rightarrow$  force

# No bias:  $\Rightarrow$

$\Rightarrow$  voltage difference = 0


Current = 0

FB	$R_B$	NB
(i) $V_D \rightarrow V_D > 0$ $V_D = (V_P - V_N)$	$V_D < 0$ $V_P < V_N$	$V_D > 0$ $V_P = V_N$
(ii) $I_D \rightarrow$ high $(P \rightarrow N)$	Almost zero $(N \rightarrow P)$	$I_D = 0$
(iii) majority $\rightarrow \checkmark$	$\times$	$\times$
(iv) minority $\rightarrow \times$	$\checkmark$	$\times$

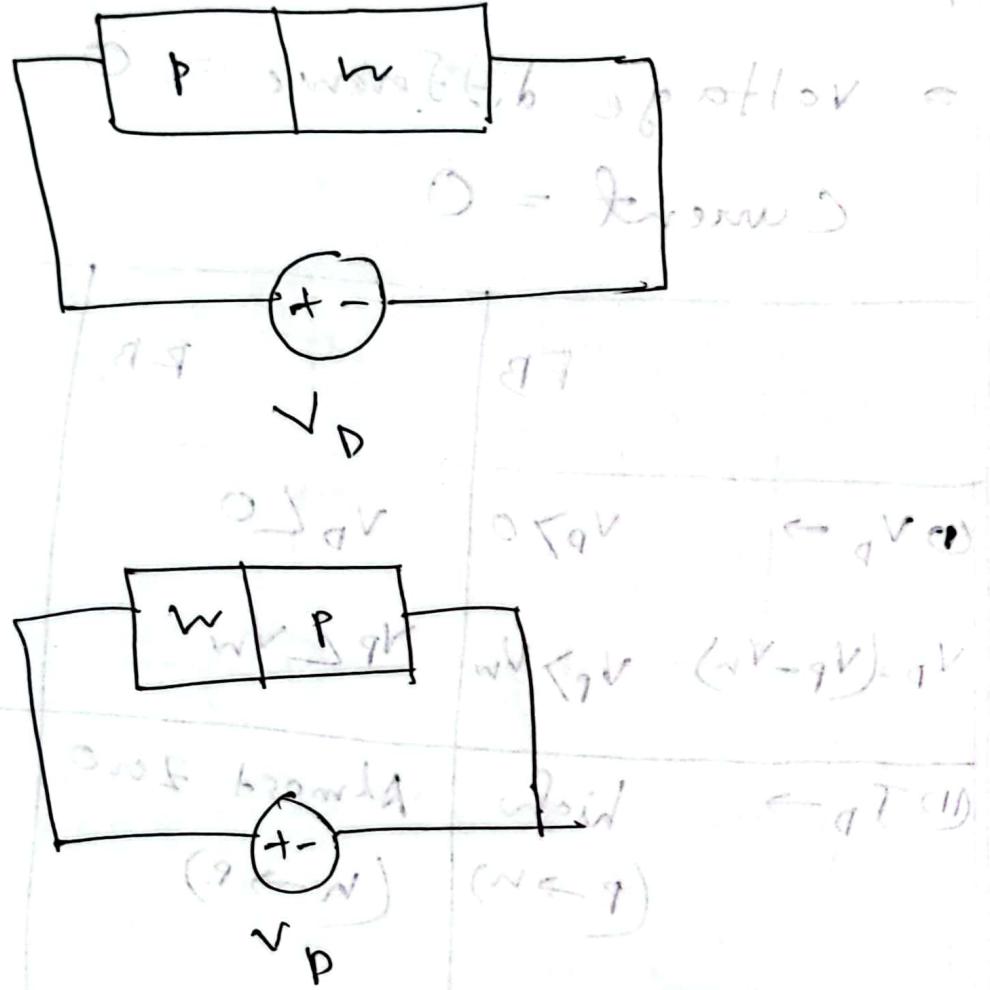

$\rightarrow V_D = 10V \rightarrow$  Reverse bias

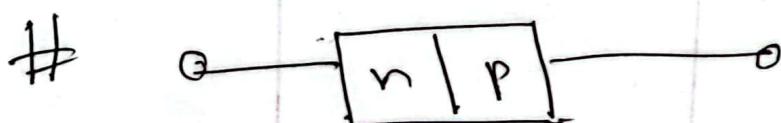$\rightarrow V_D = -10V \rightarrow$  forward bias



(a) +5V  $+5V \rightarrow$  No bias

(b) +5V  $-5V \rightarrow$  reverse

(c) -5V  $+5V \rightarrow$  forward

# Class Test : 1 (Sunday) P


# Assignment : 2 (Sunday)

C.W  
u. 6. 23

Circuit symbol of diode



# I-V curve of diode  $\Rightarrow$

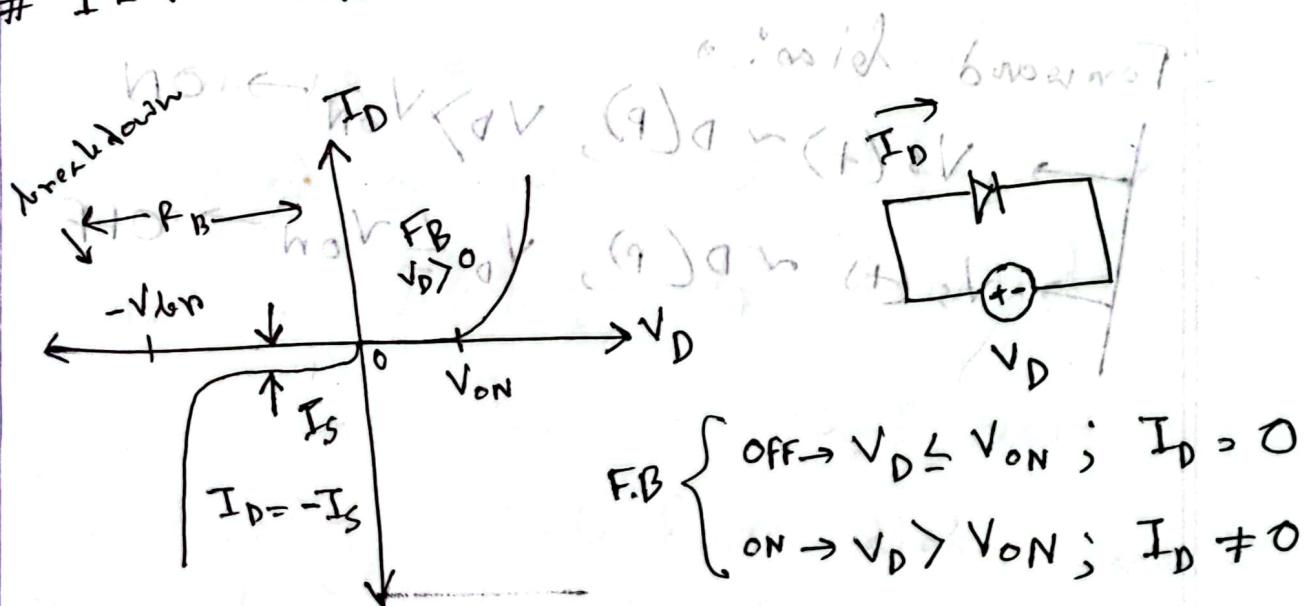

$$V_T = \frac{kT}{q}$$

$k$  = Boltzmann constant  
 $= 1.38 \times 10^{-23} \text{ J/Kelvin}$   
 $T$  = Temperature in Kelvin  
 $= \text{Degree} + 273$

$$I_D = I_S e^{\frac{V_D}{nV_T}}; V_D > V_{ON}$$

$I_S$  = Reverse Saturation Current  
 $n$  = Ideality factor  
 $V_T$  = Thermal voltage

$q = \text{charge of an electron}$

$$= 1.6 \times 10^{-19} \text{ C}$$

(forward biasing)

Reverse bias:  $\Rightarrow$

$$\rightarrow V_s(+)\sim D(w), |V_D| < |V_{br}|$$

shock to load  $\rightarrow P\beta$

$$\rightarrow V_s(+)\sim D(w); |V_D| \geq |V_{br}|$$

$\rightarrow$  Breakdown

Forward bias:  $\Rightarrow$

$$\rightarrow V_s(+)\sim D(p), V_D > V_{on} \rightarrow \text{ON}$$

$$\rightarrow V_s(+)\sim D(p), V_D \leq V_{on} \rightarrow \text{OFF}$$

$D \propto T$  ( $T \neq qV_{on}$ )

$O \propto kT$  ( $kT \leq qV_{on}$ )

so  $kT \ll qV_{on}$


$$kT \propto \frac{qV}{T} \Rightarrow qV = kT \cdot \frac{T}{\beta} = rV$$

Known resistance  $r = \frac{V}{I}$   $\Rightarrow$   $I = \frac{V}{r} = \frac{V}{kT/\beta} = \frac{\beta V}{kT}$

so  $I = \frac{\beta V}{kT}$   $\propto V$   $\propto \frac{1}{T}$   $\propto \frac{1}{T}$

so  $I = \frac{\beta V}{kT} = \frac{V}{R}$   $\Rightarrow R = \frac{kT}{\beta}$

L.W

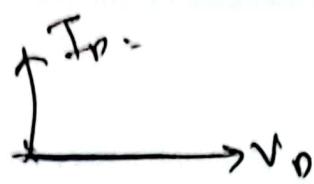

Electronics

F.B

$$I_D > 0 ; V_D \leq V_{on}$$

$$I_D = I_s e^{\frac{V_D}{nV_T}}$$

$$V_D > V_{on}$$

R.B

$$I_D = \alpha (V_D - V_{br})$$

$$I_D = -I_s W_D (V_{br})$$

the following voltage

# A voltage of one point two volt is applied across a diode whose turn on voltage is breakdown voltage are 2 volt & 5 volt

respectively. Calculate diode current if  $T_{br} = 1$  and  $I_s = 100 \text{ nA}$ .

(a)  $V_D = 2 \text{ volt}$


(c)  $T_{br} = 5, V_D = -10 \text{ volt}$

(b)  $V_D = 10 \text{ volt}$

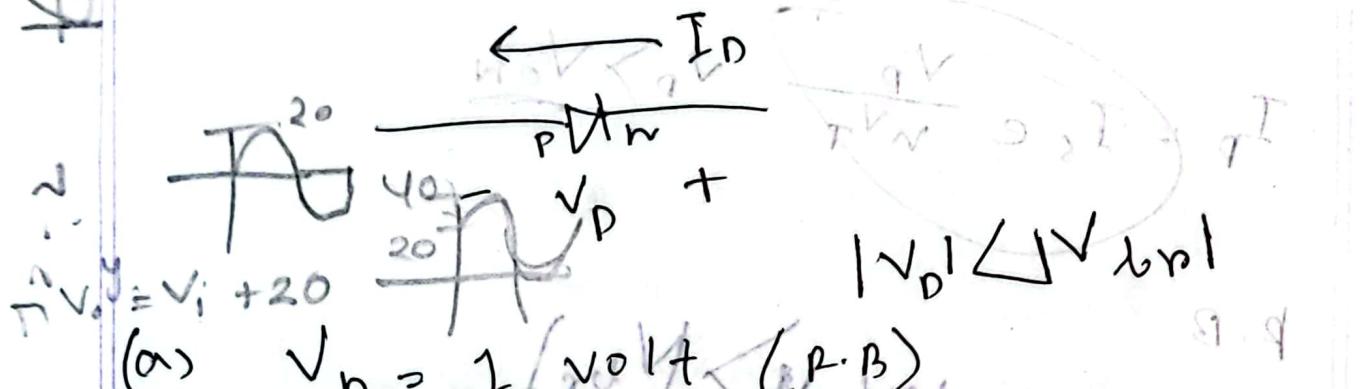(d)  $V_D = -2 \text{ volt}$

Assume the temperature to be  $27^\circ$


(centrifuge in hall cases,  $T = \frac{qV}{e}$ )



$$(a) V_D = 1 \text{ volt (R.B)}$$

$$\text{For f. B. } I_D = I_S e^{\frac{V_D - V_0}{kT}} = 10^{-10} \text{ nA}$$

$$(b) V_D = 10 \text{ (R.B)}$$

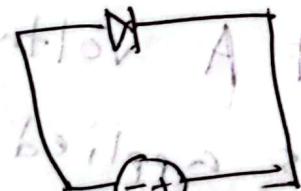

$$I_D = 2 \text{ nA (in opt. 2)} \quad \text{now opt. 2}$$

Now drift velocity

$$(c) V_D = 20 - \frac{V}{5} \text{ (f. B.)} \quad 5 \rightarrow 2$$

$$I_D = -I_S e^{\frac{V_D}{kT}}$$

$$\sqrt{T} = \frac{kT}{e}$$

$$\therefore = -I_S \cdot 1.6 \times 10^{-19} \times 10^{85} = \frac{1.38 \times 10^{-23} \times 300}{1.6 \times 10^{-19}} = 0.0259 \text{ V}$$

$$(a) V_D = -1 \text{ V } \underline{\underline{V_D = 2}}$$

$$I_D = 0$$

# The current  $I_D = 5 \text{ mA}$ . flows through the following diode for  $V_D = 0.76 \text{ V}$  at  $30^\circ \text{ centigrade}$ .



$$\rightarrow I_D$$

Assuming the ideality factor, n to be unity and the  $V_{ON}$  to be  $0.75 \text{ V}$  at  $30^\circ \text{ centigrade}$ ,

calculate the reverse saturation current.

P.T.

$$V_D > V_{ON}$$

$$\Rightarrow I_D = I_S e^{\frac{V_D}{nV_T}} \quad \left| \begin{array}{l} V_T = \frac{1.38 \times 10^{-23} \times 303}{1.6 \times 10^{-19}} \\ \Rightarrow 0.026 \end{array} \right.$$

$I_D$  increases with  $T$

$$\Rightarrow I_{Sbulk} = \frac{e^{\frac{V_D}{nV_T}}}{e^{\frac{V_D}{nV_T}}} \text{ with } T \text{ increase}$$
 $= \frac{0.76}{e^{-0.026}}$

at  $T = 25^\circ C$

 $= 1.009 \times 10^{-12} \text{ mA}$

effect of temperature on turn ON voltage with its results

$$T \uparrow \quad V_{ON} \downarrow$$

$$T \downarrow \quad V_{ON} \uparrow$$

$$2.5 \text{ mV} / 2^\circ \text{C}$$

# The turn-on voltage of an  $n-p-n$  diode is 1.2 volt at room temperature. Calculate the new value of  $V_{on}$  if the temperature is increased by  $50^\circ$  Centigrade.

$$\Rightarrow V_{on} = 1.2 + 2.5 \times 10 \times 10^{-3} \times 50$$

$$\Rightarrow 1.175 \text{ V}$$

# Effect of temperature on  $I_s$ .

$\uparrow T \rightarrow I_s \uparrow$  (Extrinsic)  $\downarrow T \rightarrow I_s \downarrow$  (Intrinsic)

$$(qV) \tau \cdot A \cdot F \cdot g \leftarrow 10^8 \cdot qV \cdot 2 \cdot 10^{-12}$$

$$\text{Ans} = qT \cdot \cancel{e^{\frac{qV}{kT}} \leftarrow nV}$$

#  $I_s = 2 \text{ nA}^{\circ} \text{ at } 10^{\circ} \text{ centigrade}$

calculate  $I_s$  at  $70^{\circ}$  centigrade.

now with steady state

$$20^{\circ} \text{ C} \rightarrow 2 \text{ nA}$$

$$20^{\circ} \text{ C} \rightarrow 2 \text{ nA}$$

$$30^{\circ} \text{ C} \rightarrow 4 \text{ nA}$$

$$40^{\circ} \text{ C} \rightarrow 8 \text{ nA}$$

$$50^{\circ} \text{ C} \rightarrow 16 \text{ nA}$$

$$T = 60^{\circ} \text{ C} \rightarrow 32 \text{ nA}$$

$$70^{\circ} \text{ C} \rightarrow 64 \text{ nA}$$

# ~~the~~ calculate diode current  $I_D$  at  $343 \text{ K}$  for the same value of  $V_D$ .

$$30^{\circ} \text{ C} \rightarrow 0.76 \text{ V} (V_D)$$

$$V_{ON} \rightarrow 0.75 \text{ V}, I_D = 2 \text{ mA}$$

# Assignment - 2 ques 1 solve

(fall 22 - spring 23)

# CT: 2 (Today class)


Sunday

21.6.23

# Chptn - 2

equivalent

circuit of diode :-

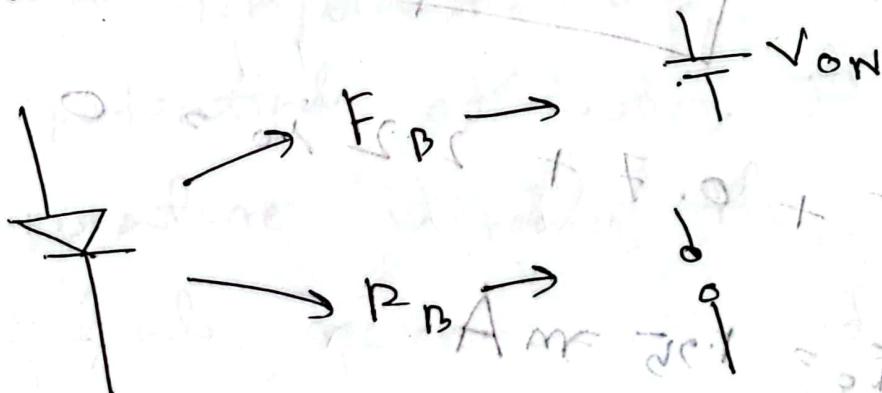

$V_{on}$


Given  $\rightarrow 0.3 \text{ V}$

$$V_{(Z_D + S_D)} = 0.6$$


$S_i \rightarrow 0.7 \text{ V}$

$$V_{F_O} = 0.6$$

$V_{unA_3} \rightarrow 2.2 \text{ V}$

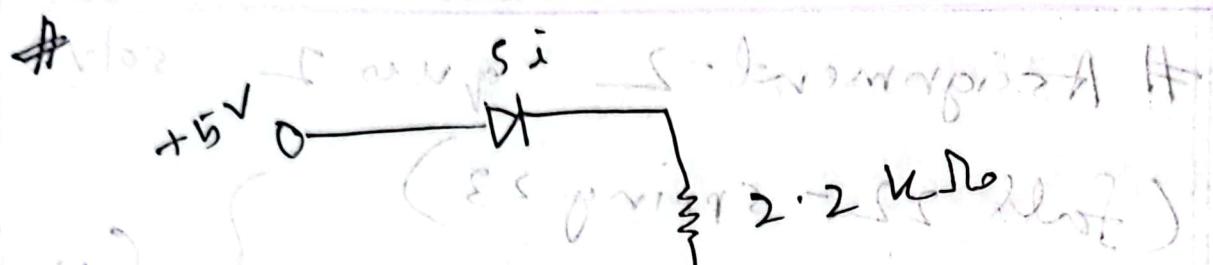

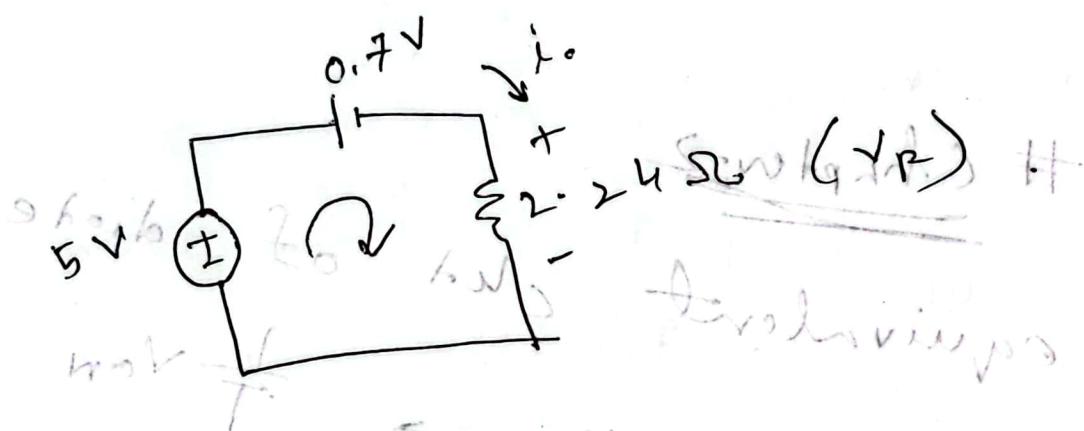Result (Ans)  $\rightarrow$   $I_D = 1.95 \text{ mA}$



$$-5 + 0.7 + 2.2I_D = 0$$

$$\Rightarrow I_D = 1.95 \text{ mA}$$

$$V_D = (2.2 \times 1.95) \text{ V}$$

$$V_D = 0.7 \text{ V}$$

~~7.6.23~~

Mid-Spring-22

Electronics

(a)

$$2 \text{ nA} \rightarrow 10^\circ \text{C} \quad \frac{qV}{kT} = \frac{qV}{25 \text{ mV}} \quad (i)$$

$$4 \text{ nA} \rightarrow 20^\circ \text{C} \quad \frac{qV}{kT} = \frac{qV}{25 \text{ mV}}$$

$$8 \text{ nA} \rightarrow 30^\circ \text{C}$$

$$16 \text{ nA} \rightarrow 40^\circ \text{C}$$

$$32 \text{ nA} \xrightarrow[0.1 \times 55.8 \text{ mV}]{\text{wl}} 50^\circ \text{C} \quad \frac{qV}{kT} = \frac{qV}{25 \text{ mV}}$$

(b) Yes, temperature affect the turn on potential of diodes. If the temperature increases, the turn on potential decreases and if the temperature decreases, the turn on potential increases.

$$T \uparrow V_{on} \downarrow \quad \frac{qV}{kT} = \text{const}$$

$$T \downarrow V_{on} \uparrow$$

$$(i) I_D = I_S e^{\frac{V_D}{n\sqrt{T}}} \quad n \approx 8 \quad V_T = \frac{1.38 \times 10^{-2} \times 308}{1.6 \times 10^{-9}}$$

$$\Rightarrow e^{\frac{V_D}{n\sqrt{T}}} = \frac{I_D}{I_S} \quad A \approx N = 0.0266 \text{ V}$$

$$\Rightarrow \frac{V_D}{n\sqrt{T}} = \frac{I_D}{I_S} \quad A \approx N = 8$$

$$\Rightarrow \frac{V_D}{n\sqrt{T}} = \frac{5 \times 10^{-3}}{6 \times 10^{-9}} \quad A \approx N = 1$$

$$\Rightarrow e^{\frac{V_D}{0.0266}} = \ln(8.33 \times 10^5)$$

$$\Rightarrow V_D = 13.633 \times 0.0266 \quad (\text{d})$$

Ans.  $V_D = 0.366 \text{ V}$  to nearest no

$$(ii) \frac{V_D}{0.0266} = \ln(0) \quad \text{antilog}$$

Ans.  $V_D = 0$  nearest digit no

$$(iii) \frac{V_D}{0.0266} = \ln(-1) \quad \text{antilog}$$

$\Rightarrow V_D = 0$   
 $\sqrt{\text{no}} \propto T$

$\propto \log \propto T$

Spring 2023

$$(a) \text{ if } V_D > V_{ON} \text{ then } V_D = 0.76 \text{ V}$$

$$I_D = I_s e^{\frac{V_D}{nV_T}} \quad \leftarrow I_D = 5 \text{ mA}$$

$$A = e^{\frac{V_D}{nV_T}} \quad \leftarrow n = 2$$

$$\Rightarrow I_s = \frac{5 \text{ mA}}{e^{\frac{0.76}{0.026}}} \quad \leftarrow V_T = \frac{1.38 \times 10^{-23} \times 303}{1.6 \times 10^{-19}}$$

$$= 0.026 \text{ V}$$

$$V_P = 0.026 \quad \rightarrow 1.0097 \times 10^{-12} \text{ mA}$$

$$A = \frac{0.026}{P_{S2.0}} \times 10^{12} \quad \leftarrow P_{S2.0} = 303 \rightarrow 1.0097 \times 10^{-12} \text{ mA}$$

$$313 \rightarrow 1.202 \times 10^{-12} \text{ mA}$$

$$323 \rightarrow 4.04 \times 10^{-12} \text{ mA}$$

$$333 \rightarrow 8.08 \times 10^{-12} \text{ mA}$$

$$343 \rightarrow 1.616 \times 10^{-11} \text{ mA}$$

$$\therefore I_D = 1.616 \times 10^{-11} \times e^{\frac{0.76}{0.026}} \quad \leftarrow V_T = \frac{1.38 \times 10^{-23} \times 343}{1.6 \times 10^{-19}}$$

$$= 2.287 \text{ mA}$$

$$= 0.0296 \text{ V}$$

B

8800 pmin

$$(4) \text{ At } 30^\circ\text{C} \rightarrow 1.0097 \times 10^{-12} \text{ mA}$$

$$\text{At } 20^\circ\text{C} \rightarrow 5.05 \times 10^{-13} \text{ mA}$$

$$\text{At } 10^\circ\text{C} \rightarrow 2.53 \times 10^{-13} \text{ mA}$$

$$N_T = \frac{1.38 \times 10^{-23} \times 283}{1.6 \times 10^{-19}}$$

$$\text{Ans}^{st} 01 \times F800.1 \quad 0.024 \text{ V}$$

$$\therefore I_D = 2.53 \times 10^{-13} \times e^{\frac{0.76}{0.024}} \text{ mA}$$

$$\text{Ans}^{st} 19.315 \text{ mA}$$

$$\text{Ans}^{st} 01 \times 100 \text{ N} \leftarrow 888$$

$$\text{Ans}^{st} 01 \times 80.8 \leftarrow 888$$

$$\text{Ans}^{st} 01 \times 315.1 \leftarrow 888$$

$$\frac{F800.1}{01 \times 315.1} = 7V$$

$$V_{d800.0} = \text{Ans}^{st} 888.5 \text{ V}$$

Full - 2022

16

2(b)

$$V_{ON} = 2V, V_{NR} = 5V$$

i.  $V_D = 1V$  (Reverse bias)

$|V_D| < |V_{NR}|$  (breakdown)

(will break)  $I_D = -I_S = I_S$

ii.  $V_D = -2V$  (forward bias)

$|V_D| < V_{ON}$  [OFF situation]  
 $I_D = 0$

iii.  $V_D = 10V$  (Reverse bias)

$|V_D| > |V_{NR}|, I_D = 0$

iv.  $V_D = -10V$  (forward bias)

$V_D > V_{ON}$  [ON situation]

(will break)

$$I_D = -I_S e^{\frac{V_D}{hV_T} - \frac{V_T}{V_D}}$$

$$(170) \frac{10}{0.043} \rightarrow I_S = -0.043$$

$$\frac{-23}{1.38 \times 10 \times 53} = -0.043$$

$$\frac{-16 \times 10 - 17}{-0.043}$$

Summer - 2022

2 (a)  $V_D = 9V$   $V_S = 9V$



(d) i

$$V_D = 9V$$

Cat. 2 (forward)  $|V_D| \geq |V_A|$

$$2T = 2T \quad V_A = 0.7V = 10^{-5}$$

(cat. 6 forward)  $5V$  (forward bias)

$$V_D > V_{DN} (\text{ON})$$

[without no]

$$V_D = 5 - 10 = -5V$$
 (Reverse bias)

( $|V_D| > |V_{BR}|$ )  $V_{D1} = 9V$

3

$$V_D = 9V$$

$$V_D = 9V - 2 = 7V$$
 (reverse bias)

(without no)  $V_{D1} = 9V$


$$9V < 9V$$

4

$$V_D = -3 - (-5) = 2V$$
 (forward bias)

$V_D < V_{DN}$  (OFF)

(a)

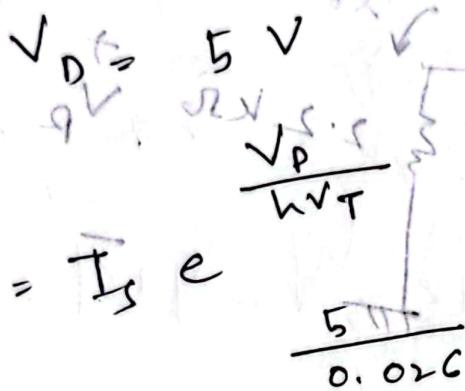

(a. g)

$$I_S = 10 \text{ nA}$$

$$V_T = \frac{1.38 \times 10^{-23} \times 298}{1.6 \times 10^{-19}}$$

$$\rightarrow 0.026 \text{ V}$$

$$I_D = I_S e$$

$$\frac{5}{0.026}$$

$$\rightarrow 10 e$$

$$\approx 3.278 \times 10^{18} \text{ A}$$

(b)  $I_S$   $T \uparrow$   $V_{ON}$

$$25^\circ \rightarrow 10 \text{ nA}$$

$$35^\circ \rightarrow 20 = 0.1 \times 10^9 \text{ A}$$

$$45^\circ \rightarrow 40$$

$$55^\circ \rightarrow 80$$



$$65^\circ \rightarrow 160$$

$$75^\circ \rightarrow 320 \text{ nA} \quad T \uparrow I_S \uparrow$$

Ans

ANS

# Electronics

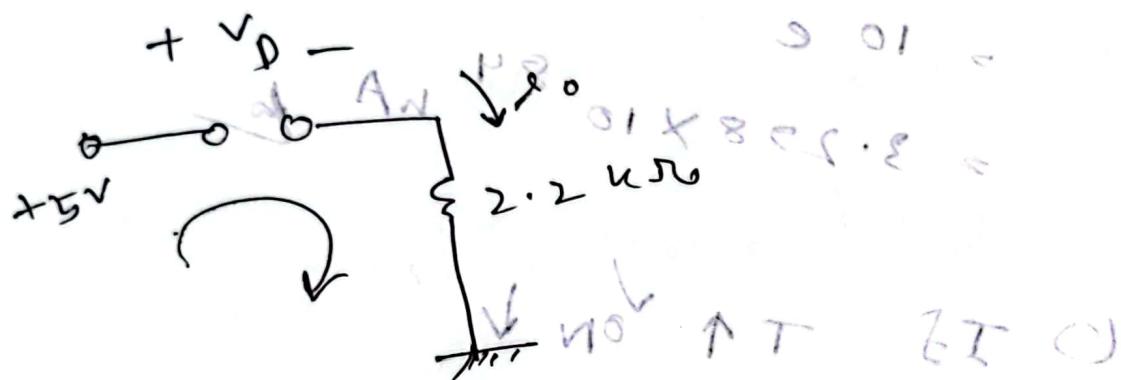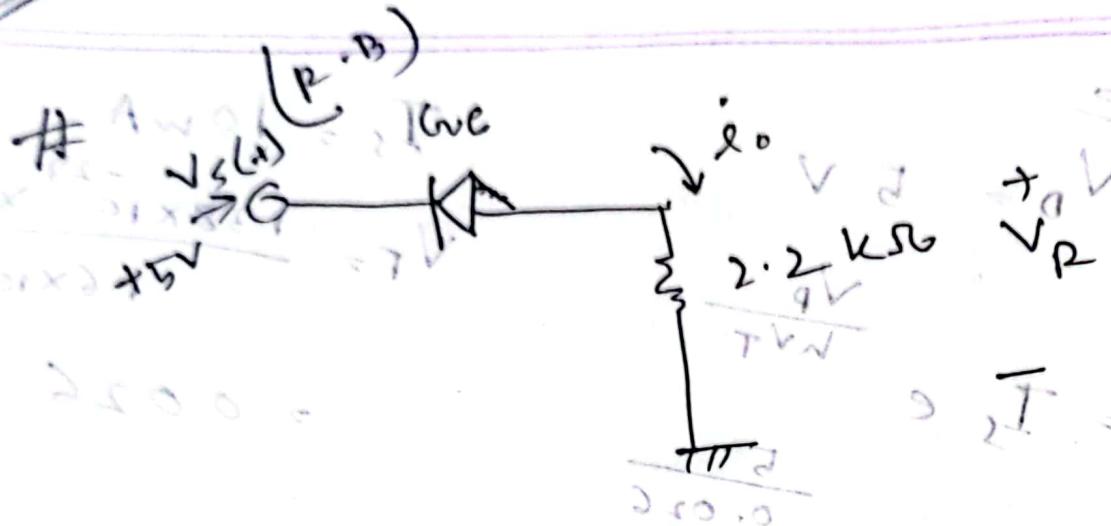


$$i_o = 0 \quad A_w = 0.1 \quad \leftarrow 25^\circ \text{ C}$$

$$V_p = 2.2 \times i_o = 0 \quad \leftarrow 25^\circ \text{ C}$$

$$-5 + V_p + 2.2 I_o = 0 \quad \leftarrow 25^\circ \text{ C}$$

$$\Rightarrow V_p = 5 \quad A_w = 0.1 \quad \leftarrow 25^\circ \text{ C}$$

P.T.

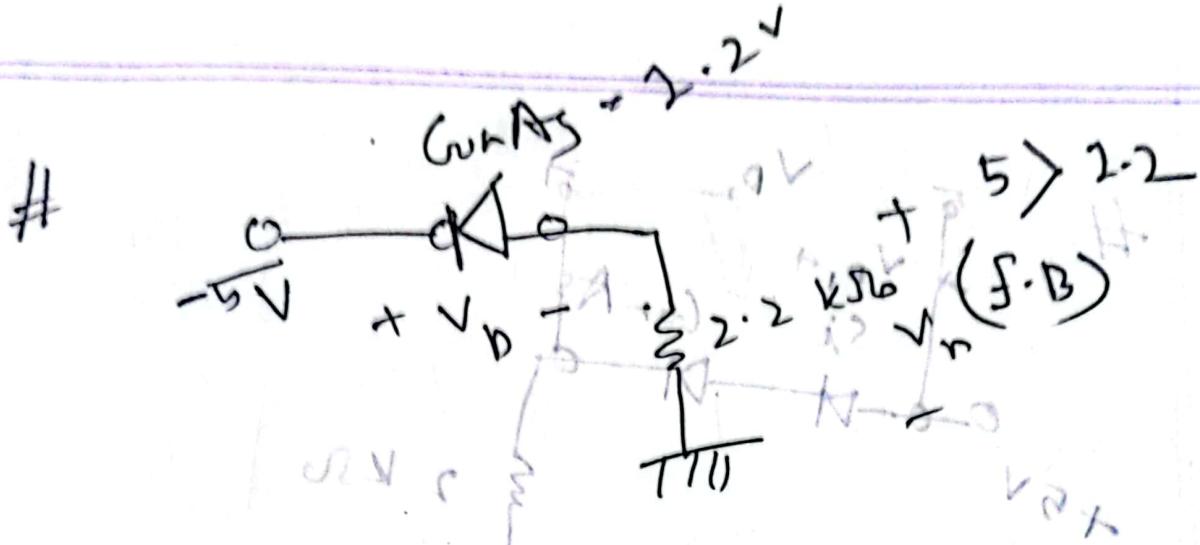


$$+5 - 2 \cdot 2 + 2 \cdot 2 i_o = 0$$

$$\Rightarrow i_o = -1.72 \text{ mA}$$

$$V_P = 2 \cdot 2 \times (-1.72) = -3.8 \text{ V}$$

$$V_D = -1.2 \text{ V}$$

P.T.O.

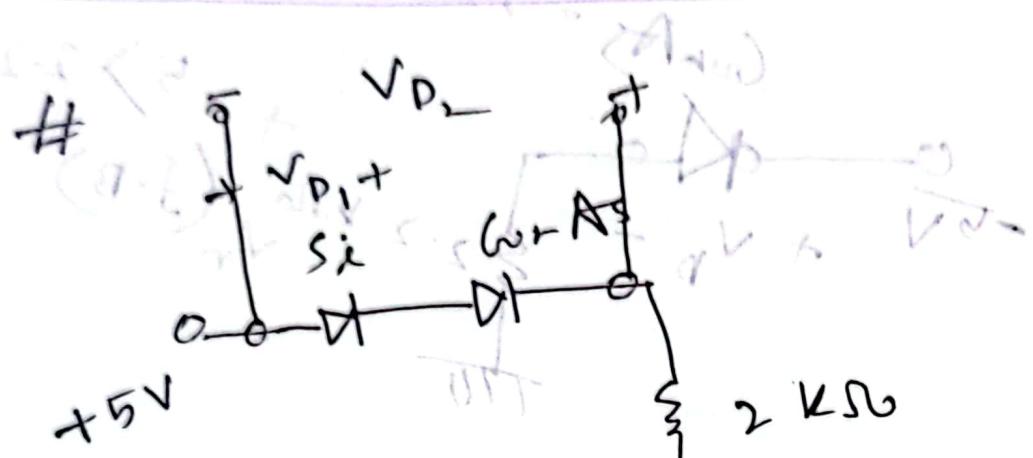

$$0 = -5 + 0.7 + 1.2 + 2 \cdot 10^{-2} \cdot 2 \cdot 10^3$$

$$-5 + 0.7 + 1.2 + 40 = 0$$

$$8.5 - 8.5 = 0$$

$$V_{D_1} = 0.7 \text{ V}$$

$$(5V - 0.7) + 8.5 = 9V$$


for  $V_{D_2}$

$$V_{D_2} = 0.7 \text{ V}$$

$$-V_{D_2} - 0.7 - 1.2 = 0$$

$$\Rightarrow V_{D_2} = -1.9 \text{ V}$$


1.9

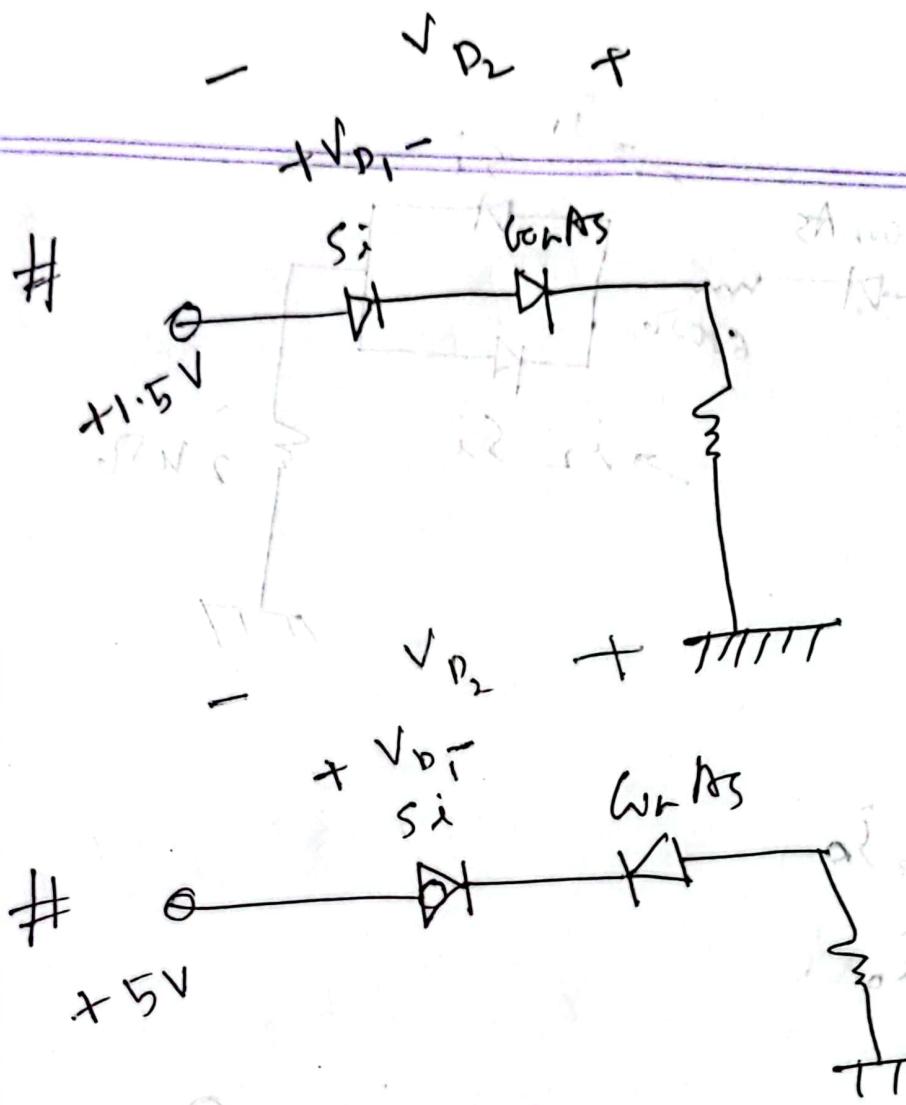

$$-5 - \sqrt{D_2} + 2 I_o = 0$$

$$\Rightarrow \sqrt{D_2} = 5 \text{ V}$$

GW  
111123

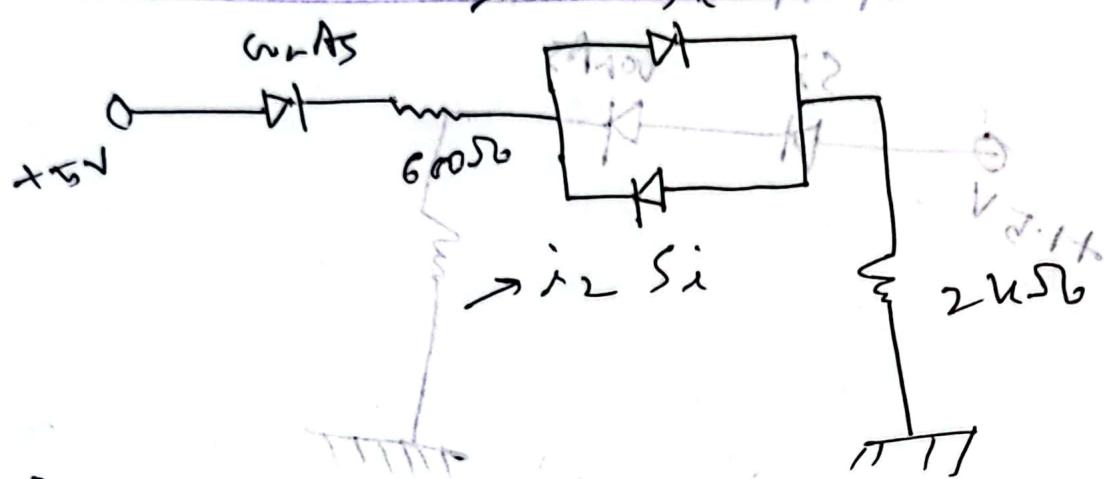

$$i_2 = 0$$

$$i_1 + i_2 = i_0$$


$$\Rightarrow i_1 = i_0$$

$$-5 + 1.2 + 0.6i_0 + 0.7 + 2i_0 = 0$$

$$0 = 0.7 + 0.6V_A - 2 - 0$$

$$V_A = 0.6V_C$$

P.T.

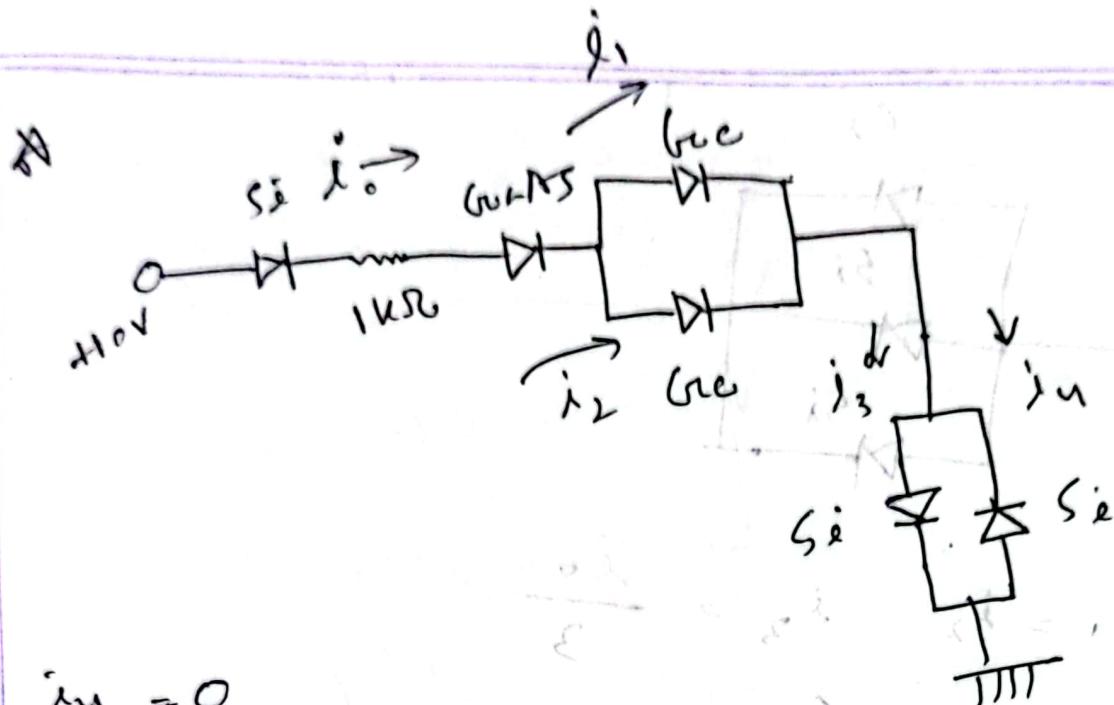


$$i_1 = 0$$


$$i_3 = i_0 \quad \text{Q.E.D.}$$

$$-10 + 0.7 + i_0 + 1.2 + 0.3 + 0.7 = 0$$


$$\Rightarrow i_0 = 7.1 \text{ mA}$$
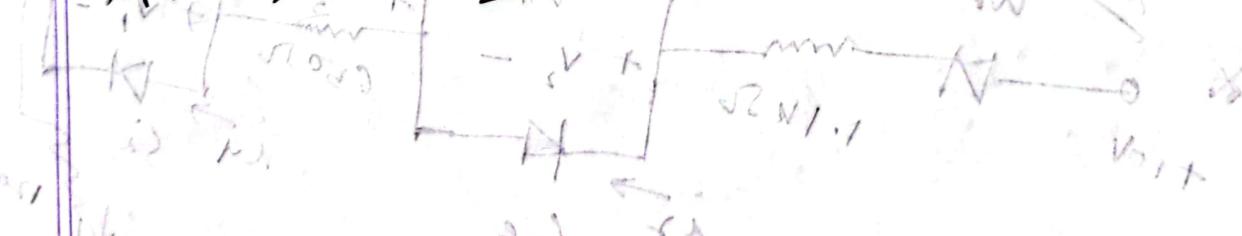
$$i_1 = i_2 = \frac{i_0}{2} = 3.55 \text{ mA}$$




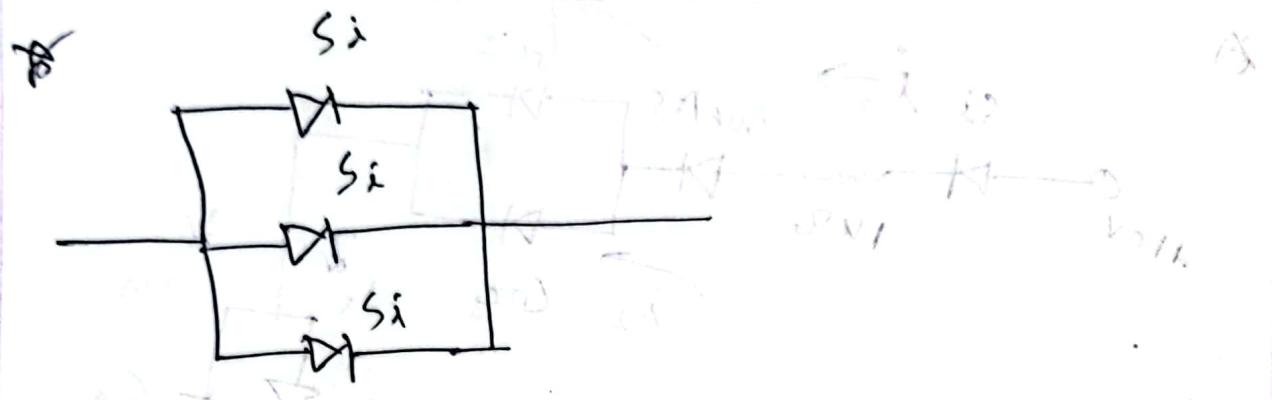
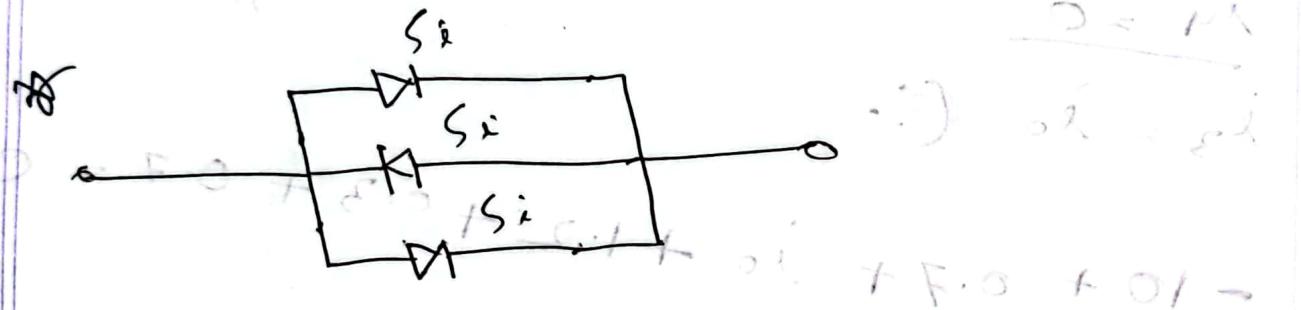
$$\Rightarrow i_1 = i_2 \Rightarrow i_3 = \frac{i_0}{3}$$


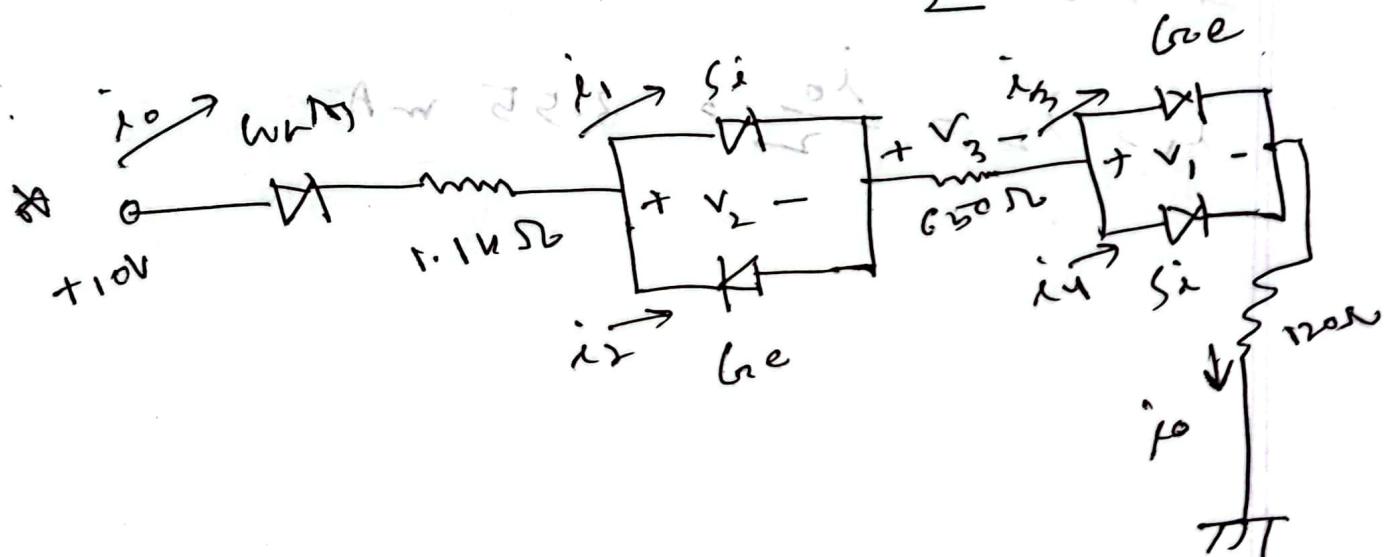
$$\Rightarrow i_2 = 0 \Rightarrow i_1 = i_3 = \frac{i_0}{2}$$



$$\Rightarrow i_2 = 0, \quad i_4 = 0, \quad i_3 = i_0$$

$$i_1 = i_0$$

$$-10 + 1.2 + 1.1i_0 + 0.7 + 0.65i_0 + 0.3 +$$

$$0.12i_0 = 0$$

$$\Rightarrow \cancel{0.12} \cdot 1.87i_0 = 7.8$$

$$\Rightarrow i_0 = 4.17 \text{ mA}$$

~~if two parallel connected diode are forward biased and the diodes are different than, ~~the~~~~

~~which diodes voltage value is small that will be counted & the bigger value voltage diode will be vanished.~~


$$V_1 = 0.3 \text{ V}$$

$$V_2 = 0.7 \text{ V}$$

P.T.O

$$V_3 = IR = 4.17 \text{ mA} \times 0.65 \text{ k}\Omega$$


$$= 2.7105 \text{ V}$$

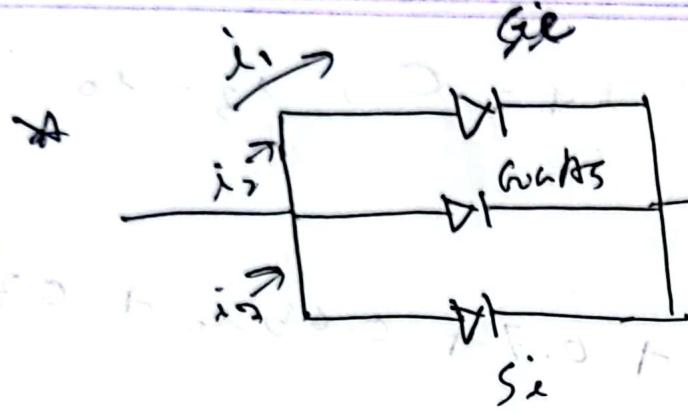

$$\Rightarrow i_2 = 0, \quad i_3 = 0, \text{ and } i_1 > 0$$


S.F. = 0.877 at 30°

Am F.P. = 0.877

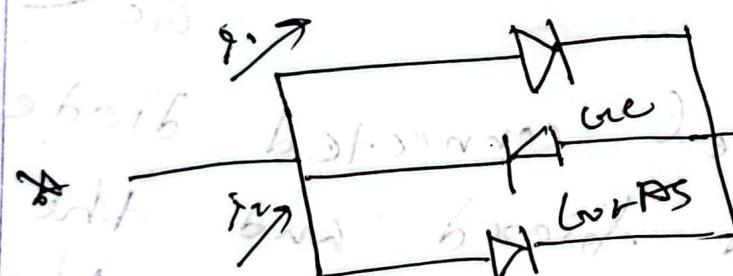

$$i_1 = i_2 = i_3 = 0$$

$\Rightarrow$   $i_1 = i_2 = i_3 = 0$

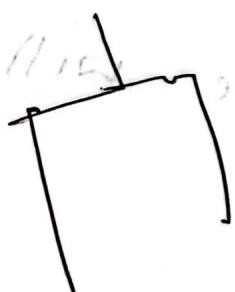


$$V_E = 0 \text{ V}$$


$$V_F = 0 \text{ V}$$

In 22.0 K.Am F.P.  $\Rightarrow I = 0$

$\Rightarrow V_{ZD} = 0 \text{ V}$

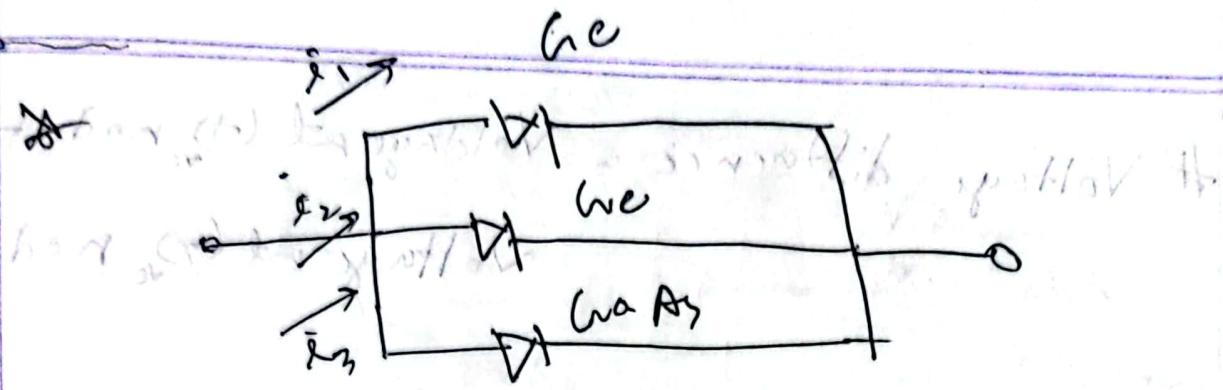
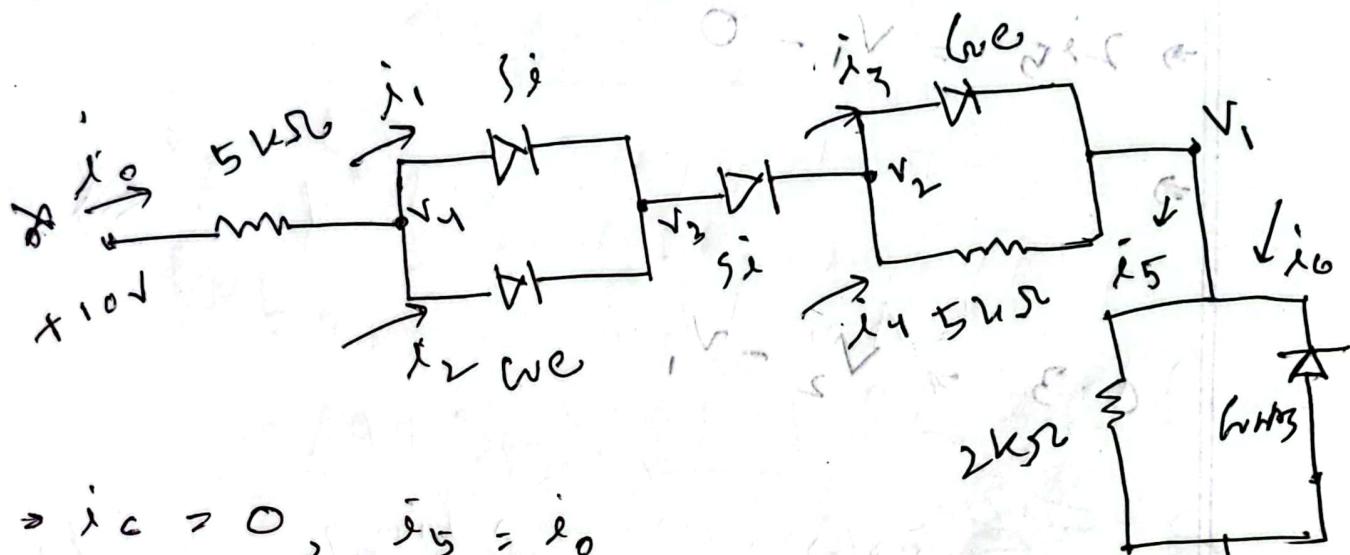
$$\Rightarrow i_3 = 0, \quad i_1 = i_2 = \frac{10}{2} \text{ mA}$$



$$\Rightarrow i_C = 0, \quad i_5 = i_0$$

$$i_1 = 0, \quad i_2 = i_0$$

$$-10 + 5i_0 + 0.3 + 0.7 + 0.3 + 2i_0 = 0$$

$$\Rightarrow 7i_0 = 8.7$$

$$\Rightarrow i_0 = 1.24 \text{ mA}$$

$$i_0 = i_3 + i_4$$

$$\Rightarrow i_3 = i_0 - i_4 = 1.18 \text{ mA}$$

$$V_s, iR$$

$$\Rightarrow i_4 = \frac{V}{R}$$


$$= \frac{0.3}{5}$$

$$= 0.06 \text{ mA}$$

# Voltage difference = Voltage at (+) node -  
Voltage at (-) node

$$V_{2 \text{ k}\Omega} = V_1 - 0$$

$$\Rightarrow 2 \times 5 = V_1 - 0$$

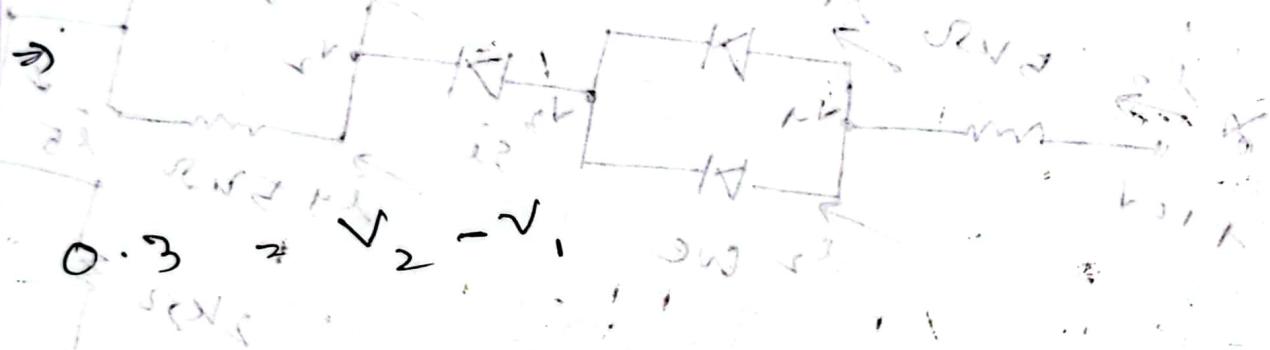

$$0.3 = V_2 - V_1$$

$$\Rightarrow 0.7 = V_3 - V_2$$

$$\Rightarrow 0.3 = V_4 - V_3 \text{ or } V_{5\Omega} = 10 - V_4$$


$$\Rightarrow 0.3 = V_4 - V_3 \text{ or } 5\Omega = 10 - V_4$$

Ans 1st part = 0.3

Ans 2nd part = 0.0

Ans 3rd part = 0.3

Ans 4th part = 0.0

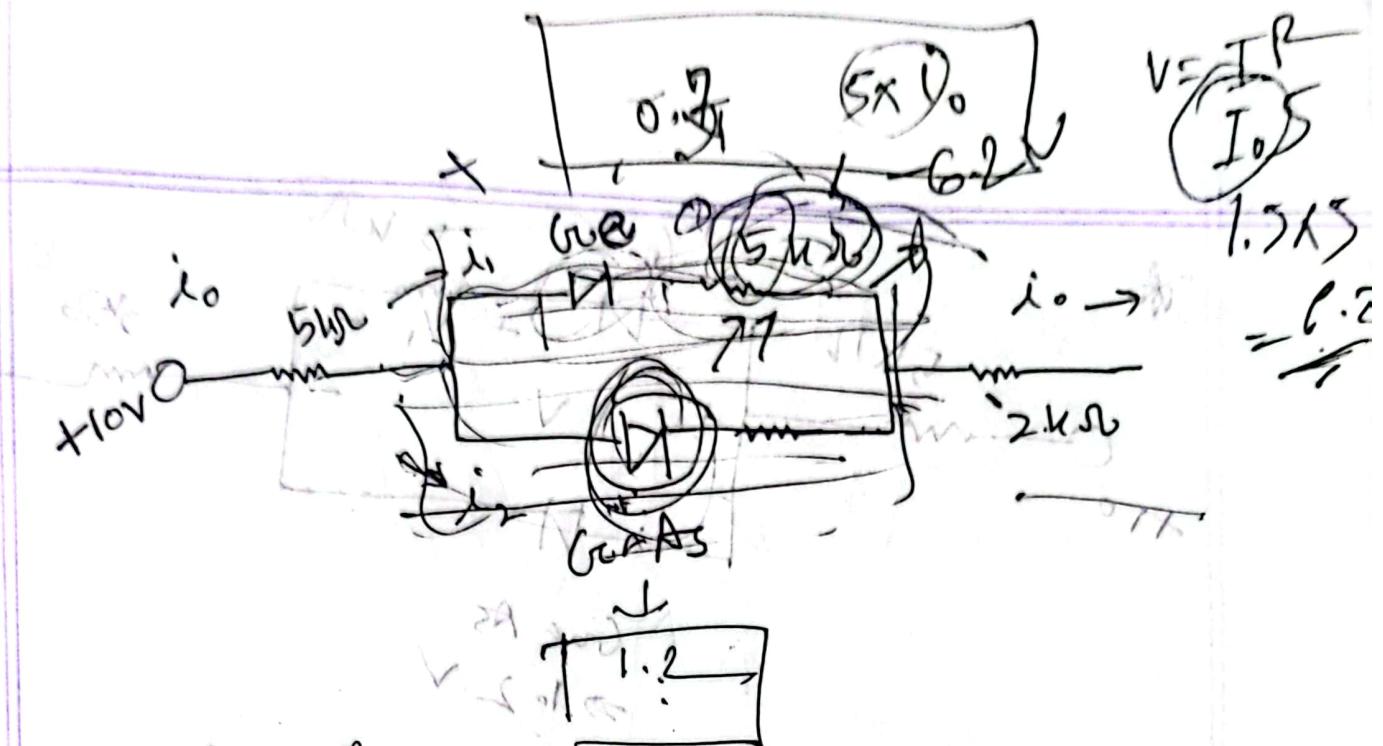


$$i_2 = i_0$$

$KVL$ ,


$$-10 + 5i_0 + \underline{1.2} + 2i_0 = 0$$

$$\Rightarrow 6i_0 - \underline{6.2} = 0$$

$$\Rightarrow i_0 = \frac{3.8}{7}$$

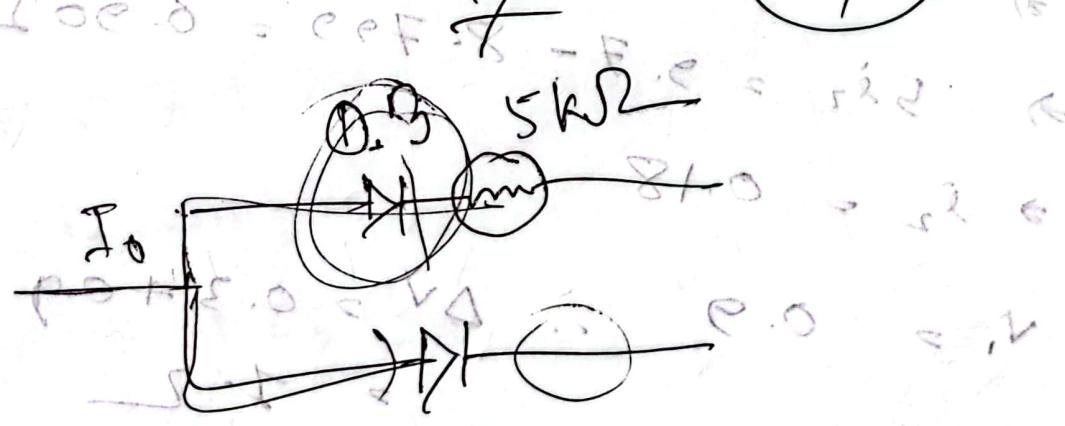

1.7

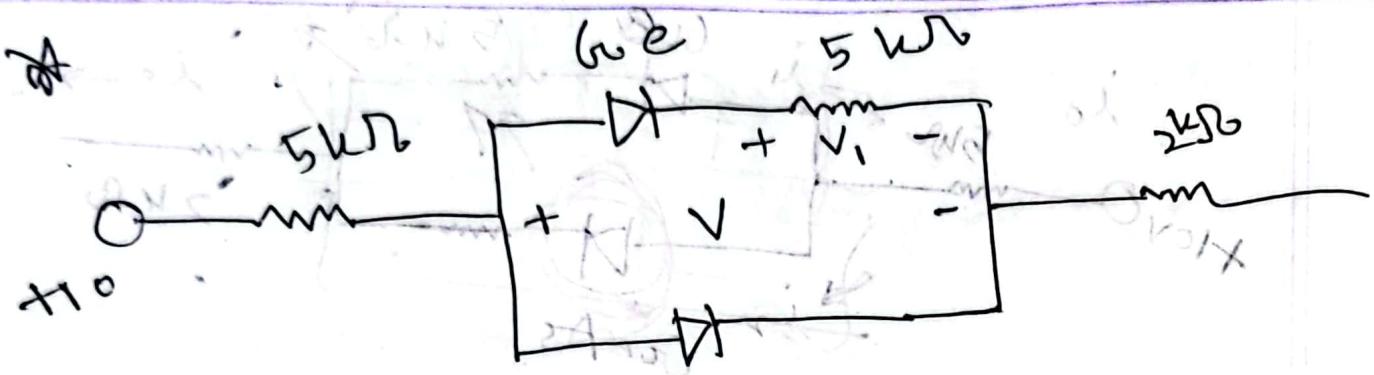

$$\text{Grob AS} \\ \Rightarrow 1.2V$$

$$i_0 = -10 +$$

$$-10 + 5i_0 + 1.2 + 2i_0 = 0$$

$$\Rightarrow 7i_0 = -8.8$$

$$\Rightarrow i_0 = 1.257 \text{ mA}$$

$$-10 + 5i_0 + 0.3 + 5i_2 + 2i_0 = 0$$

$$\Rightarrow 7i_0 + 5i_2 = 9.7$$


$$\Rightarrow 5i_2 = 9.7 - 8.799 = 0.901$$

$$\Rightarrow i_2 = 0.18$$

$$V_1 = 0.9 \quad \therefore \Delta V = 0.3 + 0.9$$

$$= 1.2$$

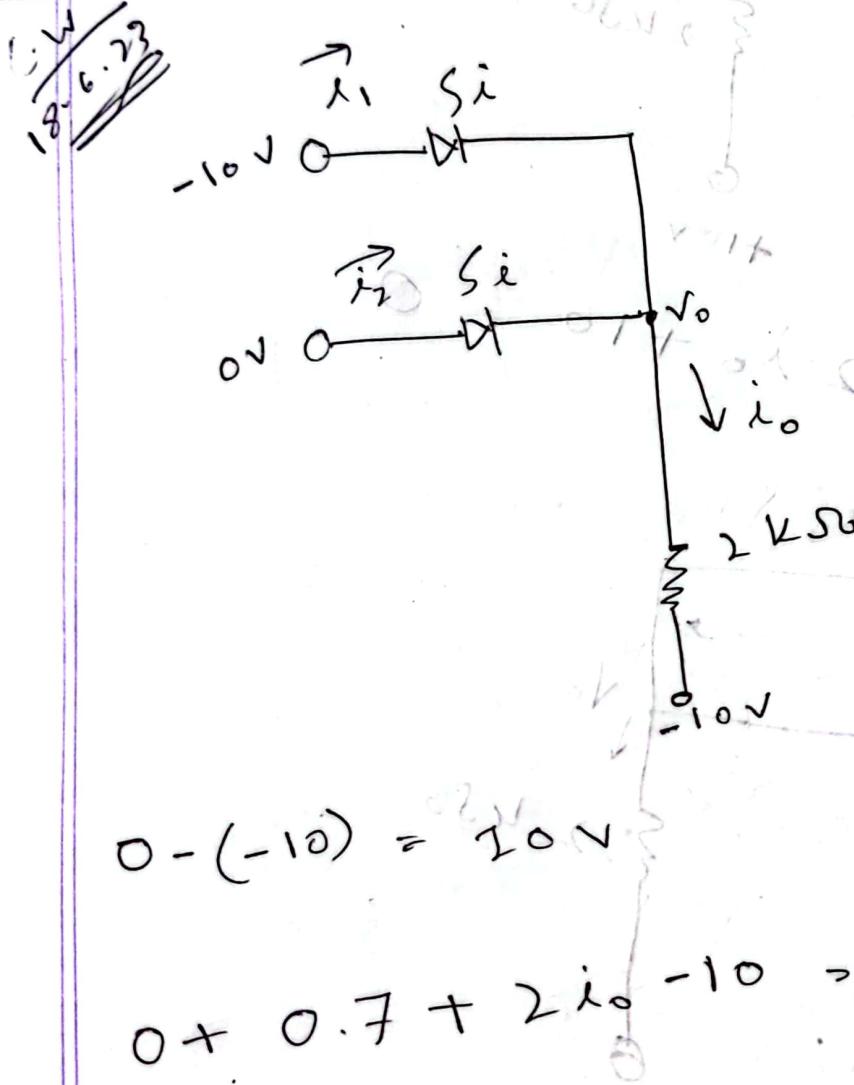~~Chapt 2~~  
5, 8, 11, 12, 13, 14, 22, 23, 24, 25, 26,  
27, 28, 29



$$0 - (-10) = 10\text{V}$$


$$0 + 0.7 + 2i_0 - 10 = 0$$

$$\Rightarrow 2i_0 = 9.3$$


$$\Rightarrow i_0 = 4.65 \text{ mA} = 0.465 \text{ A}$$

$$10 - 10 = 0$$

$$10 - 10 = 0$$

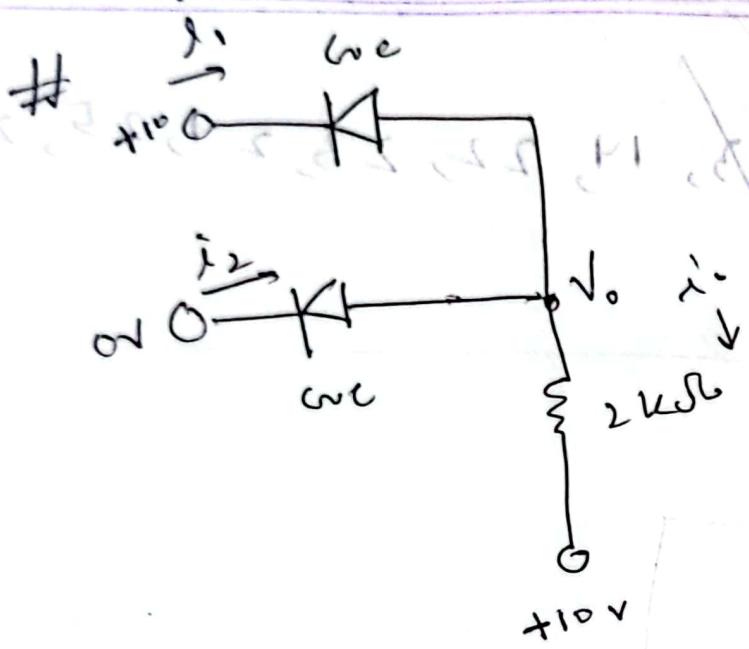

$$-10 - 0.3 + 2i_0 + 10 = 0$$

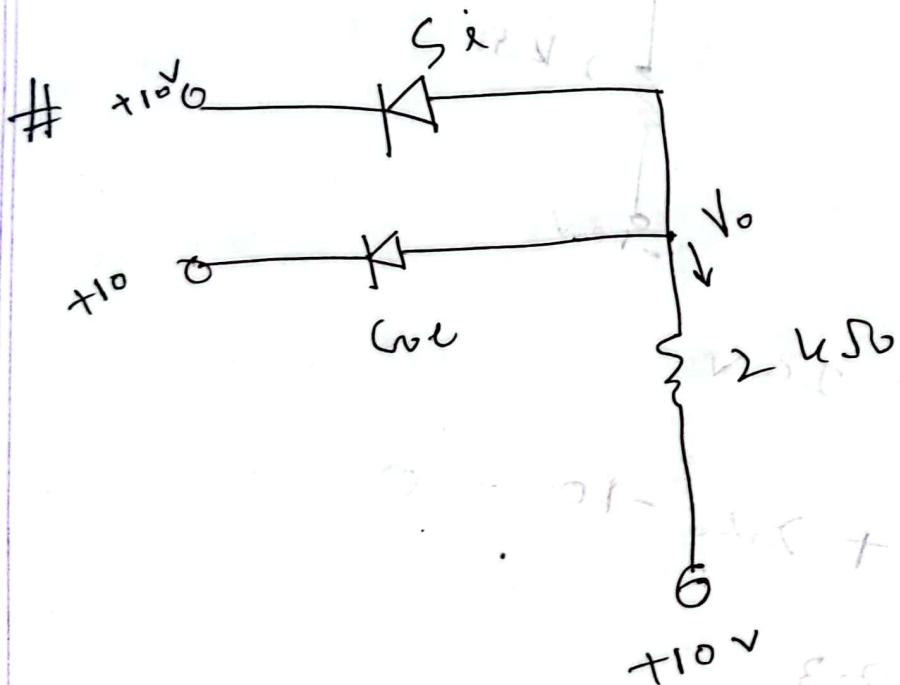

$$V_{2uR} = V_0 - (+10V)$$

$$\Rightarrow 0 = V_0 - 10$$


$$\Rightarrow V_0 = 10V$$

6. v  
7. 6. 7. 3

wave, DC voltage

Electromy


## Rectifier Circuit

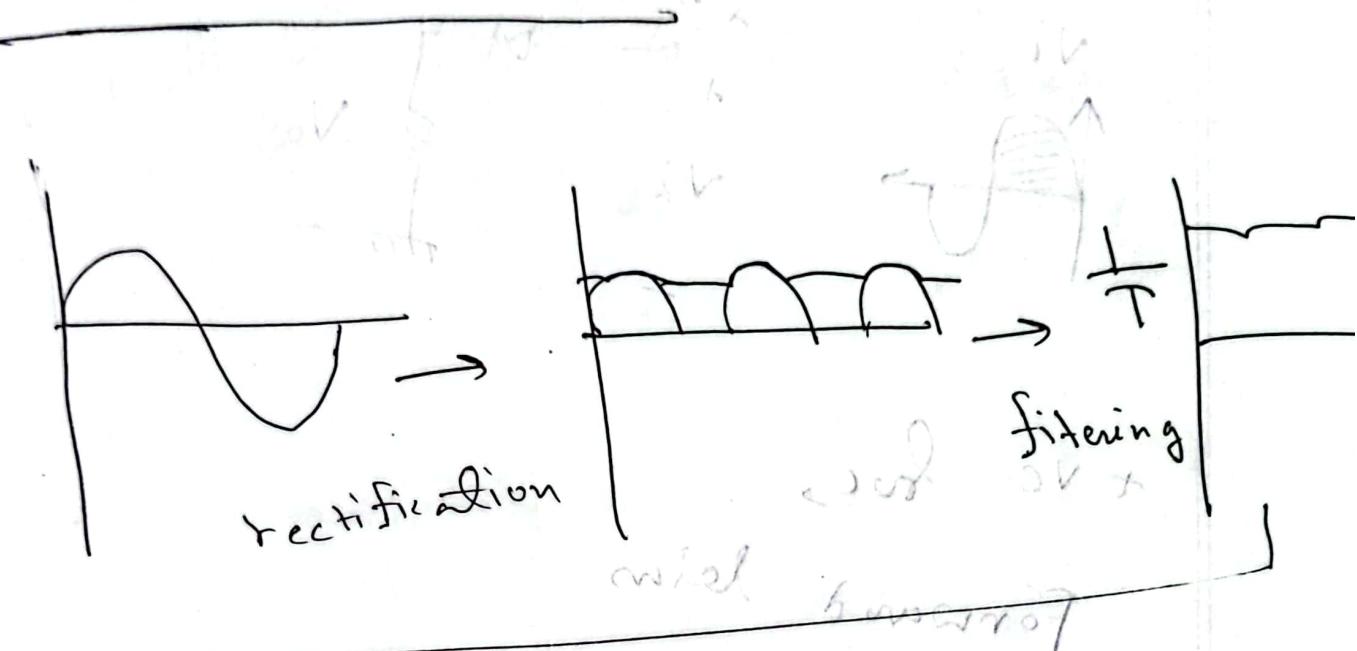

$$P = 0V + n \cdot V + k$$

$$\text{not } -V = 0V$$


(stabilizer)

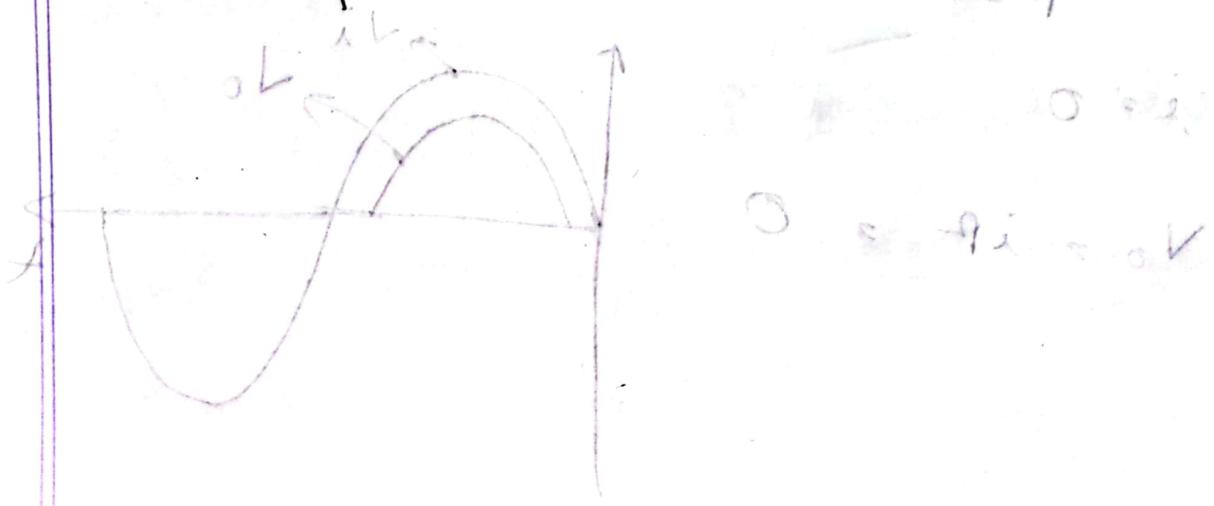

1.2

## Half wave rectifier

Electronics

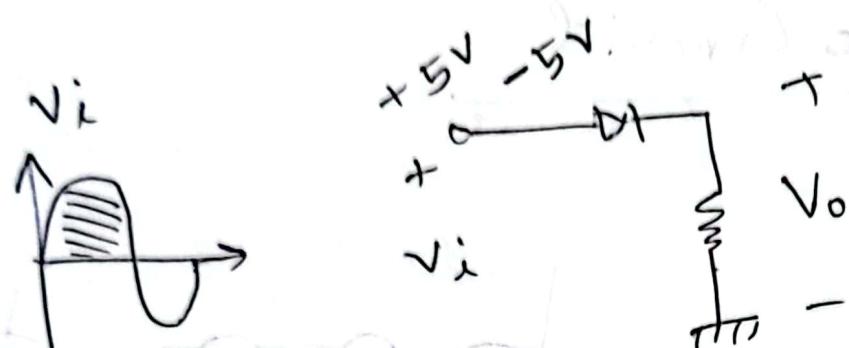

Forward bias

+ve bias

Forward bias

$$-V_i + V_{on} + V_o = 0$$


$$\Rightarrow V_o = V_i - V_{on}$$


-ve bias

Reverse bias

$$i = 0$$

$$V_o = iR = 0$$

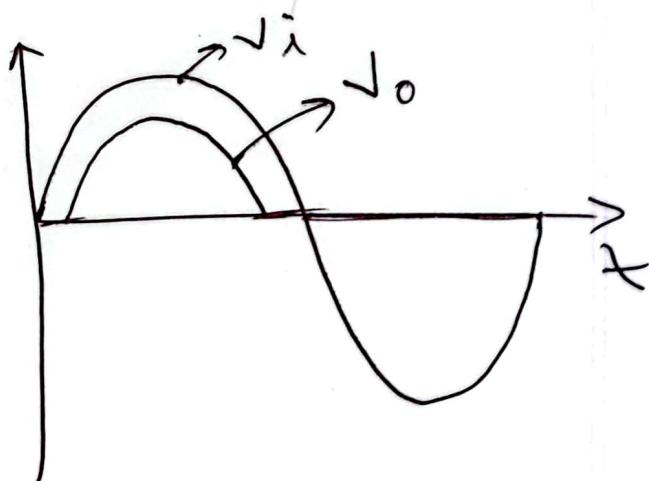

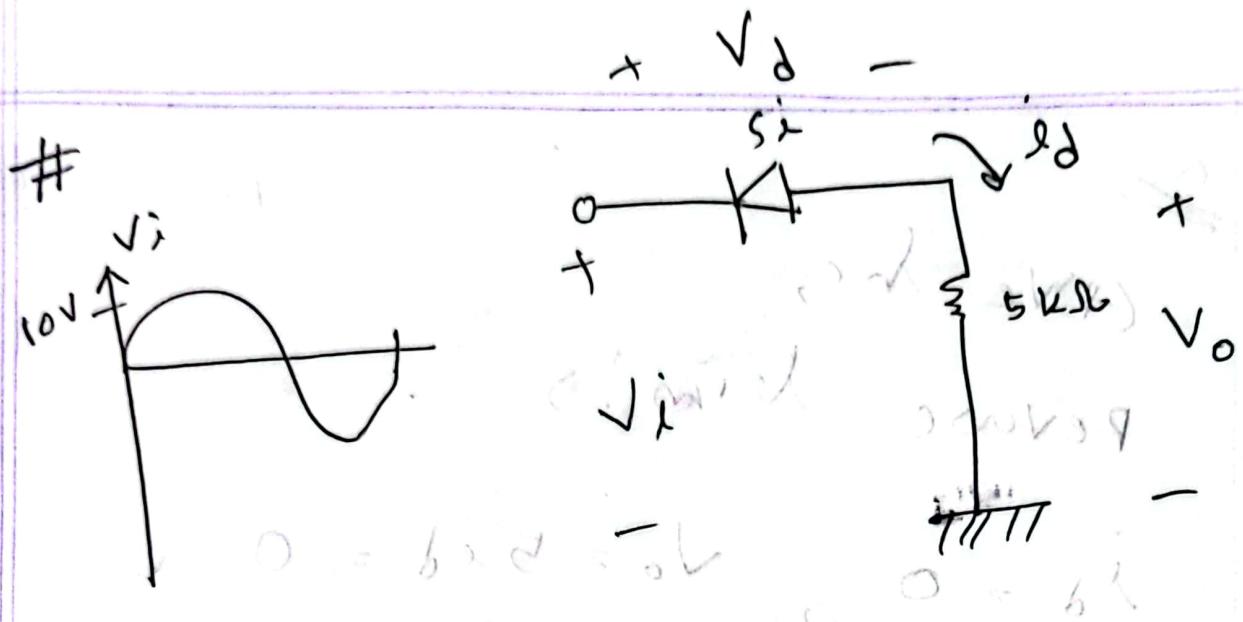

- # Q<sub>1</sub>: Derive the expressions of  $V_o$ ,  $V_d$ ,  $i_d$  & sketch them.
- Q<sub>2</sub>: calculate the average and R.M.S values of  $V_{ic}$  &  $i_d$
- Q<sub>3</sub>: calculate the maximum and average values (dc level),  $V_o$
- Q<sub>4</sub>: calculate P.I.V of the diode and comment on the breakdown voltage of it.

~~(+) Ne h.c.~~

Reverse bias  $\rightarrow$

$$i_d = 0, V_o = 5i_d = 0$$

$$-V_i + V_d + V_o = 0 \text{ since } i_d = 0$$

$\Rightarrow V_d = V_i$

$(-) Ne h.c. \rightarrow V_o \text{ to cathode} \leftarrow 0.7 \text{ V}$

Forward bias  $\rightarrow V_o \text{ to anode} \leftarrow 0.7 \text{ V}$

$$-V_i + V_d + V_o = 0$$

$\Rightarrow V_o \rightarrow V_i + 0.7 \text{ V}$

$$i_d = \frac{V_o}{5} \text{ mA}$$

$+i$  to option


$$V_d = -0.7 \text{ V}$$

$$V_o = \left\{ \begin{array}{l} 0; +ve \text{ h.c.} \\ V_i + 0.7; -ve \text{ h.c.} \end{array} \right.$$


$$i_d = \left\{ \begin{array}{l} 0; +ve \text{ h.c.} \\ \frac{V_o}{5}; -ve \text{ h.c.} \end{array} \right.$$

$$V_d = \left\{ \begin{array}{l} V_i; +ve \text{ h.c.} \\ -0.7, -ve \text{ (p.h.c.)} \end{array} \right.$$

$$V = \frac{21}{57} = (0.37) \text{ V}$$

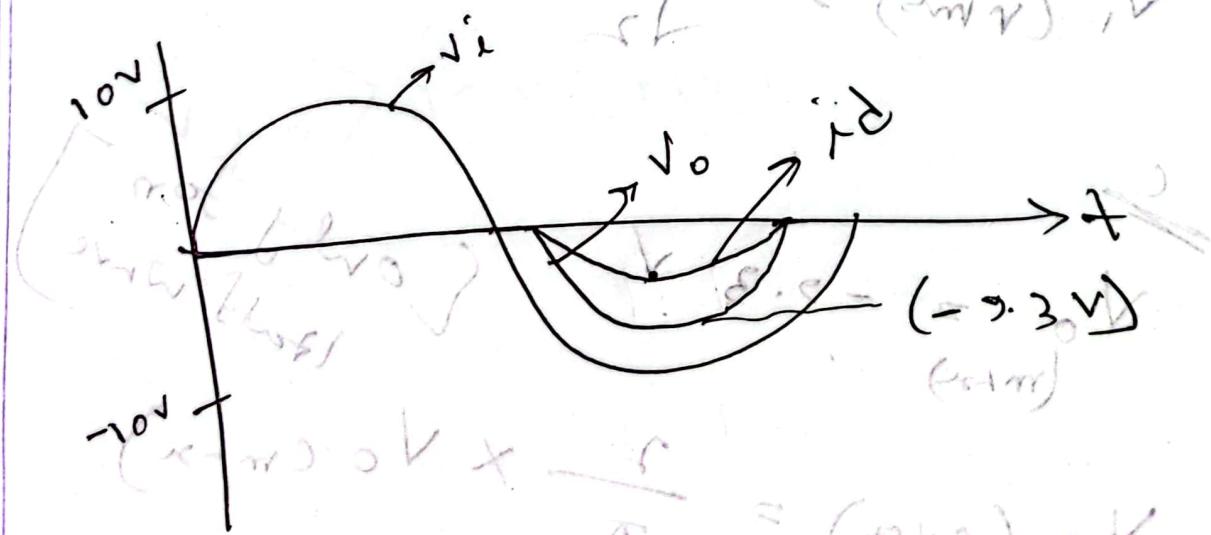


$$V = \frac{21}{57} = (0.37) \text{ V}$$

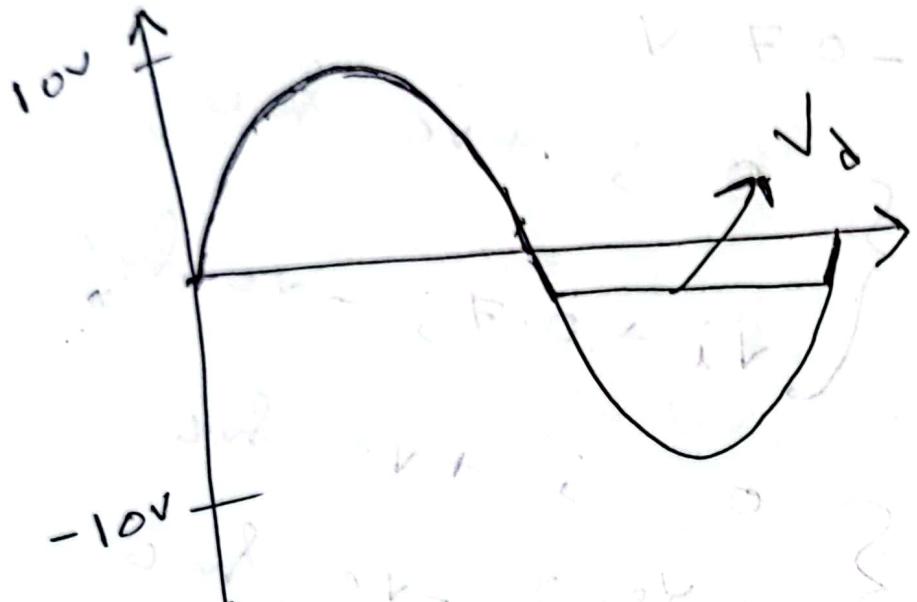

~~b~~

$$V_i (\text{avg}) = 0 \text{ V}$$
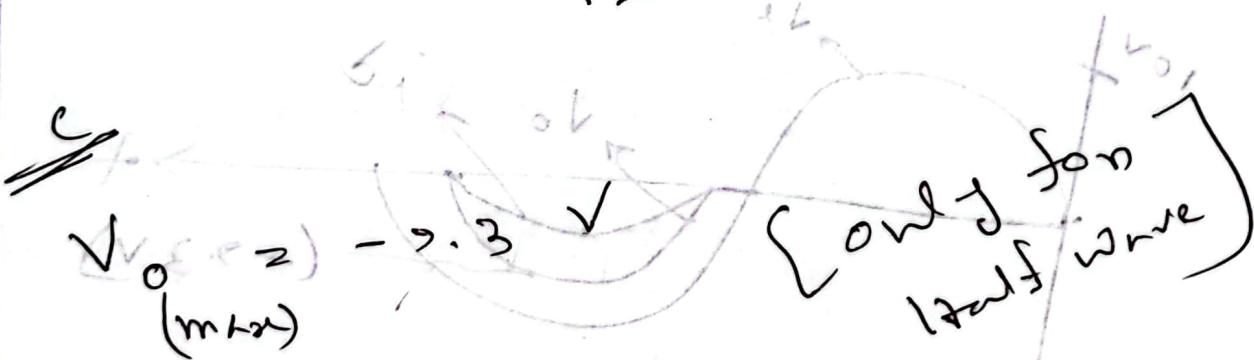
$$V_i (\text{rms}) = \frac{10}{\sqrt{2}} \text{ V}$$



$$V_o (\text{avg}) = \frac{2}{\pi} \times V_o (\text{max})$$

=

\* P.I.V  $\rightarrow$  Pick Reverse Voltage  
 $\rightarrow$  maximum voltage that can be  
 found across a diode during  
 reverse biasing.



$$P.I.V = 10V \quad \times V_{DR},$$


$+ PIV -$

$$-V_i + PIV + 5i_d = 0$$

$$PIV = V_i$$

$$= 10V$$

$$\Rightarrow V_{DR} > 10V [PIV]$$

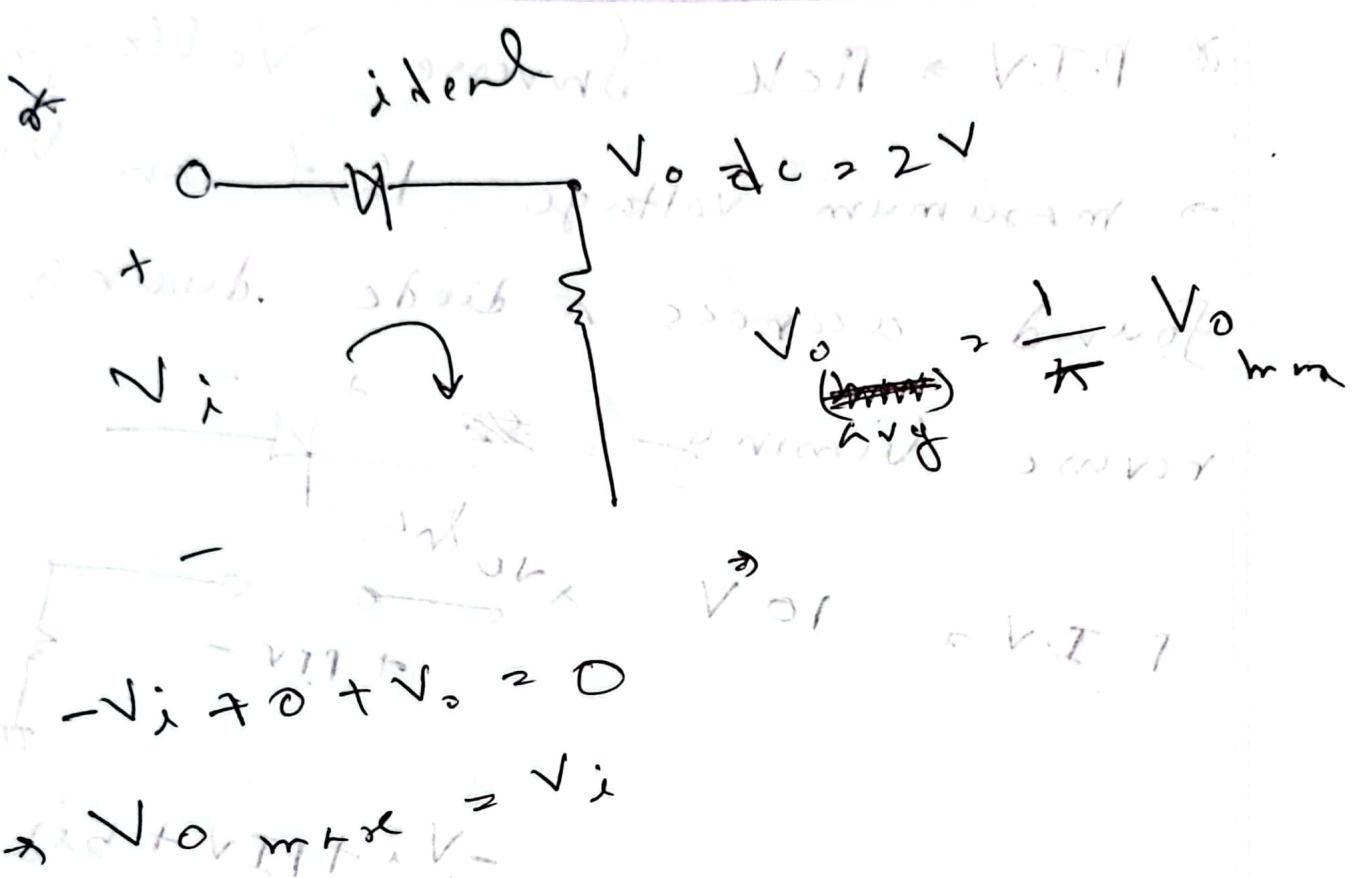

$$2V = V_i$$


$$V_o =$$

Ch3 v o f o r k

6.W  
2.5.6.23

Elec

## full wave diode bridge rectification

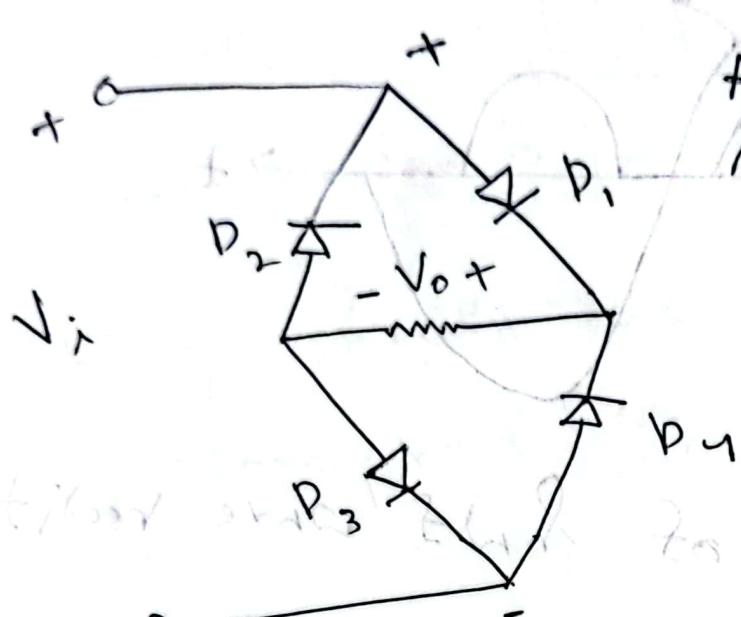


All diodes should be identical

$$\text{(x) } \text{for } D_1 \text{ to be forward biased, } -V_i + V_{on} + V_o + V_{on} = 0 \text{ mV} \quad (1)$$

$$V_o = V_i - 2V_{on}$$


$\Rightarrow$  for  $D_2, D_4$  to be forward biased,  $-V_i - 2V_{on} = 0 \text{ mV} \quad (2)$

$$V_o = -V_i - 2V_{on}$$

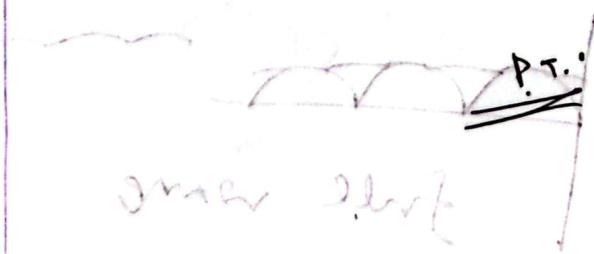

more later
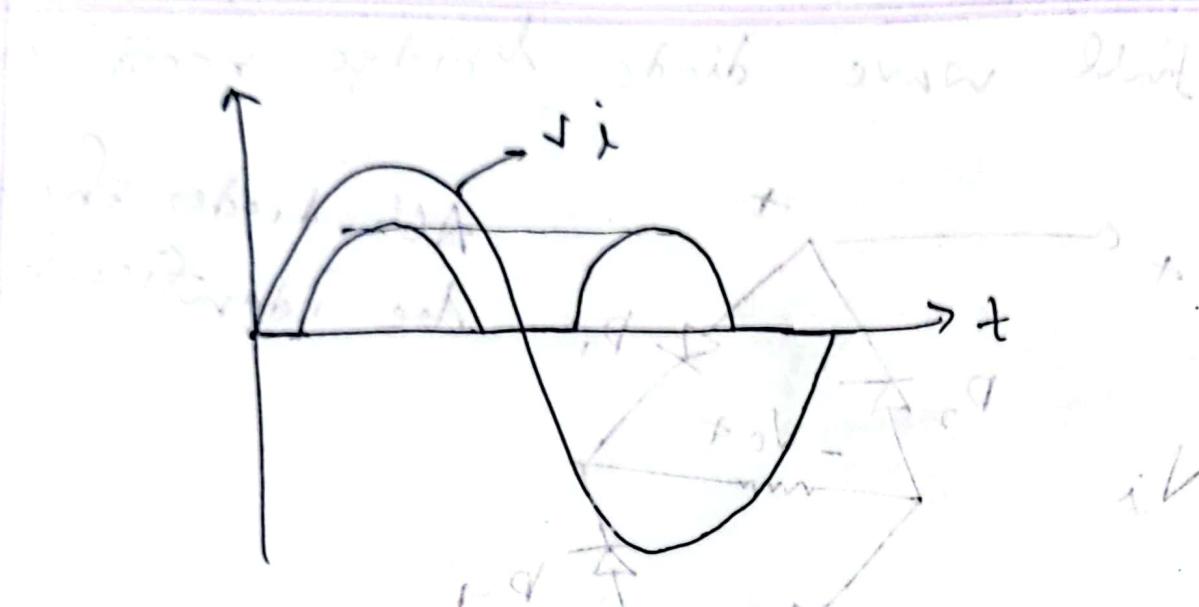
$$V_o = \begin{cases} V_i - 2V_{ON}, & V_i > V_{ON} \\ 0, & V_i < V_{ON} \end{cases}$$




\* Advantages of Half Wave Rectifier

- (i)  $V_o, \text{ max} \uparrow$  with full wave
- (ii) cost  $\uparrow$

\* Advantages of full Wave rectifier

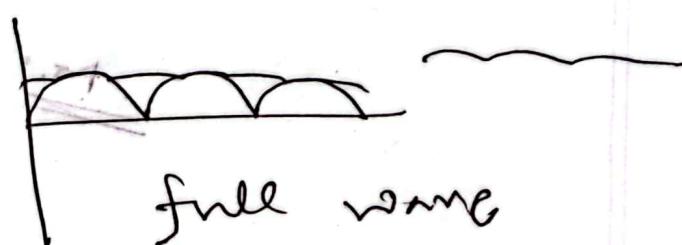- (i)  $V_o, \text{ avg} \uparrow$
- (ii) rectification



Overall

coupling  $\rightarrow$  half wave

rectification  $\rightarrow$  full wave

\* Why should all 4 diodes in full wave rectifier be identical?


$\Rightarrow$


$$V_o = V_i - 2V_{ON} \rightarrow V_o = V_i + (V_{ON1} + V_{ON3})$$

$$V_o = -V_i - 2V_{ON} \rightarrow V_o = -V_i - (V_{ON2} + V_{ON4})$$

1 = ideal, 2 = C.R.C, 3 = S.I., 4 = G.R.
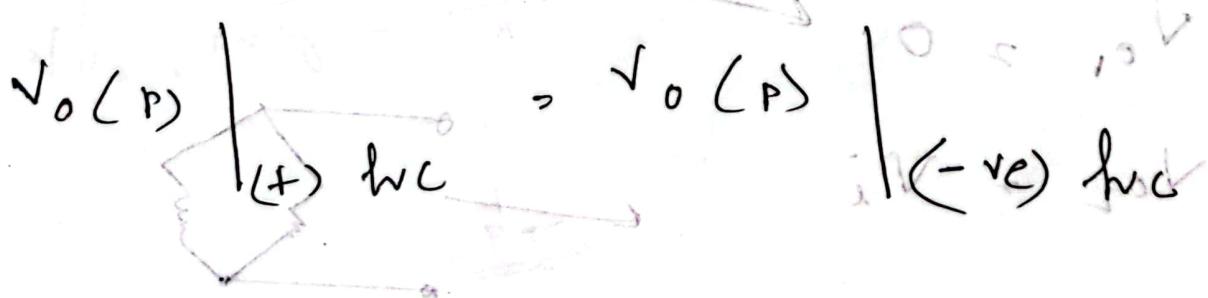
$$\begin{aligned} V_{ON1} &= V_i - 0.7 \\ V_{ON2} &= -V_i - 1.5 \end{aligned}$$



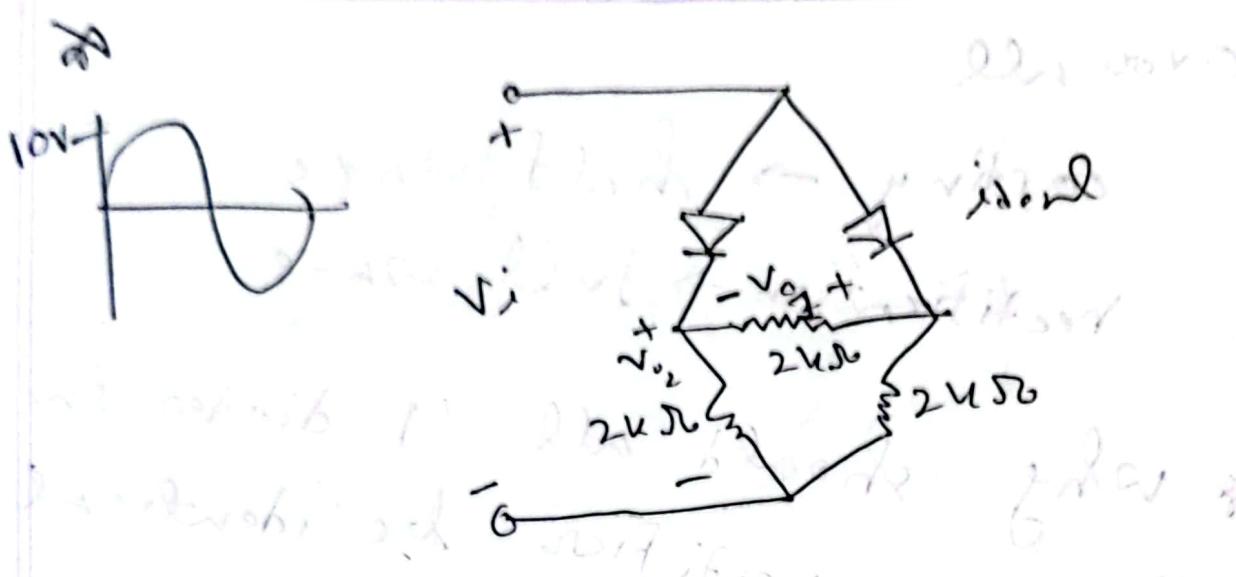

(a) Derive the expression of  $V_o$

(sketch it, take note of  $V_{D1}, V_{D2}$ )



(b) Calculate  $V_{o, \text{max}}$  &  $V_{o, \text{avg.}}$

(c) Calculate PIV of any diode.

~~(d)~~ h.c.

$$V_{o1} = 0$$

$$V_{o2} \rightarrow V_i$$

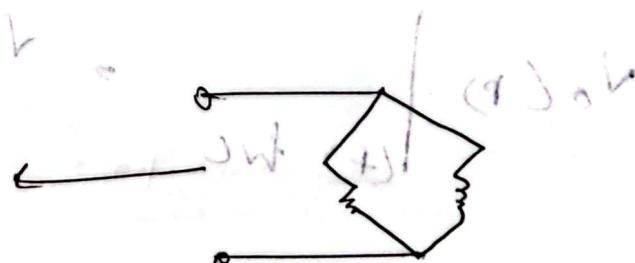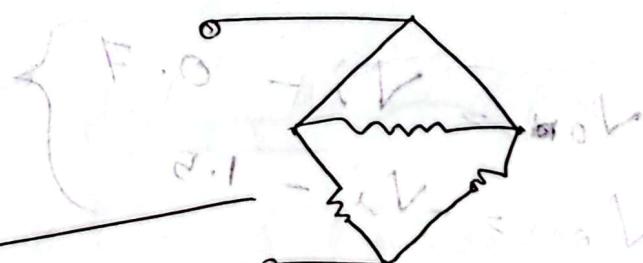


$\leftarrow \text{Inv}^{\circ}$ ,

$i = 0$

$V_{o_2} = 0$

$V_{o_1} = 0$

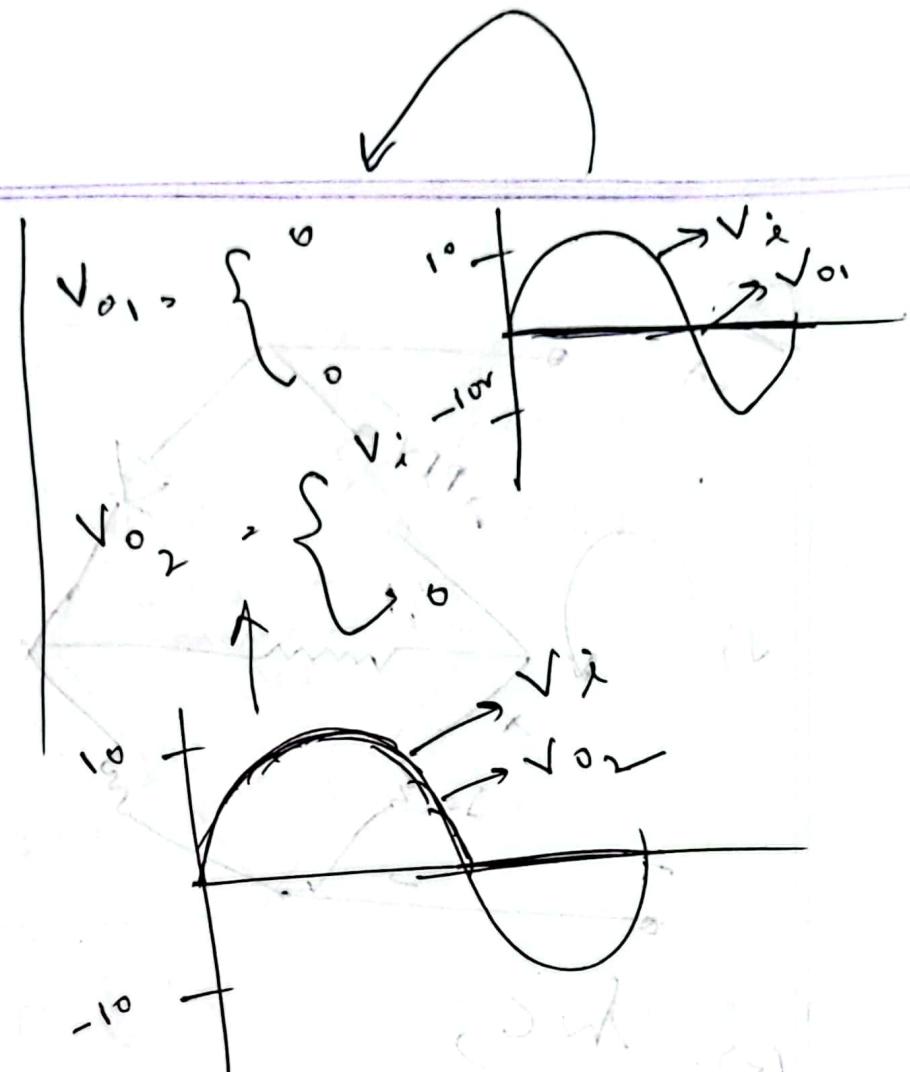


(N)  $V_{o_2}, \text{max} = 0$

$V_{o_1}, \text{avg} (= 0)$

$$V_{o_2} = 20 \text{ V}$$

$$V_{o_2, \text{avg}} = \frac{10}{\pi} \text{ V}$$

P.T.

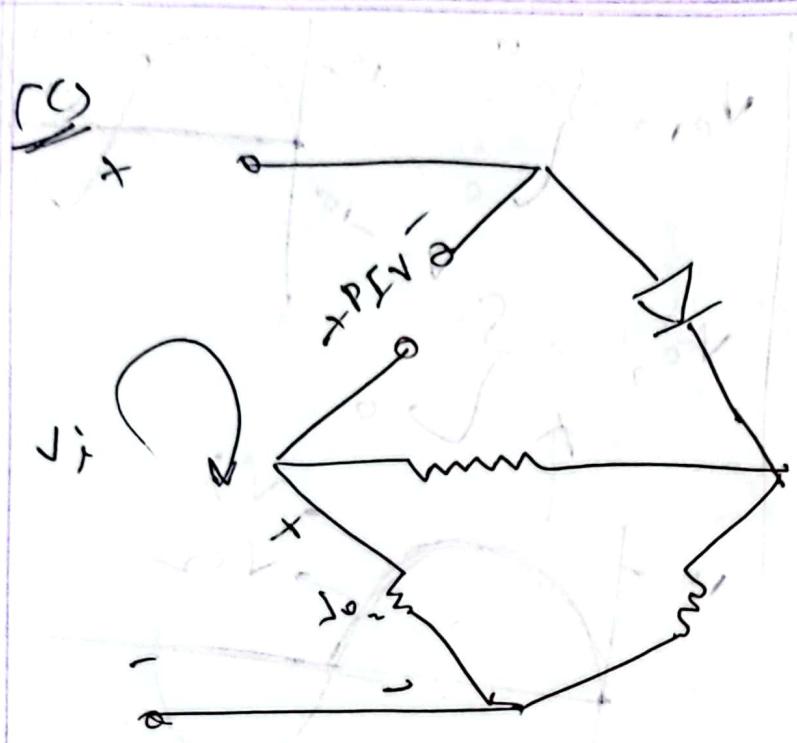


$\rightarrow \text{hc}$

$$\begin{aligned}
 -V_i - P1V + V_{02} &= 0 && \left( \begin{array}{l} \rightarrow \text{hc}, \\ V_{02} = 0 \end{array} \right) \\
 \Rightarrow P1V &= -V_i \\
 &= -(-10) \\
 &= 10V
 \end{aligned}$$

P1V

full wave



24

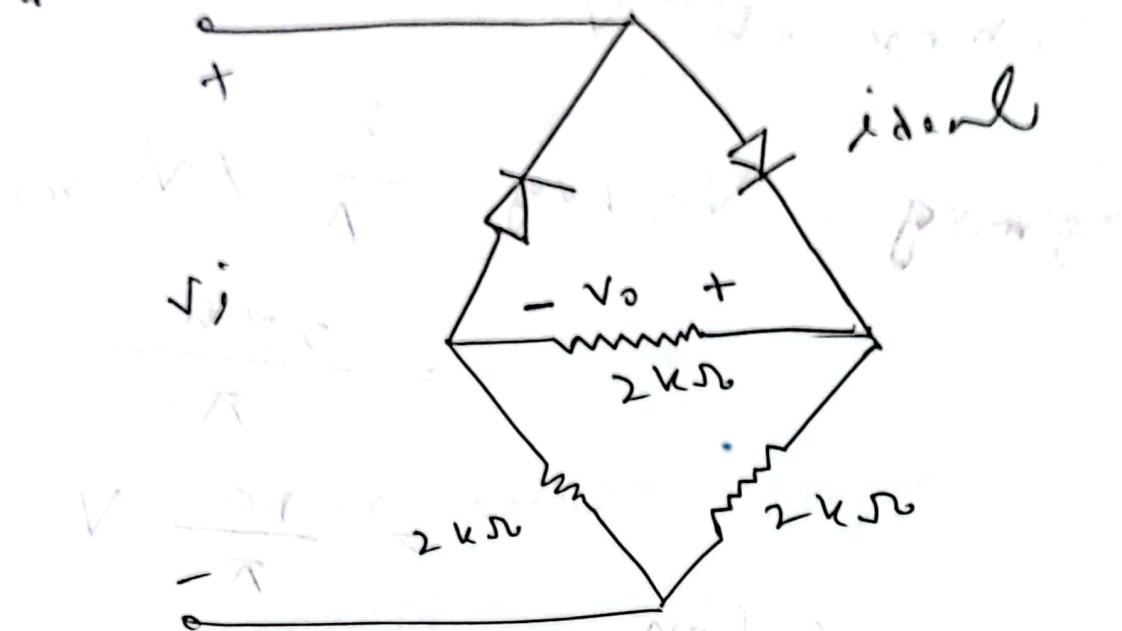

(+) inc




$V_{01}$

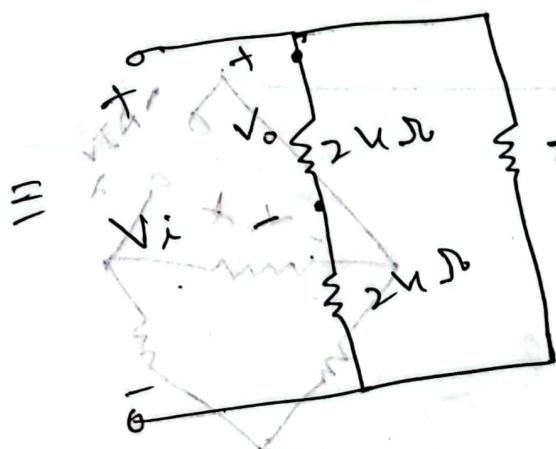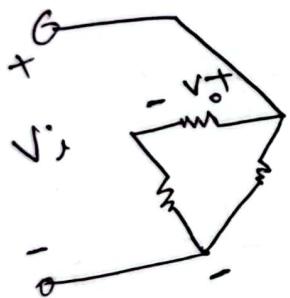

$$V_0 = \frac{V_i}{2}$$

(-) inc

$$V_0 = -\frac{\sqrt{i}}{2} V_0 = 5.0$$

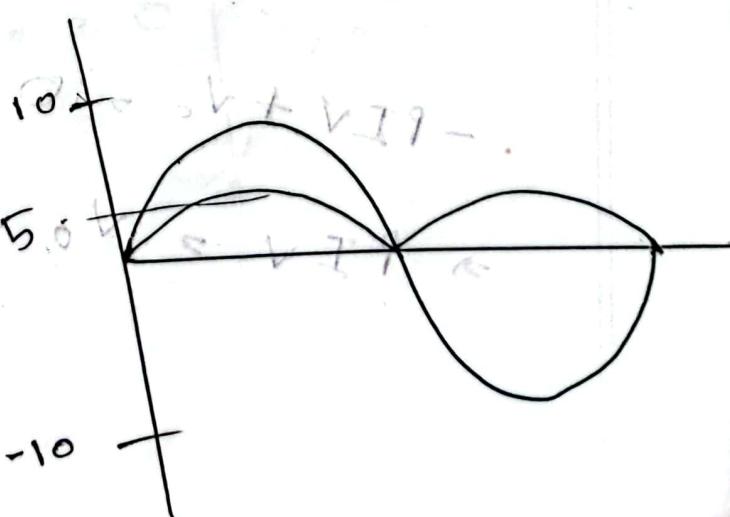



$$V_{0, \text{max}} = 5 \text{ V}$$

$$V_{0, \text{avg}} = \frac{2}{\pi} \times V_{0, \text{max}}$$

$$= \frac{2 \times 5}{\pi} \text{ V}$$

$$V_{0, \text{avg}} = \frac{10}{\pi} \text{ V}$$

PIV calculation

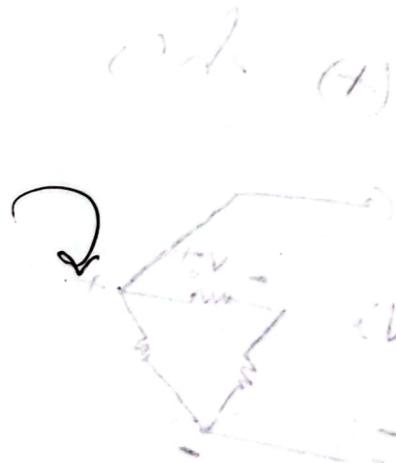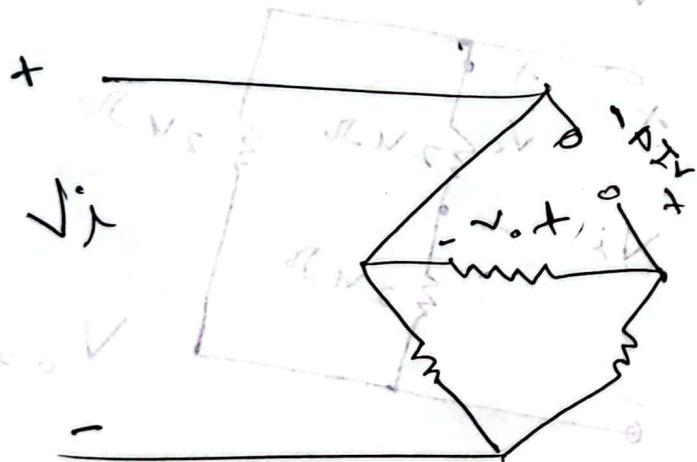

$$-PIV + V_0 = 0$$

$$\rightarrow PIV = V_0 \approx 5 \text{ V}$$


C.T.-4, July 12

\* Rectifier, half, full wave.

~~GW  
S.F. 2~~ ~~(clippers)~~


\* Half wave rectifier can be considered as a clipper.

$$V_i \rightarrow \text{sine } 10V (r)$$

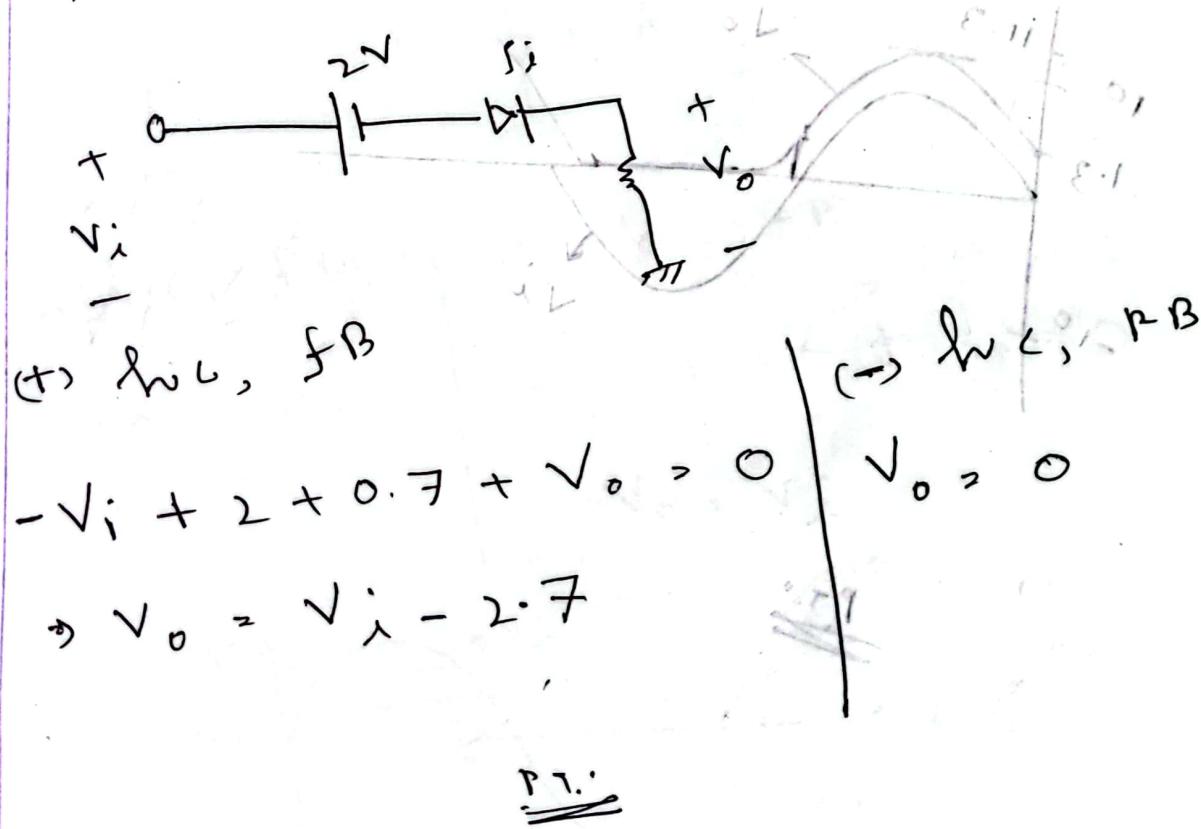

$$-V_i + 2 + 0.7 + V_o > 0 \quad V_o = 0$$

$$\Rightarrow V_o = V_i - 2.7$$

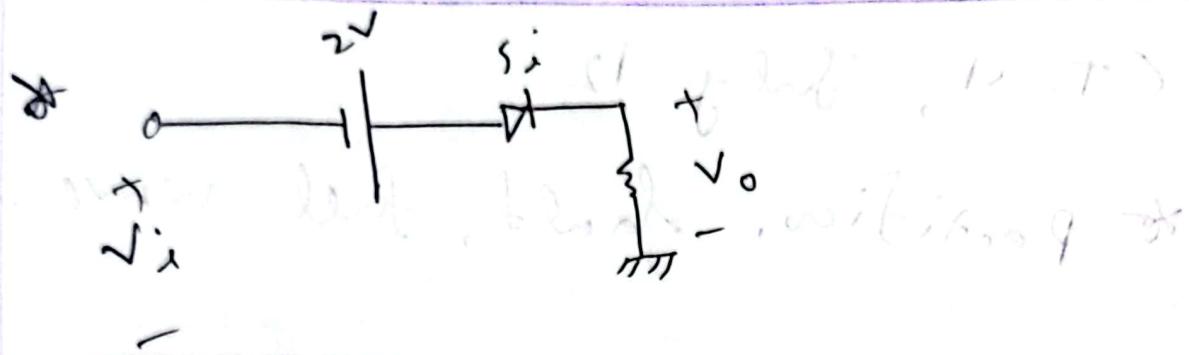


(+) h.c. f.B

$$-V_i - 2 + 0.7 = V_o \text{ (approx)}$$

$$\Rightarrow V_o = V_i + 1.3$$


$\rightarrow$  h.c. R\_B

$$V_o = 0$$

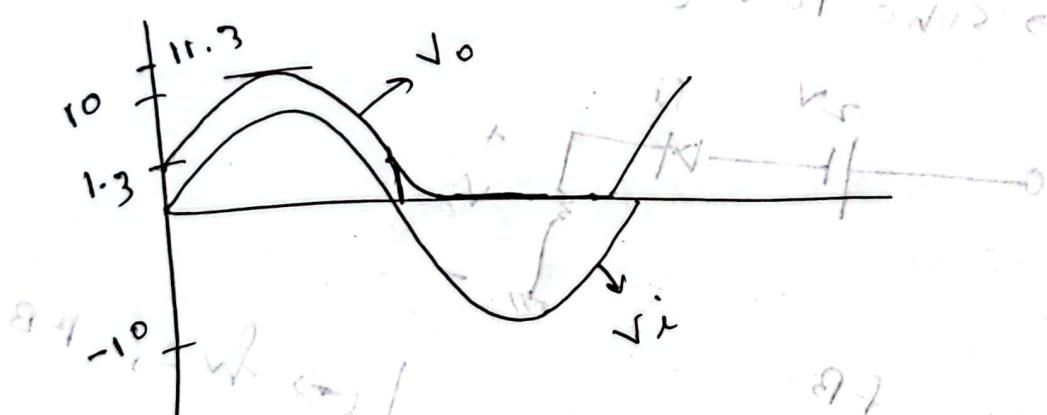

(a) V\_o vs V\_i with R\_L

~~P.T.O.~~

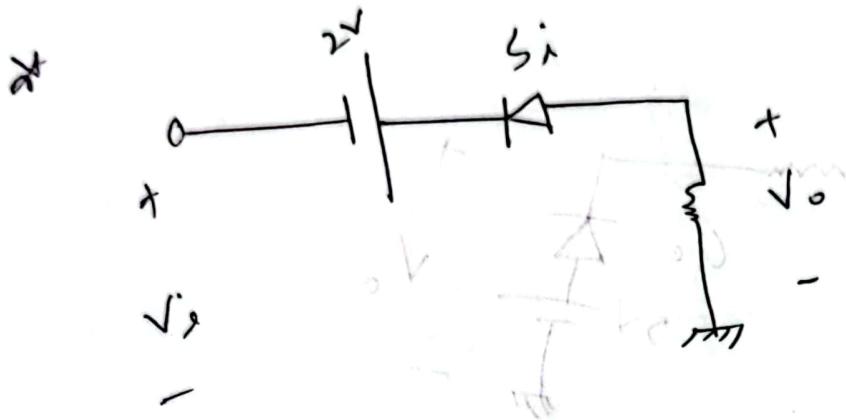


(x)  $h_{ic}$ , P.B.

$$V_o = 0$$

$\rightarrow h_{ic}, f.B.$

$$-V_i - 2 - 0.7 + V_o = 0$$

$$\Rightarrow V_o = V_i + 2.7$$

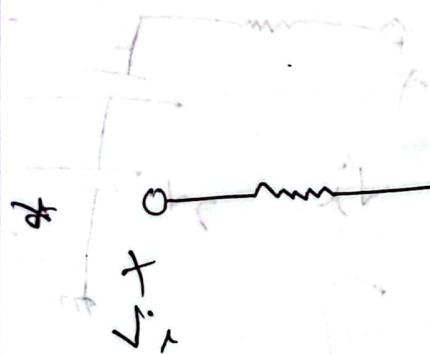


(x)  $h_{ic}$ , F.B.

$$V_o = 1.2$$


$\rightarrow h_{ic}$ , P.B.

$$-V_i + iR + V_o = 0$$


$$V_o = V_i$$

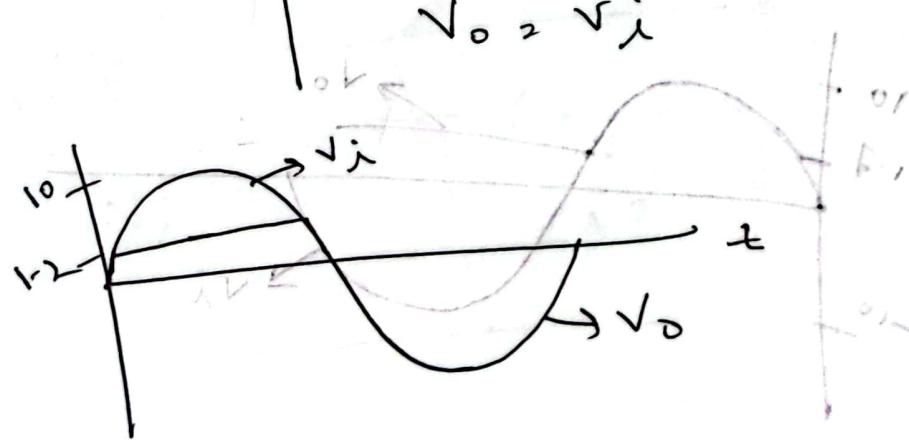

8

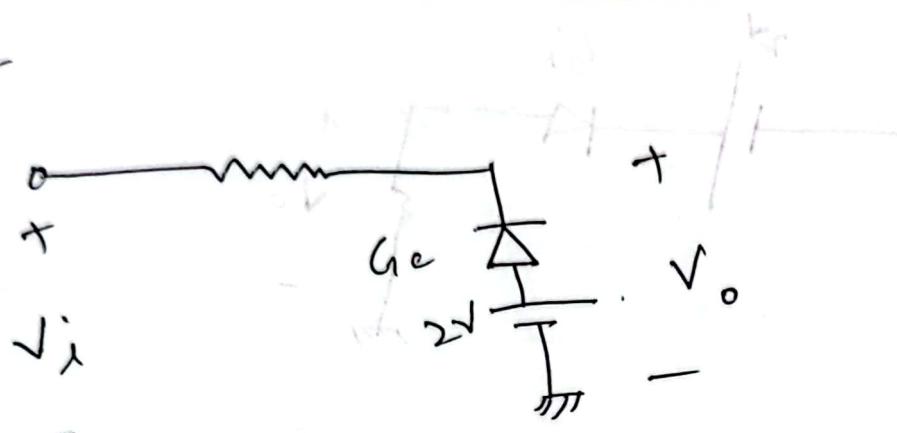

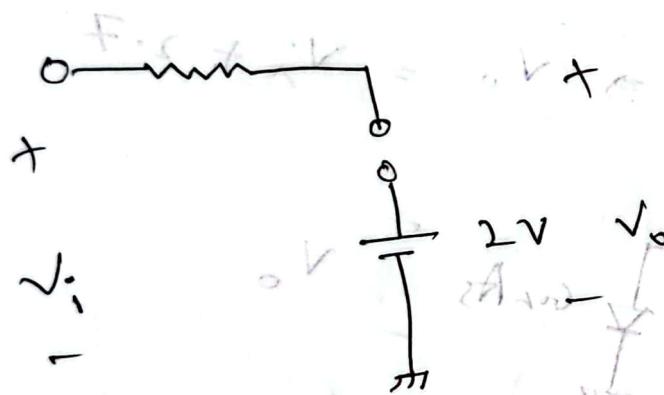
(F)  $h_{ic}, h_{re}, B_F, B_E - r_o, r_s$



$$\Rightarrow -V_i + 2V + V_o = 0$$


$$\Rightarrow V_o = V_i - 2V$$

(G)  $h_{ic}, f_B, B_F$

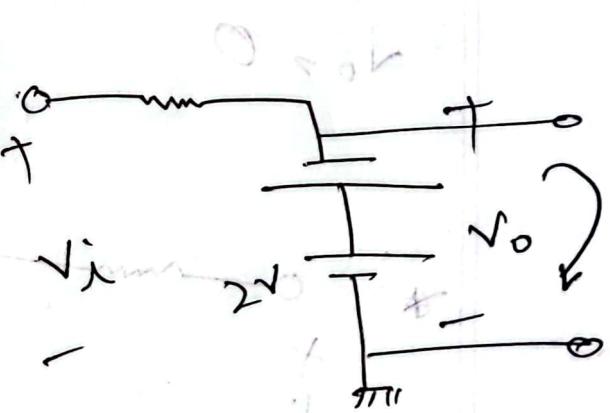


$$-2 + 0.3 + V_o = 0$$


$$\Rightarrow V_o = 1.7V$$

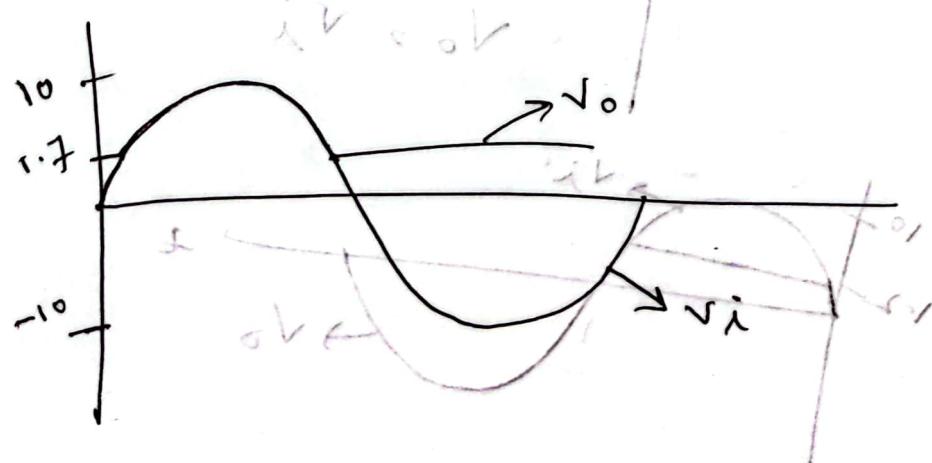

\*

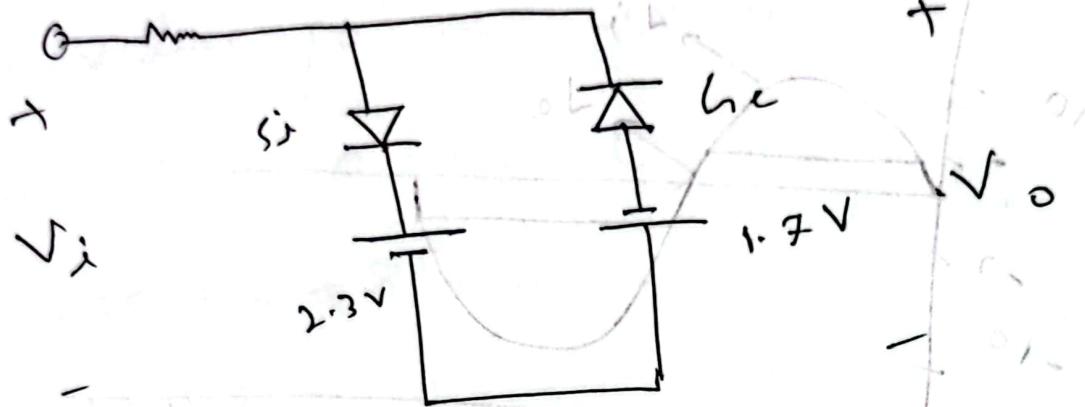


(\*) M1, FB

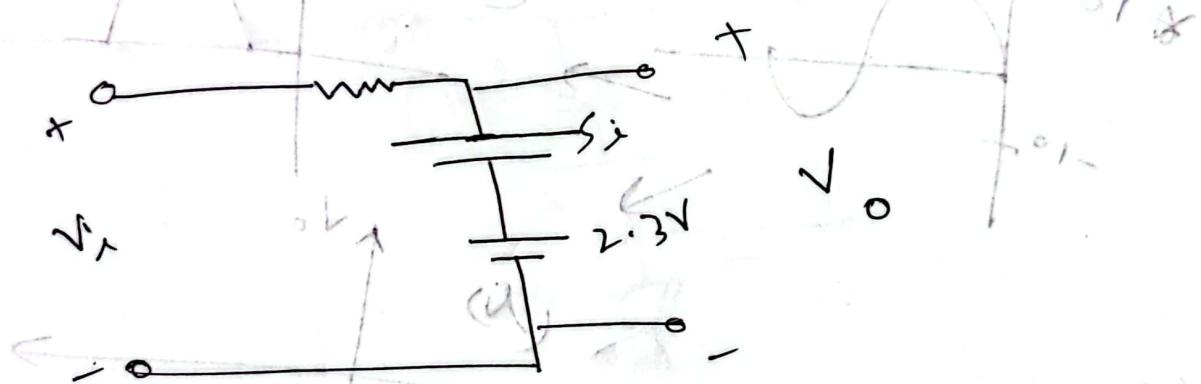


$$\rightarrow -2.3 + 0.7 + V_o = 0$$

$$\Rightarrow V_o = 3V$$

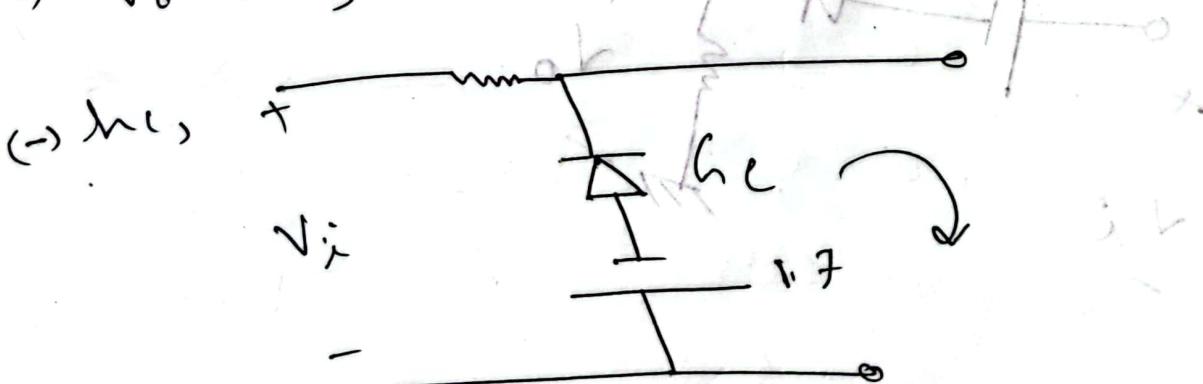

$$V_o = -2$$

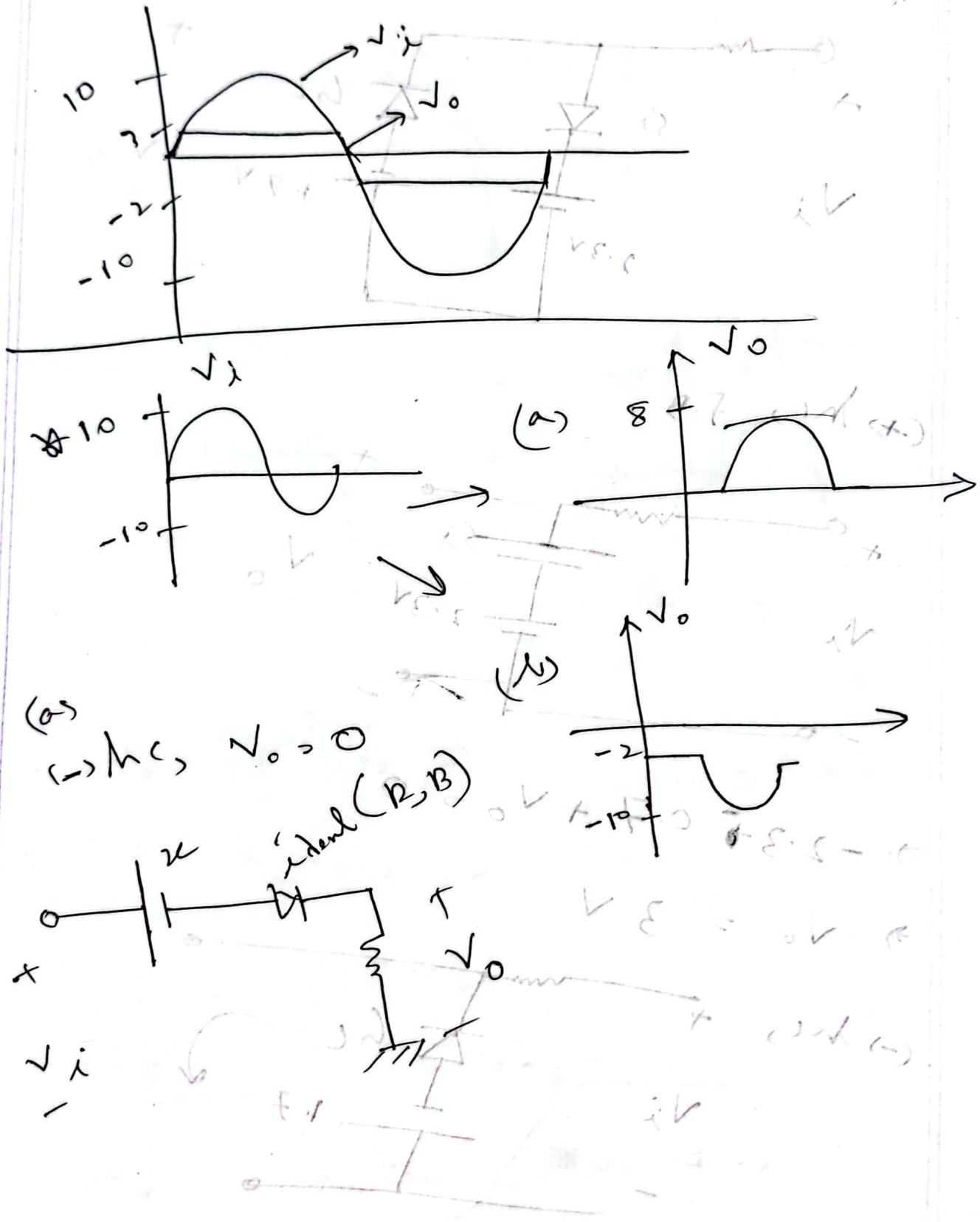


~~(a)~~

for value of  $x$ , ( $\rightarrow$ )  $\text{dc}$ ,


$$-\sqrt{i} + x + 0 + \sqrt{o} = 0$$

$$\Rightarrow -10 + x + 8 = 0$$

$$\Rightarrow x = 2\sqrt{ }$$

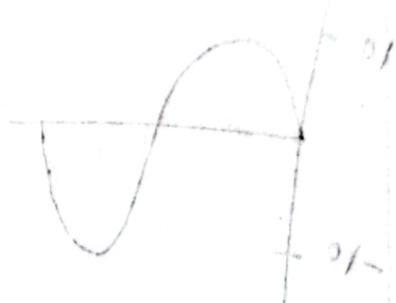

(b)

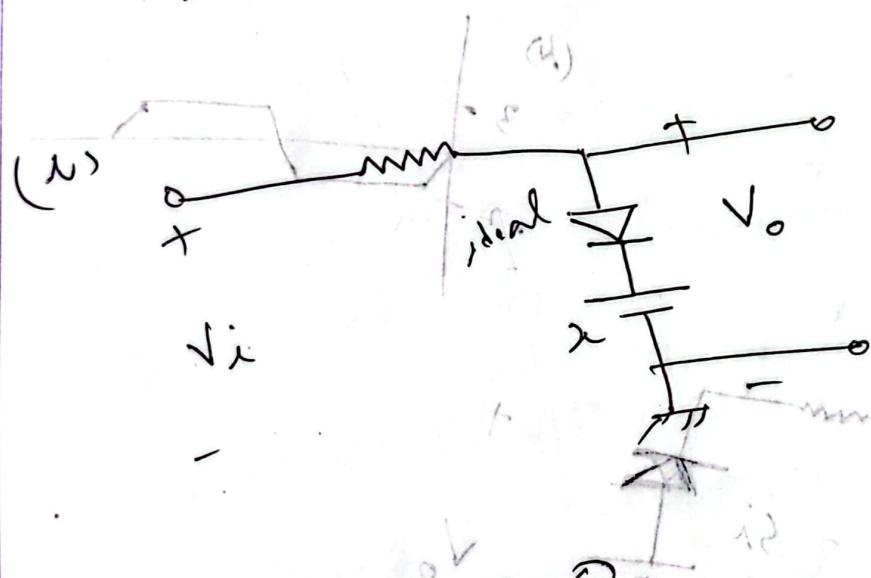

$$\Rightarrow -x + 0 + 2\sqrt{ } = 0$$

$$\Rightarrow -x + 2\sqrt{ } = 0$$

$$\Rightarrow x = 2\sqrt{ }$$

at  $\text{dc}$





$$0 = \sqrt{i} + 0 + x -$$

$$0 = \sqrt{o} + 0 + x -$$

$$0 = \sqrt{i} + \sqrt{o} + x -$$

~~179~~

CW  
2.2.23

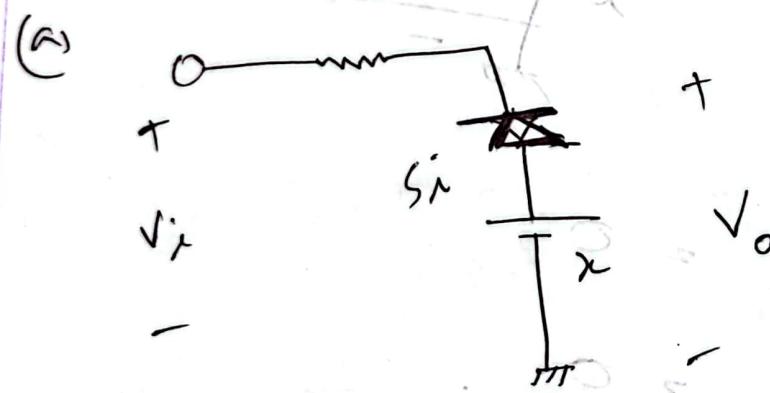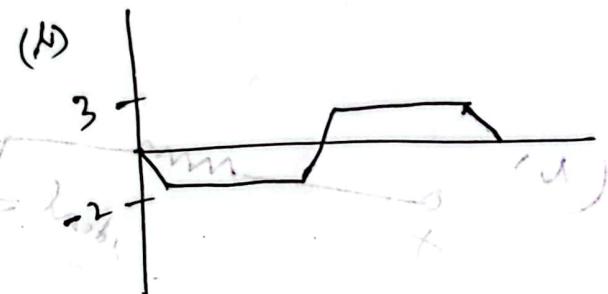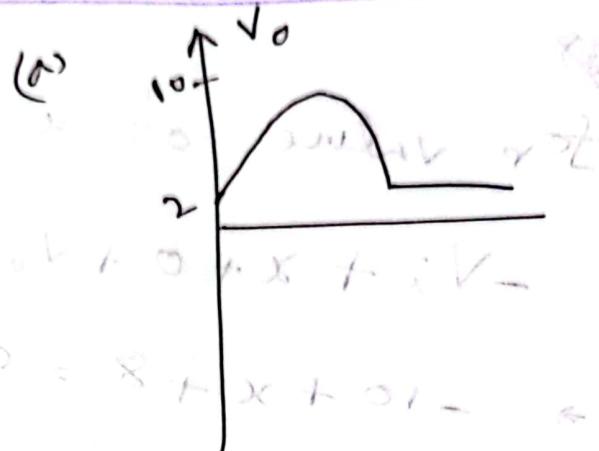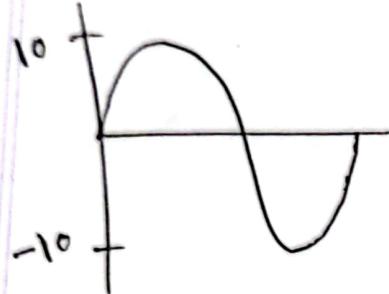

$\leftarrow$  sh. FB

$$-x + 0.7 + V_o = 0$$


$$\Rightarrow -x + 0.7 + 2 = 0$$

$$\Rightarrow x = 2.7 \text{ V}$$

$\leftarrow$  sh. FB  
 $V_o = 2$

PTI

(b)

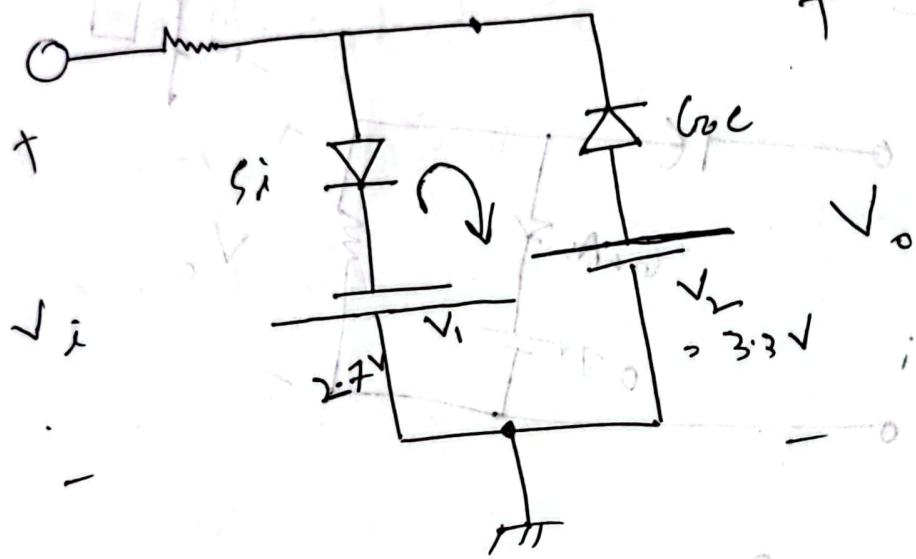

(c)  $\Delta V_C$

$$-v_1 - 0.7 + v_o = 0$$

$$-v_1 - 0.7 - 2 = 0$$

$$\Rightarrow v_1 = -2.7$$

$\rightarrow \Delta V_C$


$$v_2 + 0.3 + v_o = 0$$

$$\Rightarrow v_2 + 0.3 + 3 = 0$$

$$\Rightarrow v_2 = -3.3$$

P.T.O


Clampen

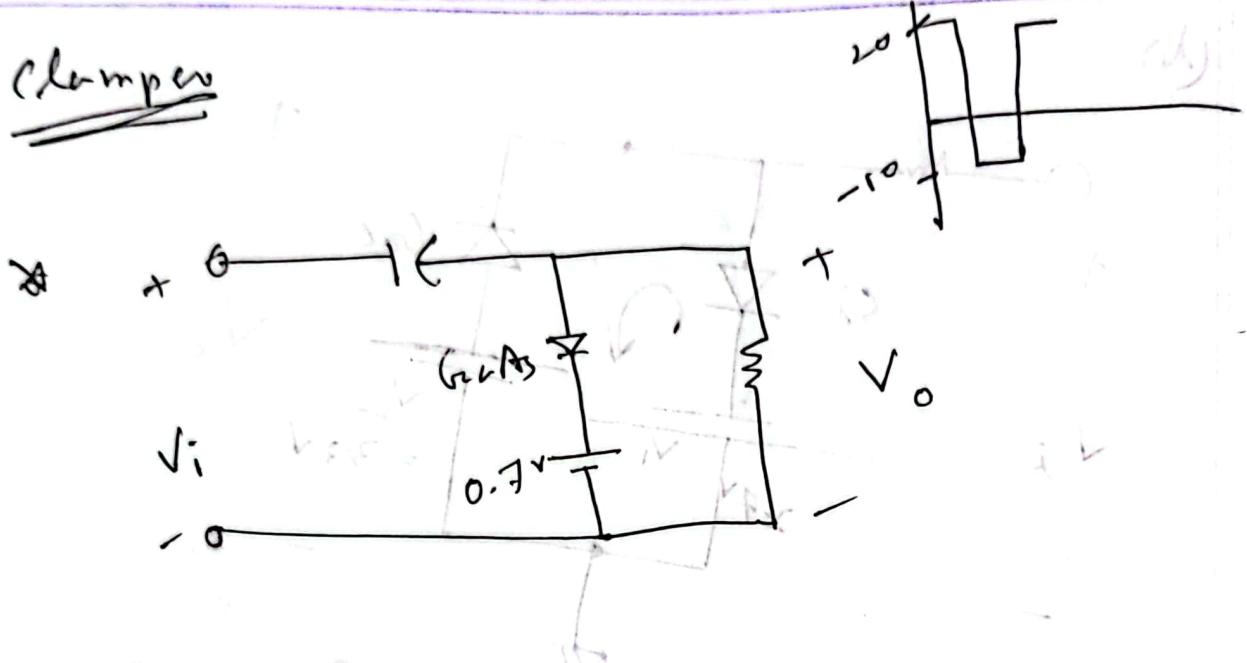

(+) h.c. f.B.

$$-0.7 - 1.2 + v_o = 0$$

$$\rightarrow v_o = 1.9 \text{ V}$$

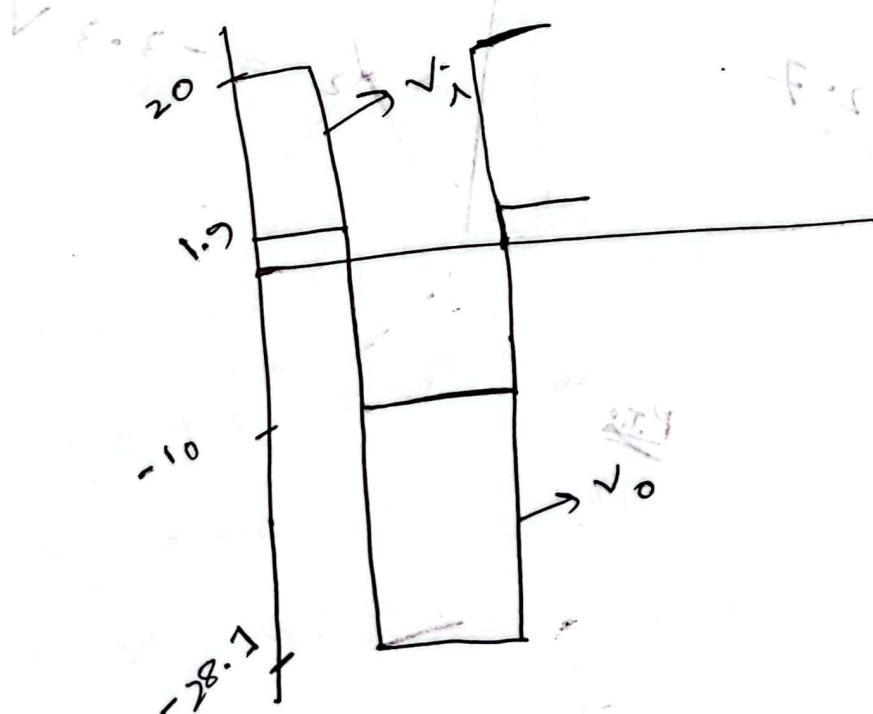



$$V_i(p-p) = V_o(p-p)$$

$$\Rightarrow 20 - (-10) = 1.9 - x$$

$$\Rightarrow 30 \rightarrow 1.9 - x$$

$$\Rightarrow -x = 28.1$$


$$\Rightarrow x = -28.1$$

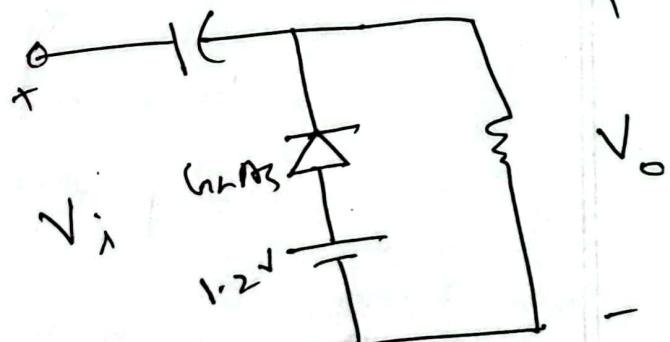
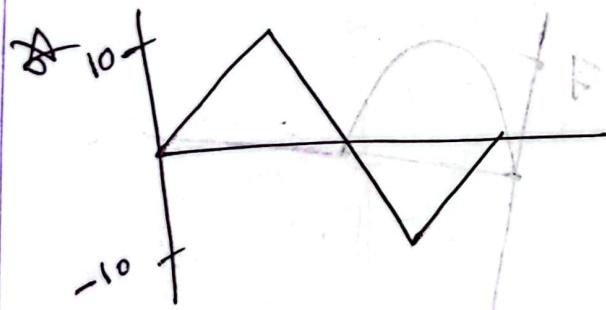


(-)  $\Delta C$ ,  $f-B$ ,

$$-1.2 + 1.2 + V_o$$

$$\Rightarrow V_o = 0$$

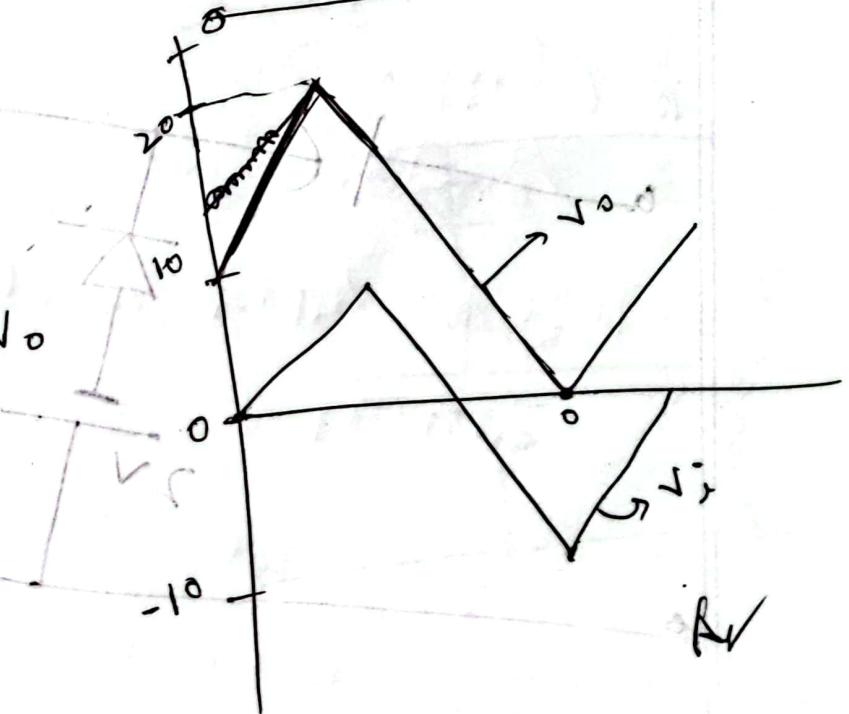


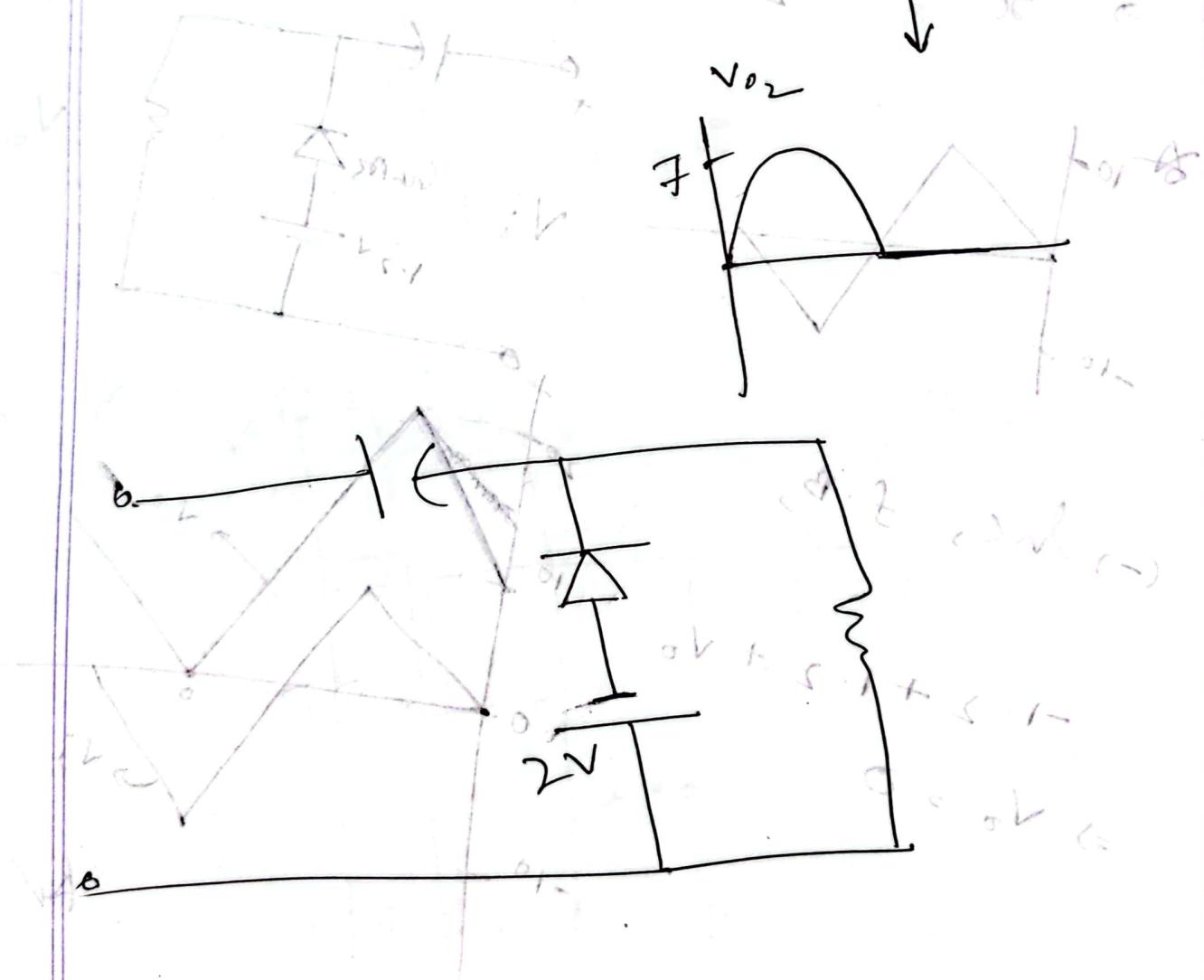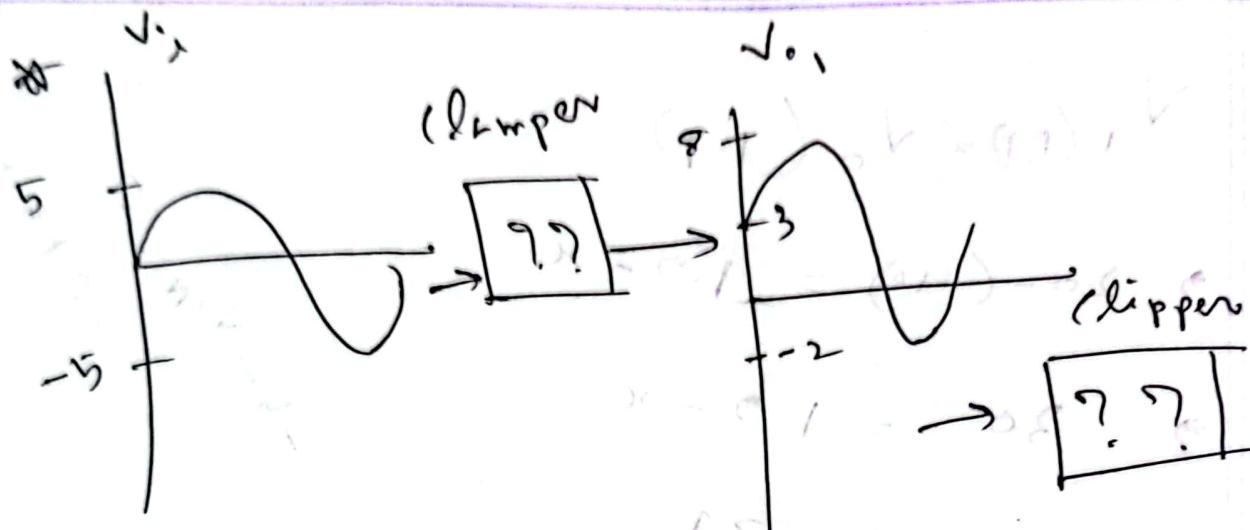

$\Rightarrow \Delta c$

$$-x + 0 + \sqrt{0} = 0$$


$$\Rightarrow -x - 2 = 0$$

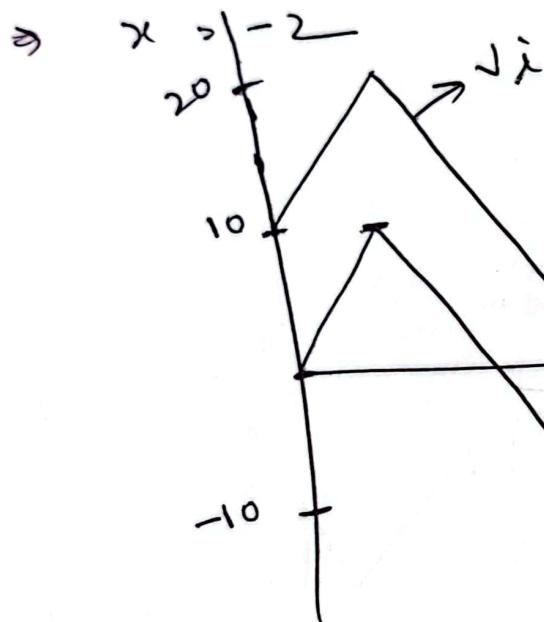

$$-10 + \sqrt{0} = 0$$

$$\sqrt{0} \rightarrow 10 \text{ (rigid)}$$

It's a rigid rotation

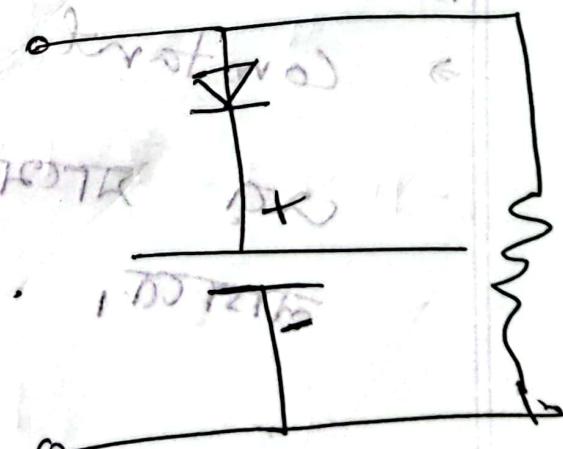

Ans,

$$\Leftrightarrow V_o = 3.2$$

$\Leftrightarrow$  for f.B,

$$-x + 0.7 + 3.2 = 0$$

$$\Rightarrow x = 3.9$$

$\Leftrightarrow$



\* Clipper  $\rightarrow$

$\Rightarrow$  Constant value  $\rightarrow$  f.B


or যদি KVL মনে রাখা

হয়ে

\* Clamp:

→ positive half cycle:  $\Rightarrow$  output

forward bias

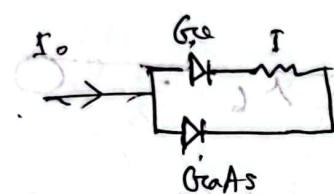

positive feedback + PII

$\delta = \sin \phi$

$P_I = \delta I$

$8I = P_I + P_{II} = \sin^2 \phi$

$$\cancel{-12 \cdot 3 + 0 \cdot 3} + i_5 - 2 = 0$$

$$\Rightarrow i_5 = 14$$

$$-\cancel{v} + 0.7 + 2 \cdot 7 + 14 - 2 = 0$$

$$\Rightarrow -v + 15.4$$

$$\Rightarrow v = 15.4$$

$$\cancel{-12 \cdot 3 + 0 \cdot 3} + 2 i_6 = 0$$

$$\Rightarrow \cancel{2 i_6} = \cancel{12}$$

$$\Rightarrow i_6 = \cancel{6}$$

$$\therefore \cancel{i_4} = \cancel{i_5 + i_6} =$$

$$-11.4 + 0.7 + 2 \cdot 7 + 2 i_6 = 0$$

$$\Rightarrow 2 i_6 = 8$$

$$\Rightarrow i_6 = 4$$

$$\therefore \cancel{i_4} = 14 + 4 = 18$$

Ques 11


11/12/2019

$$-\sqrt{i} + 0.7 + 200i = 300 \text{ Amperes}$$

$$\begin{aligned}\Rightarrow 200i &= \sqrt{i} - 0.7 \\ \Rightarrow i &= \frac{5 - 0.7}{200} \\ &= 0.0225 \text{ A}\end{aligned}$$

$$\therefore -\sqrt{i} + 0.7 + 2.15 + V_o = 0$$
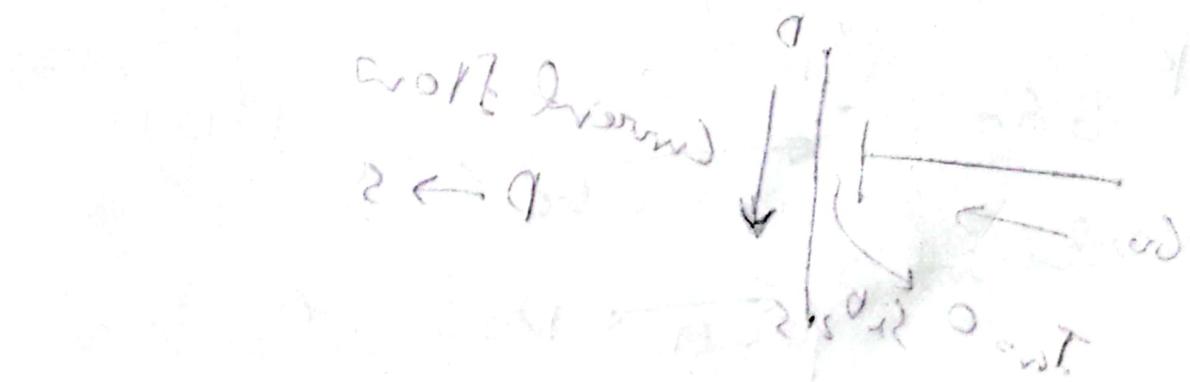
$$\begin{aligned}\Rightarrow \sqrt{0} &\text{ max } \sqrt{i} - 2.85 \\ &\text{Principle} \quad \text{Electron flow} \\ &\text{opposite direction} \quad \text{opposite direction}\end{aligned}$$




Ans

~~CW  
26.7.23~~

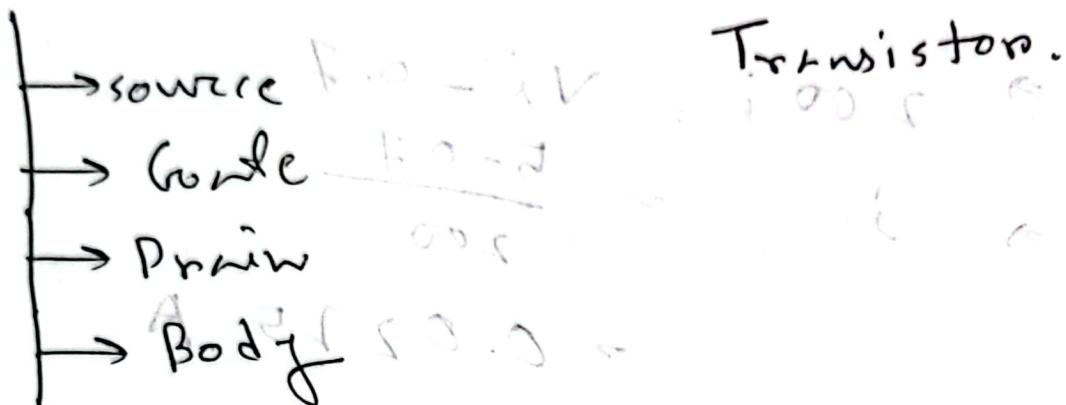
## MOSFET

Electronics

\* Metal Oxide Semiconductor Field Effect Transistor.



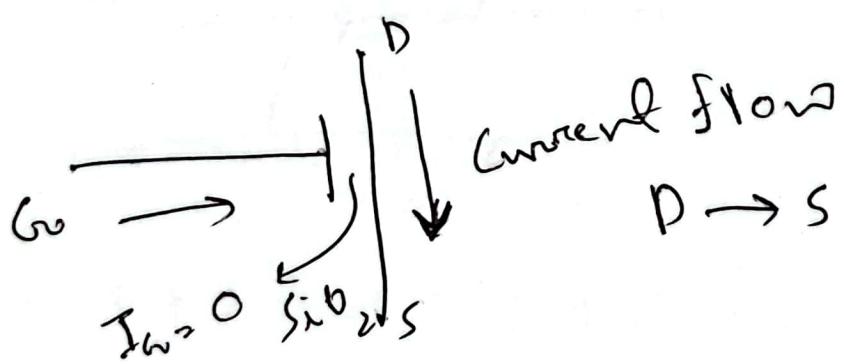$V_g > V_t$  - threshold voltage  
 $V_d = 0$  - drain voltage  
 $N_{D_s} > N_{A_b}$  - drain side heavily doped  
 $N_{A_b} \gg N_{D_s}$  - body side moderately doped



P.T.S

## Overdrive Voltage

$$V_{ov} = V_{gs} - V_t$$

\* MOSFET ON state

~~Step 1~~  $V_{gs} \geq V_t$

~~Step 2~~ MOSFET Triode region or  
~~Saturation~~ Saturation region  $\rightarrow$  GATE

form

$$* V_{ds} < V_{ov} \rightarrow \text{Triode}$$

$$* V_{ds} \geq V_{ov} \rightarrow \text{Saturation}$$

6.2

$C_{ox}$  : Oxide Capacitance

$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} \quad t_{ox} = 2\text{nm} = 2 \times 10^{-9} \text{ m}$$

$$\frac{3.9 \times 10^{-11}}{8 \times 10^{-9}}$$

$$= 4.875 \times 10^{-3} \text{ F/m}^2$$

$$K_w = \mu_w C_{ox}$$

$$= 450 \times (10^{-2}) \times 4.875 \times 10^{-3}$$

$$= 1.99 \times 10^{-9} \text{ A/V}$$

~~Triode~~

$$* I_D = k'w \left( V_{GS} - V_t \right) V_{DS} - \frac{1}{2} V_{DS}^2$$

$$\approx k'w \frac{V_{GS} - V_t}{L} \left[ (V_{GS} + V_{DS}) - \sqrt{\frac{1}{2} V_{DS}^2} \right]$$

~~Saturation~~

$$* I_D = \frac{1}{2} k'w \frac{V_{GS} - V_t}{L} (V_{GS} - V_t)^2$$

$$* V_{DS}^{\min} = V_{DS}$$

$$(a) * I_D = \frac{1}{2} k'w \frac{V_{GS} - V_t}{L} (V_{GS} - V_t)^2$$

$$\Rightarrow (V_{GS} - V_t) = \frac{2 I_D L}{k'w w}$$

$$\frac{2 \times 100 \times 10^{-6} \times 0.8}{2 \times 1.34 \times 10^{-4} \times 8}$$

$$\Rightarrow V_{GS} - V_t = 0.32 \quad ; \quad V_{GS} = 0.32 + 0.7 \\ = 1.02 \text{ V}$$

## Triode

$$I = k'w \frac{W}{L} (V_{GS} - V_T) V_{DS}$$

$$\Rightarrow \frac{I}{V_{DS}} = k'w \frac{W}{L} (V_{GS} - V_T)$$

$$\Rightarrow \frac{I}{R} = k'w \frac{W}{L} (V_{GS} - V_T)$$

$$\Rightarrow V_{GS} - V_T = \frac{I \times L}{R \times k'w \times W}$$

$$\Rightarrow \frac{2 \times 0.8}{r_{o} \times 1.24 \times 10^{-4} \times 8}$$

$$\Rightarrow \frac{1.6}{0.515} \text{ (Ans)}$$

$$\Rightarrow V_{GS} = 0.515 + 0.7$$

$$= 1.215 \text{ V}$$



Q4. 0.80 = 20k ... 48.0 = 10 - 20k =  
8.0 = 10 - 20k  
20k = 10 - 8.0  
20k = 2.0  
k = 0.1

$$V_{DS} = V_D - \sqrt{s} \rightarrow 0.5 - \sqrt{s}$$

$$V_{OV} = V_{GDS} - \sqrt{t} = V_G - \sqrt{s} - \sqrt{t}$$

$$\rightarrow 0 - \sqrt{s} - \sqrt{t}$$

$$\rightarrow -\sqrt{s} - 0.7$$

$$V_{DS} > V_{OV} \rightarrow \text{saturation}$$

$$I_D = \frac{1}{2} k' w \frac{V_P \cdot \omega}{L} (-V_{GS} - \sqrt{t})$$

$$\rightarrow I_D = \frac{1}{2} k' w \frac{\omega}{L} (V_G - \sqrt{s} - \sqrt{t})$$

$$\rightarrow \cancel{I_D = \frac{1}{2} k' w \frac{\omega}{L} (-\sqrt{s} - \sqrt{t})}$$

$$\rightarrow (-\sqrt{s} - \sqrt{t}) = \frac{I_D \times 2 \times L}{k' w \times \omega} = \frac{0.4 \times 10^{-3} \times 2}{100 \times 10^{-6} \times 3}$$

$$\rightarrow -\sqrt{s} - \sqrt{t} = \frac{1}{2} \rightarrow \frac{1}{4}$$

$$\rightarrow -\sqrt{s} = \frac{1}{2} + 0.7 = 1.2, \quad \sqrt{s} = -1.2 \text{ V}$$

$$\therefore P_S = \frac{V_S - V_{SS}}{I_D}$$


$$= 1.2 + 2.5$$

$$P_S = \frac{0.4 \times 10^{-3}}{0.4 \times 10^{-3}}$$

$$R_D = 2k\Omega$$

$$= 3250 \Omega$$

~~CW  
31.7.23~~

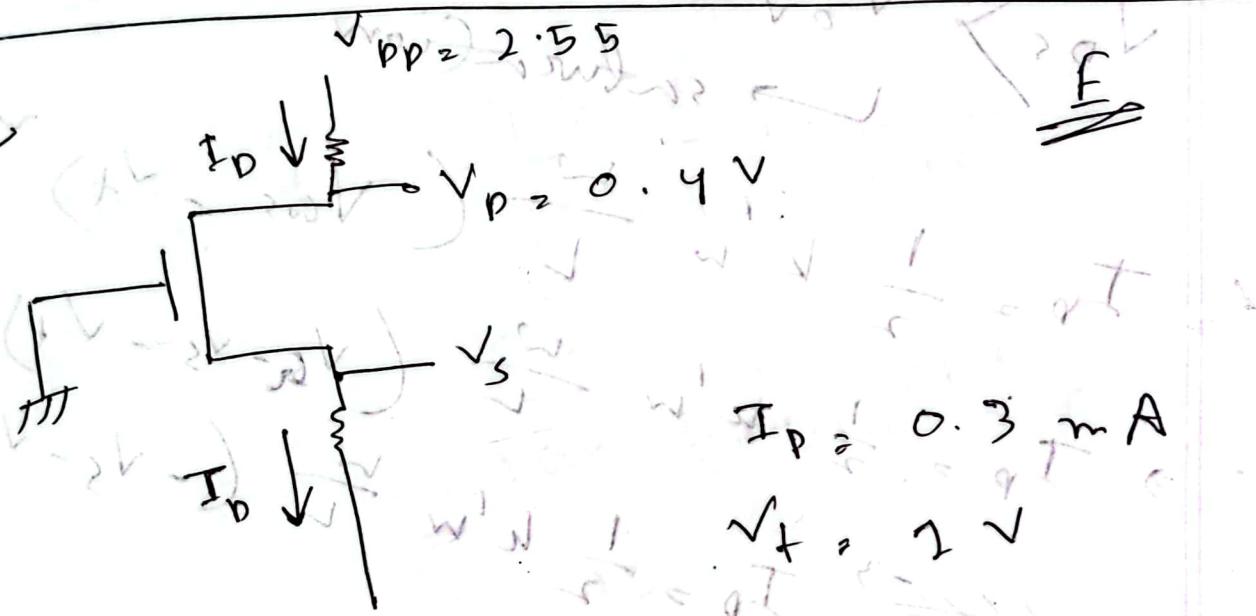

$$V_{DS} = -2.5 V$$

$$I_D = 0.3 \text{ mA}$$

$$V_F = 2 V$$

$$\frac{W}{L} = \frac{8}{0.8} \mu m$$

$$I_D = \frac{W}{L} \cdot V_{DS}^2 / 2$$

$$\frac{1}{L}$$

$$V_{DS} = 2 V$$

$$V_t = 2 \sqrt{2 \times 10^{-6} \times 10^6} = 2 \sqrt{2} \approx 2.82 \text{ V}$$

$$\mu_n C_{ox} = 60 \frac{\mu\text{A}}{\text{V}^2}$$

$$C_{ox} = 60 \times 10^{-6} \frac{\text{F}}{\text{m}^2}$$

$$V_{DS} = V_D - V_S$$

$$= 0.4 - V_S$$

$$V_{DS} = V_{GS} - V_T$$

$$= V_G - V_S - V_T$$

$$= -V_S - V_T$$

$$V_{DS} > V_{GS} \quad [\text{saturation}]$$

$$ID = \frac{1}{2} k' w \frac{\omega}{L} (\sqrt{\omega_s} - \sqrt{f})^2$$

$$\Rightarrow (\sqrt{\omega_s} - \sqrt{f})^2 = \frac{2 T_{DL}}{k' w \times \omega}$$

$$\Rightarrow \frac{2 \times 0.3 \times 10^{-3} \times \cancel{3} \times 10^{-6}}{60 \times 10^{-6} \times \cancel{8} \times 10^{-6} \times 120} = \cancel{12} \frac{1}{4}$$

$$\Rightarrow \sqrt{\omega_s} - \sqrt{f} = \cancel{1} \frac{1}{\sqrt{2}}$$

$$\Rightarrow \sqrt{\omega_s} = \cancel{1} \sqrt{2} + \frac{1}{\sqrt{2}} = 1.5$$

$$\Rightarrow -\sqrt{s} = \cancel{1.5}$$

$$\Rightarrow \sqrt{s} = -\cancel{1.5}$$

$$\frac{2.5 - 0.4}{0.3}$$

$$R_D =$$

~~7 uV~~

~~A<sub>in</sub> = 300~~

$$R_S = \frac{\sqrt{s_2} \sqrt{s_3}}{0.3}$$

$$\frac{-2.5 + 2.5}{2 \times 0.3 + 0.3}$$

$$= 3.33 \text{ uV}$$

~~A<sub>in</sub> = 300~~


~~1000~~

~~1000~~

~~1000~~

~~1000~~

~~1000~~

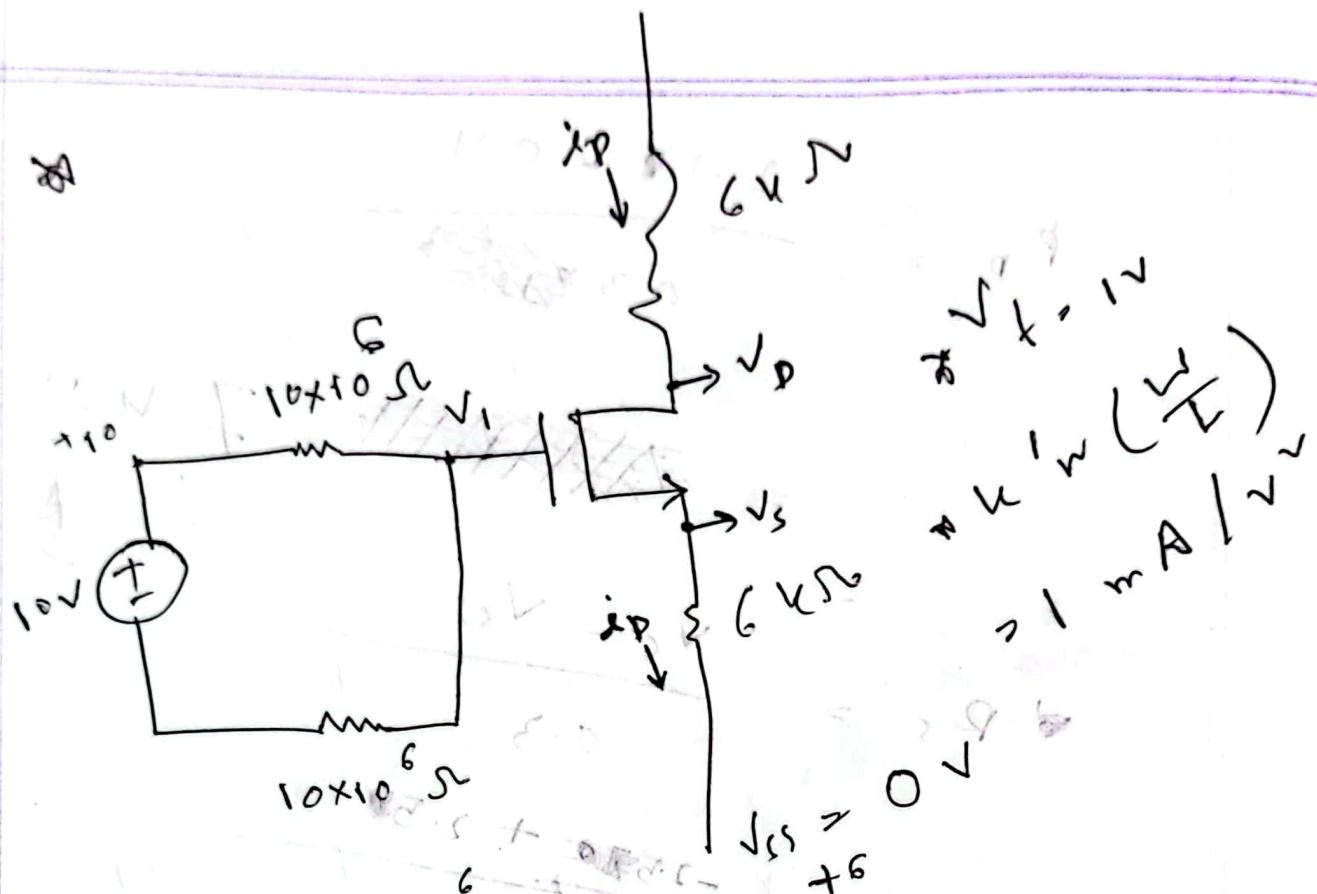

$$-10 + 10 \times 10^6 i + 10 \times 10^6 i = 0$$

$$\Rightarrow 2 \times 10^7 i = 10$$

$$\Rightarrow i = \frac{10}{2 \times 10^7} = 5 \times 10^{-8} \text{ A}$$

$$V_{10} = 10 - V_1$$

$$\Rightarrow 5 = 10 - V_1$$

$$\Rightarrow 5 - 10 = -V_1 \quad \therefore V_{10} = 5 \text{ V}$$

$$\Rightarrow V_1 = 5 \text{ V}$$

$$10 - V_D = 6i_D$$

$$\Rightarrow V_D = 10 - 6i_D$$

$$V_S - 0 = 6i_D$$

$$V_S = 6i_D$$

$$\therefore V_{DS} = 10 - 6i_D - 6i_D$$

$$\Rightarrow \boxed{10 - 12i_D} \rightarrow x$$

$$V_{OV} = V_a - V_s - V_t$$

$$\Rightarrow \boxed{5 - 6i_D} - 1 \rightarrow \frac{1}{2}x$$

$$\cancel{= 5 - 6i_D}$$

$$= \frac{1}{2}x - 1$$

$$V_{DS} > V_{OV}$$

so it is in saturation mode.

$$i_D = \frac{1}{2} k_n \frac{W}{L} (V_{GS} - V_T)^2$$

$$\frac{1}{2} (5 - 6i_D - 1)^2$$

$$\Rightarrow 2i_D = (4 - 6i_D)$$

$$\Rightarrow 2i_D = 16 - 48i_D + 36i_D^2$$


$$\Rightarrow 2i_D - 36i_D^2 + 48i_D - 16 = 0$$

$$50i_D - 36i_D^2 - 16 = 0$$

$$36i_D^2 - 50i_D + 16 = 0$$

$$\Rightarrow i_D = \frac{8}{9} > \frac{1}{2} \text{ mA}$$
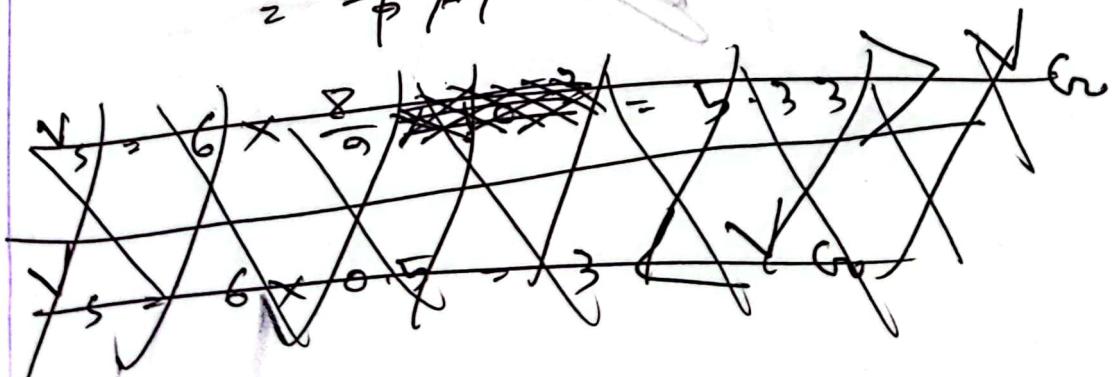
$$= \cancel{\frac{8}{9}} \cancel{(\text{Ans})}$$



in saturation

$$\checkmark V_{GS} > V_T \quad \checkmark V_T = 2V$$

$$\begin{aligned} V_{GS} &= V_G - V_S \\ &= 5 - 6 I_D \quad [I_D = \frac{8}{3}] \\ &= -0.33 \quad V_T \quad [\text{not possible}] \end{aligned}$$


$$V_{GS} \geq 5 - 6 I_D \quad [I_D = 0.5]$$

$$\Rightarrow 2 \geq V_T$$


$$\therefore I_D = 0.5 \text{ mA}$$

$$\begin{aligned} V_D &= 10 - 6 I_D \\ &= 7V \end{aligned}$$

$$\checkmark V_S = 3V$$

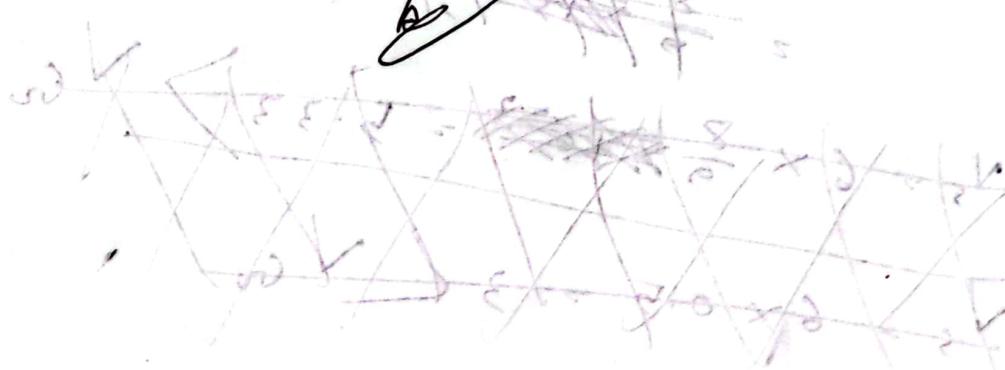

Q8

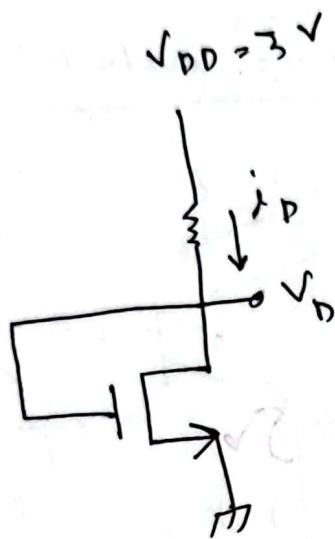


$$V_{DD} = 3 \text{ V}$$

$$I_D = 80 \times 10^{-6} \text{ A}$$

$$V_T = 0.6 \text{ V}$$

$$k'w = 200 \times 10^{-6} \text{ A/V}^2$$

$$\frac{w}{v} = \frac{4}{0.8}$$

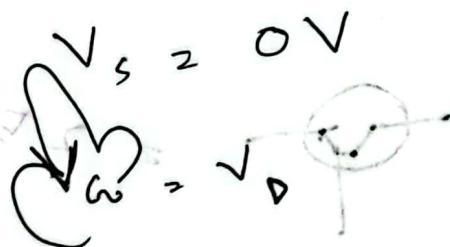

$$V_{DS} = V_D - V_S$$

$$\Rightarrow V_D$$

$$V_{OV} = V_{WS} - V_T$$

$$V_{OV} = V_W - V_S - V_T$$

$$\Rightarrow V_D - V_T$$

$$V_{DS} > V_{OV}$$

$$I_D = \frac{1}{2} k'w \frac{w}{l} (V_W - V_S - V_T)$$


$$\Rightarrow 80 \times 10^{-6} = \frac{1}{2} \times 200 \times 10^{-6} \times \frac{4}{0.8} (V_D - 0.6)$$

$$\Rightarrow (V_D - 0.6) = \frac{4}{25} \Rightarrow V_D - 0.6 = \frac{2}{5}$$

$$\Rightarrow V_D = 2 \text{ V}$$

$$V_{DD} - V_D \rightarrow R_D I_D$$

$V_D = 0.7V$

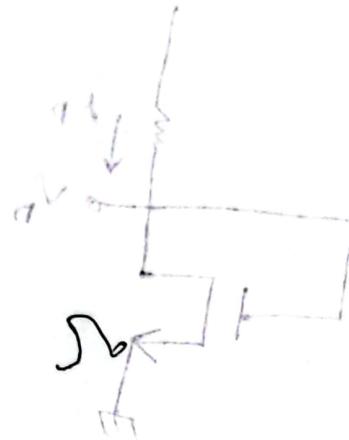

$$V_D = 0.7V$$

$$R_D = \frac{V_{DD} - V_D}{I_D}$$

$$= \frac{3 - 0.7}{80 \times 10^{-6}} = 25000 \Omega$$

$$A_V = -\beta R_L / (r_o + R_L)$$

$$A_V = -\beta R_L / r_o$$

$$A_V = -\beta R_L / r_o$$


$$(A_V = -\beta R_L / (r_o + R_L)) = -\frac{\beta R_L}{r_o + R_L} = -\frac{25000 \times 10^3}{0.1 + 25000} = -0.998$$

$$\left( A_V = -\frac{\beta R_L}{r_o + R_L} \right) = -0.998$$

$$\frac{V_o}{V_i} = 0.998 \approx 1$$

$$V_o = 0.998 V_i$$

# Bipolar Junction Transistor

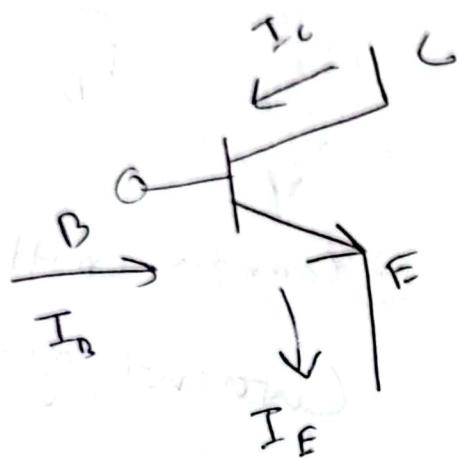


E = Emitter

B = Base

C = Collector

$$I_B = I_B + I_C$$

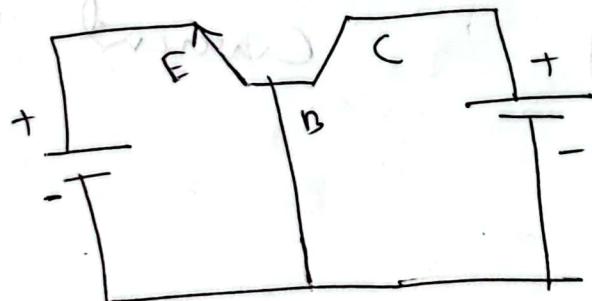

Cut-off

A

P (connected)  $\rightarrow$  (-)

w ( $\curvearrowleft$ )  $\rightarrow$  (+)

N B J T

$$i_c = i_s e^{\frac{\sqrt{B_E}}{\sqrt{T}}}$$

$$i_B = \frac{i_c}{\beta}$$

$$i_E = \frac{i_c}{2}$$

$$\frac{\sqrt{B_E}}{\sqrt{T}}$$

$$\beta, \frac{I_c}{I_B}$$

Common emitter  
Current gain

$$\alpha = \frac{I_c}{I_E} < 1$$

Common base  
Current gain

$$\alpha = \frac{I_c}{I_E}$$

$$\alpha = \frac{I_c}{I_E} \approx 1$$

$$\alpha = \frac{I_c}{I_E} \approx 1$$

$$V_{BE} = 0.7 \text{ V}, I_C = 2 \text{ mA}$$

$$I_C = I_S e^{\frac{V_{BE}}{V_T}}$$


$$\Rightarrow I_S = \frac{I_C}{e^{\frac{V_{BE}}{V_T}}} = \frac{1}{e^{\frac{0.7}{0.024}}} = 2.153 \times 10^{-7} \text{ mA}$$

$$\therefore I_C = I_S e^{\frac{V_{BE}}{V_T}}$$

$$\Rightarrow \ln\left(\frac{I_C}{I_S}\right) = \frac{V_{BE}}{V_T}$$

$$\Rightarrow V_{BE} = \ln\left(\frac{I_C}{I_S}\right) \cdot V_T \Rightarrow 0.64 \text{ V}$$

~~Exm: 5.1~~

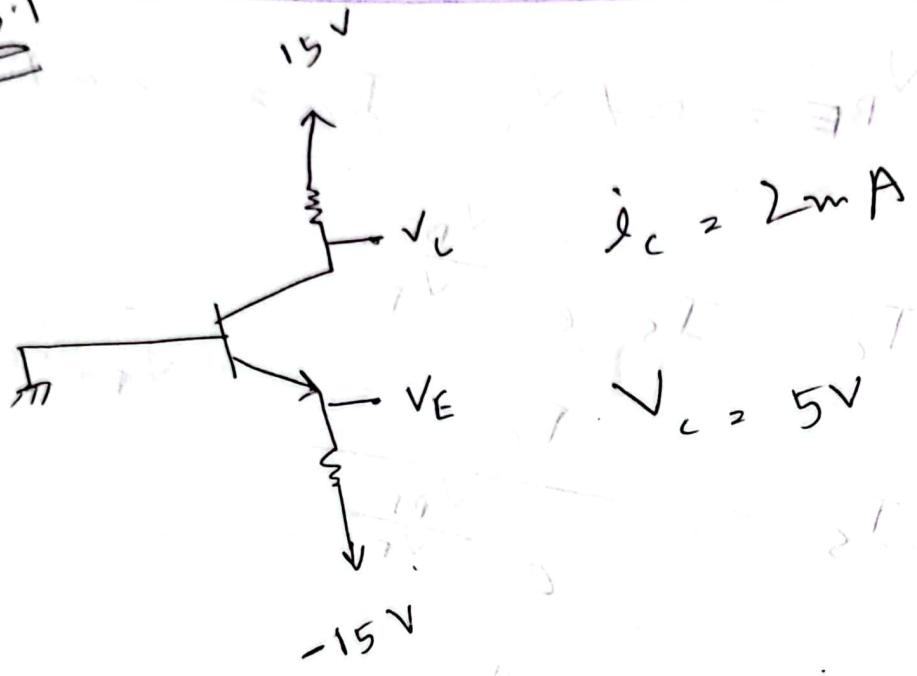

$$R_C = \frac{15 - 5}{2} \text{ k}\Omega$$

$$A_v = 5 \text{ V/V}$$

$$V_{BE} = V_B - V_E$$

$$\Rightarrow 0.7 = 0 - V_E$$

$$\Rightarrow V_E = -0.7 \text{ V}$$

$$I_E = I_B + I_C = 2 \text{ mA}$$

$$\therefore R_E = \frac{-0.7 + 15}{0.2} = 7.15 \text{ k}\Omega$$

$$\beta = 15$$

$$i_B = \frac{i_C}{\beta} = 0.02 \text{ mA}$$


$$\therefore I_E = 0.02 + 2 = 2.02$$

$$\therefore R_E = \frac{-0.7 + 15}{2.02} = 7.079 \text{ k}\Omega$$

$A_m = 800 = 4T$

$$800 = \frac{22}{14} \times \frac{9}{21} = 5$$
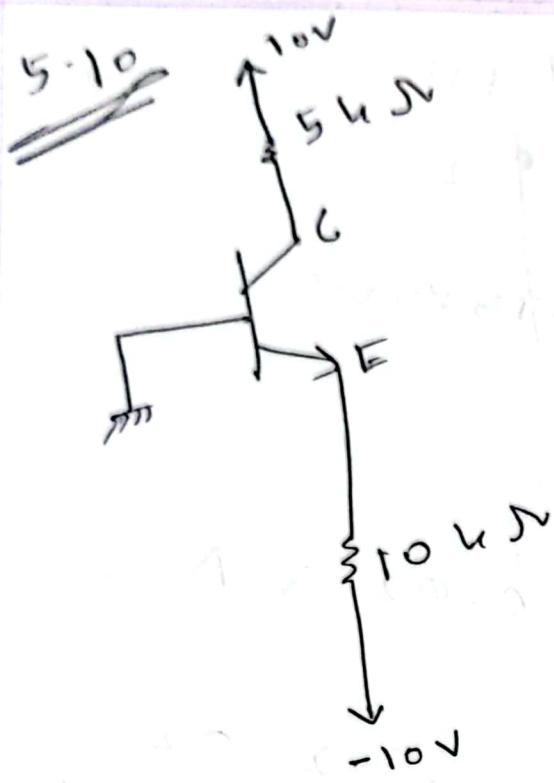
$$A_m \text{ P.M.D.} = 5T = \frac{5T}{T} = 5$$



$$\beta = 50$$

$$V_B = -0.7$$

$$V_B = 0$$

$$\therefore \frac{-0.7 + 10}{10} = I_E$$

$$\therefore I_E = 0.23 \text{ mA}$$

$$\alpha = \frac{\beta}{1+\beta} = \frac{50}{51} = 0.98$$

$$\therefore \alpha, \frac{I_C}{I_E} \therefore I_C = 0.9114 \text{ mA}$$

$$I_E = I_C + I_B$$

$$\Rightarrow I_B = 0.069 \text{ mA}$$

~~Active~~  $\downarrow$   $I_{BE} \approx 0.7 \text{ V}$

(i)  $E \text{ B } J [F \cdot B]$

$$\sqrt{V_{BE}} = 0.7 \text{ V}$$

$$\sqrt{V_{BE}} > \sqrt{V_{BE \text{ on}}} \Rightarrow [\sqrt{V_{BE \text{ on}}} = 0.5]$$

(ii)  $C \text{ B } J [P \cdot B]$

$$V_{CE} \geq 0.3 \text{ V}$$

Saturation

(i) EDS [F·D]  $\approx I + \frac{V_o}{T}$

$$\sqrt{V_{BE}} = 0.7 \text{ V} \quad V_C = 0 \text{ V}$$

(ii) CBS [F·B]  $V_C$

$$V_{CE} = 0.2 \text{ V}, \begin{cases} \text{At the edge of} \\ \text{sat, } V_{CE} = 0.3 \text{ V} \end{cases}$$


$\beta$  forced  $I_C$  (sat)

Overdrive factor =  $\frac{\beta_f I_{C0}}{(\alpha \cdot \beta_{\text{forced}})}$

$$V_{CE} \approx 0.3 \text{ V}$$

\*

$$\beta = 50 \text{ to } 150$$

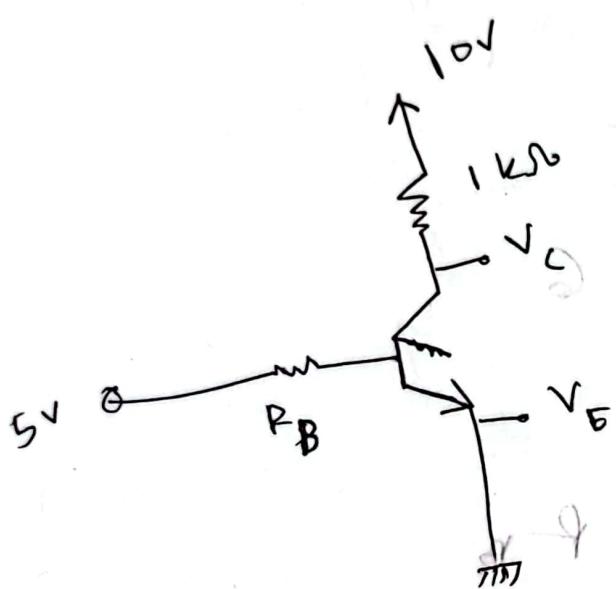

$$\frac{\beta_f}{\beta_{\text{force}}} \rightarrow 10$$

at least 10  
minimum  
 $\beta_f$

$$V_{BE} = 0.7, \quad V_{CE} = 0.2$$

$$\therefore \frac{10 - 0.2}{1} \rightarrow i_C = 7.8 \text{ mA}$$

$$\Rightarrow 10 = \frac{50}{\beta_{\text{force}}} = 5$$

$$\Rightarrow \beta_{\text{forced}} = 5$$

$$\beta = \frac{i_c}{i_B}$$

$$\Rightarrow i_B = \frac{9.8}{5}$$

$$\Rightarrow 1.96$$


$$\therefore \frac{5 - 0.7}{1.96} = R_B$$

$$\Rightarrow 2.2 \text{ m}\Omega$$

$$A = \frac{E_o}{I} = \frac{10}{0.7} = 14.2857$$

$$\tan \theta = \frac{10}{7} \approx 0.1428$$

$$\tan \theta = 0.1428$$

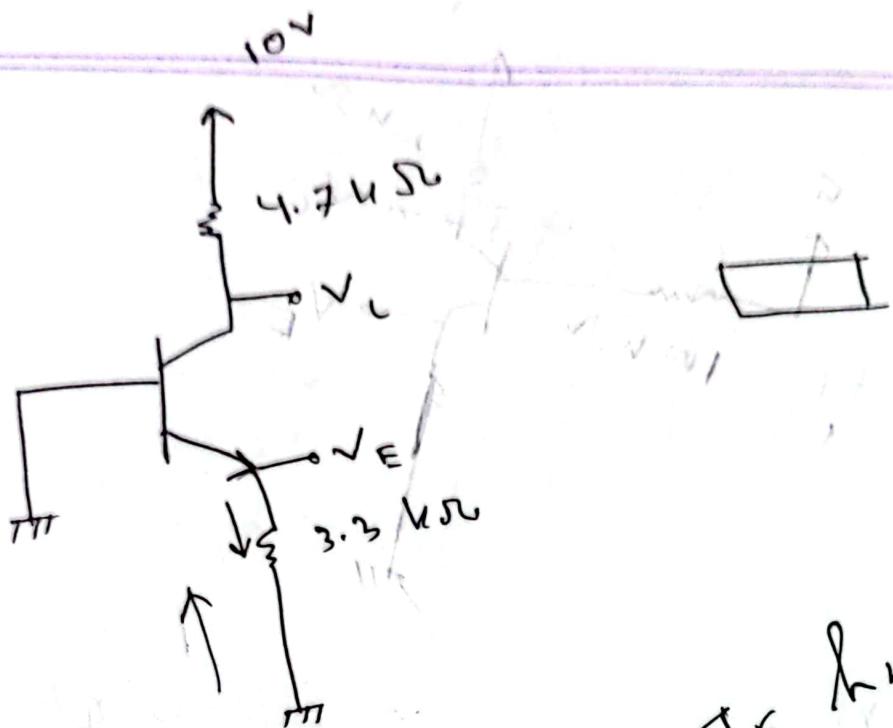

$$V_B = 0$$

$$\begin{aligned} V_{CB} &= V_C - V_B \\ &= V_C \end{aligned}$$

$$\Rightarrow V_{BE} = V_B - V_E$$

$$\Rightarrow 0.7$$

$$\Rightarrow V_E = -0.7$$

$$I_E^{\text{forward}} = \frac{-0.7}{3.3}$$


$$= -0.21 \text{ mA}$$

$I_E$  (Reverse Bias)

$$I_E = 0 \text{ mA}$$

$$I_B = 0 \text{ mA}$$

$$I_C = 0 \text{ mA}$$

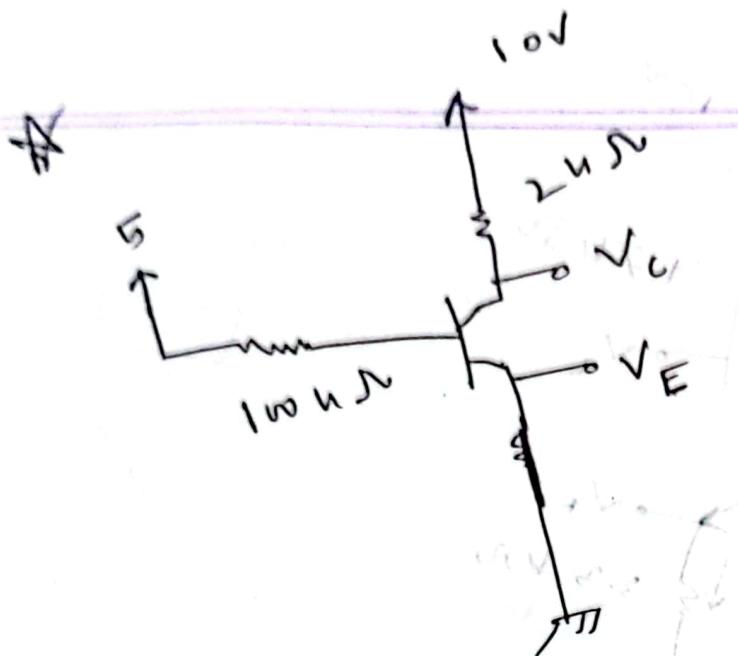

$$V_E = 0$$

$$V_{BE} = V_B - V_E$$

$$\Rightarrow V_B = 0.7$$

$$\frac{5 - 0.7}{100} = I_B$$

$$\Rightarrow I_B = 0.043 \text{ mA}$$

~~$$I_C = \beta I_B$$~~

$$= 100 \times 0.043$$

$$= 4.3 \text{ mA}$$

$$\therefore I_F = 4.343 \text{ mA}$$



$$10 - V_C = 8.6$$

$$\Rightarrow V_C = 1.4 \text{ V}$$

~~from~~  $V_{DS}$   $\rightarrow$  MOSFET

$$V_D = 7 \text{ V}$$

$$V_D = 7.5 \text{ V}$$

$$V_D = 7.5 \text{ V} \quad I_F = 38 \text{ mA} = 38 \text{ V}$$

$$\frac{37}{87} = 0.43$$

$$I_D = 38 \text{ mA}$$

$$V_D = 9 \text{ V}$$

$$V_D + 0.7 = 9.7 \text{ V}$$

$$V_D = 9.7 \text{ V}$$

$$\frac{10}{9} = 1.11$$

$$\frac{10}{9} = 1.11$$

$$A_m 1.0$$


$$5$$

$$A_m = 2$$

13.8.23

$$V_{CC} = 10 \text{ V}$$

## Electronics

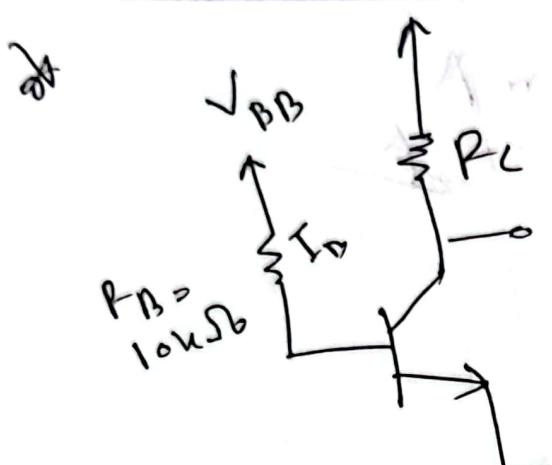

$$V_E = 0 \text{ V}$$

$$V_{CE} = 5 \text{ V}$$

$$V_{BE} = 0.7 \text{ V} \quad V_{CE} = 5 \text{ V}$$

$$V_B = 0.7$$

$$\beta = 50$$

$$\beta = \frac{I_C}{I_B}$$

$$I_L = \frac{V_{CC} - 5}{2}$$

$$= \frac{10 - 5}{2}$$

$$= 5 \text{ mA}$$

$$\Rightarrow I_B = \frac{I_C}{\beta}$$

$$= \frac{5}{50}$$

$$= 0.1 \text{ mA}$$

$$\checkmark \quad \checkmark \quad \checkmark \quad \checkmark \quad \checkmark$$

$$\Rightarrow V_{BB} = 26 \text{ V}$$

$$V_{BB} - 0.7 = 1$$

$$\Rightarrow V_{BB} = 1.7 \text{ V}$$



$$2 = 1 \text{ V}$$

$$V_{CE} = 0.3$$

$$F.O. = 7.9 \text{ V}$$

$$V_C = 0.3 \text{ V}$$

$$F.O. = 7 \text{ V} \rightarrow 2$$

$$\therefore I_C = \frac{V_{CC} - 0.3}{2} \text{ A}$$


$$A_m = \frac{10 - 0.3}{1} = 9.7 \text{ V}$$

$$\therefore I_P = \frac{9.7}{50} = 0.194 \text{ A}$$

$$\therefore V_{BB} = 0.7 + (10 \times 0.194)$$

$$= 2.64 \text{ V}$$



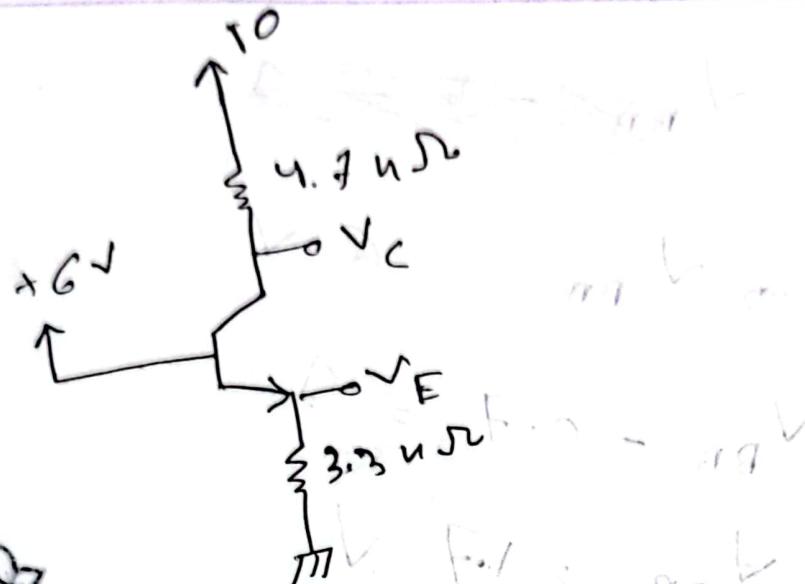

$$V_B = 6$$

$$\therefore V_{BE} = 0.7$$

$$\Rightarrow 6 - V_E = 0.7 \quad V_E = 5.3$$

$$\Rightarrow V_E = 5.3$$

$$I_E = \frac{5.3}{3.3} \rightarrow 1.62 \text{ mA}$$

$$\beta = 50 \text{ (approx)}$$

$$(1.62 + 0) \text{ mA}$$

$$V_{RDG}$$

$$\alpha = \frac{\beta}{\beta + 1} = 0.98$$

$$\therefore \alpha = \frac{I_C}{I_E}$$

$$\Rightarrow I_E = \alpha I_E$$

$$= 0.98 \times 1.63$$

$$= 1.5778 \text{ mA}$$

$$\Rightarrow I_B = I_E - I_{LW}$$

$$\approx 0.032$$

$$\therefore V_C = (4.7 \times 1.5778)$$

$$\Rightarrow V_C = 10 - 7.42$$

$$V_{CB} = 2.58 - 6 = -3.42 \angle -0.4^\circ$$

(Saturation)

$$V_{CE} = 0.2 \text{ V}$$


$$\Rightarrow V_C - V_E = 0.2$$

$$\Rightarrow V_C = 0.2 + 5.3 \\ = 5.5$$

$$I_C = \frac{100 - 5.5}{4.7} \text{ mA} = 17 \text{ mA}$$


$$= 0.017 \text{ A}$$
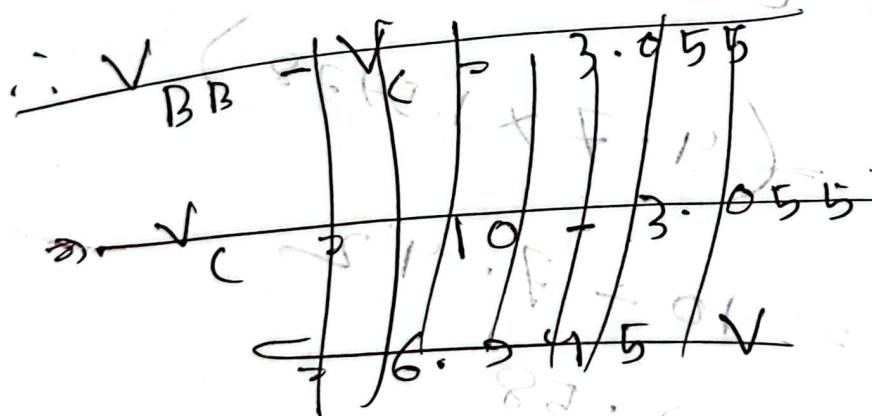
$$\therefore I_B = 0.65 \text{ mA} = 17 \text{ mA}$$



$$\text{Power dissipated} = \frac{I_C}{I_B} = 1.5$$
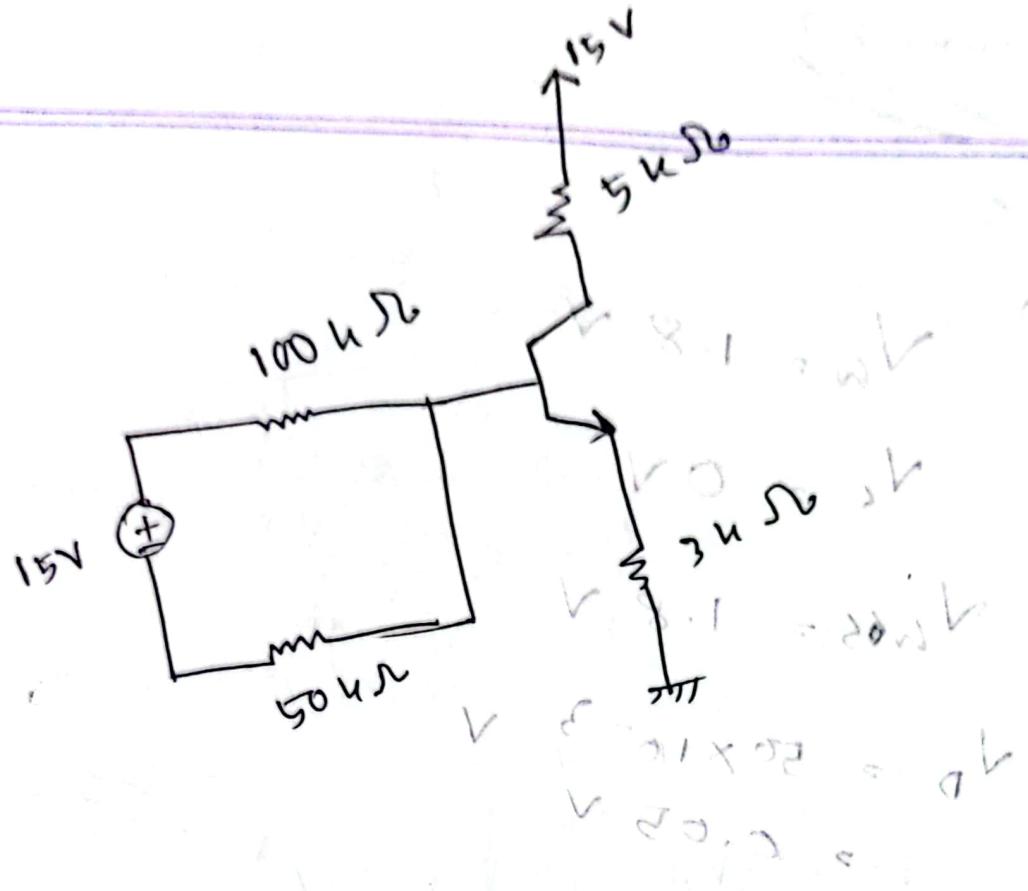
$$\text{Power dissipated} = \frac{I_C}{I_B} = 1.5$$



$$-15 + 100i + 50i = 0 \quad \text{or} \quad i = 0.1 \text{ mA}$$

$$15 - V_B = 10 \quad \text{or} \quad V_B = 5 \text{ V}$$

~~Sum = 22~~

~~22~~

(a)

$$V_{GS} = 1.8 \text{ V}$$

$$V_S = 0 \text{ V}$$

$$V_{GDS} = 1.8 \text{ V}$$


$$V_D = 50 \times 10^{-3} \text{ V}$$
$$\Rightarrow 0.05 \text{ V}$$

$$V_{DS} = 0.05 \text{ V}$$

$$V_{DS} < V_{OV}$$

$$\frac{V_{OV}}{2} = \frac{V_{GS} - V_T}{2}$$
$$= \frac{1.8}{2} - 0.5$$
$$\approx 1.3 \text{ V}$$

~~b~~

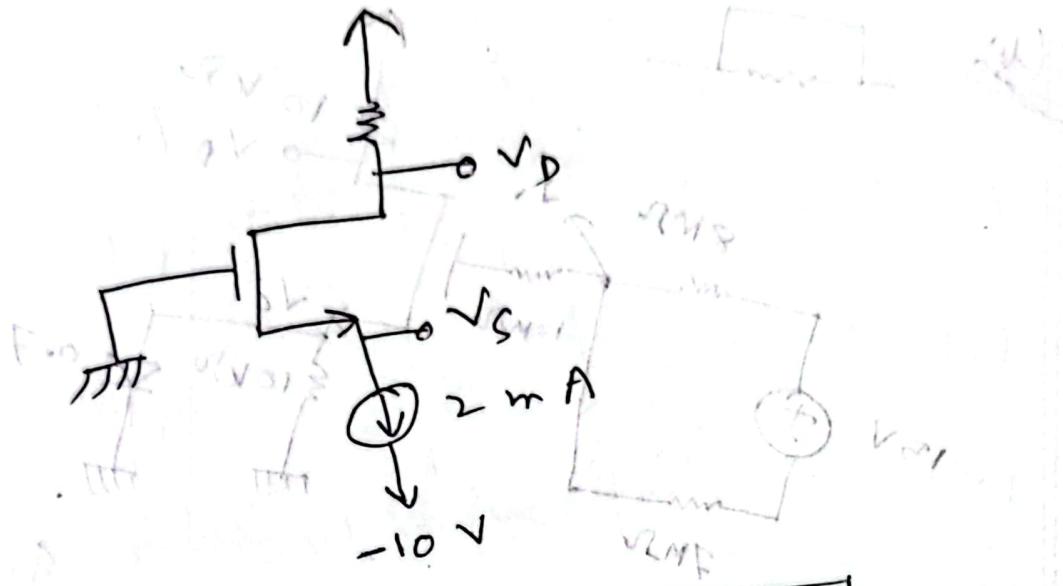

$$V_{GS} = 0\text{V}$$

$$10 - V_D = 4 + 2$$

$$\Rightarrow 10 - V_D = 8$$

$$\Rightarrow V_D = 2\text{V}$$

$$\boxed{\begin{aligned} V_D &= 10 - 4I_D \\ V_S &= -10 + 2 \end{aligned}}$$

$$\Rightarrow V_D = 0.7$$


$$\Rightarrow V_{DS} = 0 - V_S - 0.7$$

$$\begin{aligned} V_{DS} &\rightarrow 2 - V_S \\ &\rightarrow -V_S + 2 \end{aligned} \quad \Rightarrow -V_S - 0.7$$

$$V_{DS} > V_{OV} \quad (\text{saturation})$$

$$V_{DD} = 15 \text{ V}$$

(b)

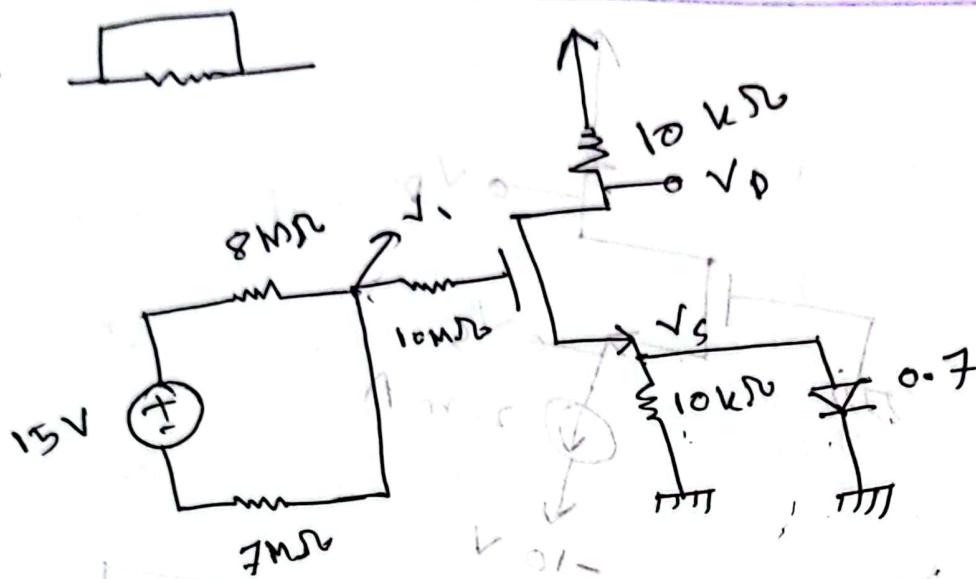

$$\begin{aligned} 0.7i_D - 0.1 &= V_D \\ -15 + 8i + 0.7i &= 3V \end{aligned}$$

$$\Rightarrow 15 = 8.7i$$

$$\Rightarrow i = 2 \mu\text{A}$$

$$\Rightarrow i = 2 \times 10^{-3} \text{ mA}$$

$$i_D = 0.7 \times 10^{-3} \text{ mA}$$

$$V_o = 7(V_{DD} - 0.7i_D)$$

$$V_o = 7(15 - 0.7 \times 2 \times 10^{-3})$$

$$15 + V_D = 10 i_D$$

$$\Rightarrow V_D = 15 - 10 i_D$$

$$V_s = 0.7$$

Assume ~~saturated~~ Saturation,  $V_{DS} = 20 \text{ mV}$

$$i_D = \frac{1}{2} k' w \frac{w}{l} (V_{DS} - V_t) \frac{1}{2} V_{DS}$$

$$i_D = \frac{1}{2} k' w \frac{w}{l} (V_{WS} - V_t) \frac{1}{2} (7 - 0.7 - 0.75)$$

$$i_D = \frac{1}{2} \times 2.5$$

$$= 38.5 \text{ mA}$$

$$V_{DS} = 15 - (38.5 \times 10) - V_s$$

$$= -370.7$$

$$V_{DS} = V_{WS} - V_t$$

$$= 7 - 0.7 - 0.75$$

$$= 5.55$$

~~20823~~

Not gate

Cmos  
Complementary

Active:

$A = 0$ : (low voltage)



NMOS: off

PMOS: on

$A = 1$  (High voltage)

NMOS: ON

PMOS: OFF

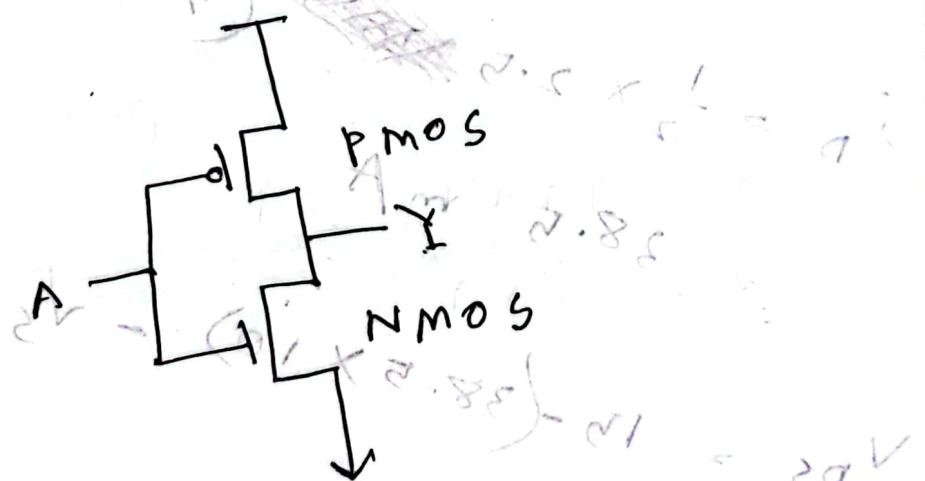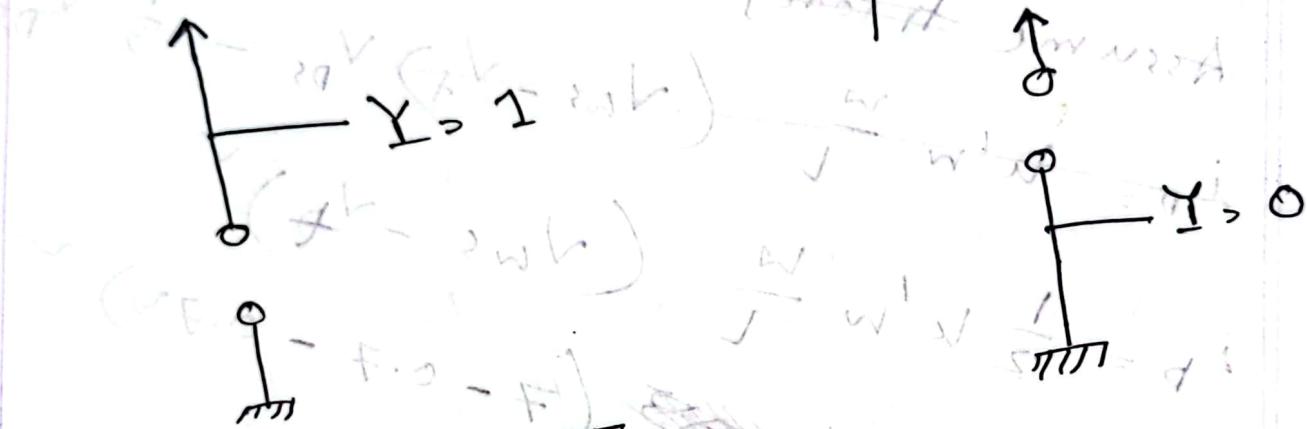

$A = 0$

$F = 1$

$F = 0$

$A = 1$

प्रोफाइल इनपुट मेंका गेटर  
N MOS बाटा,

## NAND gate (NMOS)

\* Input जैसे ही आवारा 2 न्यून ओर्डर


NAND gate series का गेटर, A  
N MOS

\* ~ ~ ~ ~ ~ ~ ~


NAND gate parallel का गेटर,  
N MOS

(PMOS ऑपोजिट)
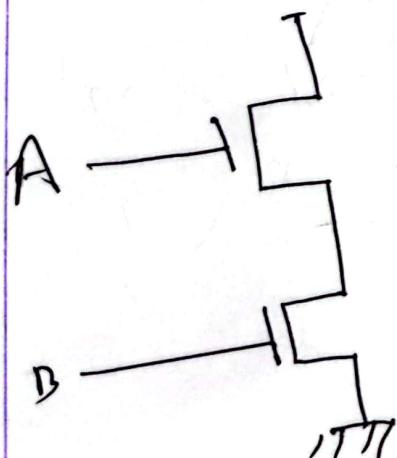
$$Y = \overline{AB} \quad (\text{NMOS})$$





$$(PMOS)$$

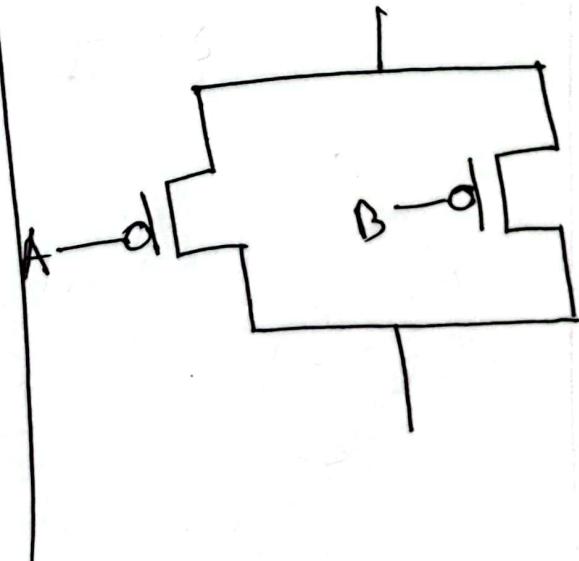

the more logic we add



more complex

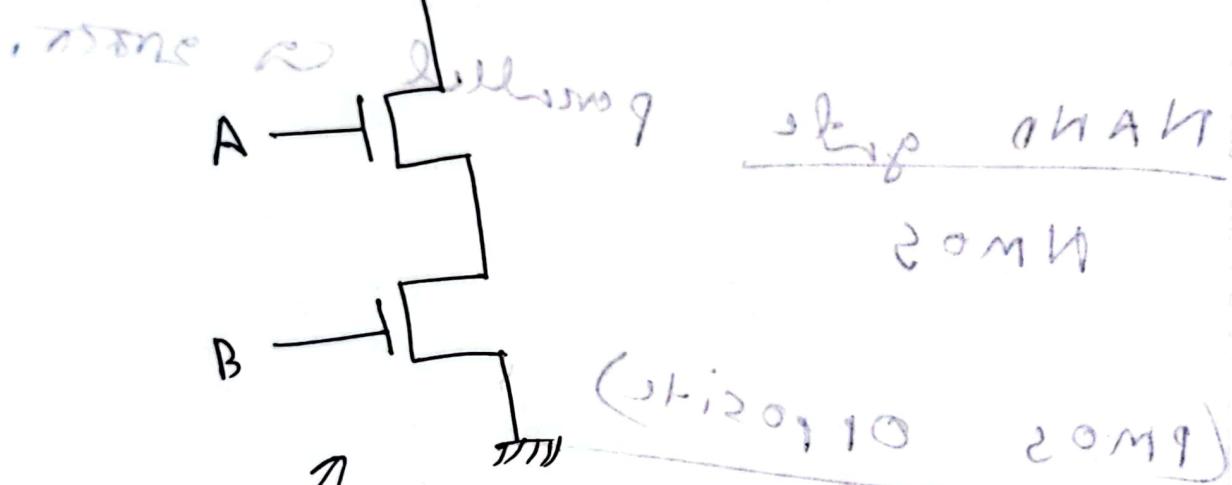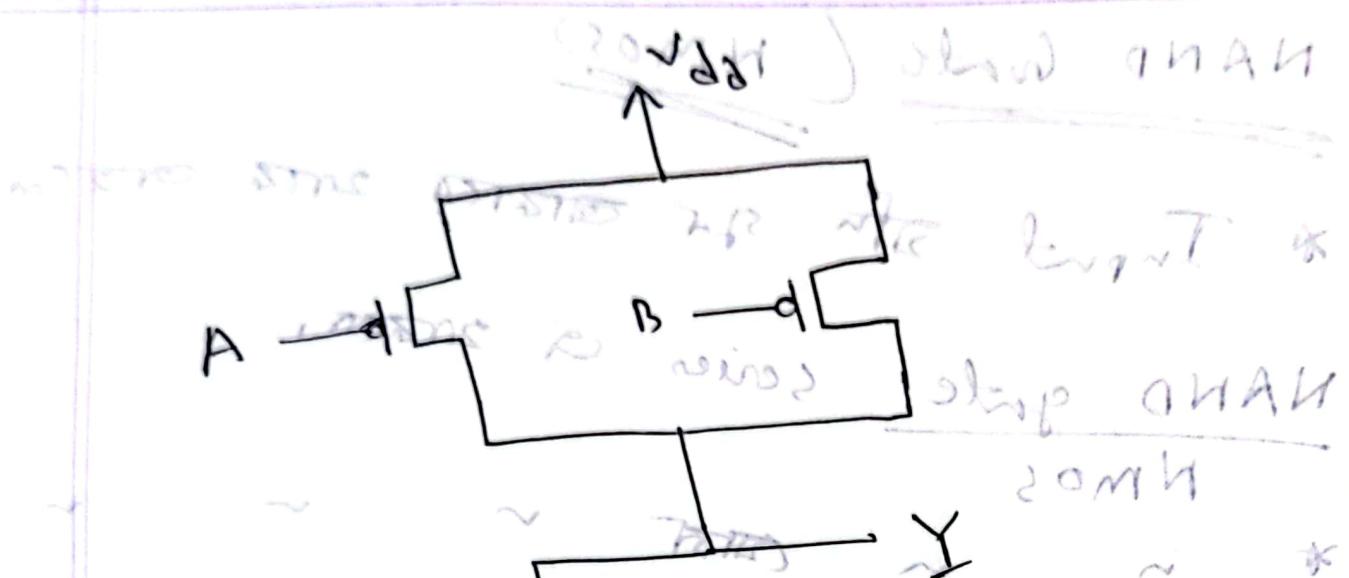


~~(2019)~~  $J = \overline{AB}$

~~(2019)~~  $J = \overline{AB}$  (NAND Gate)  
Not

$\overline{\overline{AB}} = Y$

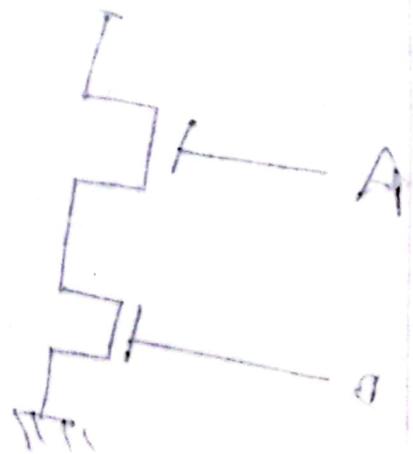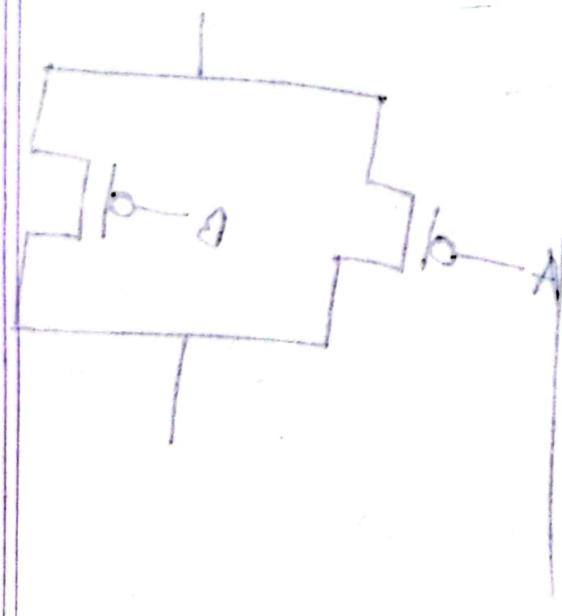

$$J = \overline{A + B}$$

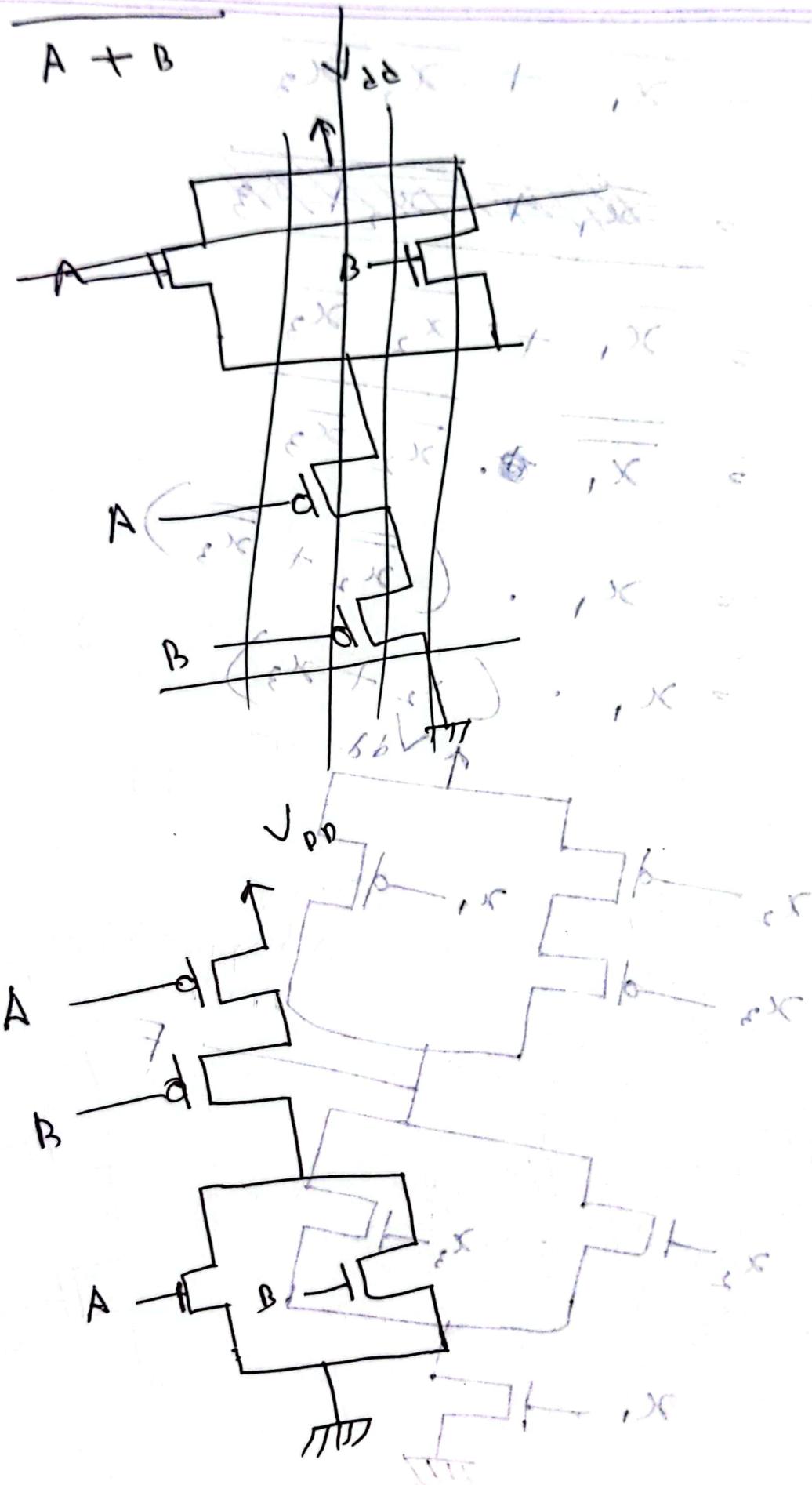

$$F = \overline{x_1} + \overline{x_2} \overline{x_3}$$

$a + A = b$



$$\overline{F} = \overline{x_1} + \overline{x_2} \overline{x_3}$$

$$= \overline{x_1} \cdot \overline{x_2} \overline{x_3}$$

$$= x_1 \cdot (x_2 + x_3) \quad a$$

$$= x_1 \cdot (x_2 + x_3) \quad a$$

